

Name: _____

Student ID #: _____

**ECE 113A
Homework #6**

Due 10 A.M. Wednesday, November 26, 2003

Please *staple* this sheet to the front of your homework.

1	2a	2b	2c	2d	2e	2f	2g	2h	2i	2j	Total
/42	/6	/6	/6	/6	/6	/6	/6	/6	/6	/4	/100


1) In class we made some simplifying assumptions to prove the ideal diode equation:

$$I = I_0 \left(e^{qV_{diode}/kT} - 1 \right)$$

However, in real life things are not quite so simple. Real life diodes usually have I-V curves which can be described as

$$I = I_0 \left(e^{\eta qV_{diode}/kT} - 1 \right),$$

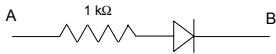here η is called the “ideality factor”. For an ideal diode, $\eta=1$. In the following, I want you to assume that $\eta=0.9$. Also, take $I_0=10^{-14}$ A. For the circuit shown, fill in the following table:




V_{AB} (V)	V_{diode} (V)	I_{AB} (A)
0		
0.5		
1		
1.5		
2		
2.5		
3		
3.5		
4		
4.5		
5		
5.5		
6		
6.5		
7		
7.5		
8		
8.5		
9		
9.5		
10		

Name: _____

Student ID #: _____

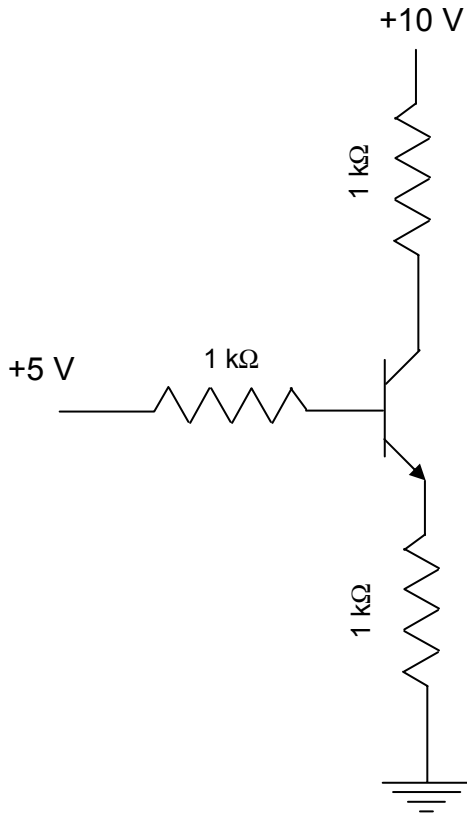- 2) For the circuit shown below, find I_B , I_E , I_C , V_C , V_B , V_E , V_{BE} , V_{CE} , V_{BC} defined in figure 10.2b of the text. Hints: the BE voltage drop is about 0.6 V. Take $\beta = 100$. Then $I_C = 100 I_B$. The rest is just applications of Kirchoff's current and voltage laws. Is the transistor biased in active mode?



Please fill out table on this paper. Show your work on attached paper. As usual, no units, no credit.

$I_E =$	
$I_B =$	
$I_C =$	
$V_E =$	
$V_B =$	
$V_C =$	
$V_{BE} =$	
$V_{CE} =$	
$V_{BC} =$	
Active? Y or N	