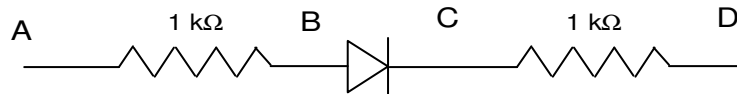


## EECS 170A Section B Homework Solution #4

1) In class we found:

$$I = I_0(e^{qV_{diode}/kT} - 1)$$

Take  $I_0 = 10^{-14}$  A. For the circuit shown, fill in the following table:



**Solution:**

By applying Kirchoff's Law to this circuit, we obtain

$$V_{AD} = RI + V_{diode} + RI = 2RI + V_{diode} \quad (2)$$

Substitute eqn (1) into (2), we get:

$$V_{AD} = V_{diode} + I_0(e^{qV_{diode}/kT} - 1) \times 2R$$

Substitute  $I_0 = 10^{-14}$  A and  $R = 1 \text{ K}\Omega$ , we get:

$$\begin{aligned} V_{AD} &= V_{diode} + 10^{-14} \text{ A} \times (e^{qV_{diode}/kT} - 1) \times 2 \text{ K}\Omega \\ V_{AD} &= V_{diode} + 2 \times 10^{-11} \times (e^{qV_{diode}/kT} - 1) \\ (e^{qV_{diode}/kT} - 1) &= (V_{AD} - V_{diode}) / 2 \times 10^{-11} \\ V_{diode} &= \frac{kT}{q} \ln \left( \frac{(V_{AD} - V_{diode})}{2 \times 10^{-11}} + 1 \right) \end{aligned}$$

*(2pts for showing the equations)*

Since we can not explicitly solve for  $V_{diode}$  the above transcendental equation can be solved in an iterative process. To begin with, lets take  $V_{diode}$  in the log as 0.6V for the condition that  $V_{AD} = 1\text{V}$ ,

$$\begin{aligned} V_{diode} &= 0.026\text{V} \times \ln \left( \frac{(1\text{V} - 0.6\text{V})}{2 \times 10^{-11}} + 1 \right) \\ V_{diode} &= 0.6167\text{V} \end{aligned}$$

For the second iterative step we can use the updated value of  $V_{diode}$  as 0.62V and further enhance our precision of  $V_{diode}$ . Now we get,

$$\begin{aligned} V_{diode} &= 0.026\text{V} \times \ln \left( \frac{(1\text{V} - 0.62\text{V})}{2 \times 10^{-11}} + 1 \right) \\ V_{diode} &= 0.6154\text{V} \end{aligned}$$

For the third iterative step we can use the updated value of  $V_{\text{diode}}$  as 0.6156V and further enhance our precision of  $V_{\text{diode}}$ . Now we get,

$$V_{\text{diode}} = 0.026V \times \ln(1V - 0.6156V) / 2 \times 10^{-9} + 1)$$

$$V_{\text{diode}} = 0.6156V$$

If a further iterative step does not change  $V_{\text{diode}}$  appreciably then we can stop the iteration. In this case, the iterative results in the same value to the thousandths place so the final answer is  $V_{\text{diode}} = 0.6156V$  for  $V_{\text{AD}} = 1V$ .

Now that we know  $V_{\text{diode}}$  we can solve for the current  $I_{\text{AD}}$  and obtain:

$$I_{\text{AD}} = 10^{-14} A \times (e^{(0.6156V/0.026V)} - 1) = 2.71 \times 10^{-7} A$$

With the same approach, we can obtain the results for each  $V_{\text{AD}}$  value:

$V_{\text{AD}}$ (V)	$V_{\text{diode}}$ (V) = $V_{\text{BC}}$	$I_{\text{AD}}$ (A)
0	0	0
0.5	0.4913	$1.94 \times 10^{-6}$
1	0.6156	$1.92 \times 10^{-4}$
1.5	0.6366	$4.30 \times 10^{-4}$
2	0.6484	$6.77 \times 10^{-4}$
2.5	0.654	$9.23 \times 10^{-4}$
3	0.6626	$1.17 \times 10^{-3}$
3.5	0.6676	$1.41 \times 10^{-3}$
4	0.6718	$1.66 \times 10^{-3}$
4.5	0.6754	$1.91 \times 10^{-3}$
5	0.6786	$2.16 \times 10^{-3}$
5.5	0.6814	$2.41 \times 10^{-3}$
6	0.6840	$2.66 \times 10^{-3}$
6.5	0.6863	$2.91 \times 10^{-3}$
7	0.6884	$3.15 \times 10^{-3}$
7.5	0.6904	$3.40 \times 10^{-3}$
8	0.6922	$3.65 \times 10^{-3}$
8.5	0.6939	$3.90 \times 10^{-3}$
9	0.6956	$4.15 \times 10^{-3}$
9.5	0.6971	$4.40 \times 10^{-3}$
10	0.6985	$4.65 \times 10^{-3}$

*(0.25 pts for correct answers)*

Now do the same, assuming the resistors are 1 MΩ instead of 1 kΩ.

Substitute  $I_0 = 10^{-14}$  A and  $R = 1 \text{ M}\Omega$ , we get:

$$V_{diode} = \frac{KT}{q} \ln \left( \frac{V_{AD} - V_{diode}}{2 \times 10^{-8}} + 1 \right)$$

$V_{AD}$ (V)	$V_{diode}$ (V) = $V_{BC}$	$I_{AD}$ (A)
0	0	0
0.5	0.4008	$4.952 \times 10^{-8}$
1	0.4458	$2.772 \times 10^{-7}$
1.5	0.4619	$5.189 \times 10^{-7}$
2	0.4719	$7.640 \times 10^{-7}$
2.5	0.4792	$1.010 \times 10^{-6}$
3	0.4849	$1.258 \times 10^{-6}$
3.5	0.4896	$1.505 \times 10^{-6}$
4	0.4935	$1.753 \times 10^{-6}$
4.5	0.4970	$2.002 \times 10^{-6}$
5	0.5000	$2.250 \times 10^{-6}$
5.5	0.5027	$2.499 \times 10^{-6}$
6	0.5052	$2.747 \times 10^{-6}$
6.5	0.5075	$2.996 \times 10^{-6}$
7	0.5095	$3.245 \times 10^{-6}$
7.5	0.5115	$3.494 \times 10^{-6}$
8	0.5132	$3.743 \times 10^{-6}$
8.5	0.5149	$3.993 \times 10^{-6}$
9	0.5165	$4.242 \times 10^{-6}$
9.5	0.5180	$4.491 \times 10^{-6}$
10	0.5194	$4.740 \times 10^{-6}$


*(0.25 pts for correct answers)*

How much does this effect the “on voltage” by?

The resistances differ by 3 order of magnitude (from 1kΩ to 1MΩ), but the on voltage only change by approximately 0.18V. The effect is relatively small.

*(2pts)*

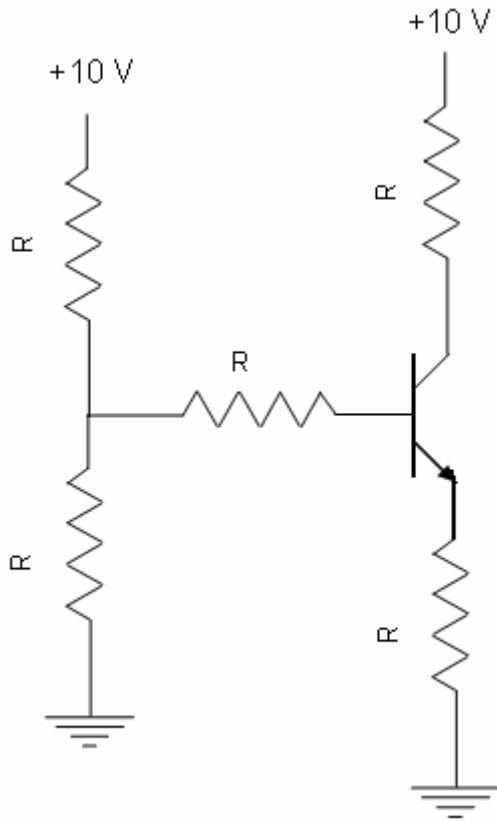2) For the circuit shown below, find  $I_B$ ,  $I_E$ ,  $I_C$ ,  $V_C$ ,  $V_B$ ,  $V_E$ ,  $V_{BE}$ ,  $V_{CE}$ ,  $V_{BC}$  defined in figure 10.2 of the text. Hints: the BE voltage drop is about 0.6 V. Take  $\beta = 100$ . Then  $I_C = 100 I_B$ . The rest is just applications of Kirchoff's current and voltage laws. Is the transistor biased in active mode? Assume  $R = 1 \text{ k}\Omega$ .



**Solution:**

Assuming the transistors is in active mode,

$$V_{BE} = V_B - V_E = 0.6 \text{ V} \quad (2.1) \quad (4\text{pts})$$

$$I_C = \beta I_B = 100 I_B \quad (2.2) \quad (4\text{pts})$$

$$I_E = I_B + I_C = 101 I_B \quad (2.3) \quad (4\text{pts})$$

$$I_C = (10 - V_C) / R \quad (2.4) \quad (4\text{pts})$$

$$I_B = (5 - V_B) / (R + R/2) \quad (2.5) \quad (4\text{pts})$$

$$I_E = V_E / R \quad (2.6) \quad (4\text{pts})$$

From eqn 2.3 and eqn 2.6:

$$101 I_B = V_E / 1\text{k}\Omega \quad (2.7)$$

Substitute eqn 2.5 into eqn 2.7:

$$101 (5 - V_B) / 1.5\text{k}\Omega = V_E / 1\text{k}\Omega \quad (2.8)$$

From eqn 2.1 and substitute into eqn 2.8:

$$101 (5 - V_B) / 1.5\text{k}\Omega = (V_B - 0.6) / 1\text{k}\Omega$$

$$101 (5 - V_B) = 1.5V_B - 0.9$$

$$\therefore V_B = 4.936 \text{ V} \quad (2.9)$$

Substitute into eqn (2.9) into eqn (2.1):

$$\begin{aligned} V_E &= V_B - 0.6 \\ &= 4.336 \text{ V} \end{aligned} \quad (2.10)$$

From eqn (2.5) and eqn (2.9):

$$\therefore I_B = (5 - V_B) / 1.5R = 4.293 \times 10^{-5} \text{ A}$$

From eqn (2.2):

$$I_C = 100 I_B = 4.293 \times 10^{-3} \text{ A}$$

From eqn (2.3):

$$I_E = 101 I_B = 4.336 \times 10^{-3} \text{ A}$$

From eqn (2.4):

$$\begin{aligned} V_C &= 10 - R I_C \\ &= 5.707 \text{ V} \end{aligned}$$

Since  $V_{BE} = V_{BE(on)}$  and  $V_{BC} < 0$ , the BJT is indeed in active mode. (4pts)

$I_E = 4.336 \times 10^{-3} \text{ A}$	(2pts)
$I_B = 4.293 \times 10^{-5} \text{ A}$	(2pts)
$I_C = 4.293 \times 10^{-3} \text{ A}$	(2pts)
$V_E = 4.336 \text{ V}$	(2pts)
$V_B = 4.936 \text{ V}$	(2pts)
$V_C = 5.707 \text{ V}$	(2pts)
$V_{BE} = 0.6 \text{ V}$	(2pts)
$V_{CE} = 1.371 \text{ V}$	(2pts)
$V_{BC} = -0.771 \text{ V}$	(2pts)