

EECS70A / CSE 70A Network Analysis I
Prof. Peter Burke

Homework # 3

Due date: 5/18/07 at 2:50pm (ICF102)

Problems from the textbook:

1. Problem 5.1
2. Problem 5.10
3. Problem 5.25
4. Problem 5.34
5. Problem 5.84: Figure 5.103 in the textbook is incorrect. Please use the circuit below instead of Figure 5.103 for this question.

