

EECS70A / CSE 70A Network Analysis I
Prof. Peter Burke


Homework # 2 solution

Q1. Considering that electric potential is defined as line integral of electric field, Kirchhoff's voltage law can be expressed equivalently with equation:

$$\oint_C \mathbf{E} \cdot d\mathbf{l} = 0,$$

Which states that line integral of electric field around closed loop C is zero.

Q2. Problem 3.1: (Using Nodal Analysis)

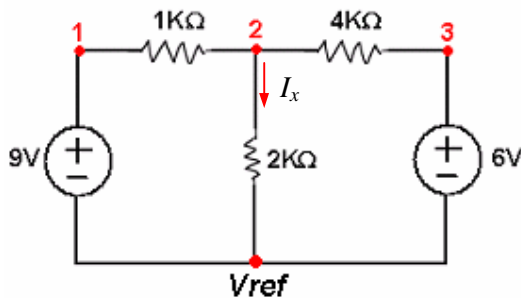

Voltage at node 1, $V_1 - V_{ref} = 9V$

Voltage at node 3, $V_3 - V_{ref} = 6V$

Apply KCL at node 2:


$$(V_2 - V_1) / 1K\Omega + (V_2 - V_{ref}) / 2K\Omega + (V_2 - V_3) / 4K\Omega = 0$$

$$(V_2 - 9 - V_{ref}) / 1K\Omega + V_2 / 2K\Omega + (V_2 - 6 - V_{ref}) / 4K\Omega = 0$$

$$\therefore V_2 - V_{ref} = 6V$$

$$\therefore I_x = (V_2 - V_{ref}) / 2K\Omega = 3 \times 10^{-3} A = 3 \text{ mA}$$

Q3. Problem 3.2: (Using Nodal Analysis)

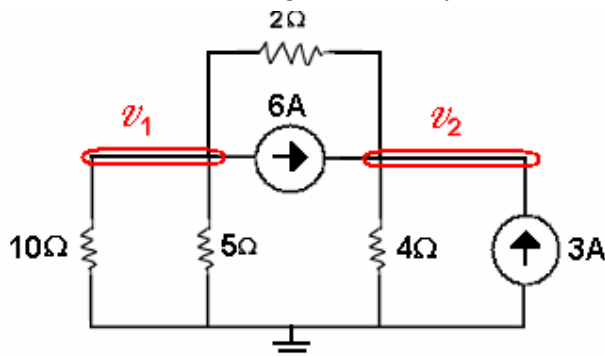

Apply KVL to node 1:

$$V_1/10 + V_2/5 + (V_1 - V_2)/2 + 6 = 0$$

$$2V_1 - V_2 = -20 \quad \text{--- (1)}$$

Apply KVL to node 2:

$$(V_1 - V_2) / 2 + 6 + 3 = V_2 / 4$$


$$2V_1 - 3V_2 = -36 \quad \text{--- (2)}$$

Eqn 1 - eqn 2,

$$2V_2 = 16 \quad \Rightarrow \quad \therefore V_2 = 8V$$

$$\Rightarrow \quad \therefore V_1 = -6V$$

Q4. Problem 3.3: (Using Nodal Analysis)

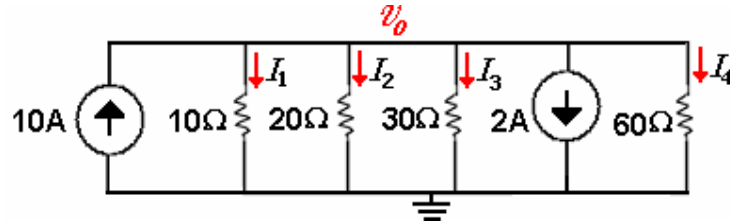

Apply KVL to the non-reference node:

$$V_o / 10 + V_o / 20 + V_o / 30 + V_o / 60 + 2 = 10$$

$$6V_o + 3V_o + 2V_o + V_o = 480$$

$$\therefore V_o = 40 \text{ V}$$

Apply Ohm's law:


$$I_1 = V_o / 10 = 4 \text{ A}$$

$$I_2 = V_o / 20 = 2 \text{ A}$$

$$I_3 = V_o / 40 = 1.33 \text{ A}$$

$$I_4 = V_o / 60 = 0.67 \text{ A}$$

Q5. Problem 3.4: (Using Nodal Analysis)

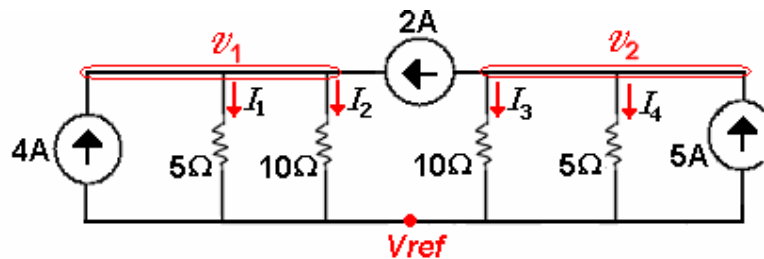

Apply KVL to node 1:

$$(V_1 - V_{ref}) / 5 + (V_1 - V_{ref}) / 10 = 4 + 2$$

$$\therefore (V_1 - V_{ref}) = 20 \text{ V}$$

Apply KVL to node 2:

$$(V_2 - V_{ref}) / 5 + (V_2 - V_{ref}) / 10 + 2 = 5$$

$$\therefore (V_2 - V_{ref}) = 10 \text{ V}$$

Apply Ohm's law:


$$I_1 = (V_1 - V_{ref}) / 5 = 4 \text{ A}$$

$$I_2 = (V_1 - V_{ref}) / 10 = 2 \text{ A}$$

$$I_3 = (V_2 - V_{ref}) / 10 = 1 \text{ A}$$

$$I_4 = (V_2 - V_{ref}) / 5 = 2 \text{ A}$$

Q6. Problem 3.5: (Using Nodal Analysis)

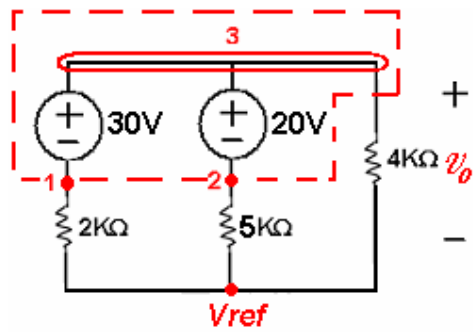

Apply KCL at supernode:

$$(V_1 - V_{ref}) / 2\text{k}\Omega + (V_2 - V_{ref}) / 5\text{k}\Omega + (V_3 - V_{ref}) / 4\text{k}\Omega = 0$$

$$10V_1 + 4V_2 + 5V_3 - 19V_{ref} = 0 \quad \text{--- (1)}$$


$$V_3 - V_1 = 30 \quad \text{--- (2)}$$

$$V_3 - V_2 = 20 \quad \text{--- (3)}$$

Substitute eqn 2 and 3 into eqn 1, we'll get

$$\therefore V_3 - V_{ref} = V_o = 20\text{V}$$

Q7. Problem 3.6: (Using Nodal Analysis)

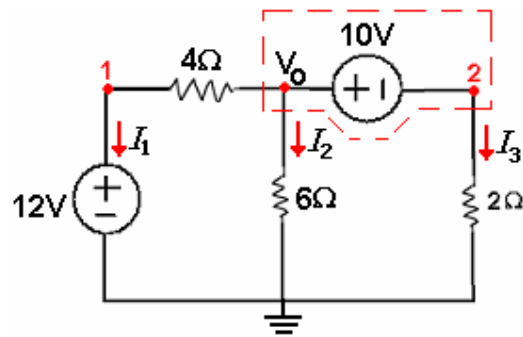

$$V_1 = 12\text{V}$$

Apply KCL at the supernode:

$$(V_o - 12) / 4 + V_o / 6 + V_2 / 2 = 0$$


$$3V_o - 36 + 2V_o + 6V_2 = 0$$

$$5V_o + 6V_2 = 36 \quad \text{--- (1)}$$

$$V_o - V_2 = 10 \quad \text{--- (2)}$$

$$6 \times \text{(2)} + \text{(1)} : 11V_o = 96 \quad \Rightarrow \quad \therefore V_o = 8.73 \text{ V}$$

Q8. Problem 3.11: (Using Nodal Analysis)

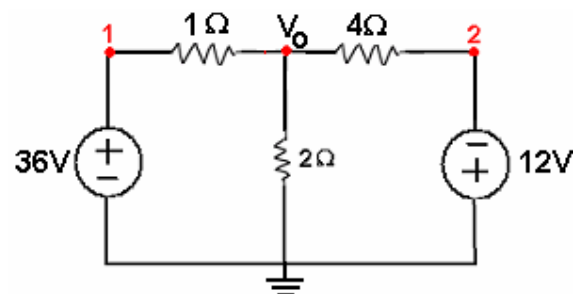

$$V_1 = 36\text{V}$$

$$V_2 = -12\text{V}$$

Apply KCL at the supernode:

$$(V_o - 36) / 1 + (V_o + 12) / 4 + V_o / 2 = 0$$

$$4V_o - 144 + V_o + 12 + 2V_o = 0$$


$$7V_o = 132 \quad \Rightarrow \quad \therefore V_o = 18.86\text{V}$$

Power dissipated in 1Ω - resistor: $P = (V_o - 36)^2 / R = (18.86 - 36)^2 / 1 = 293.9 \text{ W}$

Power dissipated in 2Ω - resistor: $P = V_o^2 / R = 18.86^2 / 2 = 177.8 \text{ W}$

Power dissipated in 4Ω - resistor: $P = (V_o + 12)^2 / R = (18.86 + 12)^2 / 4 = 238 \text{ W}$

Q9. Problem 3.13: (Using Nodal Analysis)

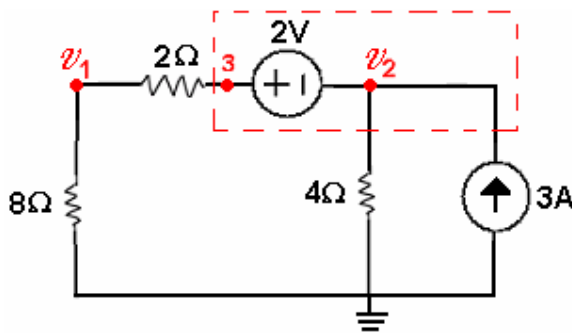

Apply KCL at supernode:

$$(V_3 - V_1) / 2 + V_2 / 4 = 3$$

$$V_3 - V_2 = 2$$


Applied KCL at node 1:

$$(V_1 - V_3) / 2 + V_1 / 8 = 0$$

Solve the three equations simultaneously, we'll get:

$$V_1 = 8 \text{ V and } V_2 = 8 \text{ V}$$

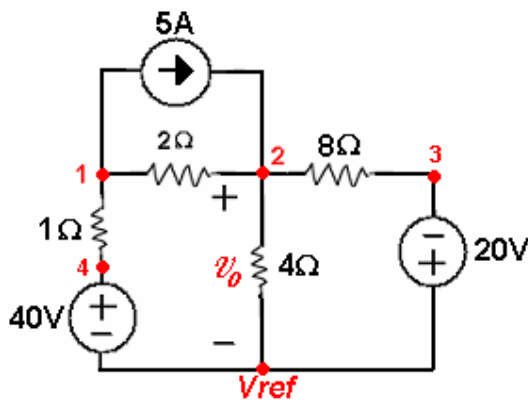Q10. Problem 3.14: (Using Nodal Analysis)



$$V_4 - V_{ref} = 40\text{V}$$

$$V_{ref} - V_3 = 20\text{V}$$

Apply KCL at node 1:


$$(V_1 - V_4) / 1 + (V_1 - V_2) / 2 + 5 = 0$$

Apply KCL at node 2:

$$(V_2 - V_1) / 2 + (V_2 - V_{ref}) / 4 + (V_2 - V_3) / 8 = 5$$

Solve simultaneously, $\Rightarrow \therefore V_2 - V_{ref} = V_o = 18.24$

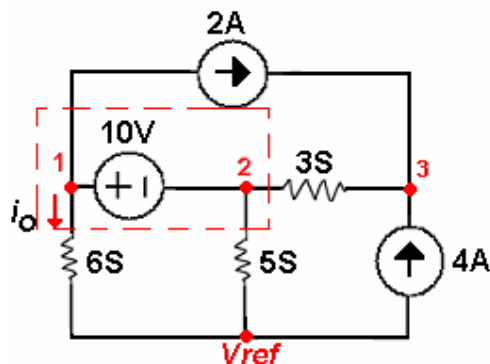Q11. Problem 3.15: (Using Nodal Analysis)



Apply KCL at node 3:

$$3(V_3 - V_2) = 4 + 2 = 6$$

$$V_1 - V_2 = 10$$

Apply KCL at supernode:

$$6(V_1 - V_{ref}) + 5(V_2 - V_{ref}) + 3(V_2 - V_3) + 2 = 0$$

Solve the equations simultaneously, we'll get:

$$\therefore V_1 - V_{ref} = 4.91 \text{ V}$$

$$V_2 - V_{ref} = -5.09 \text{ V}$$

$$V_3 - V_{ref} = -3.09 \text{ V}$$

$$\therefore i_o = 5 \cdot (V_2 - V_{ref}) = 29.45 \text{ A}$$


Power dissipated in each resistor:

$$\therefore P_{6S\text{-resistor}} = 6 \cdot (V_1 - V_{ref})^2 = 144.6 \text{ W}$$

$$P_{5S\text{-resistor}} = 5 \cdot (V_2 - V_{ref})^2 = 129.6 \text{ W}$$

$$P_{3S\text{-resistor}} = 3 \cdot (V_2 - V_3)^2 = 12 \text{ W}$$

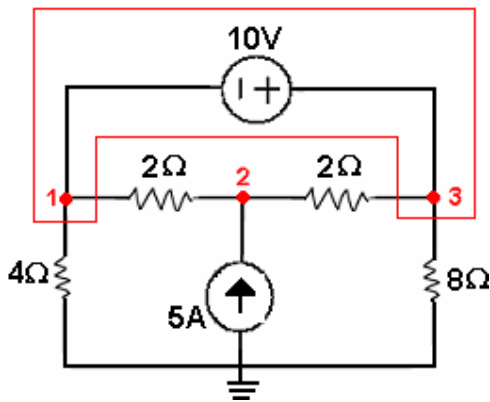Q12. Problem 3.18: (Using Nodal Analysis)



Apply KCL at supernode:

$$(V_3 - V_2)/2 + (V_1 - V_2)/2 + V_1/4 + V_3/8 = 0$$

$$(V_3 - V_1) = 10 \text{ V}$$

Apply KCL at node 2:

$$(V_2 - V_3)/2 + (V_2 - V_1)/2 = 5$$


Solve simultaneously, we'll get:

$$V_1 = 10 \text{ V}$$

$$V_2 = 20 \text{ V}$$

$$V_3 = 20 \text{ V}$$

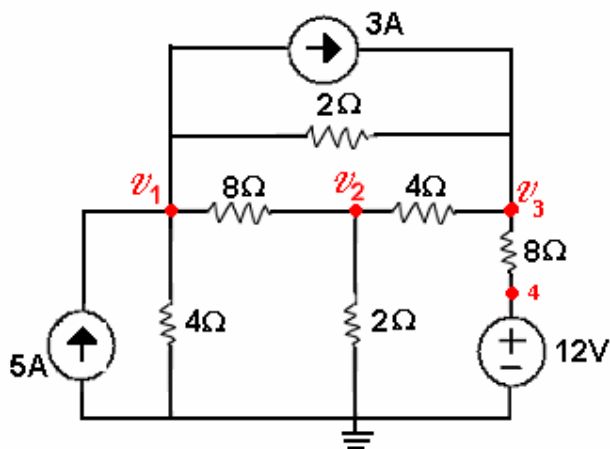Q13. Problem 3.19: (Using Nodal Analysis)



Apply KCL at node 1:

$$V_1/4 + (V_1 - V_2)/8 + (V_1 - V_3)/2 + 3 = 5$$

Apply KCL at node 2:

$$(V_2 - V_1) / 8 + (V_2 - V_3) / 4 + V_2 / 2 = 0$$

Apply KCL at node 3:

$$(V_3 - V_1) / 2 + (V_3 - V_2) / 4 + (V_3 - V_4) / 8 = 3$$

Voltage at node 4:

$$V_4 = 12 \text{ V}$$


Solve the equations simultaneously, we'll get:

$$\therefore V_1 = 10 \text{ V}$$

$$V_2 = 4.933 \text{ V}$$

$$V_3 = 12.267 \text{ V}$$

Q14. Problem 3.20:

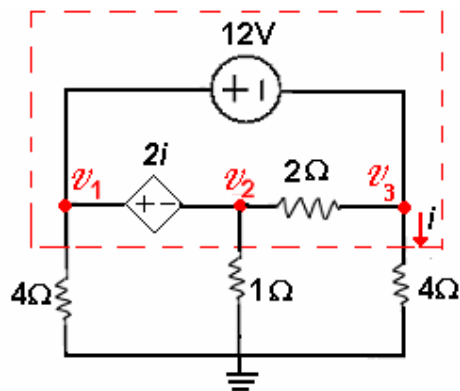

Apply KCL at supernode:

$$V_1 / 4 + V_2 / 1 + V_3 / 4 = 0$$

$$V_1 - V_3 = 12$$

$$V_1 - V_2 = 2i$$

$$V_3 / 4 = i$$


Solve simultaneously, we'll get:

$$\therefore V_1 = -3 \text{ V}$$

$$V_2 = 4.5 \text{ V}$$

$$V_3 = -15 \text{ V}$$

Q15. Problem 3.25: (Using Mesh Analysis)

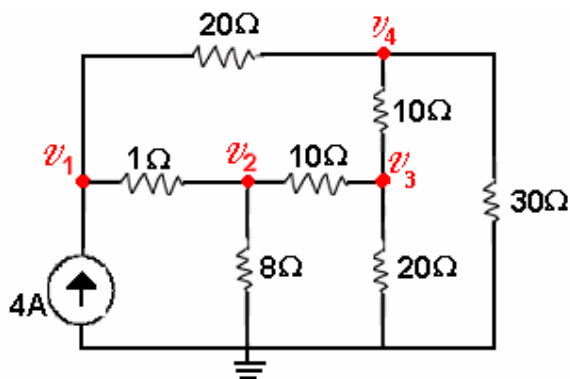

Apply KCL at node 1:

$$(V_1 - V_2) / 1 + (V_1 - V_4) / 20 = 4$$

Apply KCL at node 2:

$$(V_2 - V_1) / 1 + (V_2 - V_3) / 10 + V_2 / 8 = 0$$

Apply KCL at node 31:

$$(V_3 - V_2) / 10 + (V_3 - V_4) / 10 + V_3 / 20 = 0$$

Apply KCL at node 4:

$$(V_4 - V_1) / 20 + (V_4 - V_3) / 10 + V_4 / 30 = 0$$

Solve equations simultaneously, we'll get:


$$\therefore V_1 = 25.52 \text{ V}$$

$$V_2 = 22.05 \text{ V}$$

$$V_3 = 14.842 \text{ V}$$

$$V_4 = 15.055 \text{ V}$$

Q16. Problem 3.35:

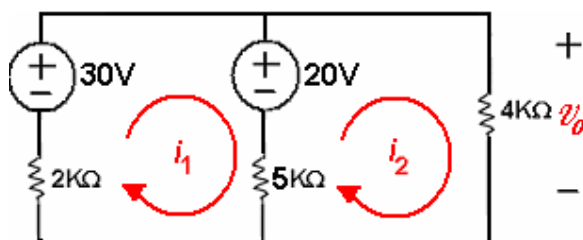

Apply KVL to mesh 1:

$$-30 + 20 + (i_1 - i_2) \cdot (5k) + i_1 \cdot (2k) = 0$$

Apply KVL to mesh 2:

$$-20 + (i_2 - i_1) \cdot (5k) + i_2 \cdot (4k) = 0$$


Solve equations simultaneously, we'll get:

$$\therefore i_1 = 5 \text{ mA}$$

$$i_2 = 5 \text{ mA}$$

$$\therefore V_o = 4k\Omega \times i_2 = 20 \text{ V}$$

Q17. Problem 3.36: (Using Mesh Analysis)

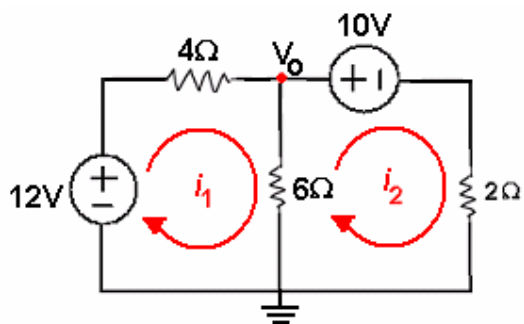

Apply KVL to mesh 1:

$$-12 + (i_1 - i_2) \cdot 6 + i_1 \cdot 4 = 0$$

Apply KVL to mesh 2:

$$10 + (i_2 - i_1) \cdot 6 + i_2 \cdot 2 = 0$$


Solve equations simultaneously, we'll get:

$$\therefore i_1 = 0.818 \text{ A}$$

$$i_2 = -0.636 \text{ A}$$

$$\therefore V_o = 6 \cdot (i_1 - i_2) = 8.73 \text{ V}$$

Q18. Problem 3.44: (Using Mesh Analysis)

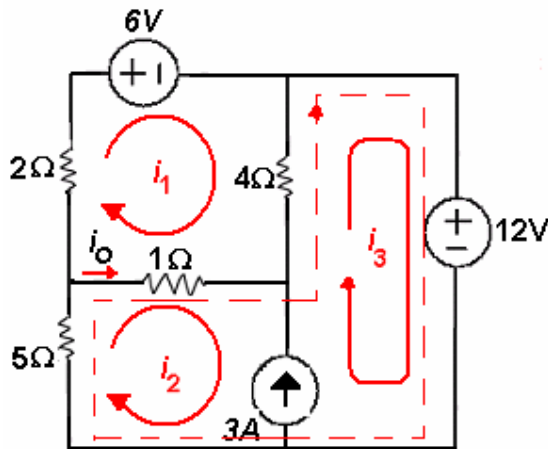

Apply KVL to supermesh:

$$12 + i_2 \cdot 5 + (i_2 - i_1) \cdot 1 + (i_3 - i_1) \cdot 4 = 0$$

Apply KVL to mesh 1:

$$6 + (i_1 - i_3) \cdot 4 + (i_1 - i_2) \cdot 1 + i_1 \cdot 2 = 0$$

$$i_3 - i_2 = 3$$

Solve simultaneously, we'll get:


$$\therefore i_1 = -1.33 \text{ A}$$

$$i_2 = -3.07 \text{ A}$$

$$i_3 = -0.07 \text{ A}$$

$$\therefore i_o = i_2 - i_1 = -1.73 \text{ A}$$

Q19. Problem 3.51: (Using Mesh Analysis)

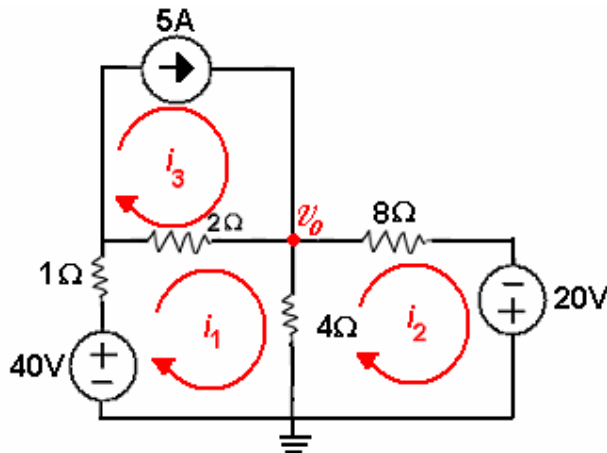

Apply KVL to mesh 1:

$$-40 + i_1 \cdot 1 + (i_1 - i_3) \cdot 2 + (i_1 - i_2) \cdot 4 = 0$$

Apply KVL to mesh 2:

$$-20 + (i_2 - i_1) \cdot 4 + i_2 \cdot 8 = 0$$

$$i_3 = 5 \text{ A}$$


Solve simultaneously, we'll get:

$$\therefore i_1 = 10 \text{ A}$$

$$i_2 = 5 \text{ A}$$

$$\therefore V_o = (i_1 - i_2) \cdot 4 = 20 \text{ V}$$

Q20. Problem 3.56: (Using Mesh Analysis)

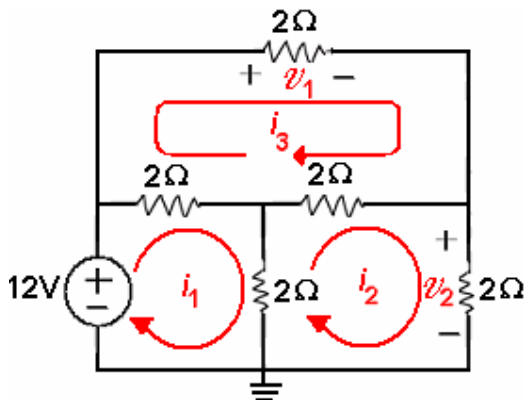

Apply KVL to mesh 1:

$$-12 + (i_1 - i_3) \cdot 2 + (i_1 - i_2) \cdot 2 = 0$$

Apply KVL to mesh 2:

$$(i_2 - i_3) \cdot 2 + (i_2 - i_1) \cdot 2 + i_2 \cdot 2 = 0$$

Apply KVL to mesh 3:

$$(i_3 - i_2) \cdot 2 + (i_3 - i_1) \cdot 2 + i_3 \cdot 2 = 0$$

Solve simultaneously, we'll get:

$$\therefore i_1 = 6 \text{ A}$$


$$i_2 = 3 \text{ A}$$

$$i_3 = 3 \text{ A}$$

Therefore, $V_1 = i_3 \cdot 2 = 6 \text{ V}$

$$V_2 = i_2 \cdot 2 = 6 \text{ V}$$

Q21. Problem 3.68: (Using Mesh Analysis)

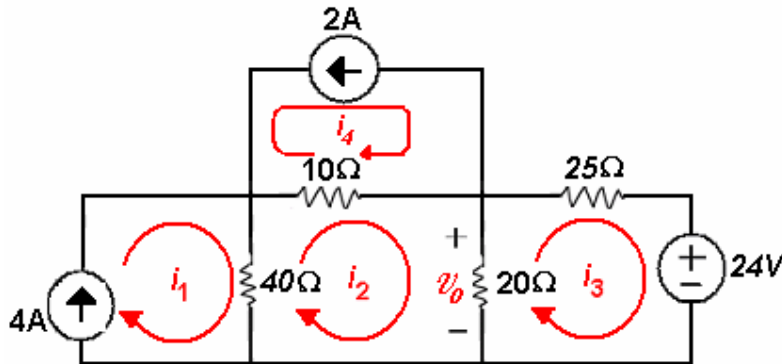

$$i_1 = 4 \text{ A}$$

$$i_4 = -2 \text{ A}$$

Apply KVL to mesh 2:

$$(i_2 - i_3) \cdot 20 + (i_2 - i_1) \cdot 40 + (i_2 - i_4) \cdot 10 = 0$$

Apply KVL to mesh 3:

$$(i_3 - i_2) \cdot 20 + i_3 \cdot 25 + 24 = 0$$

Solve simultaneously, we'll get:


$$\therefore i_2 = 2.12 \text{ A}$$

$$i_3 = 0.41 \text{ A}$$

$$\text{Therefore, } V_o = (i_2 - i_3) \cdot 20 = 34.2 \text{ V}$$

Q22. Problem 4.33: (Using Thevenin's Theorem)

(a)

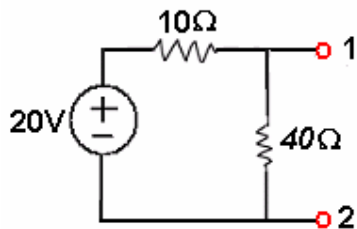


Voltage divider:

$$V_{th} = (40\Omega / (10\Omega + 40\Omega)) \times 20\text{V} = 16\text{V}$$

To find R_{th} , replacing the voltage source with a short circuit: $R_{th} = 40\Omega \parallel 10\Omega = 8\Omega$

(b)

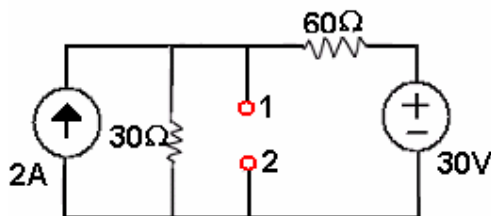

Apply KCL at terminal 1:


$$V_{th} / 30\Omega + (V_{th} - 30) / 60 = 2$$

$$\therefore V_{th} = 50\text{V}$$

To find R_{th} , replacing the voltage source with a short circuit and a current source with an open circuit:

$$\therefore R_{th} = 30\Omega \parallel 60\Omega = 20\Omega$$

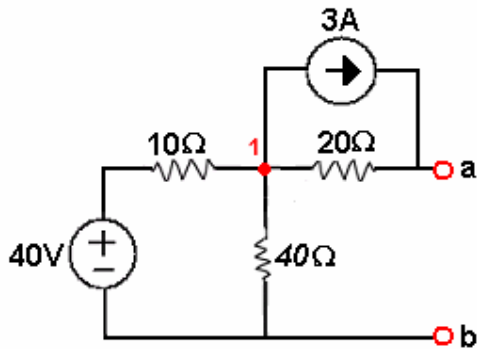Q23. Problem 4.34: (Using Thevenin's Theorem)



To find V_{th} , apply KCL at node 1:

$$(V_1 - 40) / 10 + V_1 / 40 + (V_1 - V_{th}) / 20 + 3 = 0$$

$$7V_1 - 2V_{th} = 40$$

Apply KCL at terminal a:

$$(V_{th} - V_1) / 20 = 3$$


Solve equations simultaneously, we'll get:

$$\therefore V_{th} = 32V$$

To find R_{th} , replacing the voltage source with a short circuit and a current source with an open circuit:

$$\therefore R_{th} = 20\Omega + 40\Omega \parallel 10\Omega = 28\Omega$$

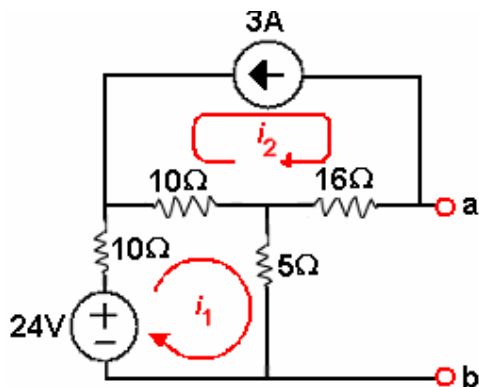Q24. Problem 4.39: (Using Thevenin's Theorem)



Apply KVL to mesh1:

$$-24 + i_1 \cdot 10 + i_1 \cdot 5 + (i_1 - i_2) \cdot 10 = 0$$

$$i_2 = -3 \text{ A}$$

Solve simultaneously, we'll get:


$$\therefore i_1 = -0.24 \text{ A}$$

$$\therefore V_{th} = i_2 \cdot 16 + i_1 \cdot 5 = -49.2 \text{ V}$$

To find R_{th} , replacing the voltage source with a short circuit and a current source with an open circuit:

$$\therefore R_{th} = 16\Omega + (5\Omega \parallel (10\Omega + 10\Omega)) = 20\Omega$$

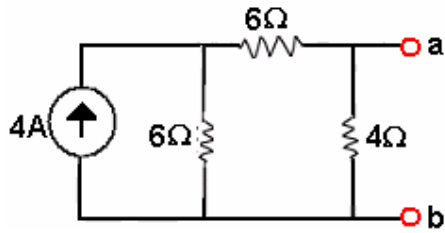Q25. Problem 4.45: (Using Norton's Theorem)




To find I_N , short terminals a and b:

$$\therefore I_N = 2A$$

To find R_N , replacing the current source with an open circuit:

$$\therefore R_N = 4\Omega \parallel (6\Omega + 6\Omega) = 3\Omega$$

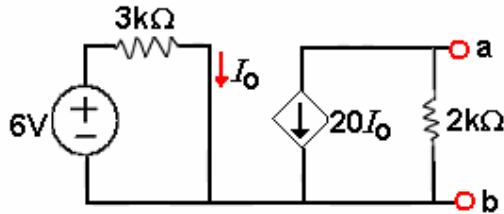Q26. Problem 4.52: (Using Thevenin's Theorem)




$$I_o = 6V / 3k\Omega = 2mA$$

$$V_{th} = -20I_o \times (2k\Omega) = -80V$$

To find R_{TH} , replacing the voltage source with a short circuit:

$$\therefore R_{th} = 2k\Omega$$

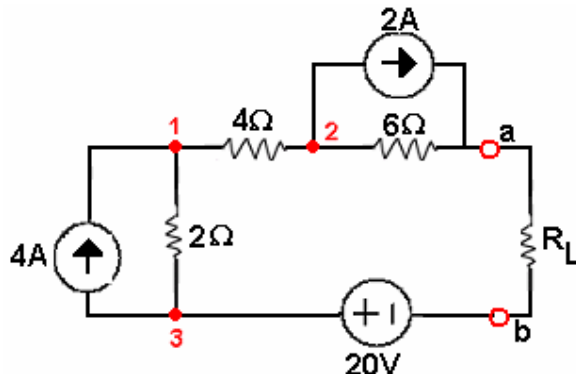Q27. Problem 4.72: (Using Thevenin's Theorem)



(a) To find V_{th} :

Apply KCL at node a:

$$I_{6\Omega}, \text{ from node a to node 2} = 2A$$

Apply KCL at node 2:

$$I_{4\Omega} = 0A$$

Apply KCL at node 1:

$$I_{2\Omega}, \text{ from node 1 to node 3} = 4A$$

$$\therefore V_{th} = 12 + 8 + 20 = 40V$$

To find R_{th} , replacing the voltage source with a short circuit and a current source with an open circuit:

$$\therefore R_{th} = 2 + 4 + 6 = 12\Omega$$


(b) When $R_L = 8\Omega$:

$$\text{Current in } R_L = 40V / (12+8) = 2A$$

(c) To have maximum power deliverable, $R_L = R_{th} = 12\Omega$

$$(d) P_{max} = V_{th}^2 / 4R_{th} = (40)^2 / (4 \times 12) = 33.3 W$$

Q28. Problem 4.75

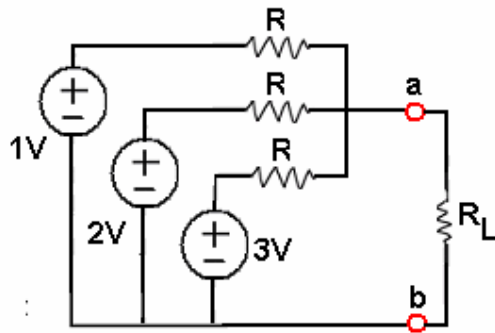

To find R_{th} , replacing the voltage sources with short circuits:

$$\therefore R_{th} = R \parallel R \parallel R = R / 3$$

To have maximum power, $R_L = R_{th} = R/3$

Apply KCL at node a:

$$(V_{th} - 1)/R + (V_{th} - 2)/R + (V_{th} - 3)/R = 0$$


$$\therefore V_{th} = 2V$$

$$\therefore \text{To have } P_{max} = 3 \text{ mW, we'll set } P_{max} = V_{th}^2 / 4R_{th} = (2)^2 / (4 \times R/3) = (3/R) = 3 \text{ mW}$$

$$\therefore R = 1k\Omega$$

Q29. Problem 4.94:

(a)

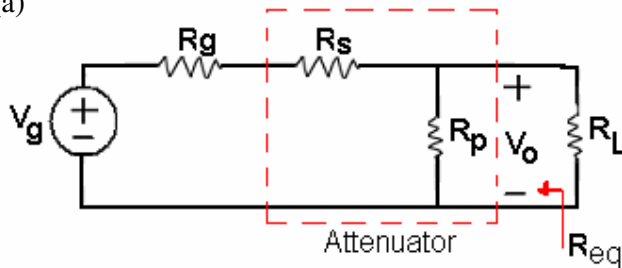

$$\text{Given: } V_o / V_g = 0.125$$

$$R_{eq} = R_{th} = R_g = 100 \Omega$$

To find R_{th} , replacing the voltage source with a short circuit:

$$R_{th} = R_p \parallel (R_s + R_g) = 100$$

$$V_o = R_p \cdot V_g / (R_s + R_p + R_g)$$

$$V_o / V_g = R_p / (R_s + R_p + R_g) = 0.125$$

Solve the equations simultaneously, we'll get:

$$\therefore R_p = 114.3 \Omega$$

$$R_s = 700 \Omega$$

(b) Given $R_g = 50 \Omega$ and $V_g = 12V$

$$I = V_{th} / (R_{th} + R_L) = V_o / (R_{th} + R_L) = 0.125V_g / (R_{th} + R_L) = 0.01 \text{ A}$$