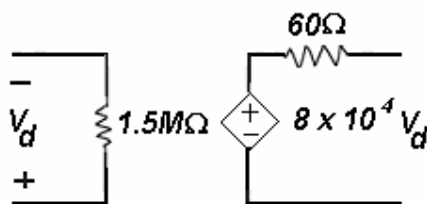


EECS70A / CSE 70A Network Analysis I  
 Prof. Peter Burke


Homework # 3 solution

Q1. Problem 5.1:



- (a) Input resistance =  $1.5 \text{ M}\Omega$
- (b) Output resistance =  $60 \Omega$
- (c) Voltage gain =  $8 \times 10^4 = 98 \text{ dB}$

Q2. Problem 5.10:

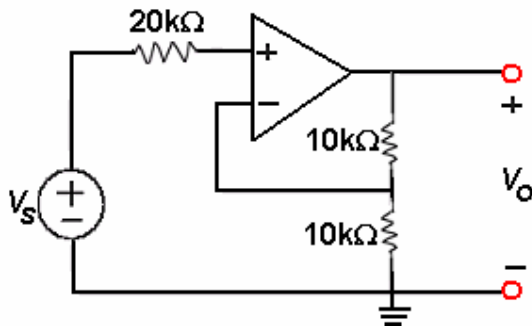

For ideal op-amp:

No currents into the input terminals.


$$\therefore V_+ = V_- = V_s$$

Voltage divider:

$$V_- = 10\text{K}\Omega / (10\text{K}\Omega + 10\text{K}\Omega) V_o$$

$$\therefore V_o / V_s = 2$$

Q3. Problem 5.25:

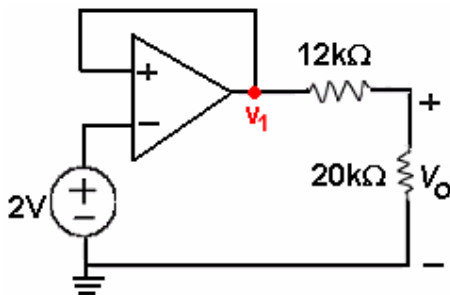


$$V_+ = V_- = V_1 = 2\text{V}$$

Voltage divider:

$$V_o = 20\text{K}\Omega / (20\text{K}\Omega + 12\text{K}\Omega) V_1$$

$$\therefore V_o = 1.25 \text{ V}$$

Q4. Problem 5.34:

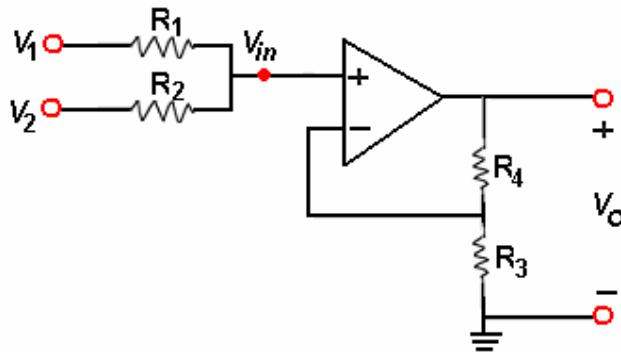

$$V_+ = V_- = V_{in}$$

Voltage divider:

$$V_- = R_3 V_o / (R_3 + R_4)$$

$$\therefore V_o = (1 + R_4 / R_3) V_{in}$$


Voltage divider:

$$V_{in} - V_2$$

$$= R_2(V_1 - V_2) / (R_1 + R_2)$$

$$\therefore V_o = (1 + R_4 / R_3) V_{in} = (1 + R_4 / R_3) (R_2 V_1 + R_1 V_2) / (R_1 + R_2)$$

Q5. Problem 5.84:

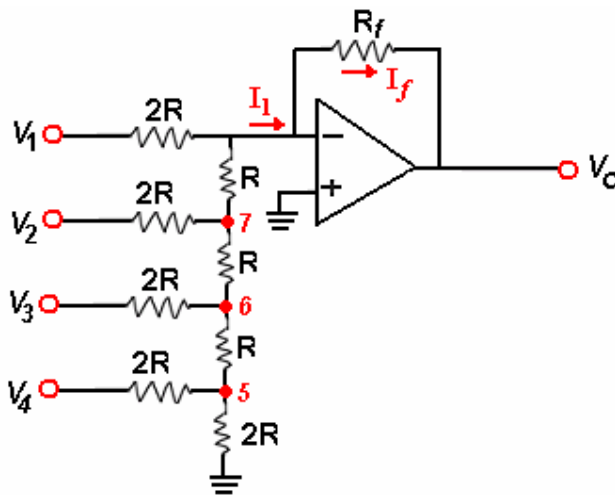

(a) Use superposition to find  $I_1$ :

We'll find  $I_1$  due to  $V_1$ , hence we will set rest of the voltages to zero.

$$I_1 = V_1 / 2R$$

Then we'll find  $I_1$  due to  $V_2$ , hence we will set rest of the voltages to zero.

$$I_1 = V_2 / 4R$$

Then we'll find  $I_1$  due to  $V_3$ , hence we will set rest of the voltages to zero.

$$I_1 = V_3 / 8R$$

Then we'll find  $I_1$  due to  $V_4$ , hence we will set rest of the voltages to zero.

$$I_1 = V_4 / 16R$$

Therefore, total  $I_1 = V_1 / 2R + V_2 / 4R + V_3 / 8R + V_4 / 16R$

Apply KCL at the inverting input terminal:

$$I_1 = -V_o / R_f$$

$$\therefore -V_o = R_f (V_1 / 2R + V_2 / 4R + V_3 / 8R + V_4 / 16R)$$

(b)  $R_f = 12 \text{ k}\Omega$  and  $R = 10 \text{ k}\Omega$

For  $[V_1 \ V_2 \ V_3 \ V_4] = [1 \ 0 \ 1 \ 1]$ ,

$$\begin{aligned} -V_o &= R_f (V_1 / 2R + V_2 / 4R + V_3 / 8R + V_4 / 16R) \\ &= (12 \times 10^3) / (10 \times 10^3) (1/2 + 0/4 + 1/8 + 1/16) \end{aligned}$$

$$\therefore |V_o| = 0.825 \text{ V}$$

For  $[V_1 \ V_2 \ V_3 \ V_4] = [0 \ 1 \ 0 \ 1]$

$$\begin{aligned} -V_o &= R_f (V_1 / 2R + V_2 / 4R + V_3 / 8R + V_4 / 16R) \\ &= (12 \times 10^3) / (10 \times 10^3) (0/2 + 1/4 + 0/8 + 1/16) \end{aligned}$$

$$\therefore |V_o| = 0.375 \text{ V}$$