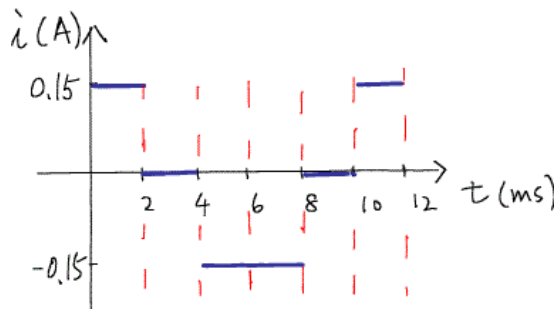


EECS70A / CSE 70A Network Analysis I  
 Prof. Peter Burke

Homework # 4 solution

Q1. Problem 6.6:


$$i = C (dV/dt)$$




Q2. Problem 6.11:

$$i = C (dV/dt)$$

$$\Rightarrow V = (1 / C) \int i(t) dt$$

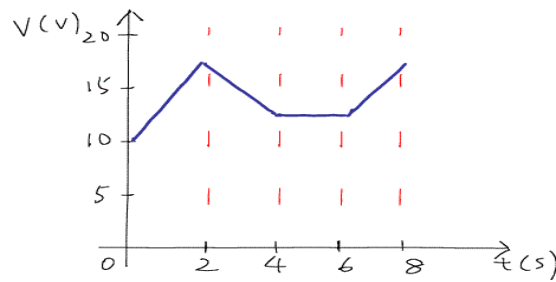

Q3. Problem 6.18:

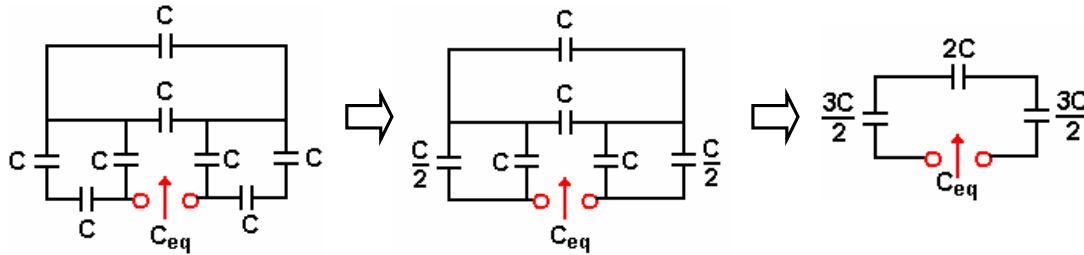


All capacitors are  $C = 4 \mu\text{F}$ .

$$\frac{1}{C_{eq}} = \frac{1}{2C} + \frac{2}{3C} + \frac{2}{3C} \quad \Rightarrow \quad \therefore C_{eq} = \frac{6C}{11} = 2.18 \mu\text{F}$$


Q4. Problem 6.42:

$$V = L (di/dt)$$

$$\Rightarrow I = (1 / L) \int V dt$$

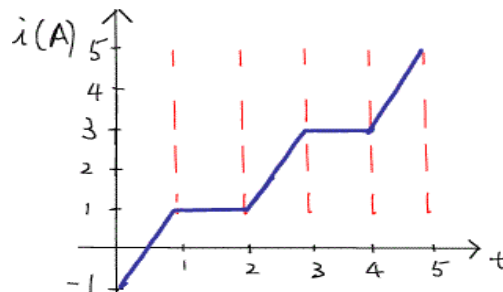


Q5. Problem 6.49:

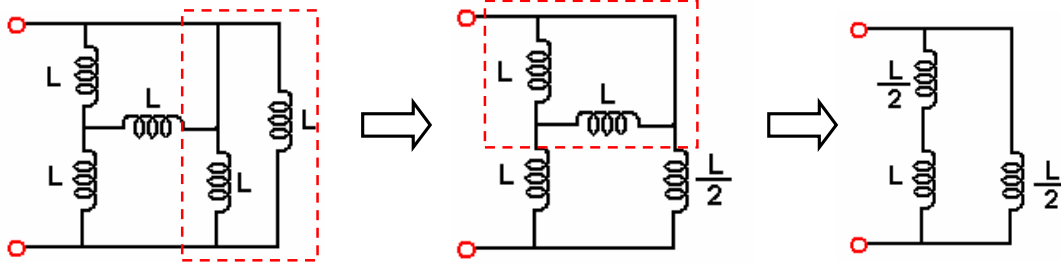

$$\therefore L_{eq} = 3L / 8 = 3.75 \text{ mH}$$

Q6. Problem 6.69:

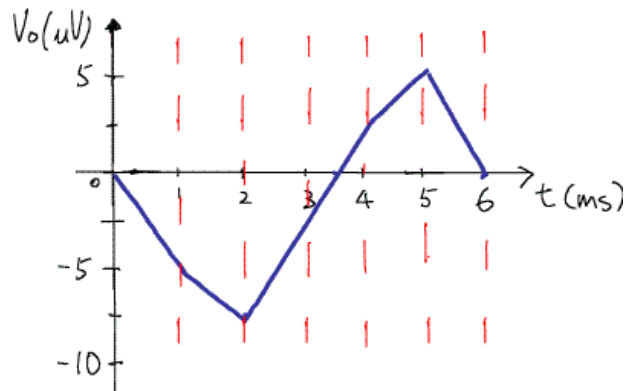

$$V_o(t) - V_o(0) = (-1/RC) \int V_i(t) dt$$

Q7. Problem 6.74:

Apply KCL at inverting terminal:

$$I = C d(V_i - V_o) / dt = -V_o / 20K\Omega$$

$$\Rightarrow V_o = - (0.01\mu F)(20K\Omega) dV_i / dt$$

$$= - (2 \times 10^{-4}) dV_i / dt$$

