

1	2	3	4	5	Total
/20	/20	/20	/20	/20	/100


**DO NOT BEGIN THE EXAM
UNTIL YOU ARE TOLD TO
DO SO.**

PROBLEM ONE: (20 points)

In a certain application, the circuit in the figure below must be designed to meet these two criteria:

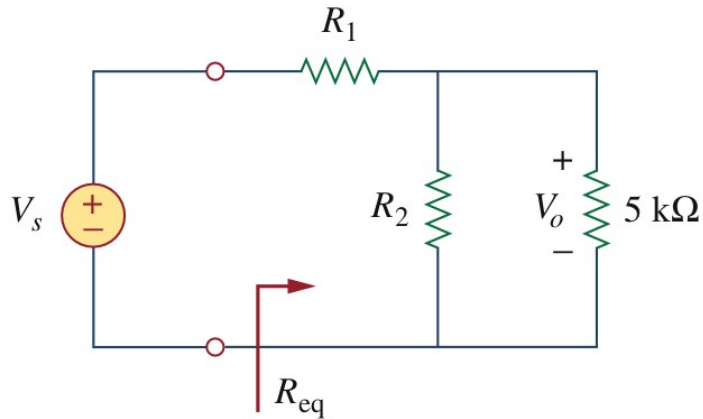- (a) $V_o / V_s = 0.05$ (b) $R_{eq} = 40 \text{ k}\Omega$

If the load resistor $5 \text{ k}\Omega$ is fixed, find R_1 and R_2 to meet the criteria.




PROBLEM TWO:

A load is connected to a network. At the terminals to which the load is connected, $R_{Th} = 10 \Omega$ and $V_{Th} = 40 \text{ V}$. Find the maximum possible power supplied to the load.

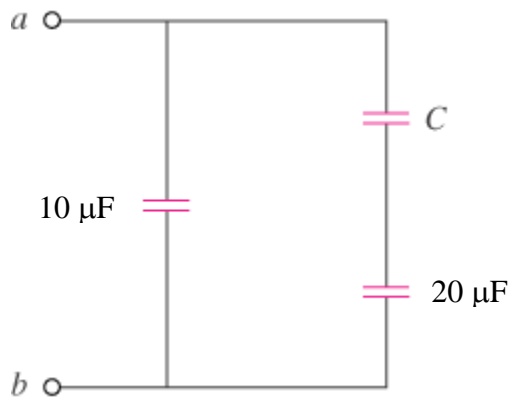
PROBLEM THREE:

The equivalent capacitance at terminals a - b in the circuit in the figure below is $20 \mu\text{F}$. Calculate the value of C .



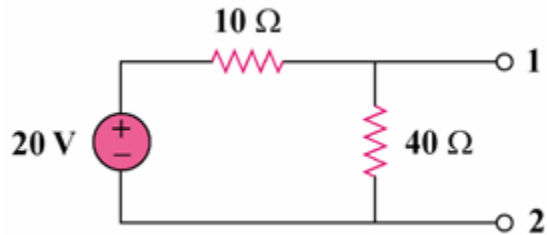PROBLEM FOUR:

Determine R_{Th} and V_{Th} at terminals 1-2 of the circuits shown below.



PROBLEM FIVE:

Obtain v_o for the op amp circuit shown below.

