

EECS70A / CSE 70A Network Analysis I
Prof. Peter Burke

Final solution

Problem 1:

A) A linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source V_{Th} in series with a resistor R_{Th} , where V_{Th} is the open-circuit voltage at the terminals and R_{Th} is the input or equivalent resistance at the terminals when the independent sources are turned off.

B) A linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source I_N in parallel with a resistor R_N , where I_N is the short-circuit current through the terminals and R_N is the input or equivalent resistance at the terminals when the independent sources are turned off.

Grading criteria: 3 pts for equivalent circuit with a resistor and a source
5 pts for mentioning R_{Th} and V_{Th} in series
5 pts for mentioning R_N and I_N in parallel

Problem 2:

Complete response = transient response + steady-state response

A complete response consists of a transient response (temporary response) and a steady-state response (permanent response). The transient response is the circuit's temporary response that will die out with time. And the steady-state response is the behavior of the circuit a long time after an external excitation is applied.

Grading criteria: 5 pts for mentioning transient and steady-state responses for the complete response
5 pts for temporary responses for the transient response

Problem 3:

$$s^2 + 4s + 8 = 0 \text{ leads to } s = \frac{-4 \pm \sqrt{16 - 32}}{2} = -2 \pm j2$$

$$v(t) = V_s + (A_1 \cos 2t + A_2 \sin 2t)e^{-2t}$$

$$8V_s = 24 \text{ means that } V_s = 3$$

$$v(0) = 0 = 3 + A_1 \text{ leads to } A_1 = -3$$

$$dv/dt = -2(A_1 \cos 2t + A_2 \sin 2t)e^{-2t} + (-2A_1 \sin 2t + 2A_2 \cos 2t)e^{-2t}$$

$$0 = dv(0)/dt = -2A_1 + 2A_2 \text{ or } A_2 = A_1 = -3$$

$$v(t) = \underline{\underline{[3 - 3(\cos 2t + \sin 2t)e^{-2t}] \text{ volts}}}$$

Grading criteria: 5 pts for correct characteristic eq. with correct roots

5 pts for choosing a correct type of solution

15 pts showing correct 2nd order circuit process without including V_s

Problem 4:

For $t < 0$, the equivalent circuit is as shown below.

$$v(0) = -12V \text{ and } i(0) = 12/2 = 6A$$

For $t > 0$, we have a series RLC circuit.

$$\alpha = R/(2L) = 2/(2 \times 0.5) = 2$$

$$\omega_0 = 1/\sqrt{LC} = 1/\sqrt{0.5 \times 1/4} = 2\sqrt{2}$$

Since α is less than ω_0 , we have an under-damped response.

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{8 - 4} = 2$$

$$i(t) = (A\cos 2t + B\sin 2t)e^{-2t}$$

$$i(0) = 6 = A$$

$$di/dt = -2(6\cos 2t + B\sin 2t)e^{-2t} + (-2 \times 6\sin 2t + 2B\cos 2t)e^{-2t}$$

$$di(0)/dt = -12 + 2B = -(1/L)[Ri(0) + v_C(0)] = -2[12 - 12] = 0$$

$$\text{Thus, } B = 6 \quad \text{and} \quad i(t) = \underline{\underline{6\cos 2t + 6\sin 2t}}e^{-2t} \underline{\underline{A}}$$

Grading criteria: 5 pts for correct equivalent circuit and initial values for $t < 0$

10 pts for correct equivalent circuit and characteristic eq. and variables for $t > 0$

3 pts for correct solution for $i(t)$

5 pts for correct process to get $i(t)$ using initial value and derivative of $i(t)$

Problem 5:

$$\begin{aligned} \mathbf{Z}_{in} &= j\omega L \parallel \left(R + \frac{1}{j\omega C} \right) \\ \mathbf{Z}_{in} &= \frac{j\omega L \left(R + \frac{1}{j\omega C} \right)}{R + j\omega L + \frac{1}{j\omega C}} = \frac{\frac{L}{C} + j\omega L R}{R + j \left(\omega L - \frac{1}{\omega C} \right)} \\ \mathbf{Z}_{in} &= \frac{\left(\frac{L}{C} + j\omega L R \right) \left(R - j \left(\omega L - \frac{1}{\omega C} \right) \right)}{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2} \end{aligned}$$

To have a resistive impedance, $\text{Im}(\mathbf{Z}_{in}) = 0$. Hence,

$$\omega L R^2 - \left(\frac{L}{C} \right) \left(\omega L - \frac{1}{\omega C} \right) = 0$$

$$\omega R^2 C = \omega L - \frac{1}{\omega C}$$

$$\omega^2 R^2 C^2 = \omega^2 LC - 1$$

$$L = \frac{\omega^2 R^2 C^2 + 1}{\omega^2 C}$$

Now we can solve for L.

$$L = R^2 C + 1/(\omega^2 C)$$

$$= (200^2)(50 \times 10^{-9}) + 1/((2\pi \times 50,000)^2(50 \times 10^{-9}))$$

$$= 2 \times 10^{-3} + 0.2026 \times 10^{-3} = \underline{\underline{2.203 \text{ mH}}}$$

Grading criteria: 3 pts for correct ω using $\omega = 2\pi f$

10 pts for showing correct total impedance (Z_T) or (Z_{in}) equation

10 pts for showing imaginary part of total impedance is zero

Problem 6:

$$H(s) = \frac{V_o}{V_i}$$

$$V_o = \frac{2}{10 + 2 + \frac{8}{j\omega}} V_i = \frac{2j\omega}{12j\omega + 8} V_i$$

$$\frac{V_o}{V_i} = \frac{2j\omega}{12j\omega + 8} = \frac{2s}{12s + 8}$$

Grading criteria: 15 pts for correct voltage divider equation

10 pts for correct current for getting V_o using Ohm's law or KVL