

EECS70A / CSE 70A Network Analysis I  
Prof. Peter Burke

Homework # 3 solution

**Chapter 3, Solution 1.**

Let  $V_x$  be the voltage at the node between 1-k $\Omega$  and 4-k $\Omega$  resistors.

$$\frac{9 - V_x}{1k} + \frac{6 - V_x}{4k} = \frac{V_x}{2k} \longrightarrow V_x = 6$$

$$I_x = \frac{V_x}{2k} = \underline{3 \text{ mA}}$$

**Chapter 3, Solution 3.**

Applying KCL to the upper node,

$$10 = \frac{v_0}{10} + \frac{v_0}{20} + \frac{v_0}{30} + 2 + \frac{v_0}{60} \longrightarrow v_0 = \underline{40 \text{ V}}$$

$$i_1 = \frac{v_0}{10} = \underline{4 \text{ A}}, i_2 = \frac{v_0}{20} = \underline{2 \text{ A}}, i_3 = \frac{v_0}{30} = \underline{1.3333 \text{ A}}, i_4 = \frac{v_0}{60} =$$


666.7 mA

**Chapter 3, Solution 6.**

$$i_1 + i_2 + i_3 = 0 \quad \frac{v_2 - 12}{4} + \frac{v_0}{6} + \frac{v_0 - 10}{2} = 0$$

$$\text{or } v_0 = \underline{8.727 \text{ V}}$$

**Chapter 3, Solution 35.**

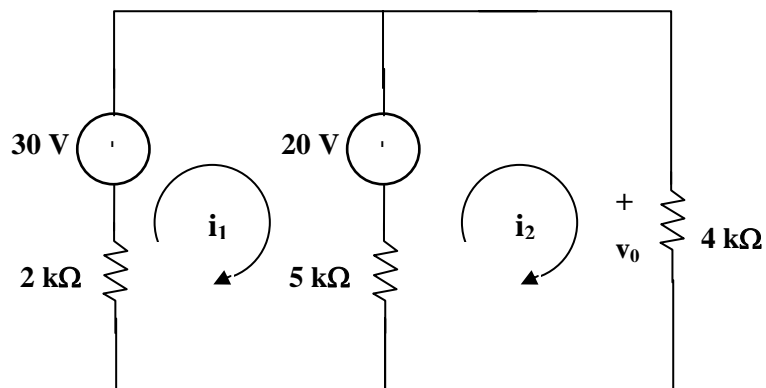

Assume that  $i_1$  and  $i_2$  are in mA. We apply mesh analysis. For mesh 1,

$$-30 + 20 + 7i_1 - 5i_2 = 0 \quad \text{or} \quad 7i_1 - 5i_2 = 10 \quad (1)$$


For mesh 2,

$$-20 + 9i_2 - 5i_1 = 0 \quad \text{or} \quad -5i_1 + 9i_2 = 20 \quad (2)$$

Solving (1) and (2), we obtain,  $i_2 = 5$ .

$$v_0 = 4i_2 = \underline{\underline{20 \text{ volts}}}.$$

### Chapter 3, Solution 36.

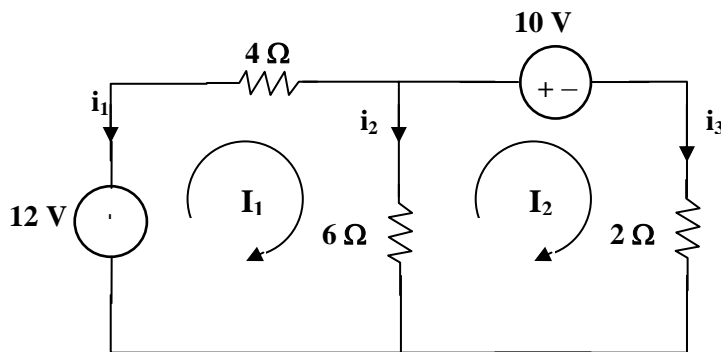

Applying mesh analysis gives,

$$12 = 10I_1 - 6I_2$$

$$-10 = -6I_1 + 8I_2$$

or

$$\begin{bmatrix} 6 \\ -5 \end{bmatrix} = \begin{bmatrix} 5 & -3 \\ -3 & 4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 5 & -3 \\ -3 & 4 \end{vmatrix} = 11, \quad \Delta_1 = \begin{vmatrix} 6 & -3 \\ -5 & 4 \end{vmatrix} = 9, \quad \Delta_2 = \begin{vmatrix} 5 & 6 \\ -3 & -5 \end{vmatrix} = -7$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{9}{11}, \quad I_2 = \frac{\Delta_2}{\Delta} = \frac{-7}{11}$$

$$i_1 = -I_1 = -9/11 = -0.8181 \text{ A}, \quad i_2 = I_1 - I_2 = 10/11 = 1.4545 \text{ A}.$$

$$v_0 = 6i_2 = 6 \times 1.4545 = \underline{\underline{8.727 \text{ V}}}.$$

**Chapter 3, Solution 68.**

$$\begin{bmatrix} 0.125 & -0.1 \\ -0.1 & 0.19 \end{bmatrix} \mathbf{V} = \begin{bmatrix} +4+3 \\ -3+24/25 \end{bmatrix} = \begin{bmatrix} 7 \\ -2.04 \end{bmatrix}$$

Using MATLAB, we get,

```
>> Y=[0.125,-0.1;-0.1,0.19]
```

```
Y =
```

```
    0.1250   -0.1000
   -0.1000    0.1900
```

```
>> I=[7,-2.04]'
```

```
I =
```

```
    7.0000
   -2.0400
```

```
>> V=inv(Y)*I
```

```
V =
```

```
    81.8909
    32.3636
```

Thus,  $V_o = \underline{\underline{32.36 \text{ V}}}$ .

Alternatively, using nodal analysis we get the same answer.

$$\text{Node 1: } -4 + \frac{V_1}{40} + \frac{V_1 - V_0}{10} - 3 = 0$$

$$\text{Node 2: } \frac{V_0}{20} + \frac{V_0 - V_1}{10} + 3 + \frac{V_0 - 24}{25} = 0$$

**Chapter 4, Solution 33.**


$$(a) \quad R_{Th} = 10 \parallel 40 = 400/50 = \underline{\underline{8 \text{ ohms}}}$$

$$V_{Th} = (40/(40 + 10))20 = \underline{\underline{16 \text{ V}}}$$

$$\begin{aligned}
 \text{(b)} \quad R_{Th} &= 30 \parallel 60 = 1800/90 = \underline{\mathbf{20 \text{ ohms}}} \\
 2 + (30 - v_1)/60 &= v_1/30, \quad \text{and} \quad v_1 = V_{Th} \\
 120 + 30 - v_1 &= 2v_1, \quad \text{or} \quad v_1 = 50 \text{ V} \\
 V_{Th} &= \underline{\mathbf{50 \text{ V}}}
 \end{aligned}$$
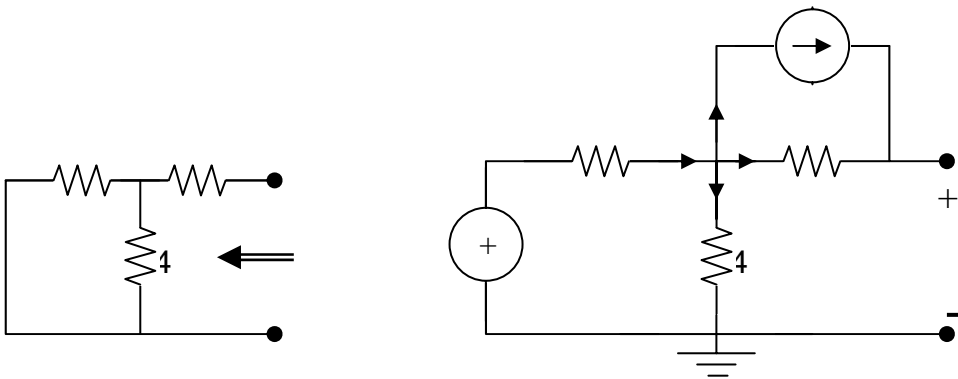
### Chapter 4, Solution 34.

To find  $R_{Th}$ , consider the circuit in Fig. (a).



$$R_{Th} = 20 + 10 \parallel 40 = 20 + 400/50 = \underline{\mathbf{28 \text{ ohms}}}$$

To find  $V_{Th}$ , consider the circuit in Fig. (b).

$$\text{At node 1,} \quad (40 - v_1)/10 = 3 + [(v_1 - v_2)/20] + v_1/40, \quad 40 = 7v_1 - 2v_2 \quad (1)$$

$$\text{At node 2,} \quad 3 + (v_1 - v_2)/20 = 0, \quad \text{or} \quad v_1 = v_2 - 60 \quad (2)$$

$$\text{Solving (1) and (2),} \quad v_1 = 32 \text{ V,} \quad v_2 = 92 \text{ V,} \quad \text{and} \quad V_{Th} = v_2 = \underline{\mathbf{92 \text{ V}}}$$

### Chapter 4, Solution 84.

Let the equivalent circuit of the battery terminated by a load be as shown below.

For open circuit,

$$R_L = \infty, \quad \longrightarrow \quad V_{Th} = V_{oc} = V_L = \underline{\mathbf{10.8 \text{ V}}}$$

$$\text{When} \quad R_L = 4 \text{ ohm,} \quad V_L = 10.5,$$

$$I_L = \frac{V_L}{R_L} = 10.8/4 = 2.7$$

$$\text{But } V_{Th} = V_L + I_L R_{Th} \longrightarrow R_{Th} = \frac{V_{Th} - V_L}{I_L} = \frac{12 - 10.8}{2.7} = \underline{0.4444\Omega}$$

### Chapter 4, Solution 85.

(a) Consider the equivalent circuit terminated with R as shown below.

$$V_{ab} = \frac{R}{R + R_{Th}} V_{Th} \longrightarrow 6 = \frac{10}{10 + R_{Th}} V_{Th} \quad \text{or } 60 + 6R_{Th} = 10V_{Th} \quad (1)$$

where RTh is in k-ohm.

Similarly,

$$12 = \frac{30}{30 + R_{Th}} V_{Th} \longrightarrow 360 + 12R_{Th} = 30V_{Th} \quad (2)$$

Solving (1) and (2) leads to

$$\underline{V_{Th} = 24 \text{ V}, R_{Th} = 30k\Omega}$$

$$(b) \quad V_{ab} = \frac{20}{20 + 30} (24) = \underline{9.6 \text{ V}}$$