

EECS70A / CSE 70A Network Analysis I  
Prof. Peter Burke

Homework # 4 solution

**Chapter 5, Solution 1.**

(a)  $R_{in} = \underline{1.5 \text{ M}\Omega}$

(b)  $R_{out} = \underline{60 \text{ }\Omega}$

(c)  $A = 8 \times 10^4$

Therefore  $A_{dB} = 20 \log 8 \times 10^4 = \underline{98.0 \text{ dB}}$

**Chapter 5, Solution 9.**


- (a) Let  $v_a$  and  $v_b$  be respectively the voltages at the inverting and noninverting terminals of the op amp

$$v_a = v_b = 4V$$

At the inverting terminal,

$$1mA = \frac{4 - v_0}{2k} \longrightarrow v_0 = \underline{2V}$$

(b)

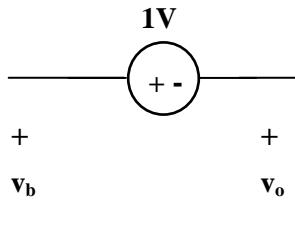

Since  $v_a = v_b = 3V$ ,

$$-v_b + 1 + v_o = 0 \quad v_o = v_b - 1 = \underline{2V}$$

**Chapter 5, Solution 17.**

(a)  $G = \frac{v_o}{v_i} = -\frac{R_2}{R_1} = -\frac{12}{5} = \underline{-2.4}$

$$(b) \quad \frac{v_o}{v_i} = -\frac{80}{5} = \underline{\underline{-16}}$$

$$(c) \quad \frac{v_o}{v_i} = -\frac{2000}{5} = \underline{\underline{-400}}$$

**Chapter 5, Solution 34.**

$$\frac{v_1 - v_{in}}{R_1} + \frac{v_1 - v_{in}}{R_2} = 0 \quad (1)$$

but

$$v_a = \frac{R_3}{R_3 + R_4} v_o \quad (2)$$

Combining (1) and (2),

$$v_1 - v_a + \frac{R_1}{R_2} v_2 - \frac{R_1}{R_2} v_a = 0$$

$$v_a \left( 1 + \frac{R_1}{R_2} \right) = v_1 + \frac{R_1}{R_2} v_2$$

$$\frac{R_3 v_o}{R_3 + R_4} \left( 1 + \frac{R_1}{R_2} \right) = v_1 + \frac{R_1}{R_2} v_2$$

$$v_o = \frac{R_3 + R_4}{R_3 \left( 1 + \frac{R_1}{R_2} \right)} \left( v_1 + \frac{R_1}{R_2} v_2 \right)$$

$$v_o = \frac{R_3 + R_4}{R_3(R_1 + R_2)} (v_1 R_2 + v_2)$$

**Chapter 5, Solution 39.**

This is a summing amplifier.

$$v_o = -\left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right) = -\left( \frac{50}{10}(2) + \frac{50}{20} v_2 + \frac{50}{50}(-1) \right) = -9 - 2.5v_2$$

Thus,

$$v_o = -16.5 = -9 - 2.5v_2 \longrightarrow v_2 = 3 \text{ V}$$

### Chapter 6, Solution 21.

$4\mu\text{F}$  in series with  $12\mu\text{F} = (4 \times 12)/16 = 3\mu\text{F}$

$3\mu\text{F}$  in parallel with  $3\mu\text{F} = 6\mu\text{F}$

$6\mu\text{F}$  in series with  $6\mu\text{F} = 3\mu\text{F}$

$3\mu\text{F}$  in parallel with  $2\mu\text{F} = 5\mu\text{F}$

$5\mu\text{F}$  in series with  $5\mu\text{F} = 2.5\mu\text{F}$

Hence  $C_{eq} = \underline{\underline{2.5\mu\text{F}}}$

### Chapter 6, Solution 23.

(a)  $3\mu\text{F}$  is in series with  $6\mu\text{F}$   $3 \times 6/(9) = 2\mu\text{F}$

$$v_{4\mu\text{F}} = 1/2 \times 120 = \underline{\underline{60\text{V}}}$$

$$v_{2\mu\text{F}} = \underline{\underline{60\text{V}}}$$

$$v_{6\mu\text{F}} = \frac{3}{6+3}(60) = \underline{\underline{20\text{V}}}$$

$$v_{3\mu\text{F}} = 60 - 20 = \underline{\underline{40\text{V}}}$$

(b) Hence  $w = 1/2 Cv^2$

$$w_{4\mu\text{F}} = 1/2 \times 4 \times 10^{-6} \times 3600 = \underline{\underline{7.2\text{mJ}}}$$

$$w_{2\mu\text{F}} = 1/2 \times 2 \times 10^{-6} \times 3600 = \underline{\underline{3.6\text{mJ}}}$$

$$w_{6\mu\text{F}} = 1/2 \times 6 \times 10^{-6} \times 400 = \underline{\underline{1.2\text{mJ}}}$$

$$w_{3\mu\text{F}} = 1/2 \times 3 \times 10^{-6} \times 1600 = \underline{\underline{2.4\text{mJ}}}$$

### Chapter 6, Solution 51.

$$\frac{1}{L} = \frac{1}{60} + \frac{1}{20} + \frac{1}{30} = \frac{1}{10}$$

$$L = 10 \text{ mH}$$

$$L_{eq} = 10 \left\| (25 + 10) = \frac{10 \times 35}{45} \right.$$

**= 7.778 mH**

**Chapter 6, Solution 52.**

$$L_{eq} = 5 // (7 + 3 + 10 // (4 + 6)) == 5 // (7 + 3 + 5) = \frac{5 \times 15}{20} = \underline{3.75 \text{ H}}$$