

EECS70A / CSE 70A Network Analysis I

Prof. Peter Burke

Homework # 7 solution

Chapter 9, Solution 38.

$$\frac{1}{6} F \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(3)(1/6)} = -j2$$

$$I = \frac{-j2}{4 - j2} (10 \angle 45^\circ) = 4.472 \angle -18.43^\circ$$

$$\text{Hence, } i(t) = \underline{4.472 \cos(3t - 18.43^\circ) A}$$

$$V = 4I = (4)(4.472 \angle -18.43^\circ) = 17.89 \angle -18.43^\circ$$

$$\text{Hence, } v(t) = \underline{17.89 \cos(3t - 18.43^\circ) V}$$

$$(a) \quad \frac{1}{12} F \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(4)(1/12)} = -j3$$

$$3 H \longrightarrow j\omega L = j(4)(3) = j12$$

$$I = \frac{V}{Z} = \frac{50 \angle 0^\circ}{4 - j3} = 10 \angle 36.87^\circ$$

$$\text{Hence, } i(t) = \underline{10 \cos(4t + 36.87^\circ) A}$$

$$V = \frac{j12}{8 + j12} (50 \angle 0^\circ) = 41.6 \angle 33.69^\circ$$


$$\text{Hence, } v(t) = \underline{41.6 \cos(4t + 33.69^\circ) V}$$

Chapter 9, Solution 49.

$$Z_T = 2 + j2 \parallel (1 - j) = 2 + \frac{(j2)(1 - j)}{1 + j} = 4$$

$$i_x = 0.5 \sin 200t = 0.5 \cos(200t - 90^\circ)$$

$$I_x = 0.5 \angle -90^\circ$$

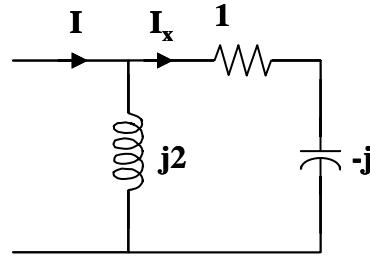

$$I = \frac{V_s}{Z_T} = \frac{V_s}{4}$$

$$I_x = \left(\frac{j2}{1+j}\right) \frac{V_s}{4} = 0.5 \angle -90^\circ \quad \text{using current divider}$$

$$V_s = (0.5 \angle -90^\circ) \cdot 4 \cdot \left(\frac{1+j}{j2}\right) = 1.414 \angle -135^\circ$$

$$v_s(t) = \underline{1.414 \cos(200t - 135^\circ)} = \underline{1.414 \sin(200t - 45^\circ)} \text{ V}$$

Chapter 9, Solution 57.

$$2H \longrightarrow j\omega L = j2$$

$$1F \longrightarrow \frac{1}{j\omega C} = -j$$

$$Z = 1 + j2 // (2 - j) = 1 + \frac{j2(2 - j)}{j2 + 2 - j} = 2.6 + j1.2$$

$$Y = \frac{1}{Z} = \underline{0.3171 - j0.1463 \text{ S}}$$

Chapter 9, Solution 64.

$$Z_T = 4 + \frac{-j10(6 + j8)}{6 - j2} = \underline{19 - j5 \Omega}$$

$$I = \frac{30 \angle 90^\circ}{Z_T} = -0.3866 + j1.4767 = \underline{1.527 \angle 104.7^\circ \text{ A}}$$

Chapter 14, Solution 48.

$$H(\omega) = \frac{R \parallel \frac{1}{j\omega C}}{j\omega L + R \parallel \frac{1}{j\omega C}}$$

$$H(\omega) = \frac{\frac{R/j\omega C}{R + 1/j\omega C}}{j\omega L + \frac{R/j\omega C}{R + 1/j\omega C}}$$

$$\underline{H(\omega) = \frac{R}{R + j\omega L - \omega^2 RLC}}$$

$H(0) = 1$ and $H(\infty) = 0$ showing that this circuit is a lowpass filter.

Chapter 14, Solution 50.

$$H(\omega) = \frac{V_o}{V_i} = \frac{j\omega L}{R + j\omega L}$$

$H(0) = 0$ and $H(\infty) = 1$ showing that this circuit is a highpass filter.

$$H(\omega_c) = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left(\frac{R}{\omega_c L}\right)^2}} \longrightarrow 1 = \frac{R}{\omega_c L}$$

$$\text{or } \omega_c = \frac{R}{L} = 2\pi f_c$$

$$f_c = \frac{1}{2\pi} \cdot \frac{R}{L} = \frac{1}{2\pi} \cdot \frac{200}{0.1} = \underline{\underline{318.3 \text{ Hz}}}$$