

EECS70A / CSE 70A Network Analysis I
Prof. Peter Burke

Midterm I solution

Grading criteria for all questions: no credits for answers without units and - 5pts for each wrong unit.

Problem 1:

$$(a) \quad i = \frac{100\text{A} \cdot \text{h}}{50} = \underline{2 \text{ A}}$$

$$(b) \quad t = \frac{100\text{Ah}}{0.001\text{A}} = \frac{100,000\text{h}}{24\text{h / day}} = \underline{4,167 \text{ days}}$$

Grading criteria: 3pts for each correct charge and time equation
4pts for each wrong unit conversion with correct steps

Problem 2:

Using voltage division,

$$V_0 = \frac{5\Omega}{(15+5)\Omega}(20\text{V}) = 5\text{V}$$

Alternatively,

$$I_0 = \frac{20\text{V}}{20\Omega} = 1\text{A} \quad V_0 = 1\text{A} \cdot 5\Omega = 5\text{V}$$

Grading criteria: 2pts for only Ohm's Law
5pts for correct voltage division equation or equation for current I_0
7.5pts for correct answer with wrong sign

Problem 3:

Applying KVL,

$$-10 + 10 + 20I - 20 = 0, \quad I = 1\text{A}$$


$$R = \frac{V}{I} = \frac{10}{1} = 10\Omega$$

- Grading criteria:
- 2pts for only Ohm's law
 - 5pts for only correct KVL with wrong current I
 - 10pts for KVL equation with correct current I
 - 15pts for correct current I with wrong resistance R

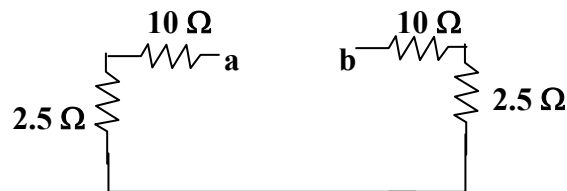Problem 4:


$$5\parallel 5 = 2.5\Omega \quad 5\parallel 5 = 2.5\Omega$$

$$R_{ab} = 10 + 2.5 + 2.5 + 10 = \underline{25\Omega}$$



- Grading criteria:
- 3pts for any correct parallel and series calculations or Delta,Y conversion
 - 5pts for only showing both 5Ω//5Ω configurations
 - 7pts for only showing correct rearrangement of resistances
 - 10pts for wrong final answer with correct steps

Problem 5:

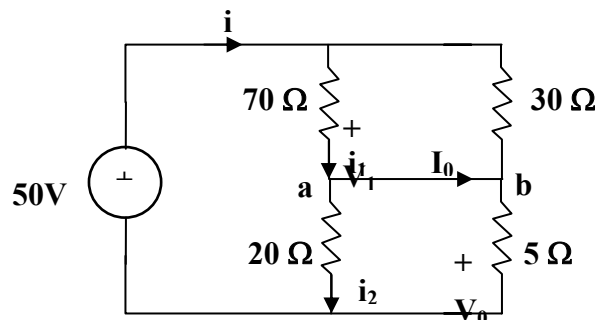

Combining the versions in parallel,

$$70 \parallel 30 = \frac{70 \times 30}{100} = 21 \Omega, 20 \parallel 5 = \frac{20 \times 5}{25} = 4 \Omega$$

$$i = \frac{50}{21 + 4} = 2 \text{ A}$$

$$v_i = 21i = 42 \text{ V}, v_0 = 4i = 8 \text{ V}$$

$$i_1 = \frac{v_1}{70} = 0.6 \text{ A}, i_2 = \frac{v_2}{20} = 0.4 \text{ A}$$

At node a, KCL must be satisfied

$$i_1 = i_2 + I_0 \quad 0.6 = 0.4 + I_0 \quad I_0 = 0.2 \text{ A}$$

Hence $v_0 = \underline{8 \text{ V}}$ and $I_0 = \underline{0.2 \text{ A}}$


Grading criteria: 5pts for only correct KCL, KVL equation or correct simplification
 7pts for wrong I_0 with correct i_1 and i_2 using correct KCL equation
 7pts for wrong V_0 with correct KVL equation
 10pts for only correct V_0 with correct simplification steps

Problem 6:

The voltage across the fuse should be negligible when compared with 24 V.

$$I_1 = \frac{p_1}{V_1} = \frac{45 \text{ mW}}{9 \text{ V}} = 5 \text{ mA}$$
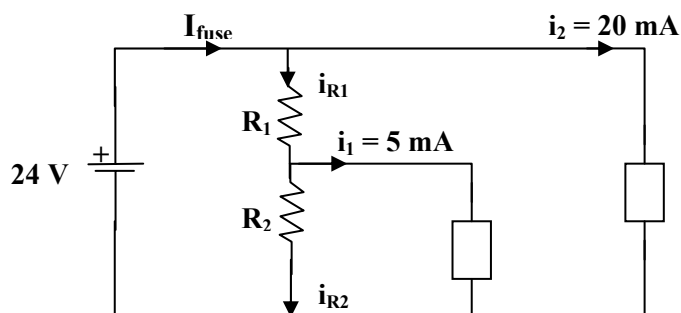
$$I_2 = \frac{p_2}{V_2} = \frac{480 \text{ mW}}{24} = 20 \text{ mA}$$



Let R_3 represent the resistance of the first device.

$$R_3 = 9/0.005 = 1,800 \Omega$$

The fuse condition (60 mA, 2 Ω) is not a fixed condition, but is the maximum condition. The voltage across R_3 must equal 9 volts. Since the circuit is powered by a battery we could choose the value of R_2 which draws the least current, $R_2 = \infty$. Thus we can calculate the value of R_1 that give 9 volts across R_3 .

$$9 = (1800/(R_1 + 1800))24 \text{ or } R_1 = (24/9)1800 - 1800 = \underline{\underline{3,000\Omega}}$$

This value of R_1 means that we only have a total of 25 mA flowing out of the battery through the fuse.

Grading criteria: 5pts for only correct power equation

7pts for each answer of $R_1=375 \Omega$, $R_2=257 \Omega$ with correct i_1

10pts for correct i_1 (device 1) with correct power equation

12pts for correct i_1 and correct $i_{R1}=40\text{mA}$ and $i_{R2}=35\text{mA}$

15pts for correct i_1 and one correct $R_1=3 \text{ K } \Omega$ or $R_2=\infty\Omega$