


## EECS70A / CSE 70A Network Analysis I

Prof. Peter Burke

## Midterm II solution

Grading criteria for all questions: no credits for answers without units and - 3pts for calculation error

Problem 1:

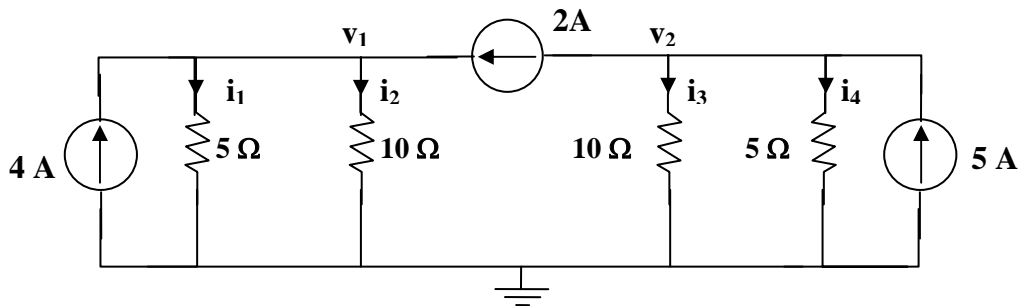

At node 1,

$$4 + 2 = v_1/(5) + v_1/(10) \longrightarrow v_1 = 20$$

At node 2,

$$5 - 2 = v_2/(10) + v_2/(5) \longrightarrow v_2 = 10$$

$$i_1 = v_1/(5) = \underline{4\text{ A}}, i_2 = v_1/(10) = \underline{2\text{ A}}, i_3 = v_2/(10) = \underline{1\text{ A}}, i_4 = v_2/(5) = \underline{2\text{ A}}$$

Grading criteria: 3pts for only KCL at ground or at one node

5pts for only KCL equation or mesh equation with wrong sign

10pts for correct KCL equation at  $V_1$  and  $V_2$  or mesh equation with incorrect answer

Problem 2:

At the top node, KVL gives

$$\frac{V_o - 36}{1} + \frac{V_o - 0}{2} + \frac{V_o - (-12)}{4} = 0$$

$$1.75V_o = 33V \quad \text{or} \quad V_o = 18.86V$$

Alternatively, mesh analysis can be used

$$i_1 = 17.14A, \quad i_2 = 7.71A$$

$$V_o = 2(i_1 - i_2) = 18.86V$$

**Grading criteria:** 5pts for only KCL or mesh equation with wrong sign  
 5pts for correct mesh current  $i_1$  and  $i_2$  on mesh analysis  
 10pts for correct KCL or mesh equation with incorrect answer

Problem 3:

We replace the box with the Thevenin equivalent.

$$\text{When } i = 1.5, \quad v = 3, \quad \text{which implies that } V_{Th} = 3 + 1.5R_{Th} \quad (1)$$

$$\text{When } i = 1, \quad v = 8, \quad \text{which implies that } V_{Th} = 8 + R_{Th} \quad (2)$$

From (1) and (2),  $R_{Th} = 10 \text{ ohms}$  and  $V_{Th} = 18 \text{ V}$ .

$$(a) \quad \text{When } R = 4, \quad i = V_{Th}/(R + R_{Th}) = 18/(4 + 10) = \underline{\underline{1.2857 \text{ A}}}$$

$$(b) \quad \text{For maximum power, } \underline{\underline{R = R_{Th}}}$$

$$P_{max} = (V_{Th})^2/4R_{Th} = 18^2/(4 \times 10) = \underline{\underline{8.1 \text{ watts}}}$$

$$= i^2 R_{Th} = (0.9)^2 \times 10 = \underline{\underline{8.1 \text{ watts}}}$$

**Grading criteria:** No credit for final answers without  $R_{Th}$ ,  $V_{Th}$   
 2pts for showing equivalent circuit in the box ( $R_{Th}$ ,  $V_{Th}$ )  
 3pts for correct  $i$  equation  
 3pts for correct power equation showing  $R = R_{Th}$


5pts for correct  $R_{Th}$  and  $V_{Th}$

Problem 4:

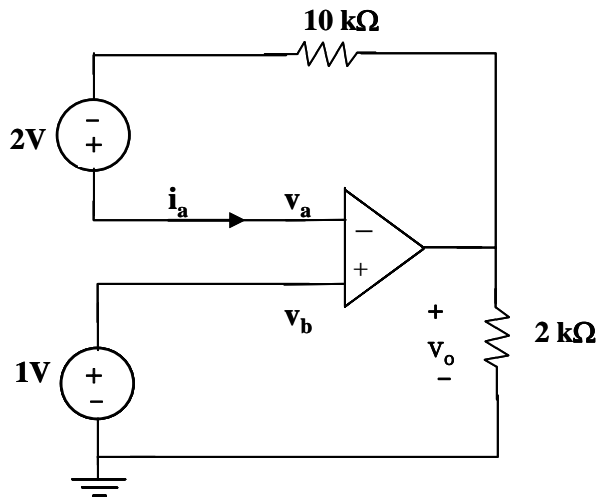
- (a) If  $v_a$  and  $v_b$  are the voltages at the inverting and noninverting terminals of the op amp.

$$v_a = v_b = 0$$

$$1\text{mA} = \frac{0 - v_0}{2\text{k}} \longrightarrow v_0 = \underline{-2\text{V}}$$



(a)

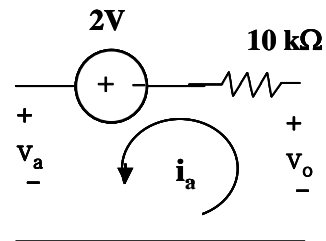

(b)

Since  $v_a = v_b = 1\text{V}$  and  $i_a = 0$ , no current flows through the 10 kΩ resistor.

From Fig. (b),

$$-v_a + 2 + v_0 = 0 \longrightarrow v_0 = v_a - 2 = 1 - 2 = \underline{-1\text{V}}$$

Grading criteria: 3 pts for correct  $V_a$  and  $V_b$  for each question

5pts for correct KCL equation for (a) with wrong answer

-3pts for wrong sign of final answer with correct steps

Problem 5:

$$C_{eq} = 3F // 6F // 4F = 3+6+4 = 13F$$

Grading criteria: 3pts for showing parallel connection with wrong answer  
-3pts for calculation error

Problem 6:

$$L // L = 0.5L, \quad L + L = 2L$$

$$L_{eq} = L + 2L // 0.5L = L + \frac{2L \times 0.5L}{2L + 0.5L} = \underline{1.4L} = \underline{\underline{1.4L}}$$

Grading criteria: 3pts for showing correct connections with wrong answer  
-3pts for calculation error