

### Chapter 7, Solution 7.

When the switch is at position A, the circuit reaches steady state. By voltage division,

$$v_o(0) = \frac{40}{40 + 20}(12\text{ V}) = 8\text{ V}$$

When the switch is at position B, the circuit reaches steady state. By voltage division,

$$v_o(\infty) = \frac{30}{30 + 20}(12\text{ V}) = 7.2\text{ V}$$



$$R_{th} = 20\text{ k} // 30\text{ k} = \frac{20 \times 30}{50} = 12\text{ k}\Omega$$

$$\tau = R_{th}C = 12 \times 10^3 \times 2 \times 10^{-3} = 24\text{ s}$$

$$v_o(t) = v_o(\infty) + [v_o(0) - v_o(\infty)]e^{-t/\tau} = 7.2 + (8 - 7.2)e^{-t/24} = \underline{7.2 + 0.8e^{-t/24}\text{ V}}$$
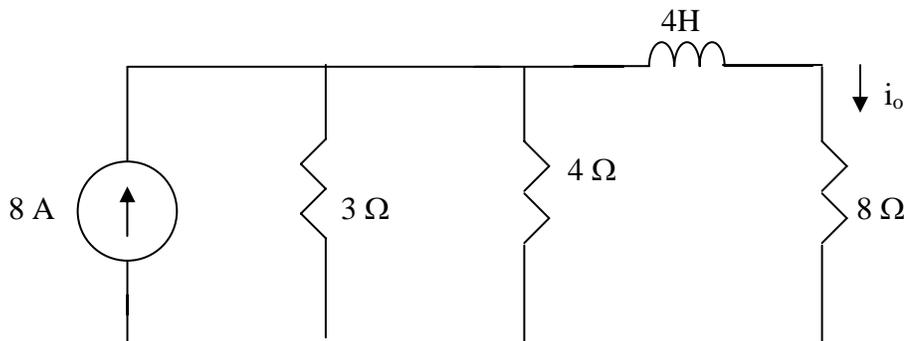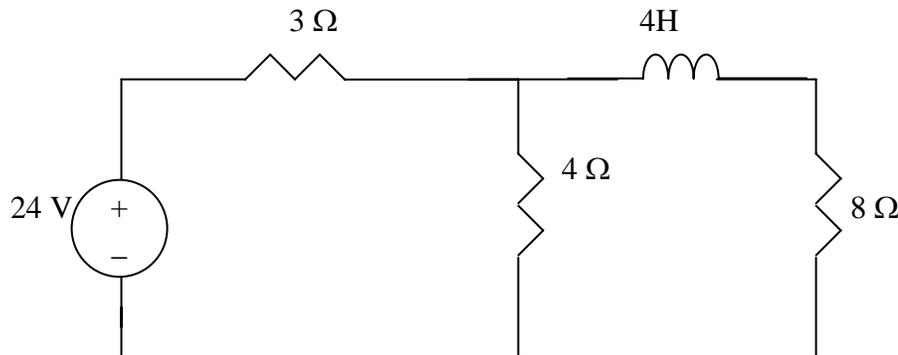
### Chapter 7, Solution 11.

For  $t < 0$ , we have the circuit shown below.



$$3//4 = 4 \times 3 / 7 = 1.7143$$

$$i_o(0^-) = \frac{1.7143}{1.7143 + 8}(8) = 1.4118 \text{ A}$$

For  $t > 0$ , we have a source-free RL circuit.

$$\tau = \frac{L}{R} = \frac{4}{4 + 8} = 1/3$$

$$i_o(t) = i_o(0)e^{-t/\tau} = \underline{1.4118e^{-3t} \text{ A}}$$

### Chapter 7, Solution 42.

$$(a) \quad v_o(t) = v_o(\infty) + [v_o(0) - v_o(\infty)]e^{-t/\tau}$$

$$v_o(0) = 0, \quad v_o(\infty) = \frac{4}{4 + 2}(12) = 8$$

$$\tau = R_{\text{eq}}C_{\text{eq}}, \quad R_{\text{eq}} = 2 \parallel 4 = \frac{4}{3}$$

$$\tau = \frac{4}{3}(3) = 4$$

$$v_o(t) = 8 - 8e^{-t/4}$$

$$v_o(t) = \underline{\mathbf{8(1 - e^{-0.25t}) \text{ V}}}$$

(b) For this case,  $v_o(\infty) = 0$  so that

$$v_o(t) = v_o(0)e^{-t/\tau}$$

$$v_o(0) = \frac{4}{4 + 2}(12) = 8,$$

$$\tau = RC = (4)(3) = 12$$

$$v_o(t) = \underline{\mathbf{8e^{-t/12} \text{ V}}}$$

**Chapter 7, Solution 59.**

Let  $i$  be the current through the inductor.

$$\text{For } t < 0, \quad v_s = 0, \quad i(0) = 0$$

$$\text{For } t > 0, \quad R_{\text{eq}} = 4 + 6 \parallel 3 = 6, \quad \tau = \frac{L}{R_{\text{eq}}} = \frac{1.5}{6} = 0.25$$

$$i(\infty) = \frac{2}{2+4} (3) = 1$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$i(t) = 1 - e^{-4t}$$

$$v_o(t) = L \frac{di}{dt} = (1.5)(-4)(-e^{-4t})$$

$$v_o(t) = \underline{6e^{-4t} u(t) \text{ V}}$$