

### Chapter 9, Solution 37.

$$Y = \frac{1}{4} + \frac{1}{j8} + \frac{1}{-j10} = \underline{0.25 - j0.025 \text{ S}} = \underline{\underline{250-j25 \text{ mS}}}$$

### Chapter 9, Solution 41.


$$\begin{aligned}\omega &= 1, \\ 1 \text{ H} &\longrightarrow j\omega L = j(1)(1) = j \\ 1 \text{ F} &\longrightarrow \frac{1}{j\omega C} = \frac{1}{j(1)(1)} = -j \\ Z &= 1 + (1+j) \parallel (-j) = 1 + \frac{-j+1}{1} = 2 - j\end{aligned}$$

$$\begin{aligned}\mathbf{I} &= \frac{\mathbf{V}_s}{Z} = \frac{10}{2-j}, \quad \mathbf{I}_c = (1+j)\mathbf{I} \\ \mathbf{V} &= (-j)(1+j)\mathbf{I} = (1-j)\mathbf{I} = \frac{(1-j)(10)}{2-j} = 6.325 \angle -18.43^\circ\end{aligned}$$

Thus,  $v(t) = \underline{\underline{6.325 \cos(t - 18.43^\circ) V}}$

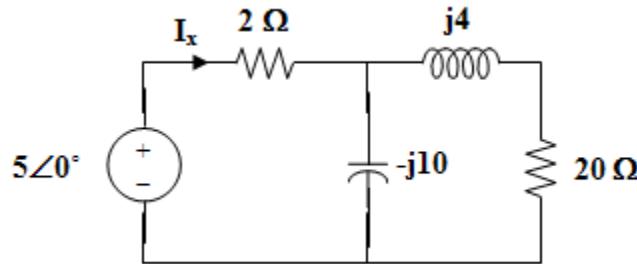**Chapter 9, Solution 47.**

First, we convert the circuit into the frequency domain.



$$I_x = \frac{5}{2 + \frac{-j10(20 + j4)}{-j10 + 20 + j4}} = \frac{5}{2 + 4.588 - j8.626} = \frac{5}{10.854 \angle -52.63^\circ} = 0.4607 \angle 52.63^\circ$$

$$i_s(t) = \underline{460.7 \cos(2000t + 52.63^\circ) \text{ mA}}$$

**Chapter 9, Solution 56.**

$$50\mu F \longrightarrow \frac{1}{j\omega C} = \frac{1}{j377 \times 50 \times 10^{-6}} = -j53.05$$

$$60mH \longrightarrow j\omega L = j377 \times 60 \times 10^{-3} = j22.62$$

$$Z_{in} = 12 - j53.05 + j22.62 // 40 = \underline{21.692 - j35.91 \Omega}$$