

EECS70A / CSE 70A Network Analysis I

Prof. Peter Burke

Homework # 2 solution

Chapter 2, Solution 1.

$$v = iR \quad i = v/R = (16/5) \text{ mA} = \underline{\underline{3.2 \text{ mA}}}$$

Chapter 2, Solution 3.

For silicon, $\rho = 6.4 \times 10^2 \Omega\text{-m}$. $A = \pi r^2$. Hence,

$$R = \frac{\rho L}{A} = \frac{\rho L}{\pi r^2} \longrightarrow r^2 = \frac{\rho L}{\pi R} = \frac{6.4 \times 10^2 \times 4 \times 10^{-2}}{\pi \times 240} = 0.033953$$

$$r = \underline{\underline{0.1843 \text{ m}}}$$

Chapter 2, Solution 5.

$$n = 9; \quad l = 7; \quad \mathbf{b} = n + l - 1 = \underline{\underline{15}}$$


Note: The loop should not have any internal loop and should be independent.
From the figure of circuit, we need to count on only independent closed loops.

Chapter 2, Solution 9.

$$\text{At A,} \quad 2 + 12 = i_1 \longrightarrow i_1 = \underline{\underline{14 \text{ A}}}$$

$$\text{At B,} \quad 12 = i_2 + 14 \longrightarrow i_2 = \underline{\underline{-2 \text{ A}}}$$

$$\text{At C,} \quad 14 = 4 + i_3 \longrightarrow i_3 = \underline{\underline{10 \text{ A}}}$$

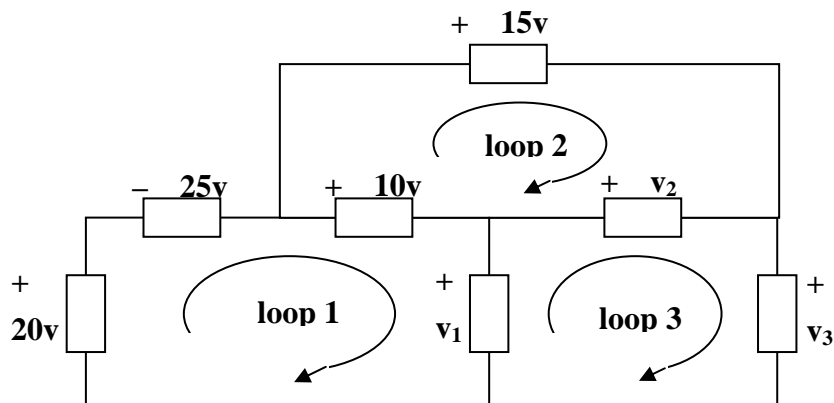Chapter 2, Solution 12.

$$\begin{array}{ll}
 \text{For loop 1,} & -20 -25 +10 + v_1 = 0 \longrightarrow \underline{v_1 = 35v} \\
 \text{For loop 2,} & -10 +15 -v_2 = 0 \longrightarrow \underline{v_2 = 5v} \\
 \text{For loop 3,} & -v_1 +v_2 +v_3 = 0 \longrightarrow \underline{v_3 = 30v}
 \end{array}$$

Chapter 2, Solution 18.

Applying KVL,

$$-30 -10 +8 + I(3+5) = 0$$

$$8I = 32 \longrightarrow I = \underline{4A}$$

$$-V_{ab} + 5I + 8 = 0 \longrightarrow V_{ab} = \underline{28V}$$

Chapter 2, Solution 43.

$$(a) R_{ab} = 5 \parallel (20 + 10) \parallel 40 = \frac{5 \times 20}{25} + \frac{400}{50} = 4 + 8 = \underline{12 \Omega}$$

$$(b) 60 \parallel 20 \parallel 30 = \left(\frac{1}{60} + \frac{1}{20} + \frac{1}{30} \right)^{-1} = \frac{60}{6} = 10 \Omega$$

$$R_{ab} = 80 \parallel (10 + 10) = \frac{80 \times 20}{100} = \underline{16 \Omega}$$

Chapter 2, Solution 45.

$$(a) 10 \parallel 40 = 8, \quad 20 \parallel 30 = 12, \quad 8 \parallel 12 = 4.8$$

$$R_{ab} = 5 + 50 + 4.8 = \underline{59.8 \Omega}$$

(b) 12 and 60 ohm resistors are in parallel. Hence, $12 \parallel 60 = 10$ ohm. This 10 ohm

and 20 ohm are in series to give 30 ohm. This is in parallel with 30 ohm to give $30 \parallel 30 = 15$ ohm. And $25 \parallel (15 + 10) = 12.5$. Thus

$$R_{ab} = 5 + 12.8 + 15 = \underline{32.5 \Omega}$$