

Spring, 2009

EECS70A / CSE 70A Network Analysis I  
Prof. Peter Burke

Homework # 4 solution

**Chapter 5, Solution 1.**

- (a)  $R_{in} = \underline{1.5 \text{ M}\Omega}$   
(b)  $R_{out} = \underline{60 \text{ }\Omega}$   
(c)  $A = 8 \times 10^4$   
Therefore  $A_{dB} = 20 \log 8 \times 10^4 = \underline{98.0 \text{ dB}}$

**Chapter 5, Solution 9.**

- (a) Let  $v_a$  and  $v_b$  be respectively the voltages at the inverting and noninverting terminals of the op amp

$$v_a = v_b = 4V$$

At the inverting terminal,

$$1mA = \frac{4 - v_0}{2k} \quad v_0 = \underline{2V}$$

- (b) Since  $v_a = v_b = 5V$ ,

$$-v_b + 2 + v_o = 0 \quad v_o = v_b - 1 = \underline{3V}$$

**Chapter 5, Solution 17.**

- (a)  $G = \frac{v_o}{v_i} = -\frac{R_2}{R_1} = -\frac{12}{10} = \underline{-1.2}$
- (b)  $\frac{v_o}{v_i} = -\frac{80}{10} = \underline{-8}$
- (c)  $\frac{v_o}{v_i} = -\frac{2000}{10} = \underline{-200}$

**Chapter 5, Solution 34.**

$$\frac{v_1 - v_{in}}{R_1} + \frac{v_1 - v_{in}}{R_2} = 0 \quad (1)$$

but

$$v_a = \frac{R_3}{R_3 + R_4} v_o \quad (2)$$

Combining (1) and (2),

$$v_1 - v_a + \frac{R_1}{R_2} v_2 - \frac{R_1}{R_2} v_a = 0$$

$$v_a \left( 1 + \frac{R_1}{R_2} \right) = v_1 + \frac{R_1}{R_2} v_2$$

$$\frac{R_3 v_o}{R_3 + R_4} \left( 1 + \frac{R_1}{R_2} \right) = v_1 + \frac{R_1}{R_2} v_2$$

$$v_o = \frac{R_3 + R_4}{R_3 \left( 1 + \frac{R_1}{R_2} \right)} \left( v_1 + \frac{R_1}{R_2} v_2 \right)$$

$$v_o = \frac{R_3 + R_4}{R_3(R_1 + R_2)} (v_1 R_2 + v_2)$$

### Chapter 5, Solution 39.

This is a summing amplifier.

$$v_o = -\left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right) = -\left( \frac{50}{10}(2) + \frac{50}{20} v_2 + \frac{50}{50}(-1) \right) = -9 - 2.5v_2$$

Thus,

$$v_o = -16.5 = -9 - 2.5v_2 \quad \longrightarrow \quad \underline{v_2 = 3 \text{ V}}$$