## Chapter 6, Solution 21.

 $4\mu F$  in series with  $12\mu F = (4x12)/16 = 3\mu F$   $3\mu F$  in parallel with  $3\mu F = 6\mu F$   $6\mu F$  in series with  $6\mu F = 3\mu F$   $3\mu F$  in parallel with  $2\mu F = 5\mu F$  $5\mu F$  in series with  $5\mu F = 2.5\mu F$ 

Hence  $C_{eq} = \underline{2.5\mu F}$ 

## Chapter 6, Solution 51.

$$\frac{1}{L} = \frac{1}{60} + \frac{1}{20} + \frac{1}{30} = \frac{1}{10}$$
 L = 10 mH

$$L_{eq} = 10 \left| \left( 25 + 10 \right) = \frac{10x35}{45} \right|$$

$$= 7.778 \text{ mH}$$

## Chapter 6, Solution 55.

(a) 
$$L//L = 0.5L$$
,  $L + L = 2L$ 

$$L_{eq} = L + 2L // 0.5L = L + \frac{2Lx0.5L}{2L + 0.5L} = \underline{1.4L} = \underline{1.4L}.$$

(b) 
$$L//L = 0.5L$$
,  $L//L + L//L = L$ 

$$L_{eq} = L//L = 500 \text{ mL}$$