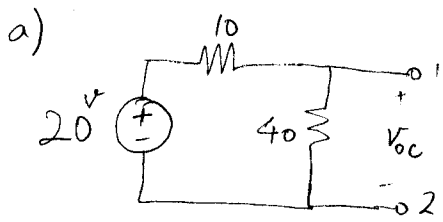



Thevenin/Norton in a different way with V_{Th}/I_{sc} :

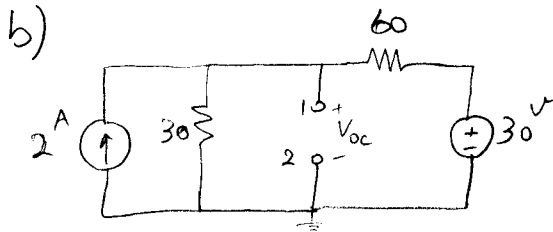4.33:



$$V_{Th} = V_{oc} = 20 \frac{40}{40+10} = 16 \text{ V}$$

$$I_{sc} = \frac{20}{10} = 2 \quad \rightarrow \quad R_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{16}{2} = 8 \Omega$$




$$V_{Th} = V_{oc}$$

$$2 - \frac{V_{oc}}{30} - \frac{(V_{oc} - 30)}{60} = 0 \Rightarrow V_{oc} = 50 \text{ V} = V_{Th}$$

$$I_{sc} = 2 \text{ A} + \frac{30}{60} = 2.5 \text{ A}$$

$$\Rightarrow R_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{50}{2.5} = 20 \Omega$$


4.36:

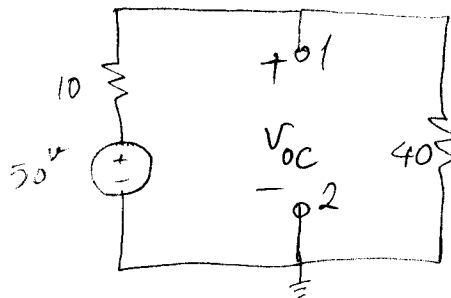

$$V_{oc}: V_{oc} = V_{Th}$$


$$\frac{(V_{oc} - 50)}{10} + \frac{(V_{oc} - 0)}{40} = 0 \Rightarrow V_{oc} = 40 \text{ V} = V_{Th}$$

I_{sc} :

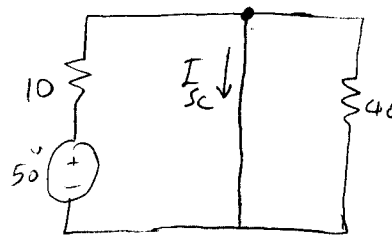

$$I_{sc} = \frac{50}{10} = 5 \text{ A}$$
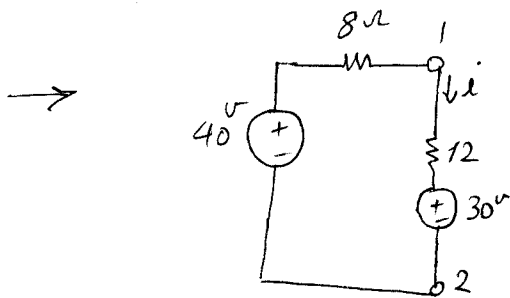
$$\Rightarrow R_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{40}{5} = 8 \Omega$$



$$I = \frac{40 - 30}{8 + 12} = \frac{10}{20} = 0.5 \text{ A} = 500 \text{ mA}$$