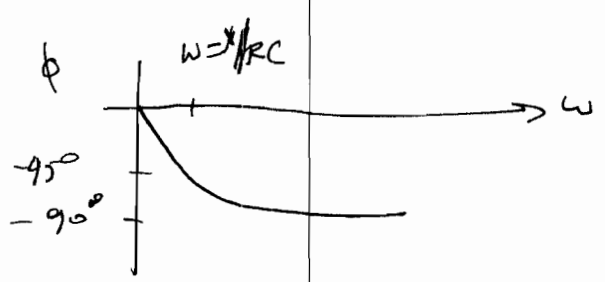


BODE PLOTS

①

RC filter phase



$H(\omega)$ mathematical properties

$$s \equiv j\omega$$

So $H(s) \equiv H(j\omega)$

Zero: Value of s such that $H(s) = 0$

Pole: Value of s such that $H(s) = \infty$

E.g. $H(s) = \frac{s(s+2)}{(s+1)(s+1)}$

~~Pole~~
Poles: $s = -2, s = 0$
~~Zeros:~~

Poles: $s = -1$ zero: $s = 0, -2$

$$\begin{aligned} \alpha \text{ dB} &\equiv 10 \log \frac{P_1}{P_2} = 10 \log \frac{V_1^2/R}{V_2^2/R} \\ &= 10 \log \frac{V_1^2}{V_2^2} = 20 \log \frac{V_1}{V_2} \end{aligned}$$

table: -

$V_{\frac{1}{\sqrt{2}}}$

dB	P_1/P_2	v_1/v_2
0		1
-10	0.1	0.33
-20	0.01	0.1
⋮		
+10	10	3.3
+20	100	10
⋮		
-3	$\frac{1}{2}$	$\frac{1}{\sqrt{2}}$
+3	2	$\sqrt{2}$

Bode Plot H (dB) vs. ω (log scale)


E.g. RC filter

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

$$H(s) = \frac{1}{1 + sRC}$$

Zero: none


Pole: $s = -\frac{1}{RC}$

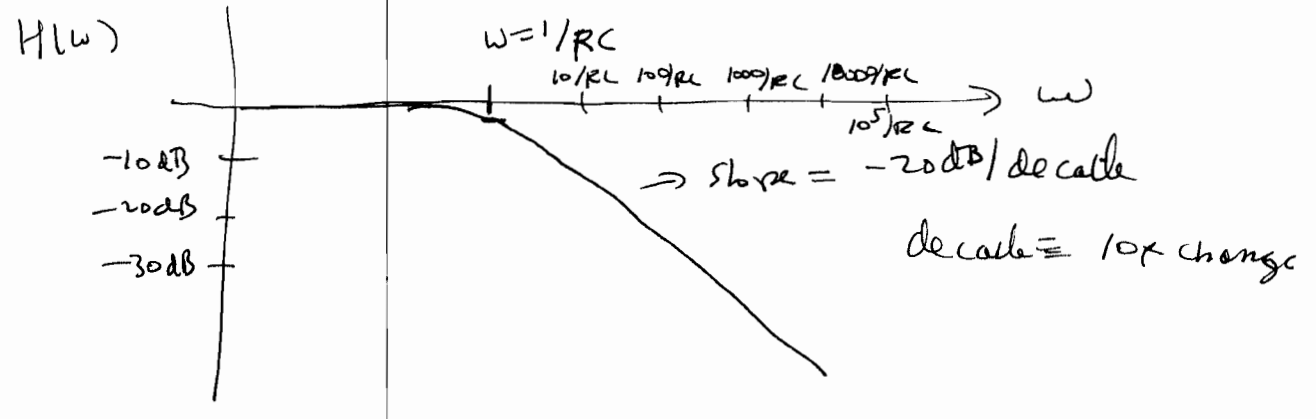

E.g. RL HPF

$$H(\omega) = \frac{j\omega RC}{1 + j\omega RC}$$

$$H(s) = \frac{sRC}{1 + sRC}$$

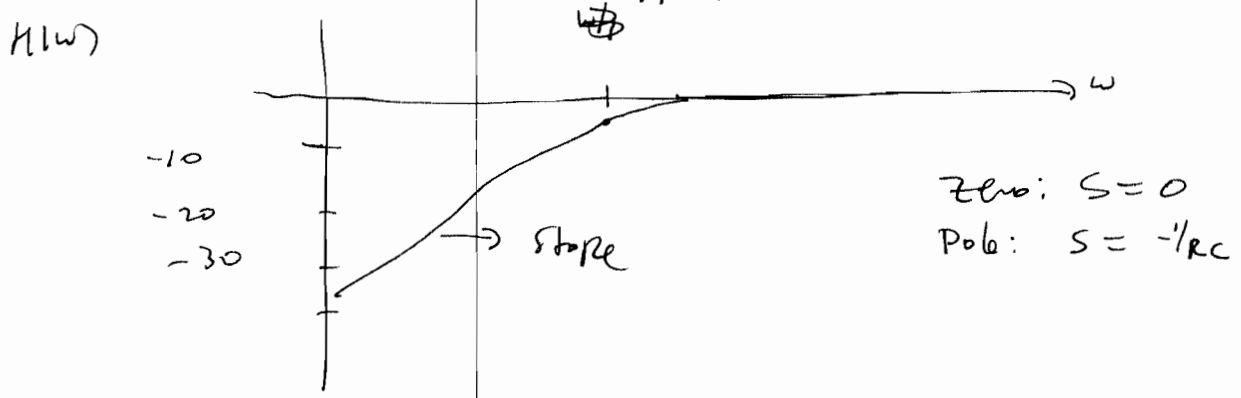

(4)

Can always write $H(s)$ as product of poles, zeros:


$$\begin{aligned} \text{Eg } H(s) &= \frac{s(s+2)}{(s+1)(s+1)} \\ &= 2 \times s \times [1 - (-s/2)] \times \frac{1}{[1 - (-s)]} \times \frac{1}{[1 - (-s)]} \end{aligned}$$

$$\begin{aligned} \text{But in dB } \log H(s) &= \log \left\{ 2 \times s \times [1 - (-s/2)] \times \frac{1}{[1 - (-s)]} \right. \\ &\quad \left. \times \frac{1}{[1 - (-s)]} \right\} \\ &= \log 2 + \log(s) + \log [1 - (-s/2)] + \\ &\quad \log [1 - (-s)] + \log [1 - (-s)] \end{aligned}$$


So to sketch $H(s)$ Bode plot, easy to do if you know behaviour of some simple cases: poles, zeros.

Simple cases


$$H(s) = s^N$$

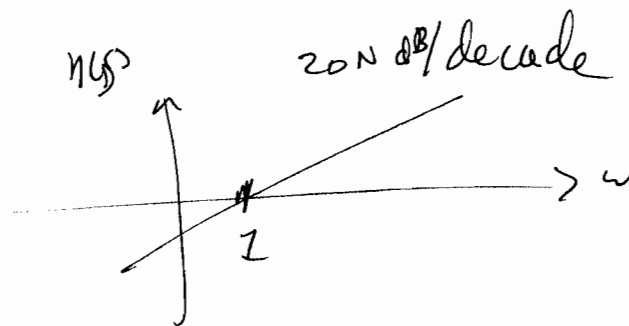


$$H(s) = s^{-N}$$

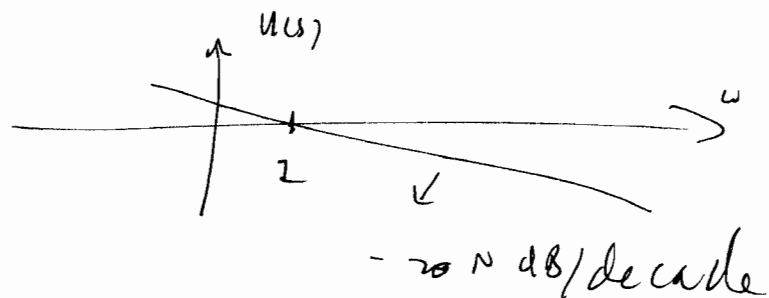


$H(s) = (1+s)^n$

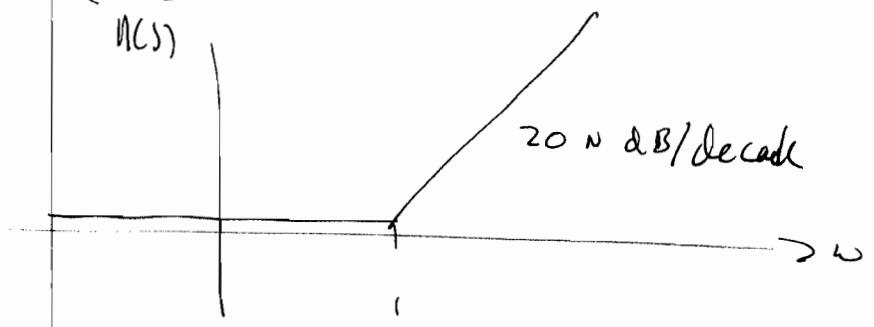

$H(s) = \frac{1}{(1+s)^n}$

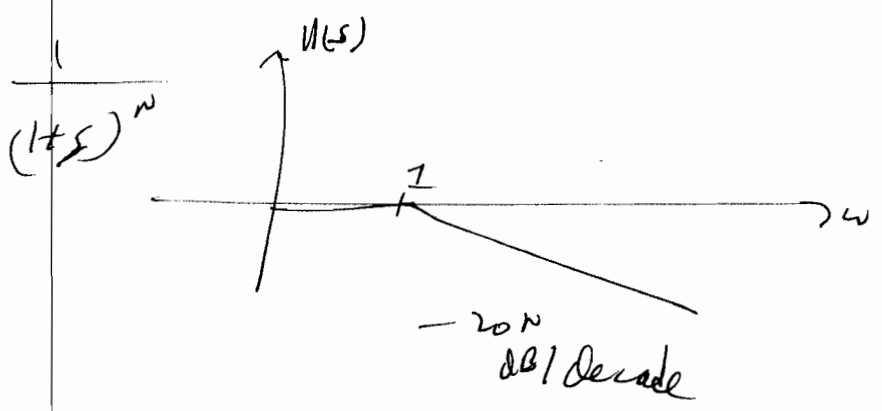

$H(s) = K$ (constant)

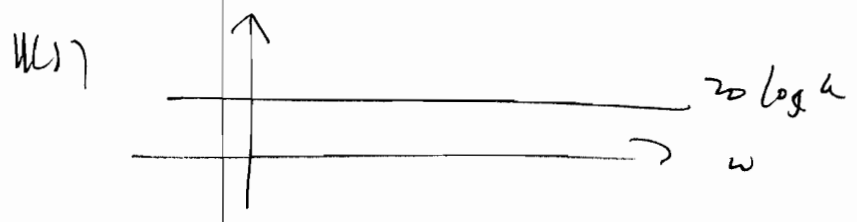

(6)

$$\text{Eq } H(s) = \frac{s(s+2)}{(s+1)(s+1)} = \frac{2s(1+s/2)}{(1+s)(1+s)}$$

