

LA PART B

$$i(t) = C \frac{dv(t)}{dt}$$

$$\Rightarrow \underline{I} \Rightarrow V = I \frac{1}{j\omega C}$$

$$\frac{V}{I} = R$$

$$j\omega L$$

$$\frac{1}{j\omega C}$$

Impedance $Z \equiv \frac{V}{I}$

Admittance $Y \equiv \frac{1}{Z}$

Thevenin ~~Theorem~~ Theorem still applies:

Source impedance

Input Impedance

E.g. source 10Ω // 20Ω


Example

$$v(t) = V_{ac} \cos(\omega t)$$

phasor

$$= \text{Re}(V_{ac} e^{i\omega t}) \Rightarrow V = V_{ac}$$

$$Z = \frac{V}{I} = i\omega L$$

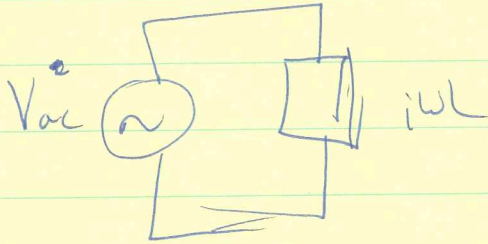

$$I(t) = \text{Re}(I e^{i\omega t})$$

$$V(t) = \text{Re}(V e^{i\omega t})$$

$$I(t) = \text{Re}\left(\frac{V}{Z} e^{i\omega t}\right)$$

$$= \text{Re}\left(\frac{V_{ac}}{j\omega L} e^{i\omega t}\right)$$

$$= \frac{V_{ac}}{\omega L} \text{Re}(-j e^{i\omega t})$$

$$= \frac{V_{ac}}{\omega L} \text{Re}\left(\frac{j \sin \omega t + \cos \omega t}{j (\cos \omega t + j \sin \omega t)}\right)$$

$$= \frac{V_{ac}}{\omega L} \sin(\omega t) = I(t)$$


could have done

$$v(t) = L \frac{dI(t)}{dt} \Rightarrow I(t) = \frac{1}{L} \int v(t) dt$$


$$= \frac{1}{L} \int V_{ac} \cos(\omega t) dt$$

$$= \frac{V_{ac}}{\omega L} \sin(\omega t)$$

Impedance in series

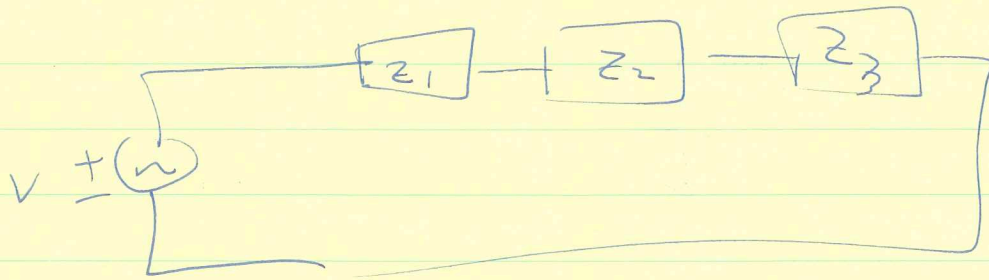



$$Z_{eq} = Z_1 + Z_2 + Z_3$$

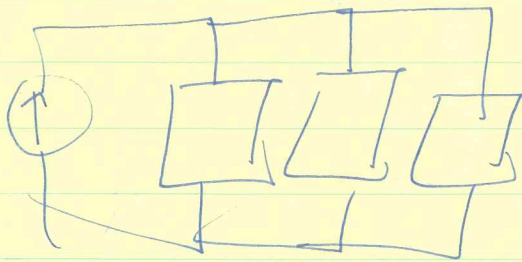

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

- RC filters
- LR filters
- RLC filters

RC LPF

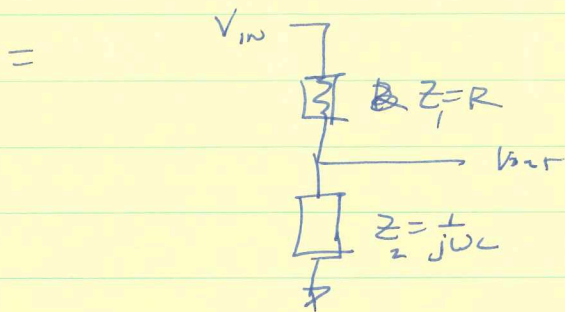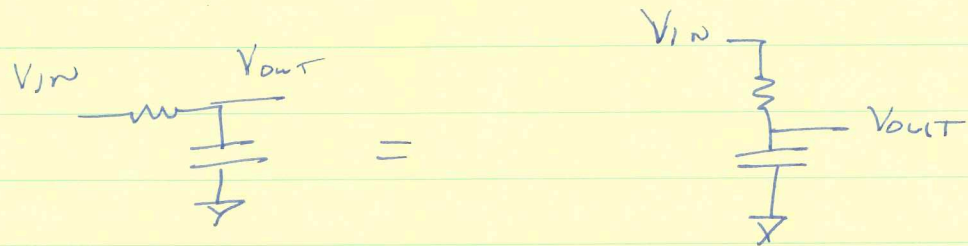


$$\frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \cdot \frac{j\omega C}{j\omega C}$$

$$= \frac{1}{1 + j\omega RC}$$

$$V_{in}^{(+)} = \text{Re} [V_m e^{i\phi_i} e^{i\omega t}]$$
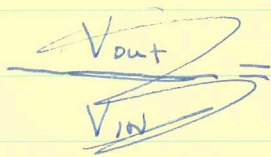
$$\Rightarrow V_{out}^{(+)} = \text{Re} \left[\frac{1}{1 + j\omega RC} V_m e^{i\phi_i} e^{i\omega t} \right]$$



Want to express $\frac{1}{1+j\omega RC} V_m e^{i\phi_i}$
as $v e^{i\phi}$

$$\frac{1}{1+j\omega RC} = \frac{1-j\omega RC}{1-j\omega RC} = \frac{1-j\omega RC}{1+(\omega RC)^2}$$

$$= \underbrace{\frac{1}{1+(\omega RC)^2}}_{\text{Real}} - \underbrace{\frac{j\omega RC}{1+(\omega RC)^2}}_{\text{Imag}}$$

$$\Rightarrow r = \sqrt{(\text{Real})^2 + (\text{Imag})^2}$$

$$= \sqrt{\left[\frac{1}{1+(\omega RC)^2}\right]^2 + \left[\frac{-j\omega RC}{1+(\omega RC)^2}\right]^2}$$

$$= \sqrt{\left[\frac{1}{1+(\omega RC)^2}\right]^2 + \left[\frac{(\omega RC)^2}{1+(\omega RC)^2}\right]^2}$$

$$= \sqrt{\left[\frac{1}{1+(\omega RC)^2}\right]^2 + (\omega RC)^2}$$

$$= \frac{1}{1+(\omega RC)^2} \sqrt{1+(\omega RC)^4}$$

$$\sqrt{1+x^4} = \sqrt{(1+x^2)(1-x^2)}$$



(3)

$$= \sqrt{\left(\frac{1}{H(\omega RC)^2}\right)^2 + \left(\frac{-j\omega RC}{H(\omega RC)^2}\right)^2}$$


$$= \frac{1}{H(\omega RC)^2} \sqrt{1 + (-j\omega RC)^2}$$

$$= \frac{1}{H(\omega RC)^2} \sqrt{1 + (\omega RC)^2} = \frac{1}{\sqrt{H(\omega RC)^2}}$$

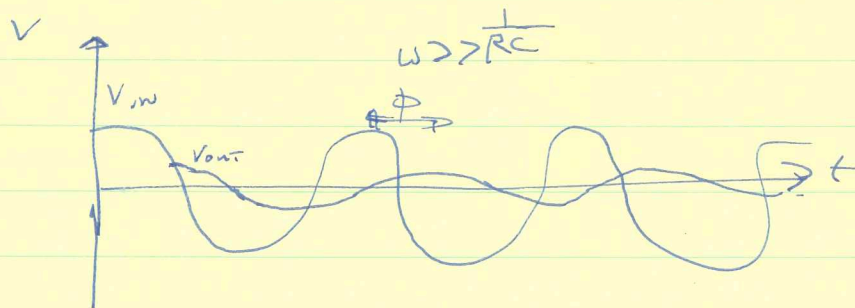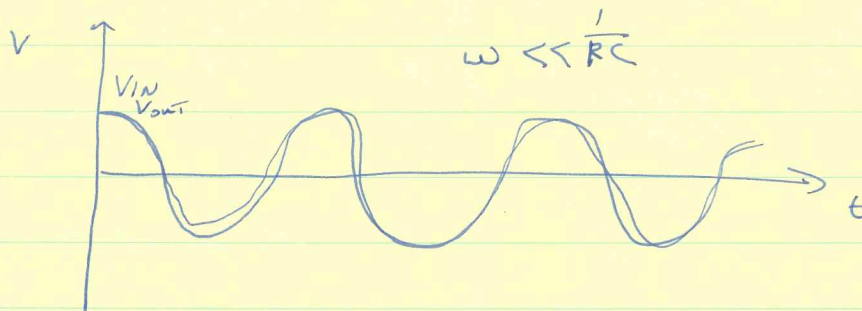
$$\phi = -\tan^{-1} \frac{\text{Im}}{\text{Re}} = -\tan^{-1}(\omega RC)$$



$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

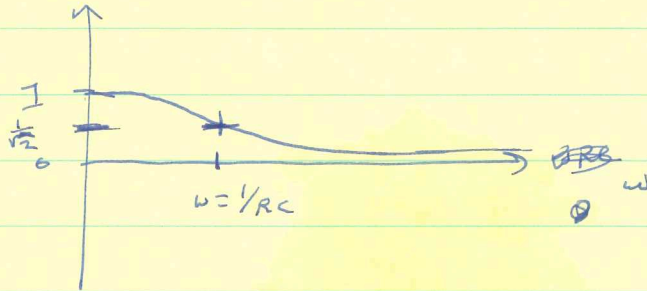



Called "Transfer Function"

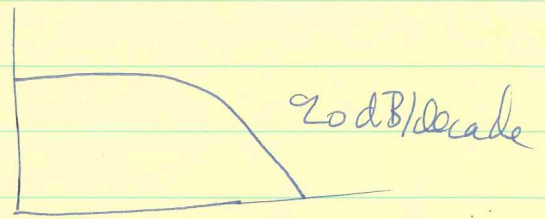

Bode plots
dB scale

~~decade~~
decade = 10x
 $\frac{1}{(\omega RC)^2} \downarrow 10$
 \Rightarrow dB \downarrow 20dB

RC HPF

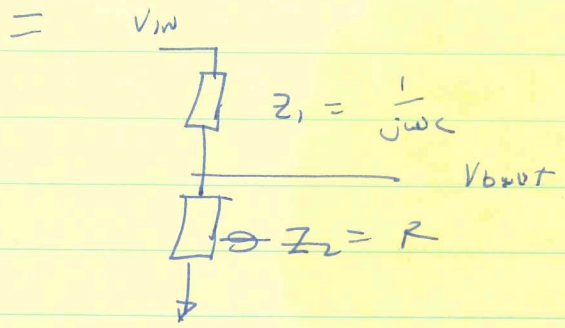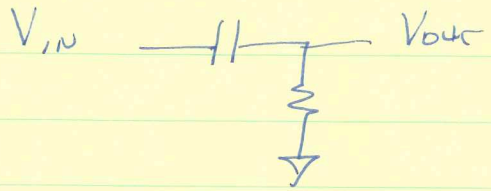


$$\frac{V_{out}}{V_{in}} = \frac{j\omega C R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{j\omega RC (1 - j\omega RC)}{1 + (\omega RC)^2} = \frac{j\omega RC + (\omega RC)^2}{1 + (\omega RC)^2}$$


~~$= j\omega RC$~~

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{(\omega RC)^2 + (\omega RC)^2}} = \frac{1}{\sqrt{(\omega RC)^2} \sqrt{1 + (\omega RC)^2}}$$

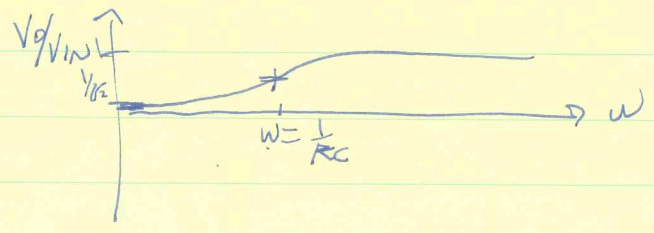
$$= \frac{(\omega RC)}{\sqrt{1 + (\omega RC)^2}}$$





(6)

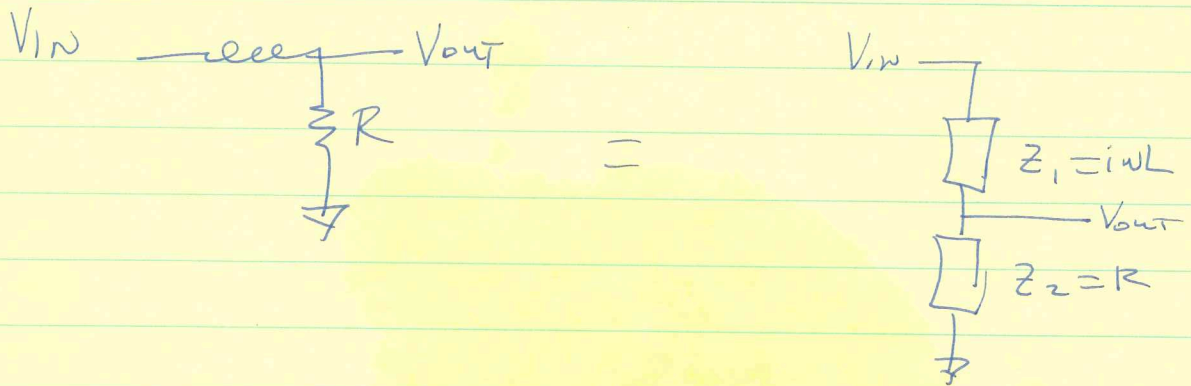

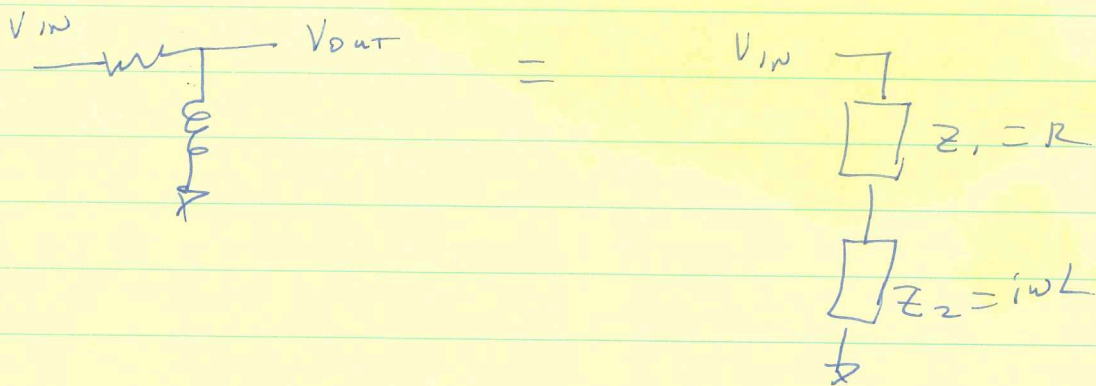$\frac{V_{out}}{V_{in}}$ as RC LPF but $\tau = L/R$
instead of $\tau = RC$



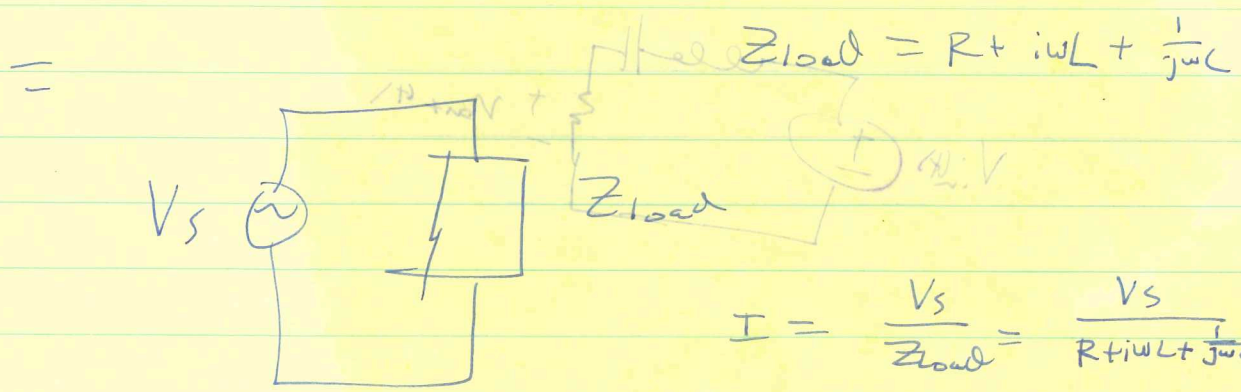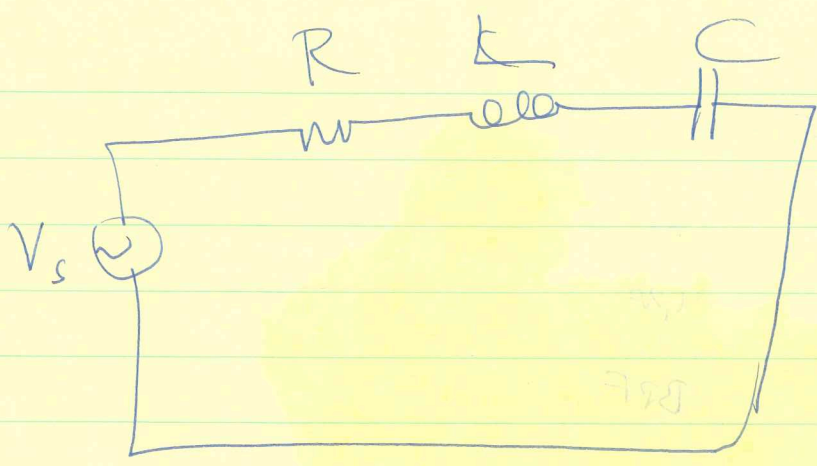$\frac{V_{out}}{V_{in}}$ as RC HPF but $\tau = L/R$
instead of $\tau = RC$




$$I = \frac{V_s}{Z_{load}} = \frac{V_s}{R + i\omega L + \frac{1}{j\omega C}}$$

At $\omega = \frac{1}{\sqrt{LC}} \Rightarrow Z_{load} = R$

$$I = \frac{V_s}{R}$$

$\omega \rightarrow \infty$ open circuit $I \rightarrow 0$

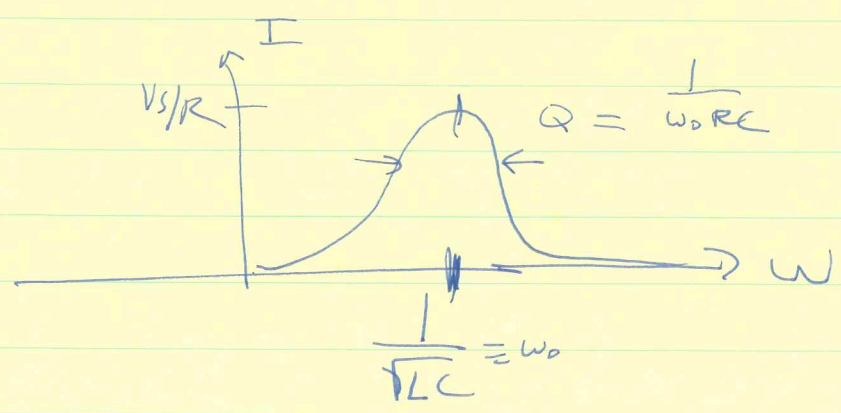$\omega \rightarrow 0$ open circuit $I \rightarrow 0$




$$I = |I| = \left| \frac{v_s}{z} \right|$$

$$z = R + j\omega L + \frac{1}{j\omega C}$$

$$|I| = \frac{v_s}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$|I|_{\max} @ \quad \omega L - \frac{1}{\omega C} = 0 \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$


Bandpass Filter

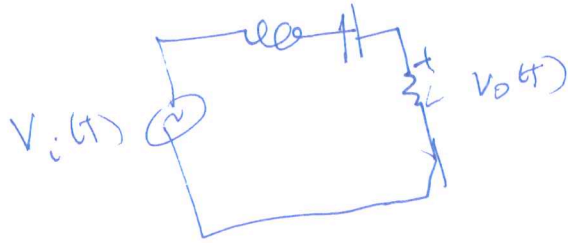

$$\frac{V_o}{V_i} = \frac{R}{R + i(\omega L - \frac{1}{\omega C})}$$

Show \equiv Transfer Function

$H(\omega) \equiv \left| \frac{V_o}{V_i} \right|$

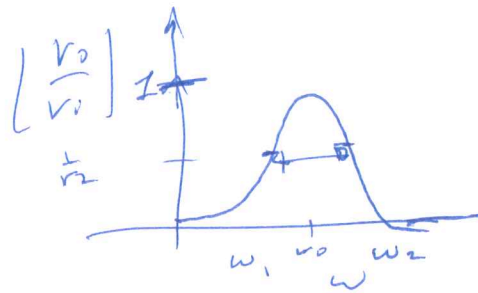

$$\Rightarrow \left| \frac{R}{R + i(\omega L - \frac{1}{\omega C})} \right| = \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow \cancel{2R} = 2R = R^2 + (\omega L - \frac{1}{\omega C})^2$$

$$\cancel{2R} - R^2 = \omega_1^2 L^2 - 2 \frac{L}{C} + \frac{1}{\omega_1^2 C^2}$$

$$\Rightarrow \omega_1^2 / C^2 (2R - R^2) = \omega_1^4 L^2 - 2 \frac{L}{C} \omega_1^2 + \frac{1}{C^2}$$

$$L^2 \omega_1^4 - [2 \frac{L}{C} + C^2(2R - R^2)] \omega_1^2 + \frac{1}{C^2} = 0$$

$$\Rightarrow \omega_1^2 = 2 \frac{L}{C}$$

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

(2)


$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$B \equiv \omega_2 - \omega_1$$

$$B = \frac{R}{L} = \frac{\omega_0}{Q} = \omega_0^2 RC$$

$$Q \equiv \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$
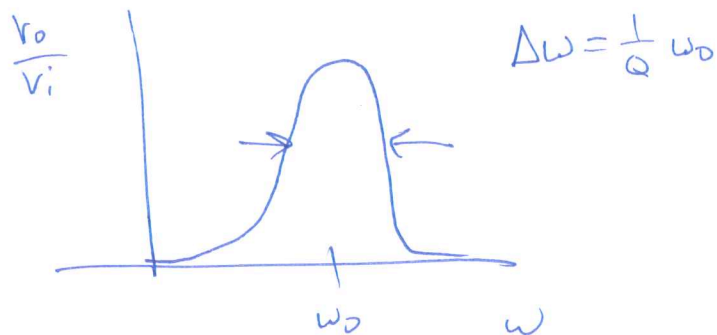
$$\frac{\Delta \omega}{\omega_0} \equiv \frac{1}{Q}$$



want large Q

$$H(\omega) \equiv \frac{V_o}{V_{in}}$$

(3)

$$V_{in}(t)$$

$$= V_1 \cos(\omega_1 t) + V_2 \cos(\omega_2 t)$$

$$= \text{Re}[V_1 e^{j\omega_1 t}] + \text{Re}[V_2 e^{j\omega_2 t}]$$

$$V_o(t) = \text{Re}[H(\omega_1) V_1 e^{j\omega_1 t}]$$

$$+ \text{Re}[H(\omega_2) V_2 e^{j\omega_2 t}]$$

If $H(\omega_2) \approx 0 \Rightarrow V_2(t) = \text{Re}[V_1 e^{j\omega_1 t}]$
 $H(\omega_1) \approx 1$ ~~Re V₁~~


Only single sine wave out
 even though ~~the~~ ~~two~~ ~~no~~ wavefins.

FILTER

OLD FASHIONED TV

100-800 MHz

TV
Cable

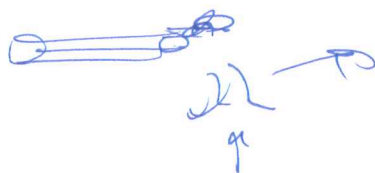

700 MHz



the ~~has~~

Channel 2-100