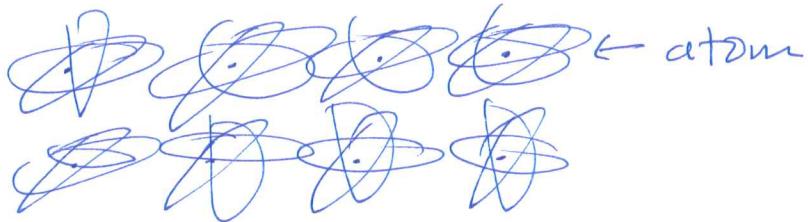


①

Solid:

Free electrons (1 per atom) can move.

Current

$$I = \frac{dq}{dt}$$

Charge per time crossing a plane

book notation

q charge

e charge on one electron
 $= -1.6 \times 10^{-19} C$

⑤



$$F = \frac{1}{4\pi\epsilon_0} \frac{q_1 q_2}{r^2} = q_1 \vec{E}(r)$$

Charge q_2 "creates" electric field.

A system of n charges creates

$$\vec{E}(r) = \frac{1}{4\pi\epsilon_0} \sum_i \frac{q_i}{r_i^2} \hat{r}$$

In general $\vec{E}(r)$ can be complicated..

For now, assume $\vec{E}(r)$ known.

~~Don't worry about~~

(3)

"What is voltage"

$$V_a - V_b \equiv V_{ab} \equiv \Delta V = - \int_b^a \vec{E} \cdot d\vec{s} = - \int_a^b E dx$$

ΔV called "potential difference"

Inside an ideal metal $E=0$.

\Rightarrow The potential difference between any 2 points inside a metal is zero.


So what is voltage?

Segway P. 764

"A variety of phrases are used to describe the potential difference between two points, the most common being voltage, arising from the unit for potential. A voltage "applied" to a device, such as a television, or "across" a device is the same as the potential difference across the device. If we say that the voltage applied to a light bulb is 120 volts, we mean that the potential difference between the two electrical contacts on the light bulb is 120 volts."

(4)

My interpretation:

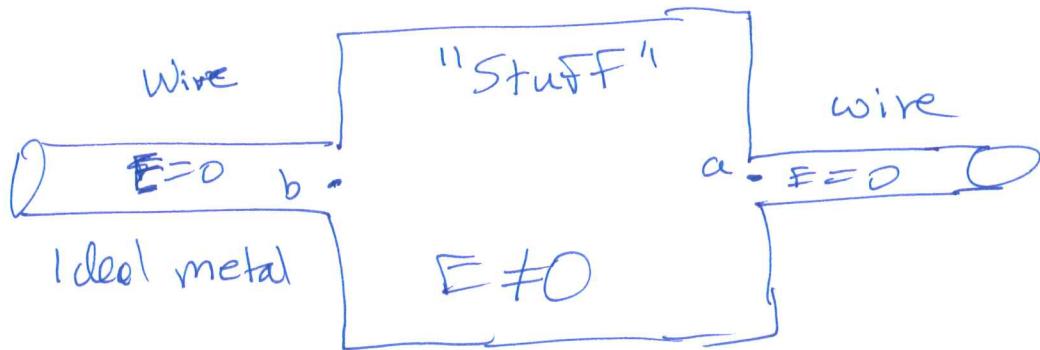

$$\Delta V = - \int_b^a E dx \neq 0$$

So inside "Stuff" there must be regions where $E \neq 0$.

In this class, we usually don't care about the details of E .

We mainly care about the relationship between I, V :

ANS

(5)

"Components"

Physical objects with ideal metal wires attached. Inside the objects $E \neq 0$.
 (Somewhere)

Resistor

$$\xrightarrow{R}$$

$$V = IR$$

Capacitor

$$\xrightarrow{C}$$

$$Q = CV \quad I = \frac{dq}{dt} = C \frac{dV}{dt}$$

Inductor

$$\xrightarrow{\text{loop}}$$


$$V = L \frac{dI}{dt}$$

Diode



$$I = I_0 (e^{qV/kT} - 1)$$

Transistor (3 terminal)

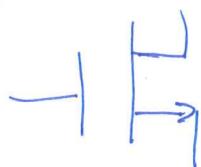

FET





BJT

(6)

An ideal voltage source Forces
 ΔV to be a constant value.

Voltage source

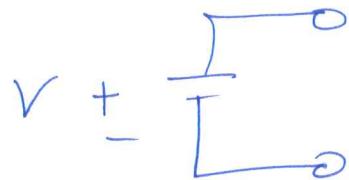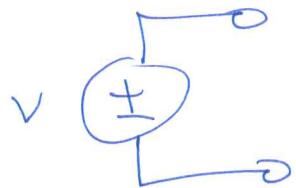


ac or dc


dc

(Battery is an almost ideal voltage source.)

Current source

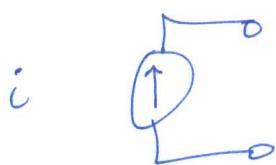

independent current source

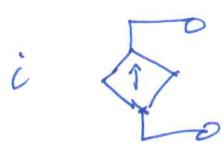

Dependent current source

i depends on what is
going on somewhere
else in circuit.

ac = alternating current

i depends on time
i independent of time

dc = direct current

Use of "ac" "dc" has evolved.

ac current = time dependent current


dc current = time independent current

ac voltage = time dependent voltage

dc voltage = time independent voltage

(+) (0) (0)

Power

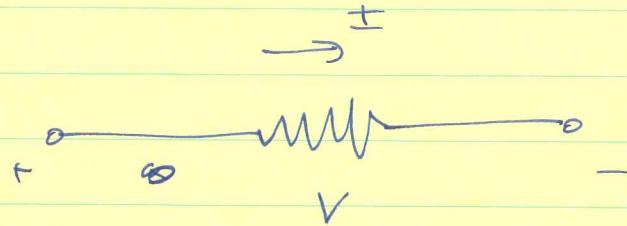

[This way
of like]

$$P = Vi \quad [\text{Watts}] = [V \cdot A]$$

Example light bulb 100 W


Oven 1 kW

wristwatch 1 mW

(8)

Fis.

Book 1.6
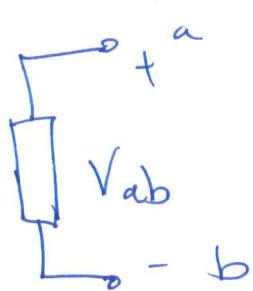
$$V_{ab} = - \int_b^a \mathbf{E} \cdot d\mathbf{x}$$

~~$$= - \int_a^b \mathbf{E} \cdot d\mathbf{x}$$~~

$$V_{ab} = \frac{dw}{dq}$$


 \equiv Δ

$$w = F \cdot x = q E_x$$

$$\frac{dw}{dq} = E_x = \int E dx$$

(4)

Some physical examples:


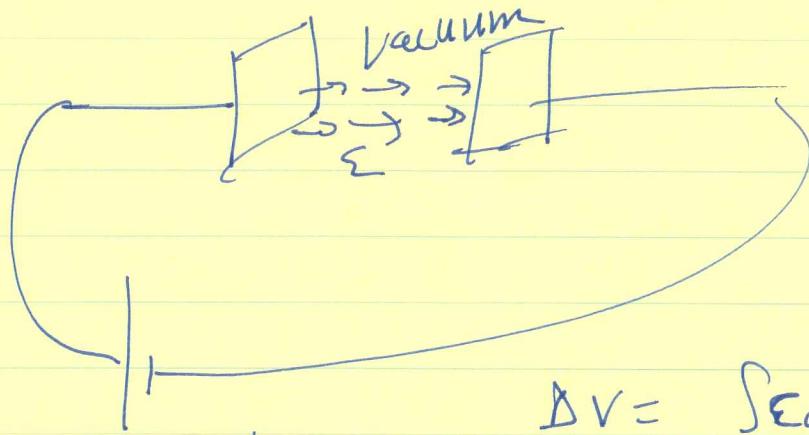


See page 767

$$\Delta V = \int \epsilon dx$$

$$= \epsilon L$$
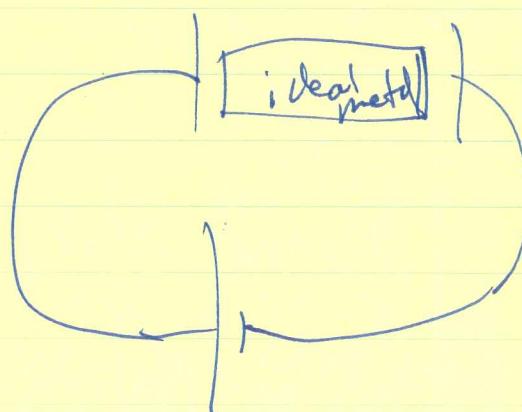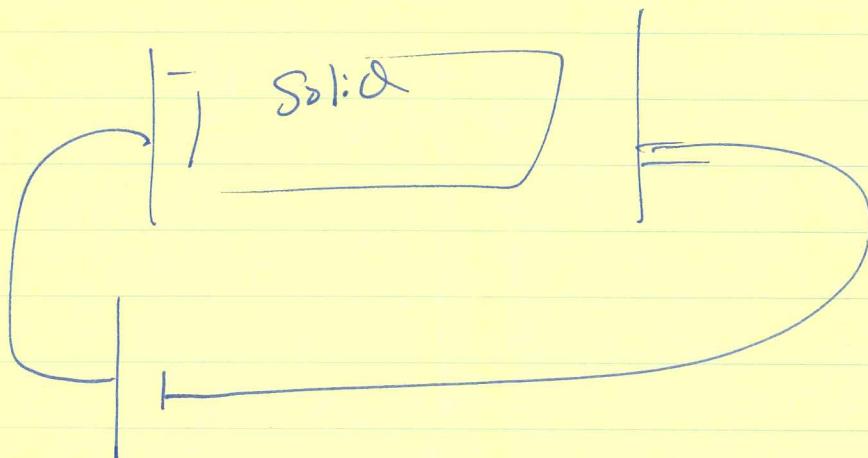
$$\Rightarrow \epsilon = \frac{\Delta V}{L}$$



It's not possible.
Source
Battery forces ΔV
but $\epsilon > 0$ everywhere.
Even an ideal voltage source
cannot make it happen for
ideal metal.