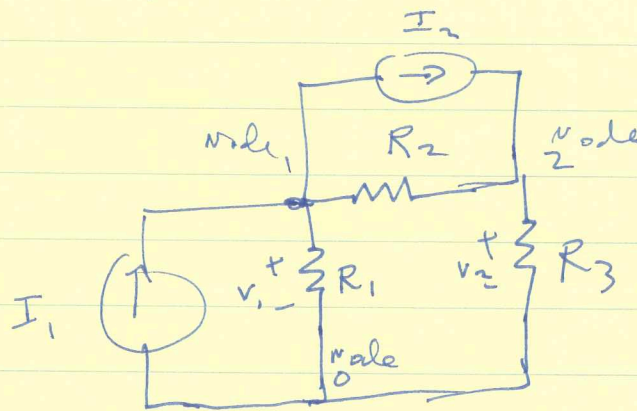


Revs. absolute. Power supply
 Nodal/Mesh analysis

Nodal


E.g.



- 1) Select ref node
- 2) KCL + Ohm
- 3) Solve V_n s.

STEP 1

Define reference node (ground)

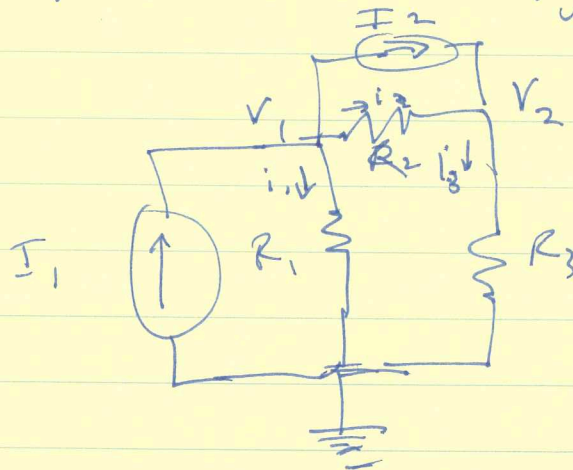

Node 0: Reference

STEP 2

Apply KCL,
 And Ohm's Laws

$$\cancel{I_1} + \cancel{I_2} \quad I_1 = I_2 + i_1 + i_2$$

$$I_2 + i_2 = i_3$$

$$i_1 = \frac{V_1 - 0}{R_1}$$

$$i_2 = \frac{V_1 - V_2}{R_2}$$

$$i_3 = \frac{V_2 - 0}{R_3}$$


Unknowns i_1, i_2, i_3
 V_1, V_2

5 eqns.

$$\begin{array}{rcl}
 (-1) i_1 & (-1) i_2 + 0 i_3 + 0 v_1 + 0 v_2 & = I_2 - I_1 \\
 (1) i_1 & + (0) i_2 + (0) i_3 + (0) v_1 + (0) v_2 & = V_1 / R_1 \\
 (0) i_1 & (-1) i_2 & + (0) i_3 + (0) v_1 + (0) v_2 = I_2 \\
 (1) i_1 & (1) i_2 & + (1) i_3 + \left(-\frac{1}{R_2}\right) v_1 + \left(+\frac{1}{R_2}\right) v_2 = 0 \\
 (0) i_1 & (0) i_2 & + (1) i_3 + (0) v_1 + \left(-\frac{1}{R_3}\right) v_2 = 0
 \end{array}$$

step 3 Solve for all 5.

If voltage source is present:

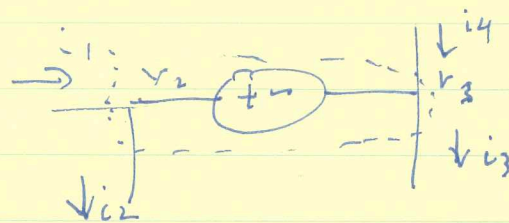

When we apply KCL, use "supernode" concept:

$$i_1 + i_4 = i_2 + i_3$$

Also need to apply KVL with a loop containing voltage source.

\Rightarrow n equations, n unknowns.

Simplify

$$I_1 = I_2 + i_1 + i_2$$

$$I_2 + i_2 = i_3$$

Express i_3 in terms of V_3 :

$$I_1 = I_2 + \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2}$$

$$I_2 + \frac{V_1 - V_2}{R_2} = \frac{V_2}{R_3}$$

Now only 2 unknowns V_1 , V_2 ($\#$ nodes)

2 eqns.

Called "Nodal analysis"

Allow us to find V s everywhere.

"Nodal analysis applies KCL to find unknown voltages in a given circuit."

"Mesh analysis applies KVL to find unknown currents."

Chapter 3, Problem 2.

For the circuit in Fig. 3.51, obtain v_1 and v_2 .

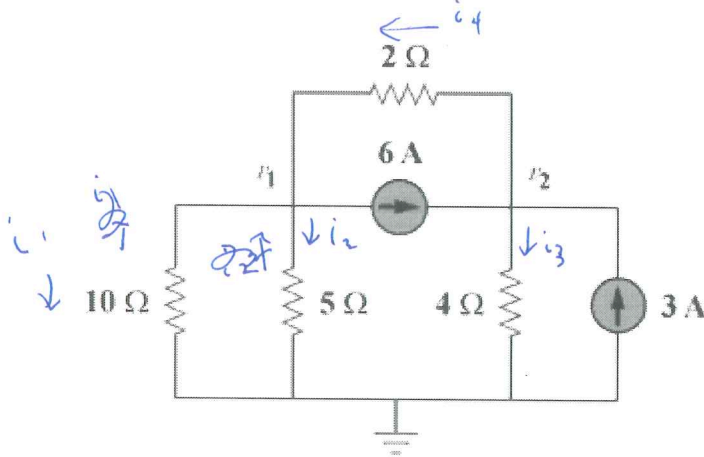


Figure 3.51

Solve voltages v_1, v_2 , currents everywhere

1) Ref
2) KCL + Ohm

Ohm

$$i_1 = \frac{v_1}{10}$$

$$i_2 = \frac{v_1}{5}$$

$$i_3 = \frac{v_2}{4}$$

$$i_4 = \frac{v_2 - v_1}{2}$$

Unknowns

$$i_1, i_2, i_3, v_1, v_2$$

Ohm reduces to:

$$v_1, v_2 \text{ unknowns}$$

KCL used to solve

KCL

$$+i_1 + i_2 + 6 = i_4$$

$$-i_4 + 6 = i_3 + 3 = 0$$

$$i_3 + i_4 = 6 + 3$$

$$\Rightarrow \textcircled{1} \quad +\frac{v_1}{10} + \frac{v_1}{5} + 6 = \frac{v_2 - v_1}{2}$$

$$\textcircled{2} \quad \frac{v_2}{4} + \frac{v_2 - v_1}{4} = 9$$

①② 2 eqns.
2 unknowns
 v_1, v_2 solve.
Kramer???

Chapter 3, Problem 15.

Apply nodal analysis to find i_o and the power dissipated in each resistor in the circuit of Fig. 3.64.

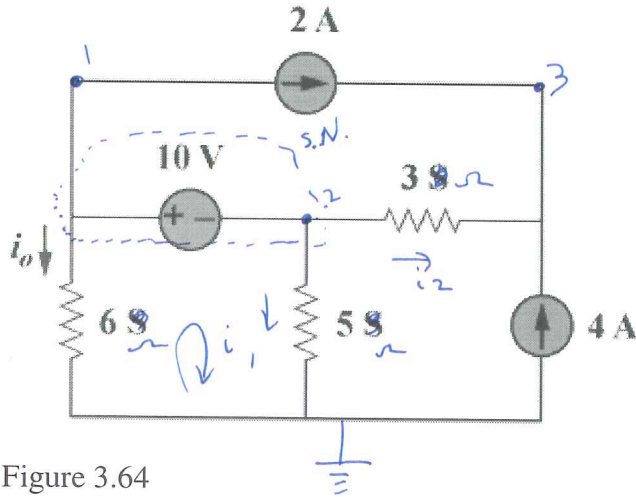


Figure 3.64

1) Ref
 2) Ohm
 KCL
 6 Unknowns
 i_o, i_1, i_2
 V_1, V_2, V_3

$$\begin{aligned} V_1 &= i_o \cdot 6 \\ V_2 &= i_1 \cdot 5 \\ V_2 - V_3 &= i_2 \cdot 3 \end{aligned} \quad \left. \begin{array}{l} \text{Ohm} \rightarrow \text{reduced to 3 unknowns} \\ i_o, i_1, i_2 \end{array} \right\}$$

S.N. KCL IN=OUT
 ① $0 = i_o + 2 + i_2 + i_1$


Node 3 KCL IN=OUT
 ~~$2 + i_2 = 4$~~ ② $2 + i_2 + 4 = 0$

Need KVL w/ loop containing voltage source

③ $-i_o \cdot 6 + 10 + i_1 \cdot 5 = 0$

3 eqn. 3 unknowns
 ① ② ③ i_o, i_1, i_2 Solve req w/ Kramer's rule

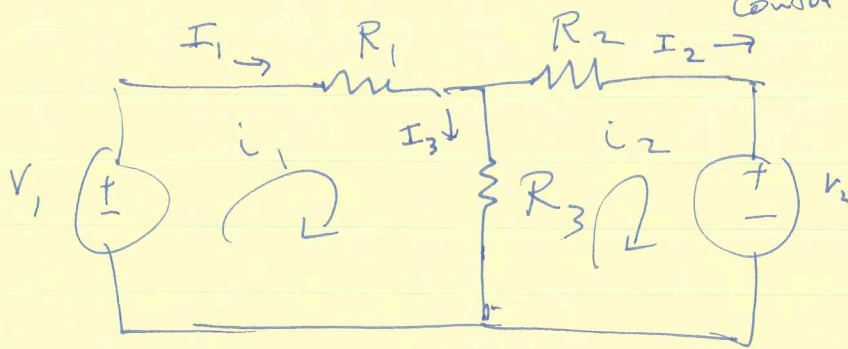Mesh: Closed loop that does not contain any other loops within it.



Mesh anal

- 1) Assign mesh currents i_1, i_2, \dots, i_n
- 2) Apply KVL
- 3) Solve eqns. for i_1, \dots, i_n

$$-V_1 + R_1 i_1 + R_3 (i_1 - i_2) = 0$$

$$R_2 i_2 + V_2 + R_3 (i_2 - i_1) = 0$$

2 eqns, 2 unknowns i_1, i_2

Solve

Nodal Anal vs Mesh Anal:

Depends on particular problem.

Chapter 3, Problem 73.

Write the mesh-current equations for the circuit in Fig. 3.117.

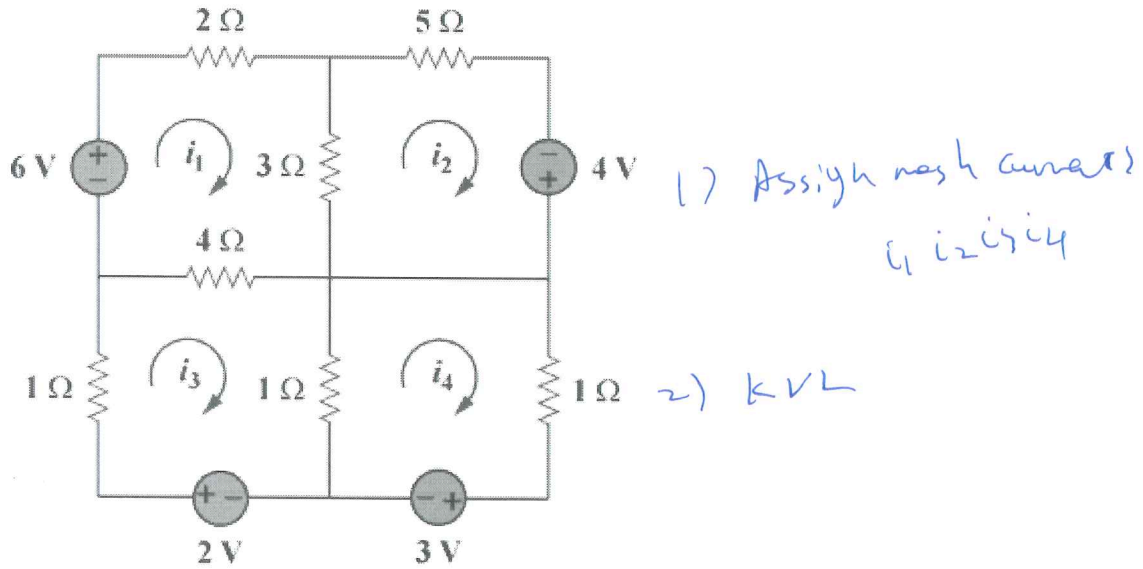


Figure 3.117

~~$-6V + 2i_1 + 3i_1 +$~~

① $-6 + 2i_1 + (i_1 - i_2)3 + (i_1 - i_3)4 = 0$

② $(i_2 - i_1)3 + i_2 5 - 4 = 0$

③ $i_3 \cdot 1 + (i_3 - i_1)4 + (i_3 - i_4)1 - 2 = 0$

④ $(i_4 - i_3) \cdot 1 + i_4 \cdot 1 + 3 = 0$

④ eqn ④ unknowns. solve.

Top mesh has current source, "supermesh", discuss in text.
lecture, time permitting.

Chapter 3, Problem 44.

Use mesh analysis to obtain i_o in the circuit of Fig. 3.90.


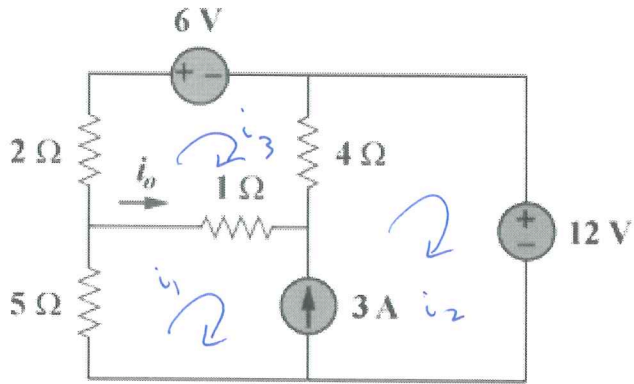


Figure 3.90

Supermesh:

- 1) Assign mesh currents
- 2) Remove current source.
- 3) Apply KVL for ~~circles~~ ~~loop~~ ~~loop~~
- 4) solve i_o in

Chapter 3, Solution 44.

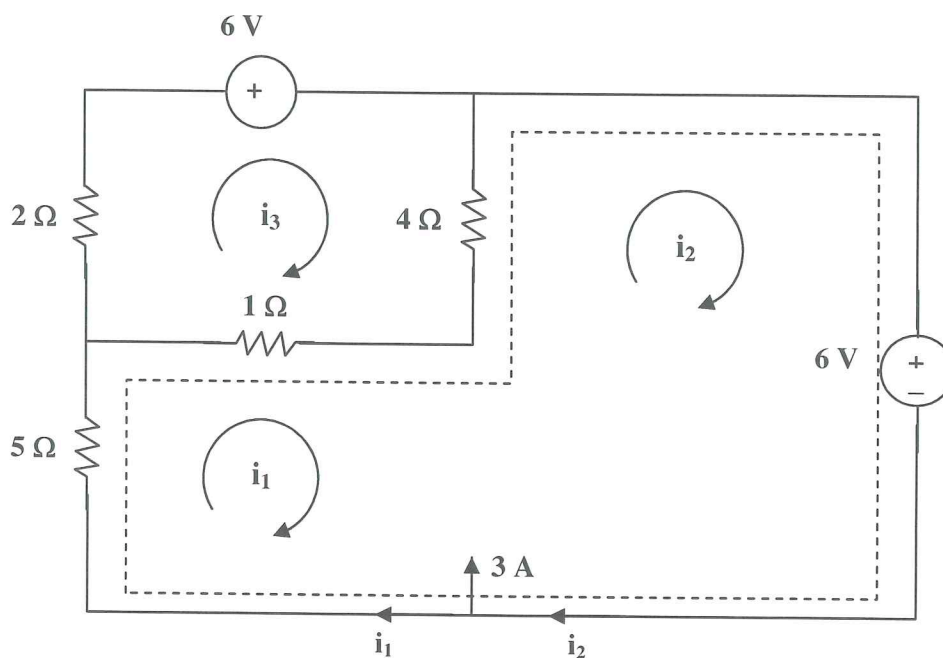

Loop 1 and 2 form a supermesh. For the supermesh,

$$5i_1 + (i_1 - i_3) \cdot 1 + (i_2 - i_3) \cdot 4 + 6 = 0$$

$$6i_1 + 4i_2 - 5i_3 + 12 = 0 \quad (1)$$

For loop 3,

$$-i_1 - 4i_2 + 7i_3 + 6 = 0 \quad (2)$$

$$i_3 \cdot 2 + 6 + (i_3 - i_2) \cdot 4 + (i_3 - i_1) \cdot 1 = 0$$

Also,

$$i_2 = 3 + i_1 \quad (3)$$

Solving (1) to (3), $i_1 = -3.067$, $i_3 = -1.3333$; $i_o = i_1 - i_3 = \underline{\underline{-1.7333 \text{ A}}}$

3 eqn $\odot \odot \odot$
 simultaneous i_1, i_2, i_3 solve \checkmark