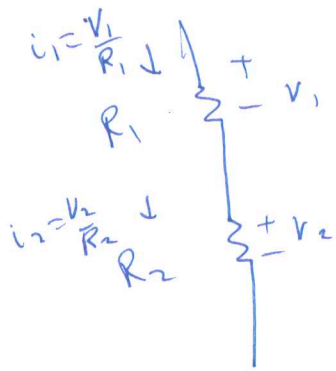



# Ch3: Nodal Analysis

## Ch 2 way



$v$  is voltage drop

## Ch 3 way

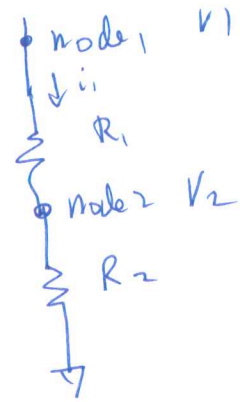

$$i_1 = \frac{v_1 - v_2}{R_1}$$


$$i_2 = \frac{v_2}{R_2}$$

$v_1$  is voltage of node 1 relative to node 0.

Two definitions, same symbol.

Sorry 😊

## Ch 2 way

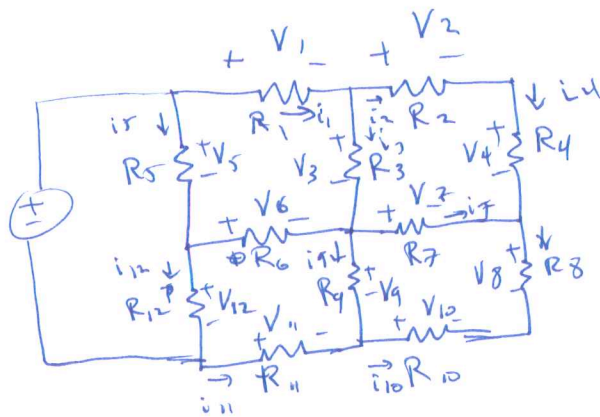

$$i_1 = V_1 R_1$$

$$i_2 = V_2 R_2$$

$$i_4 = V_4 R_4$$

$$i_8 = V_8 R_8$$

$$\vdots$$


Label voltages as drops across resistors.

Typical notation:  
 $V_1$  is voltage drop across  $R_1$ .  
 $i_1$  is current through  $R_1$ .
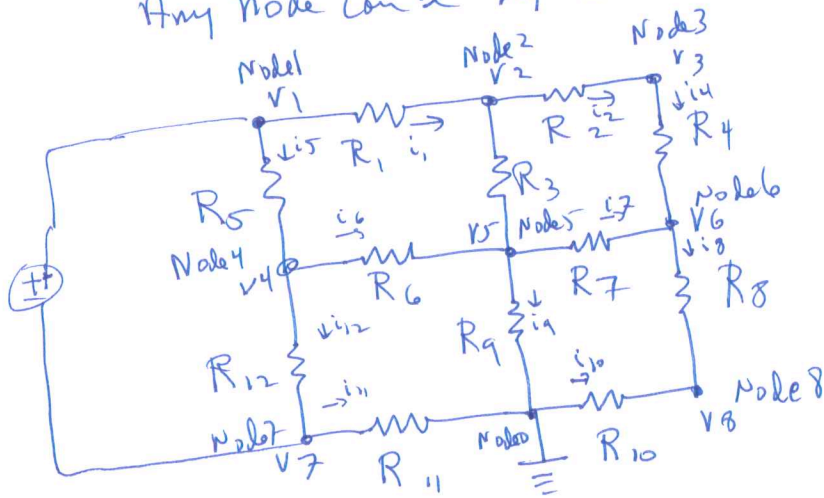
## Ch 3 way (better)

Label voltages of each node relative to a "reference" node. "Node 0"

Any node can be ref node. Typically on bottom of diagram.



Typical notation:  $i_1$  is current through  $R_1$  (same as Ch 2.)  
 $V_1$  is voltage of node 1 with respect to node 0.  
 Different.

Note: Ohm's law says  $V = IR$   
 $\uparrow$  Voltage drop across resistor

E.g.  $i_1 R_1 = \text{voltage drop across } R_1$   
 $= V_1 - V_2$

$$i_2 R_2 = V_2 - V_3$$

$$i_4 R_4 = V_3 - V_6$$

$$i_8 = V_6 - V_8$$

$$i_{10} = V_0 - V_8 = -V_8$$

$$i_{11} = V_7 - V_0 = V_7$$

$$i_{12} = V_4 - V_7$$

$$i_9 = V_5 - V_0 = V_5$$

$$i_7 = V_5 - V_6$$

$$i_6 = V_4 - V_5$$

$$i_5 = V_1 - V_4$$

Revs. absolute.


Power supply

Nodal/Mesh analysis

The break  
e.g.



Nodal or

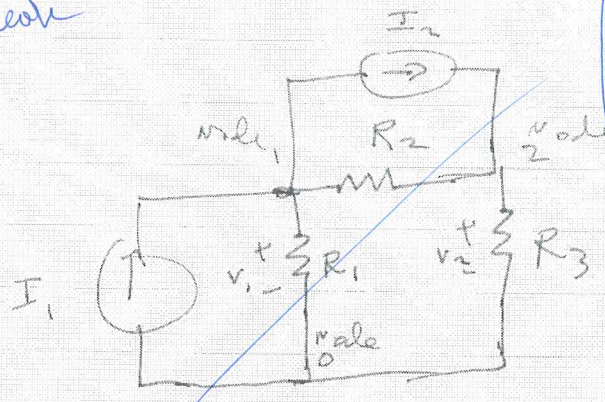- 1) Select ref node
- 2) KCL taken
- 3) Solve V's.



$n$  unknowns  $i_1, i_2, i_3, v_1, v_2$

STEP 1 Define reference node (ground)

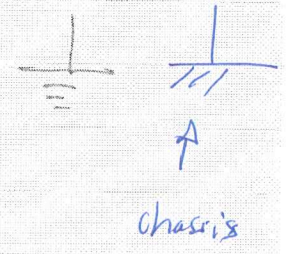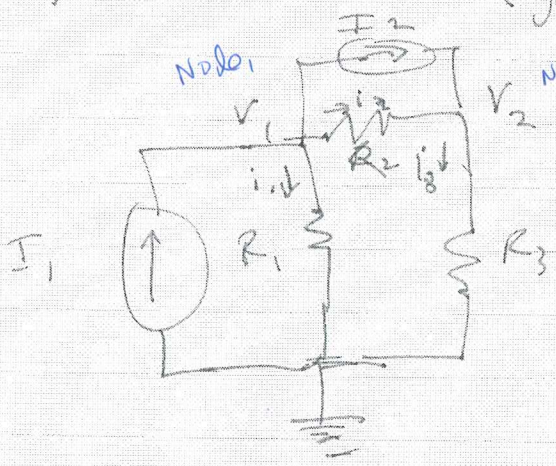

Node 0: reference

STEP 2 Apply KCL  $\leftarrow$  all nodes.  $I_1 + I_2 = I_2 + i_1 + i_2$   
 And Ohm's Laws (Not ref node.)  $I_2 + i_2 = i_3$

$$i_1 = \frac{v_1 - 0}{R_1}$$

$$i_2 = \frac{v_1 - v_2}{R_2}$$

$$i_3 = \frac{v_2 - 0}{R_3}$$

Unknowns  $i_1, i_2, i_3, v_1, v_2$

5 eqns.


Could do:

$$\begin{array}{rcl}
 (-1) i_1 & (-1) i_2 + 0 i_3 + 0 v_1 + 0 v_2 & = I_2 - I_1 \\
 (1) i_1 & + (0) i_2 + (0) i_3 + (0) v_1 + (0) v_2 & = V_1 / R_1 \\
 (0) i_1 & (-1) i_2 & (0) i_3 & (0) v_1 & (0) v_2 & = -I_2 \\
 (0) i_1 & (0) i_2 & (0) i_3 & (-\frac{1}{R_2}) v_1 & (+\frac{1}{R_2}) v_2 & = 0 \\
 (0) i_1 & (0) i_2 & (1) i_3 & (0) v_1 & (-\frac{1}{R_3}) v_2 & = 0
 \end{array}$$

~~Page 3~~ Solve for dls. (Hard way)

After p.3

voltage source is present:

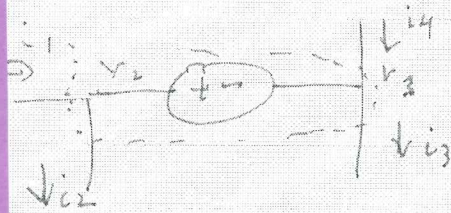

apply KCL, use "super node" concept:

$$i_1 + i_4 = i_2 + i_3$$

Also need to apply KVL with a loop containing voltage source.

$\Rightarrow$  n equations, n unknowns.

~~Easier way Step 3~~

~~Easier~~ Easier way

3

Simplify

Express all i's in terms of  $V$ 's:

$$I_1 = I_2 + i_1 + i_2$$

$$I_2 + i_2 = i_3$$

Express  $i$ 's in terms of  $V$ 's:

$$I_1 = I_2 + \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2}$$

$$I_2 + \frac{V_1 - V_2}{R_2} = \frac{V_2}{R_3}$$

Now only 2 unknowns  $V_1, V_2$  ( $\neq$  nodes)

2 eqns.

Step 3 Solve for nodal voltages. Then ohm to solve for  $i$  is called "Nodal analysis"

Allows us to find  $V$ 's everywhere.

Note: Only 2 eqns. instead of 5.

"Nodal analysis applies KCL to find unknown voltages in a given circuit."

Later

is KVL to find

**Chapter 3, Problem 3.**

Find the currents  $i_1$  through  $i_4$  and the voltage  $v_o$  in the circuit in Fig. 3.52.

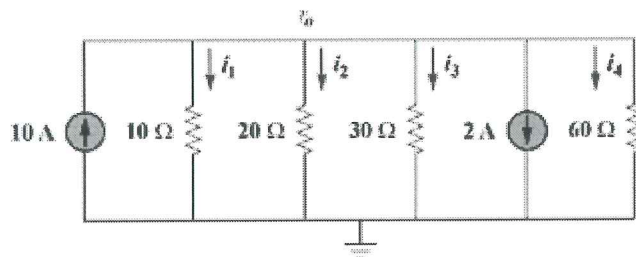


Figure 3.52

Unknowns  $i_1, i_2, i_3, i_4, v_o$

Would need 5 eqns if wanted to solve all.

Nodal Anal:

Step 1 ✓

Step 2

KCL @ all non-ref nodes:

$$10A = i_1 + i_2 + i_3 + 2A + i_4$$

then Ohm

$$v_o = i_1 \cdot 10\Omega$$

$$v_o = i_2 \cdot 20\Omega$$

$$i_1 = v_o/10$$

$$i_2 = v_o/20$$

$$i_3 = v_o/30$$

$$i_4 = v_o/60$$

Sub into KCL

$$10A = \frac{v_o}{10\Omega} + \frac{v_o}{20\Omega} + \frac{v_o}{30\Omega} + 2A + \frac{v_o}{60\Omega}$$

Step 3 Solve for nodal  $v_o$  (ages) (only 1 eqn!)

$$\Rightarrow v_o = \frac{8A}{\frac{1}{10\Omega} + \frac{1}{20\Omega} + \frac{1}{30\Omega} + \frac{1}{60\Omega}} = \frac{8A}{\frac{6+3+2+1}{60\Omega}} = \frac{8 \times 60}{12} A \cdot \Omega = 40V$$

(Go back (Ohm))  $i_1 = 4A$   $i_2 = 2A$   $i_3 = 1.33A$   $i_4 = 0.667A$

Bad news

Harder if voltage source present!


- (-1)  $i_1$  (
- (1) " + (
- (0) " (
- (1) " (
- (0) " (

- $v_2 = I_2 - I_1$
- " =  $V/R_1$
- " =  $I_2$
- " = 0
- " = 0

step 3

Solve

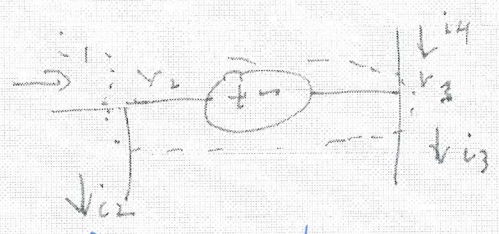If voltage source is present between 2 non-ref. nodes e.g.



Modify rules of nodal analysis:

When we apply KCL, use "super node" concept:

$$i_1 + i_4 = i_2 + i_3$$

Also need to apply KVL with a loop containing voltage source.

~~$n$  equations,  $n$  unknowns.~~



Chapter 3, Problem 15.

Apply nodal analysis to find  $i_o$  and the power dissipated in each resistor in the circuit of Fig. 3.64.

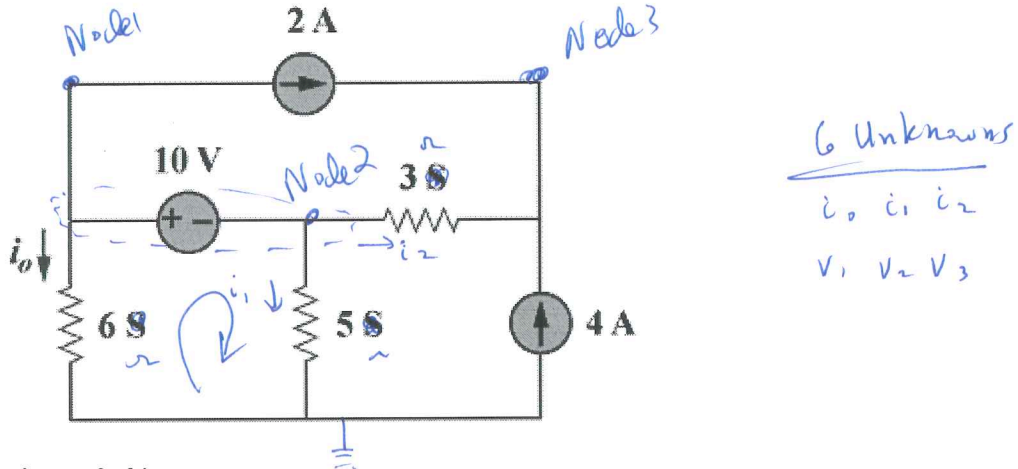


Figure 3.64

Step 1 Ref node  
 Step 2 KCL @ all nodes \*including "supernode"

KCL @ supernode

KCL @ Node 3

\* Need KVL w/ loop containing source (use  $i_s$  not  $V_s$ )

Now Ohm  $i_o = V_1/6$   $i_1 = V_2/5$   $i_2 = \frac{V_2 - V_3}{3}$

$$\left. \begin{aligned} 0 &= \frac{V_1}{6} + 2 + \frac{V_2 - V_3}{3} + \frac{V_2}{5} \\ 2 + \frac{V_2 - V_3}{3} + 4 &= 0 \\ -\frac{V_1}{6} \times 6 + 10 + \frac{V_2}{5} \times 5 &= 0 \end{aligned} \right\}$$

3 eqns.  
 3 unknowns.  
~~Solve for~~

Step 3 Solve  $V$ 's the ohm ins.

Chapter 3, Problem 2.

For the circuit in Fig. 3.51, obtain  $v_1$  and  $v_2$ .

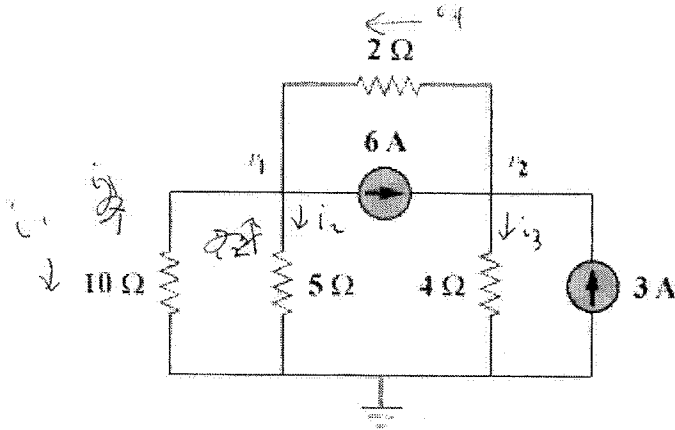


Figure 3.51

Solve voltages  $v_1, v_2$ , currents every where

1) Ref  
2) KCL + Ohm

$$i_1 = \frac{v_1}{10}$$

$$i_2 = \frac{v_1}{5}$$

$$i_3 = \frac{v_2}{4}$$

$$i_4 = \frac{v_2 - v_1}{2}$$

Ohm

Unknowns  
 $i_1, i_2, i_3, v_1, v_2$

Ohm relations to:

$v_1, v_2$  unknowns

KCL used to solve

KCL

$$+i_1 + i_2 + 6 = i_4$$

$$-i_4 + 6 = i_3 + 3 = 0$$

$$i_3 + i_4 = 6 + 3$$

$$\Rightarrow \textcircled{1} \quad \frac{v_1}{10} + \frac{v_1}{5} + 6 = \frac{v_2 - v_1}{4}$$

$$\textcircled{2} \quad \frac{v_2}{4} + \frac{v_2 - v_1}{4} = 9$$

①② 2 eqns.


2 unknowns

$v_1, v_2$  solve.

Kramer ???

Then find  $i_1, i_2, i_3$ .

Chapter 3, Solution 17.

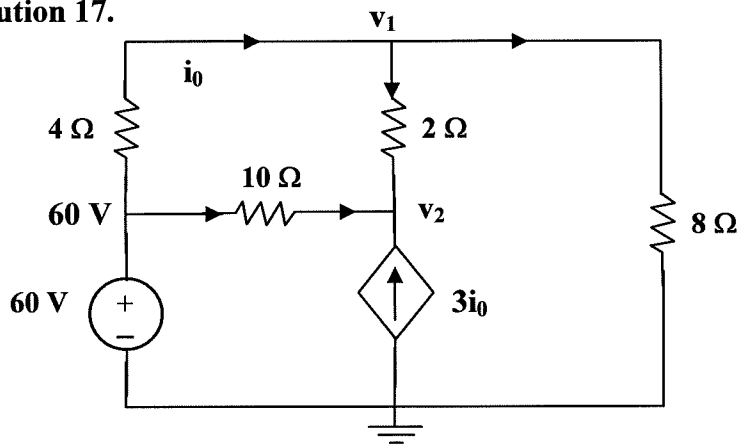

$$\text{At node 1, } \frac{60 - v_1}{4} = \frac{v_1}{8} + \frac{v_1 - v_2}{2} \quad 120 = 7v_1 - 4v_2 \quad (1)$$

$$\text{At node 2, } 3i_0 + \frac{60 - v_2}{10} + \frac{v_1 - v_2}{2} = 0$$

$$\text{But } i_0 = \frac{60 - v_1}{4}.$$

Hence

$$\frac{3(60 - v_1)}{4} + \frac{60 - v_2}{10} + \frac{v_1 - v_2}{2} = 0 \longrightarrow 1020 = 5v_1 + 12v_2 \quad (2)$$

$$\text{Solving (1) and (2) gives } v_1 = 53.08 \text{ V. Hence } i_0 = \frac{60 - v_1}{4} = \underline{\underline{1.73 \text{ A}}}$$