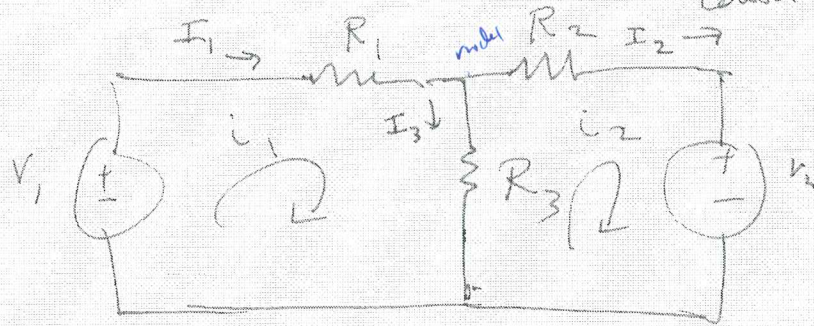


# Mesh Analysis

Mesh: Closed loop that does not contain any other loops within it.



Unknowns  $I_1$   $I_2$   $I_3$   $V_{node1}$  4

## Mesh anal

- 1) Assign mesh currents  $i_1, i_2, \dots, i_n$
- 2) Apply KVL to each mesh.
- 3) Solve eqns. for  $i_1, \dots, i_n$

$$-V_1 + R_1 i_1 + R_3 (i_1 - i_2) = 0$$

$$R_2 i_2 + V_2 + R_3 (i_2 - i_1) = 0$$

2 eqns. 2 unknowns  $i_1, i_2$


Solve

Node Anal vs Mesh Anal:

Depends on particular problem.

Chapter 3, Problem 73.

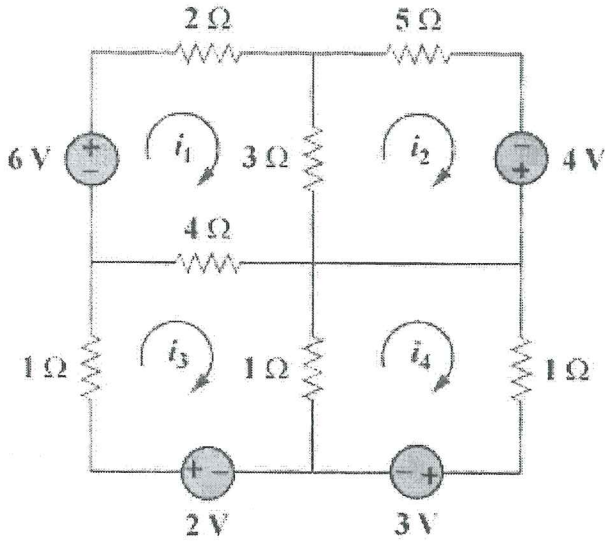Write the mesh-current equations for the circuit in Fig. 3.117.



Unknowns  
 Unknowns  
 Current thru each ~~res~~ component = 11  
 Voltage @ each node (not ref) (8V)  
 $\sum = 18$

1) Assign mesh currents  
 $i_1, i_2, i_3, i_4$

2) KVL

Figure 3.117

Mesh: 4 mesh currents

~~$-6V + 2i_1 + 3i_1 + \dots$~~

①  $-6 + 2i_1 + (i_1 - i_2)3 + (i_1 - i_3)4 = 0$

②  $(i_2 - i_1)3 + i_2 5 - 4 = 0$

③  $i_3 \cdot 1 + (i_3 - i_1)4 + (i_3 - i_4)1 - 2 = 0$

④  $(i_4 - i_3) \cdot 1 + i_4 \cdot 1 + 3 = 0$

④ eqn ④ unknowns. solve.

If mesh has current source, "supermesh", discuss in text.  
 lecture, time permitting.


Bad news @ Mesh:

If current source present:

Case 1 in only 1 mesh, easy:  
Determining current of that mesh.

Case 2 in 2 meshes

e.g.


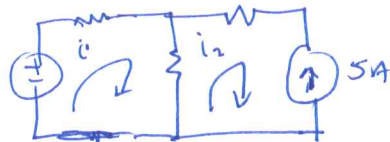


$$i_2 = -5 \text{ A}$$

Case 2 in 2 meshes:  
"Supermesh"

remove current source

Take:

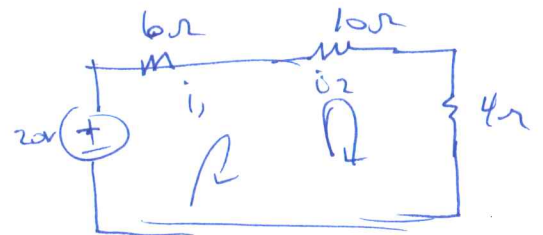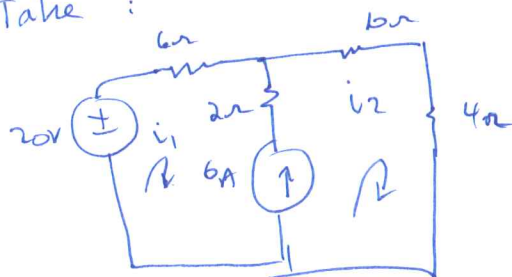

Replace:  
New rules:

KVL to each mesh as usual

$$6i_1 + 14i_2 = 20$$

\* New: KCL  $i_1 + 6 = i_2$   
to the mesh

Solve for  $i_1$ 's.

Chapter 3, Problem 44.

Use mesh analysis to obtain  $i_o$  in the circuit of Fig. 3.90.


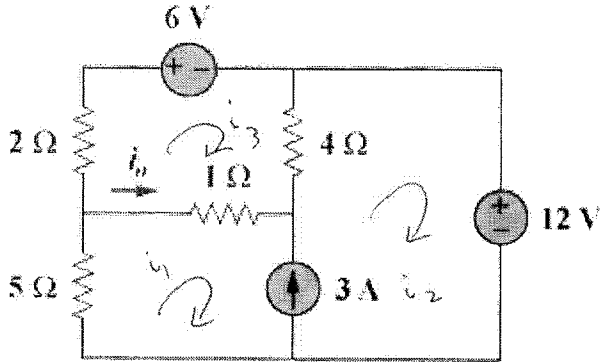


Figure 3.90

Supermesh:

- 1) Assign mesh currents
- 2) Remove current source.
- 3) Apply KVL for ~~circles~~ ~~loop~~ ~~loop~~
- 4) Solve  $i_o$  in  $i_1$

Chapter 3, Solution 44.

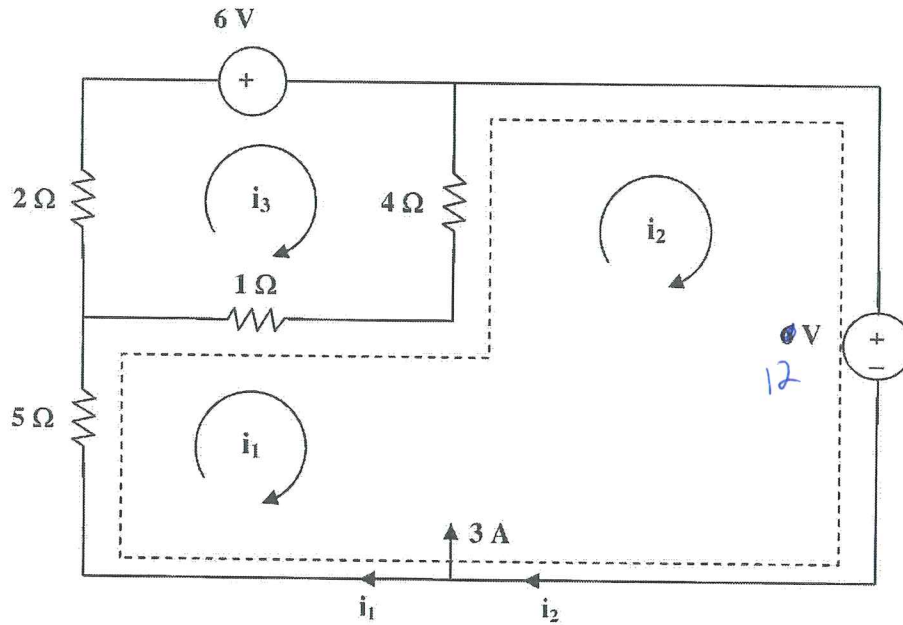

Loop 1 and 2 form a supermesh. For the supermesh,

$$5i_1 + (i_1 - i_3) \cdot 1 + (i_2 - i_3) \cdot 4 + 12 = 0$$

$$6i_1 + 4i_2 - 5i_3 + 12 = 0 \quad (1)$$

For loop 3,

$$-i_1 - 4i_2 + 7i_3 + 6 = 0 \quad (2)$$

$$i_3 \cdot 2 + 6 + (i_3 - i_2) \cdot 4 + (i_3 - i_1) \cdot 1 = 0$$

Also,


$$i_2 = 3 + i_1 \quad (3)$$

Solving (1) to (3),  $i_1 = -3.067$ ,  $i_3 = -1.3333$ ,  $i_0 = i_1 - i_3 = \underline{\underline{-1.7333 \text{ A}}}$

3 eqn  $\textcircled{1}$   $\textcircled{2}$   $\textcircled{3}$   
 simultaneous  $i_1, i_2, i_3$  solve  $\checkmark$

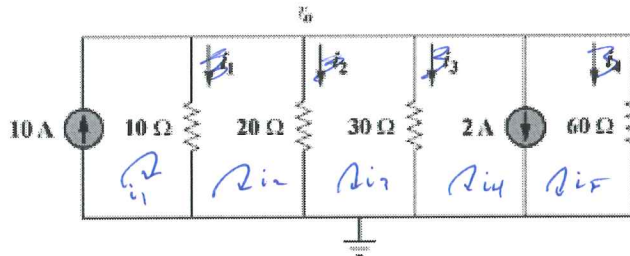**Chapter 3, Problem 3.**

Find the currents  $i_1$  through  $i_4$  and the voltage  $v_o$  in the circuit in Fig. 3.52.



Recall Nodal  $\rightarrow$  unknowns.  
But Nodal  $\Rightarrow$  only 1 eq. to solve  
Try mesh.


Figure 3.52

Mesh 5 unknowns  $i_1 - i_5$

$$i_1 = 10 \text{ A}$$

$$i_2 \cdot 10 + (i_2 - i_3) \cdot 20 = 0$$
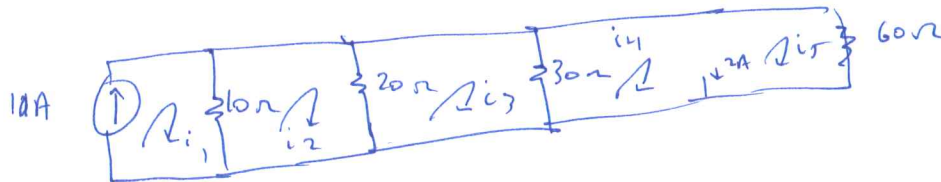
$$i_3 \cdot 30 - (i_3 - i_4) \cdot 30 = 0$$



KVL @ Supermesh  $i_4 \cdot 30 - i_5 \cdot 60 = 0$


KCL @ Supermesh  $i_4 + 2 \text{ A} - i_5 = 0$

Eqns. unknowns solve.

Nodal a better approach for this prob.

Chapter 3, Problem 73.

Write the mesh-current equations for the circuit in Fig. 3.117.

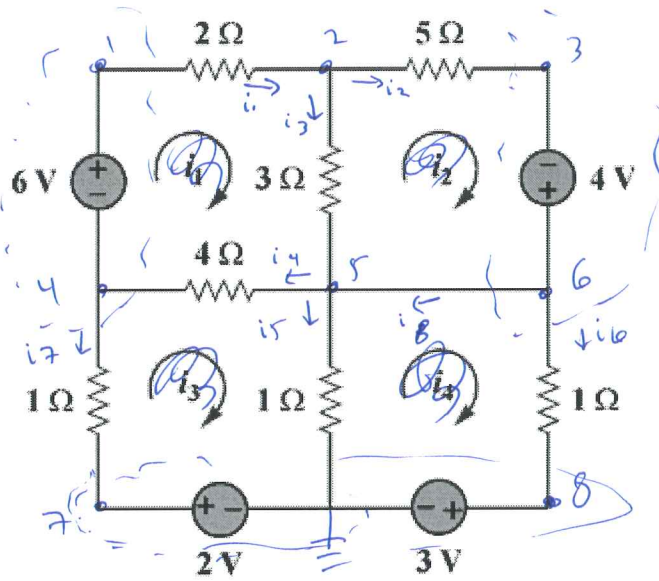

Unknowns 14  
 $V_1 - V_2$   
 $i_1 - i_8$

Figure 3.117

Try nodal:

$$V_8 = 3V$$

$$V_7 = 2V$$

KCL @ N2  $i_1 = i_2 + i_3$

N3 ...

N4 SW  $i_4 = i_1 + i_7$

SW  $i_2 = i_6 + i_8$

N5  $i_8 + i_3 = i_4 + i_5$

SN  $i_7 + i_5 + i_6 = 0$

KVL @ loop containing source (4x)

$$-6V + i_1 \cdot 2 + i_3 \cdot 3 + i_4 \cdot 4 = 0$$

$$-i_3 \cdot 3 + i_2 \cdot 5 - 4 = 0$$

$$-i_7 \cdot 1 - i_4 \cdot 4 + i_5 \cdot 1 - 2 = 0$$

$$-i_5 \cdot 1 + i_6 \cdot 1 + 3 = 0$$

Sub.

$$i_1 = \frac{V_1 - V_2}{2}$$

$$i_2 = \frac{V_2 - V_3}{5}$$

etc.

Solve 7 eqns. Unknowns ( $V_s$ ).  
 Complicated.