
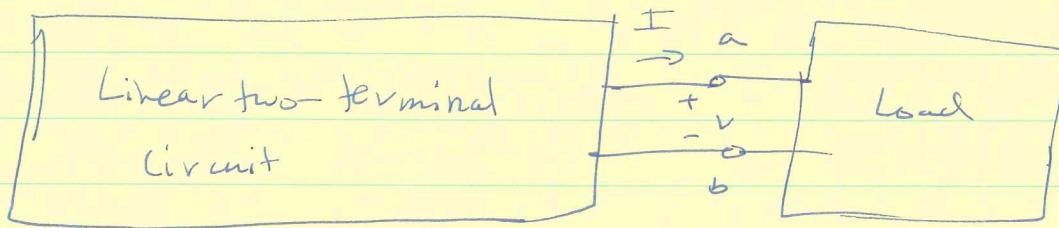


Correction  
active pp. pg + 52 ①

Thevenin Theorem      Th 4th week

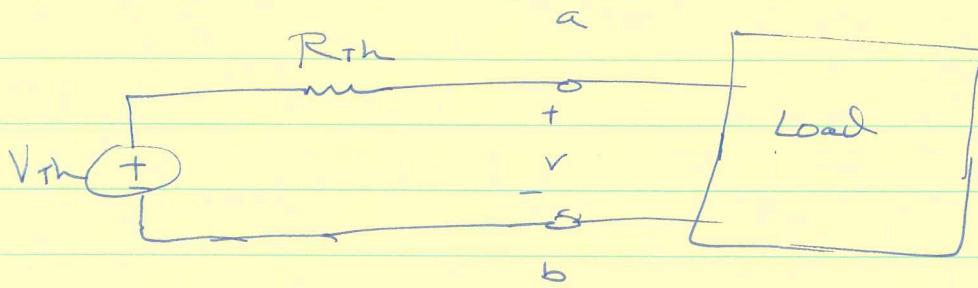

Equivalent to



$V_{Th}$  is open circuit voltage at terminals

$R_{Th}$  is input resistance when all independent sources turned off.


OR  $V_{Th}$  / Short circuited output current.

New concepts

Load

Input resistance

Load

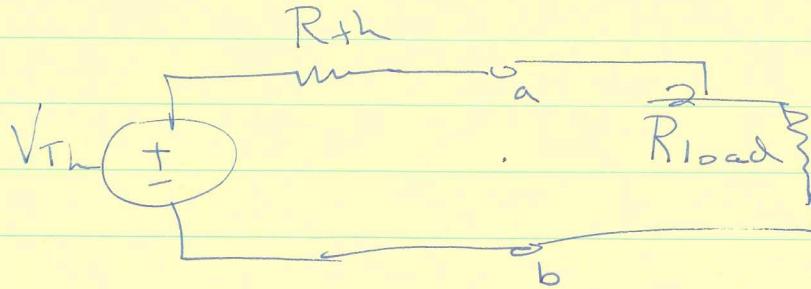


$$V_{ab} = V_{Th} \quad \text{if} \quad R_{load} \gg R_{th}$$


If  $R_{load} \approx R_{th}$  or less, it lowers  $V_{ab}$ .

We say the circuit is "loaded down".


(2)

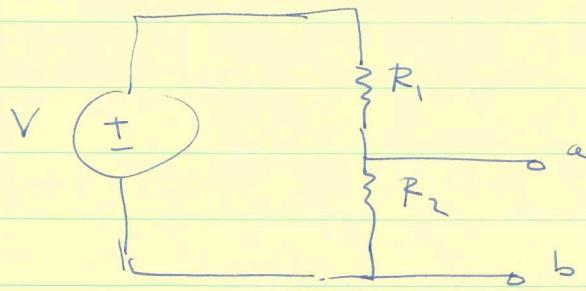Example


$$V_{Th} = V \frac{R_2}{R_1 + R_2}$$

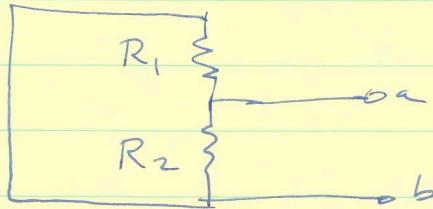To Find  $R_{Th}$ 

$$\Rightarrow R_{Th} =$$

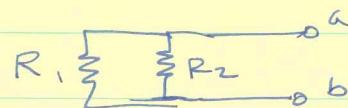

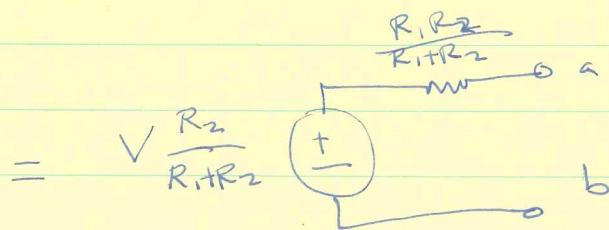
$$\Rightarrow R_{Th} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$



③


DVR

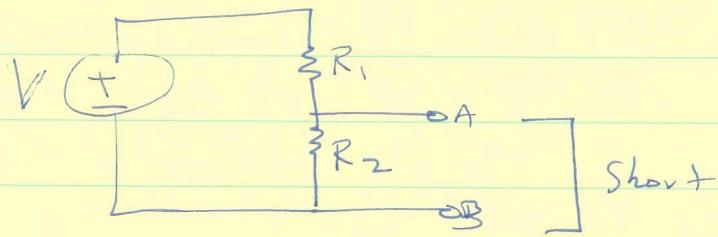

$$i = \frac{V}{R_1}$$

$$\Rightarrow R_{th} = V \frac{\frac{R_2}{R_1 + R_2}}{\frac{V}{R_1}} = \frac{R_1 R_2}{R_1 + R_2}$$

(4)

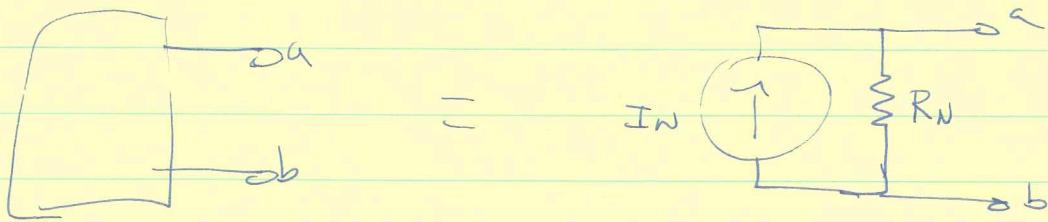Norton


Where

$$R_N = R_{th}$$

$$I_N = V_{th} / R_{th}$$

(5)


## Power

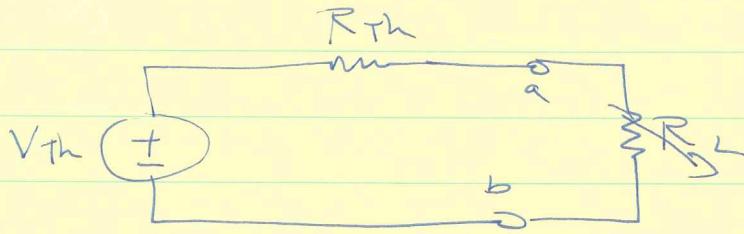

arrow means  
 $R_L$  variable

Power delivered to load:
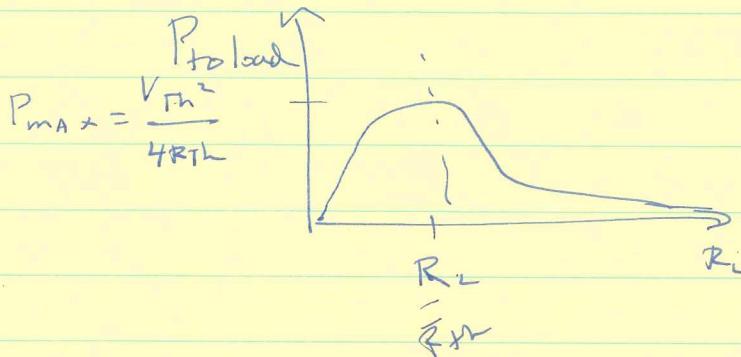
$$P = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$



$$P_{max} = \frac{V_{Th}^2}{4R_{Th}}$$