

Integrated circuit

Op amps

Show circ diagram \odot AD741

Spec sheet New \odot 1st

List of useful ones H/H


Useful for analog electronics.

Picture
Pinout

INA105

AD624
INA110

Ideal

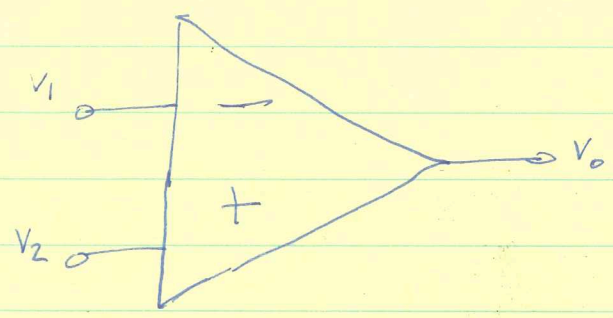


$$V_o = A V_d = A (V_2 - V_1)$$

$A \rightarrow \infty$ ideal

A large (real) $10^5 - 10^8$

Current into terminals 1, 2 = 0.

Real

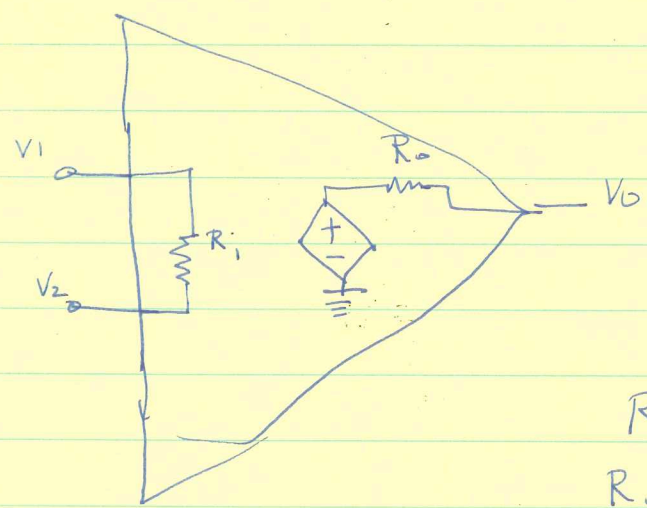



$R_i = 10^5$ to $10^{13} \Omega$ ∞ ideal

$R_o = 10$ to 100Ω 0 ideal

Need power supply $\rightarrow V_{cc}^+ V_{cc}^-$

\odot

Power supply

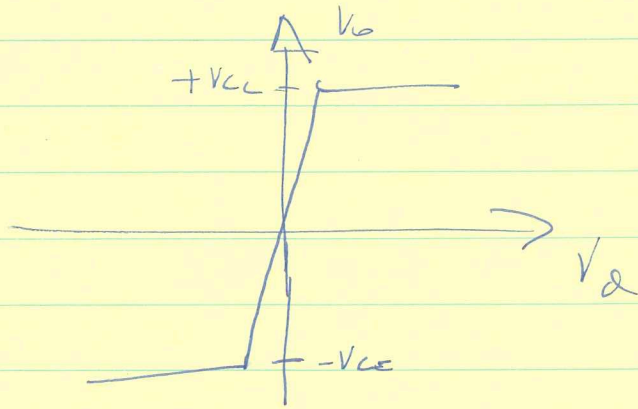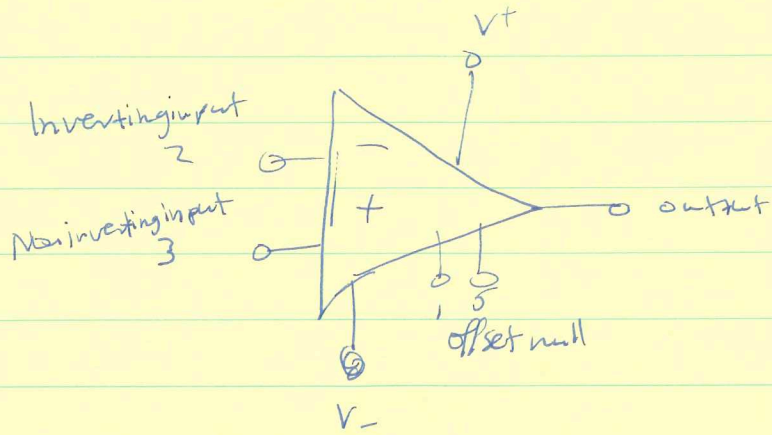

Useful circuits

Buffer.

Inverting amp

Non-inverting amp

Adder

Subtractor

PACInst amp. (CMRR) dB

CNR to voltage converter

In all analysis

 $i = 0$ inputsGain $\rightarrow \infty$ but use feedback.

Output adjusts itself so that

$$V_2 - V_1 = 0$$


General idea: ∞ gain amplifier very useful.

Generally can be made into many different circuits.

Buffer

Voltage Follower

Unity gain ~~amp~~ amplifier

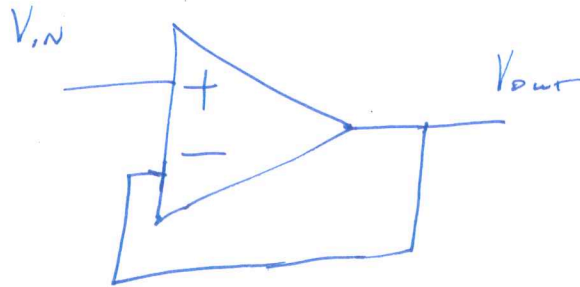


$$V_{out} = V_{in}$$


Why? won't load circuit.

Eg.

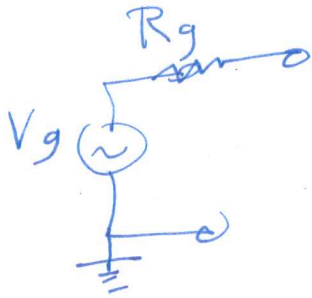
want V_g @ R_{load} even if $R_{load} \approx R_g$



Then

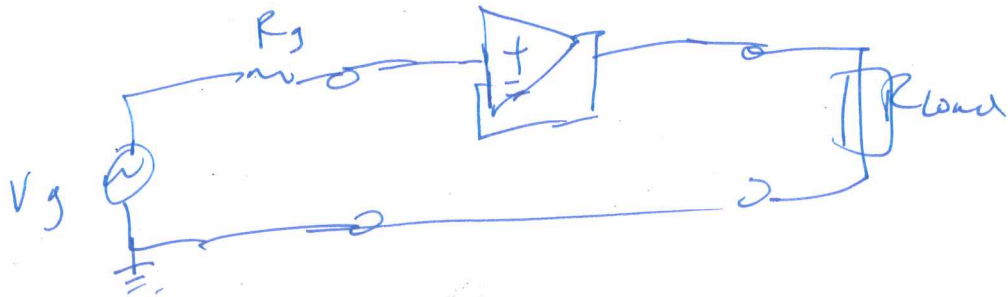

INVERTING AMP

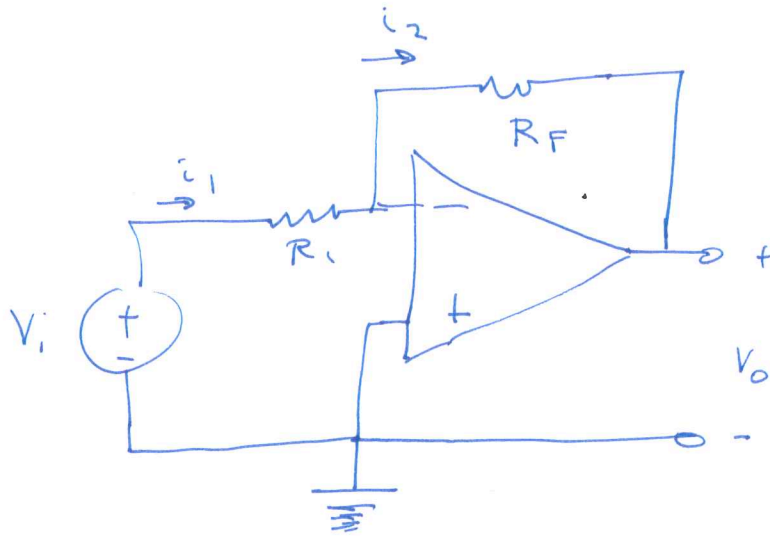

$$i_1 = i_2$$

$$\Rightarrow \frac{V_i - V_1}{R_1} = \frac{V_1 - V_o}{R_F}$$

$$V_1 = V_2 = 0$$

\Rightarrow

$$\frac{V_i}{R_1} = -\frac{V_o}{R_F}$$

$$= \boxed{\frac{V_o}{V_i} = -\frac{R_F}{R_1}}$$

What is input resistance?

R_1

eg. $R_F = R_1$

$$\frac{V_o}{V_i} = -1$$


INVERTER

$$V_i = -i_1 R_1$$

Non inverting amp

$$V_o - V_i = i_2 R_F$$

$$i_2 = i_1$$

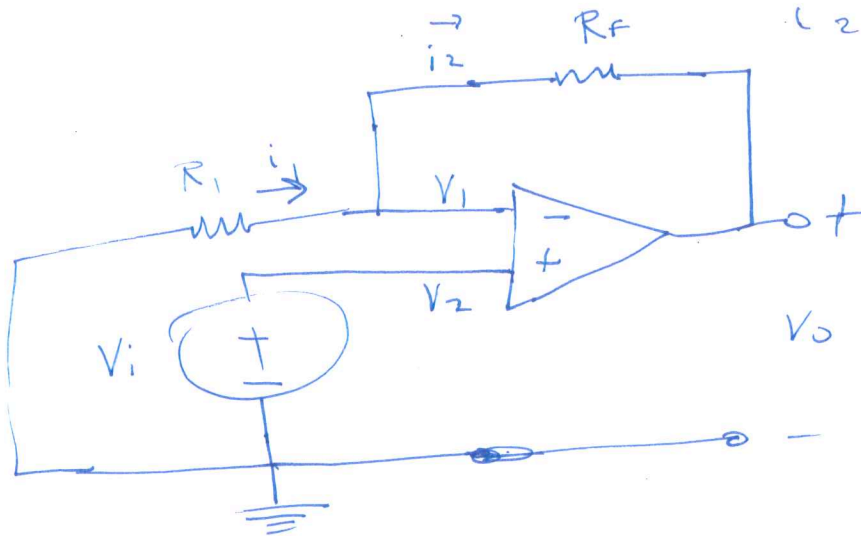

$$i_1 = i_2 = 0 \Rightarrow \frac{0 - V_1}{R_1} = \frac{V_1 - V_o}{R_F}$$


$$V_1 = V_2 = V_i$$

$$\Rightarrow \frac{-V_i}{R_1} = \frac{V_i - V_o}{R_F}$$

$$\Rightarrow V_o = \left(1 + \frac{R_F}{R_1}\right) V_i$$

$R_F = 0 \Rightarrow V_o = V_i$ voltage follower
unity gain ~~buffer~~ amplifier
"buffer"

Adder

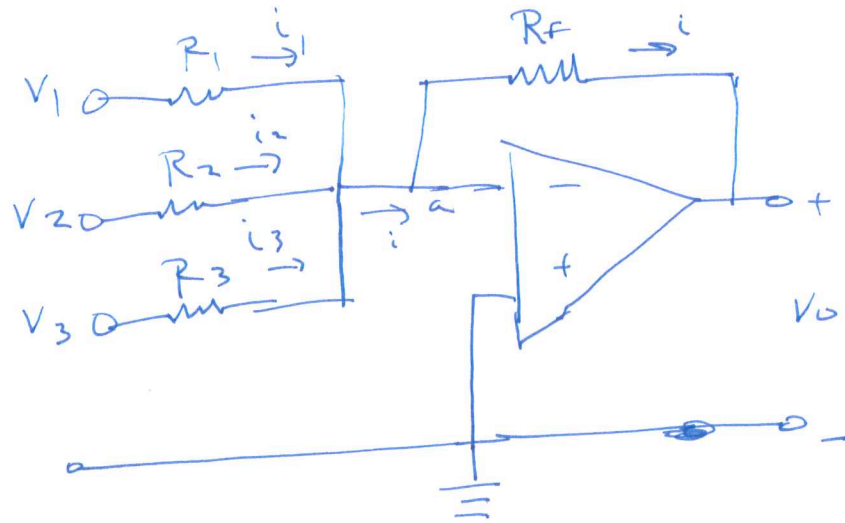

$$i = i_1 + i_2 + i_3$$


Node a @ 0.

$$\Rightarrow i_1 = \frac{V_1}{R_1} \quad i_2 = \frac{V_2}{R_2} \quad i_3 = \frac{V_3}{R_3}$$

$$i = \frac{-V_0}{R_F}$$

$$\Rightarrow V_0 = - \left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 \right)$$

Subtractor (Differential amplifier)

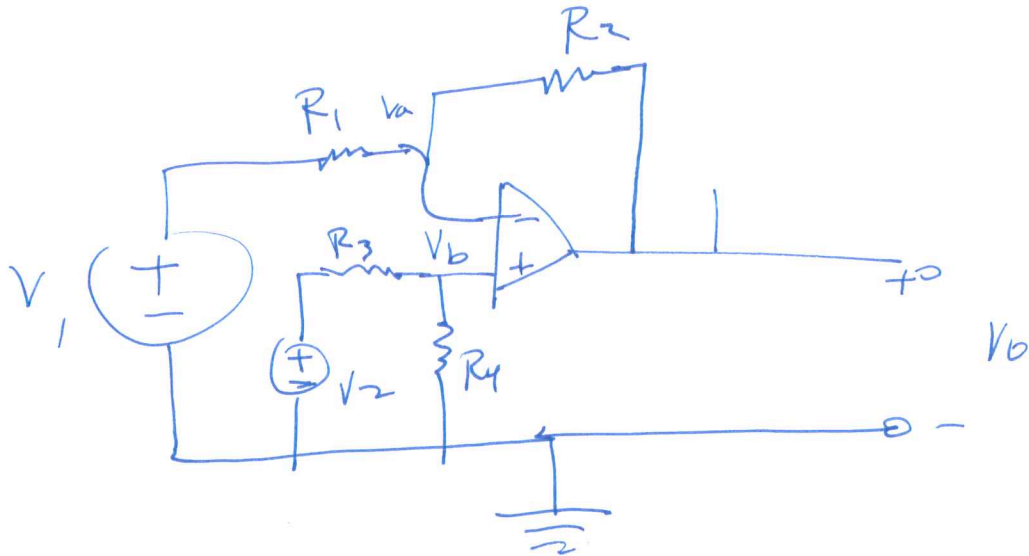

$$\frac{V_2 - V_b}{R_3} = \frac{V_b}{R_4} \Leftrightarrow V_b = \frac{R_4}{R_3 + R_4} V_2$$

$$\frac{V_1 - V_a}{R_1} = \frac{V_a - V_0}{R_2} \Leftrightarrow V_0 = \left(\frac{R_2}{R_1} + 1 \right) V_a - \frac{R_2}{R_1} V_1$$

But $V_a = V_b$

$$\Rightarrow V_0 = \left(\frac{R_2}{R_1} + 1 \right) \frac{R_4}{R_3 + R_4} V_2 - \frac{R_2}{R_1} V_1$$

$$\Rightarrow V_0 = \frac{R_2 (1 + R_1/R_2)}{R_1 (1 + R_3/R_4)} V_2 - \frac{R_2}{R_1} V_1$$


$$\text{If } \frac{R_1}{R_2} = \frac{R_3}{R_4} \Rightarrow V_0 = \frac{R_2}{R_1} (V_2 - V_1)$$

$$\text{If } R_2 = R_1 \quad R_3 = R_4 \\ \Rightarrow V_0 = V_2 - V_1$$

Differential Amp.

Show data sheet. (AD)

INST Amp

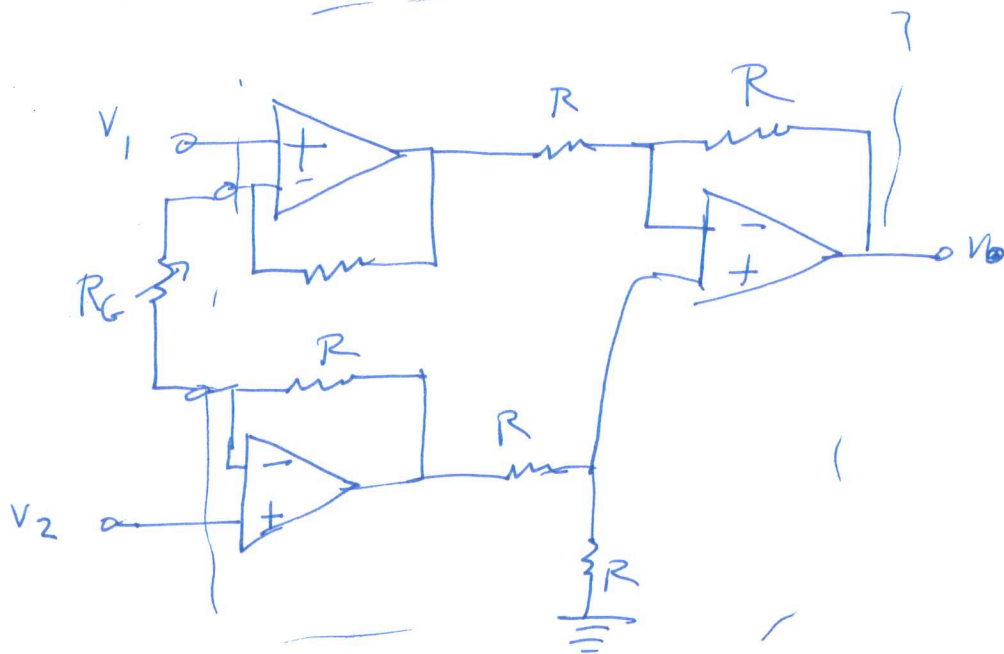

$$V_O = \left(1 + \frac{2R}{R_G}\right) V_{\text{diff}} (V_2 - V_1)$$

Features

- 1) Voltage gain set by one resistor.
- 2) V_1, V_2 high input impedance.
- 3) Good CMRR. (dB)

Show data sheet AD624

~~AD624~~

Durr Brown 110

130dB AD624

~~AD624~~



0.1µV/V

→ 10

→ 1000

90dB AD741
-120dB

~~ADC~~ DAC

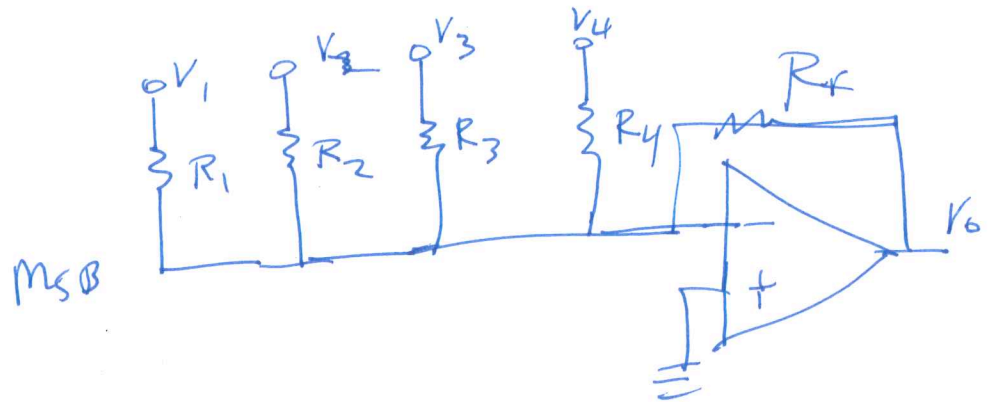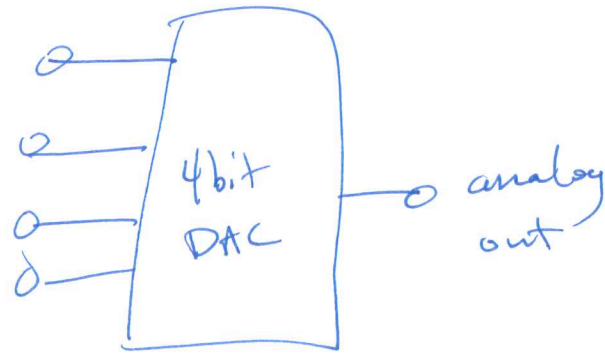

$$-V_0 = \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \frac{R_f}{R_4} V_4$$


2^4 different possible outputs V_0

depend on bits 1-4

show details here.

ADC is opposite, ~~more~~ harder to describe.

Current to voltage
converter

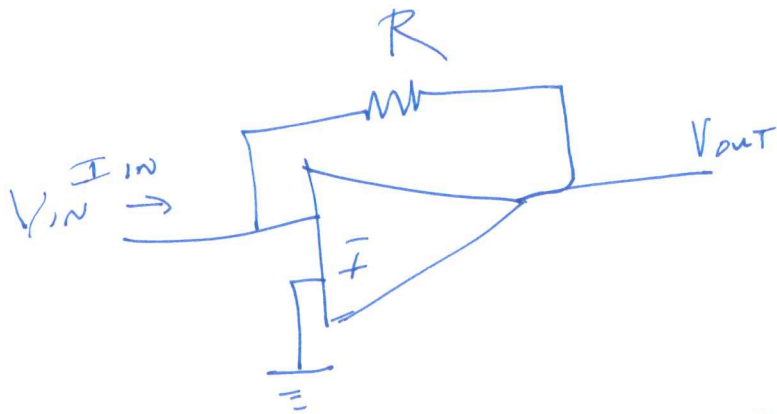

$$V_{out} = R I_{in}$$