

2nd ORDER CIRCUITS

RLC
First

(1)

Will get D.E. of Form

$$C_1 \frac{d^2 F(t)}{dt^2} + C_2 \frac{dF(t)}{dt} + C_3 F(t) = g(t)$$

C_1, C_2, C_3 constants $g(t)$ known.

To solve completely for $F(t)$
will need to know $F(t=0)$

and $\frac{dF}{dt} \Big|_{t=0}$.

Useful Part $V(t) = V(t=0)$ capacitor

$$\Rightarrow \frac{dV}{dt} \Big|_{t=0} = 0$$


$i(t) = i(t=0)$ inductor

$$\Rightarrow \frac{di}{dt} \Big|_{t=0} = 0$$

$\ddot{F} = aF$ Soln \cos, \sin with ω

$\Rightarrow F = \cos \omega t$

RLC

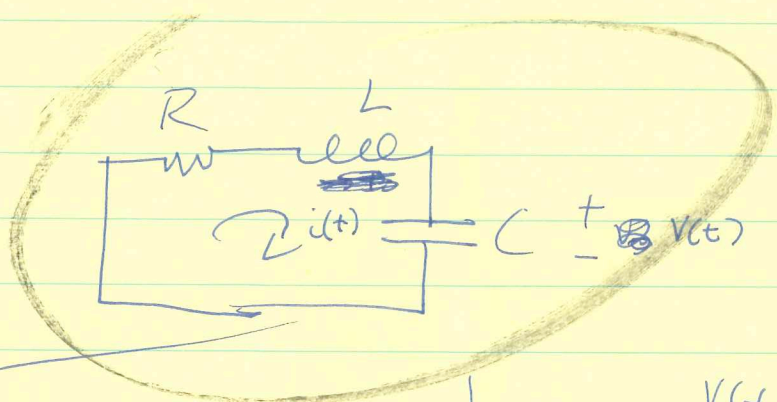

RINGING FIRST

$$V(t=0) = V_0$$

$$i(t=0) = I_0$$

RINGING ABLE
 PLUCKING & GAIN ARE STRONG
 ALL SAME MATH

KVL

$$i(t)R + L \frac{di(t)}{dt} + V(t) = 0$$

$$\Rightarrow \frac{di(t)}{dt} R + L \frac{d^2 i(t)}{dt^2} + \frac{dV(t)}{dt} = 0$$

$$\Rightarrow q(t) = CV(t)$$

$$i(t) = \frac{dq(t)}{dt} = C \frac{dV(t)}{dt}$$

$$\Rightarrow \frac{dV(t)}{dt} = \frac{1}{C} i(t)$$

$$\frac{di(t)}{dt} R + L \frac{d^2 i(t)}{dt^2} + \frac{1}{C} i(t) = 0$$

$$\Rightarrow \frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

(3)

Need to know $i(t=0)$ & $\left. \frac{di}{dt} \right|_{t=0}$

$$i(t=0) \equiv I_0$$

what about $\left. \frac{di}{dt} \right|_{t=0}$?

$$\text{KCL} \Big|_{t=0} \quad \underbrace{i(t=0)}_{I_0} R + L \left. \frac{di(t)}{dt} \right|_{t=0} + \underbrace{V(t=0)}_{V_0} = 0$$

$$\Rightarrow \left. \frac{di(t=0)}{dt} \right|_{t=0} = -\frac{1}{L} (R I_0 + V_0)$$

How to solve 2nd order D.E.?

Again, if we find $i(t)$ that

1) solves D.E.

2) solves initial values,

that solution is unique.

So "how we get there" (less important) than results

~~Ans~~ Answer is:

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

A_1, A_2 constants, determined by initial conditions.

$$s_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \quad s_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

(4)

We will try guessing $i(t) = A e^{st}$
 A, s Constants.

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

$$\Rightarrow s^2 A e^{st} + \frac{R}{L} s A e^{st} + \frac{1}{LC} A e^{st} = 0$$

$$\Rightarrow s^2 + \frac{R}{L} s + \frac{1}{LC} = 0 \quad (*)$$

Guess ~~on~~ works for any A but only for $s \Rightarrow$
 s soln. of $(*)$

$$\Rightarrow s_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$s_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Convenient to define $\omega_0 = \sqrt{\frac{1}{LC}}$ "Natural frequency"
 $\alpha = \frac{R}{2L}$ "Damping factor"

$$\Rightarrow s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\Rightarrow i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$


3 cases

"over damped" $\alpha > \omega_0$

$\Rightarrow s_1 -ve$

$s_2 -ve$

$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

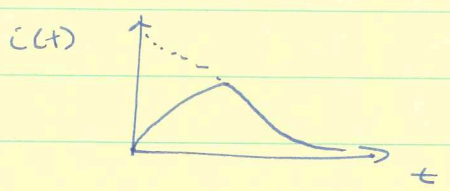


"critically damped" $\alpha = \omega_0$

$\Rightarrow s_1 = s_2 \Rightarrow i(t) = d$

Our guess was wrong.

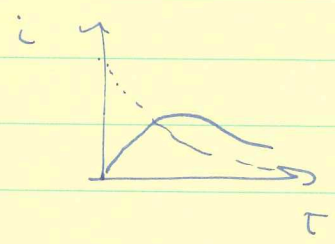$i(t) = \cancel{A_1} (A_2 + A_1 t) e^{-\alpha t}$



"Underdamped" $\alpha < \omega_0$

$$s_1 = -\alpha + \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha + j\omega_d$$

$$s_2 = -\alpha - \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha - j\omega_d$$

$$j \equiv \sqrt{-1} \quad \omega_d \equiv \sqrt{\omega_0^2 - \alpha^2} \quad \text{"damped nat. frequency"}$$

$$\Rightarrow i(t) = A_1 e^{-(\alpha - j\omega_d)t} + A_2 e^{-(\alpha + j\omega_d)t}$$


$$= e^{-\alpha t} (A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t})$$

$$e^{j\theta} = \cos\theta + j \sin\theta \quad e^{-j\theta} = \cos\theta - j \sin\theta$$


$$i(t) = e^{-\alpha t} \left[A_1 (\cos(\omega_d t) + j \sin(\omega_d t)) + A_2 (\cos(\omega_d t) - j \sin(\omega_d t)) \right]$$

$$= e^{-\alpha t} \left[\underbrace{(A_1 + A_2)}_{B_1} \cos(\omega_d t) + j \underbrace{(A_1 - A_2)}_{B_2} \sin(\omega_d t) \right]$$
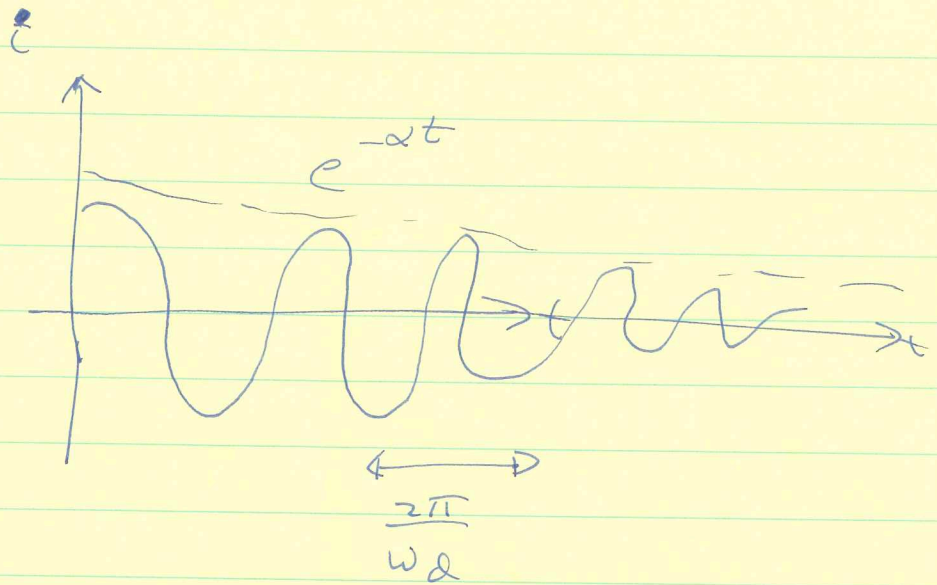
$$i(t) = e^{-\alpha t} \left[B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t) \right]$$



1st before math
 ← "Ringing" "Damping".

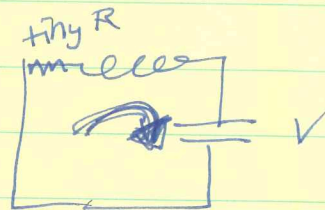

Energy
 $\frac{1}{2}Li^2$ $\frac{1}{2}Ee$ $\frac{1}{2}CV^2$

Initially $i=0$ $V \neq 0$ 0 $\neq 0$

$V \neq 0 \Rightarrow i \uparrow$

$i \neq 0 \Rightarrow V \downarrow$
 ~~$V \downarrow \Rightarrow i \downarrow$~~

$i \uparrow \Rightarrow q \downarrow$

$i \uparrow \Rightarrow \frac{di}{dt} \uparrow$

$\frac{di}{dt} \uparrow \Rightarrow V \downarrow$

$\frac{1}{2}CV^2 \downarrow$
 $\frac{1}{2}Li^2 \uparrow$

Eventually $V=0$ $i \neq 0$ $\neq 0$ 0

$$\begin{array}{ccc}
 \cancel{V} = 0 & \longleftrightarrow & i \neq 0 \\
 & & \frac{1}{2} LI^2 \\
 & & \neq 0 \\
 i \neq 0 \Rightarrow q \uparrow & & \frac{1}{2} CV^2 \\
 & & \neq 0 = 0 \\
 & & \text{⊗} \\
 q \uparrow \Rightarrow V \uparrow & &
 \end{array}$$

Energy goes back and forth between $\frac{1}{2} CV^2$ and $\frac{1}{2} LI^2$
 Frequency is ω_0 or ω_D .

$\neq P$ $R=0$, no loss of energy.

If $R \neq 0$, always losing some energy, eventually get all energy gone \Rightarrow
 $i=0$ $V=0$ \Rightarrow


Called "damping".

Damping rate R/L $\tau = L/R$
 Freq $\omega_0 = \sqrt{1/LC}$

CAPACITOR
CAPACITOR RESONANCE LIKE A SWING

2005

|| RLC

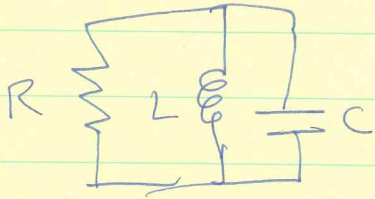

Given I_0 through L at $t=0$
 V_0 across C at $t=0$

KCL

$$\frac{V(t)}{R} + i_L(t) + i_C(t) = 0$$

$$i_C(t) = C \frac{dV(t)}{dt}$$

$$\Rightarrow \frac{V(t)}{R} + i_L(t) + C \frac{dV(t)}{dt} = 0$$

$$\frac{dV}{dt} \frac{1}{R} + \frac{di}{dt} + C \frac{d^2V}{dt^2} = 0$$

$$\frac{dV}{dt} \frac{1}{R} + \frac{V}{L} + C \frac{d^2V}{dt^2} = 0$$

$$\Rightarrow \left(\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0 \right)$$

$$V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$


OR $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Again 3 cases


Overdamped $\alpha > \omega_0$
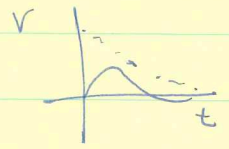
$$V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad s_1, s_2 \text{ -ve}$$



Critical damp $\alpha = \omega_0$

$$V(t) = (A_1 + A_2 t) e^{-\alpha t}$$

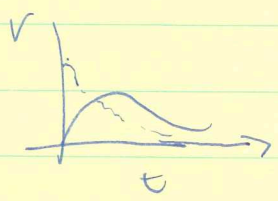

Underdamped $\alpha < \omega_0$


$$s_1 = -\alpha + \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha + j\omega_d$$

$$s_2 = -\alpha - \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha - j\omega_d$$

$$j = \sqrt{-1} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$s_{1,2} = -\alpha \pm j\omega_d \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$
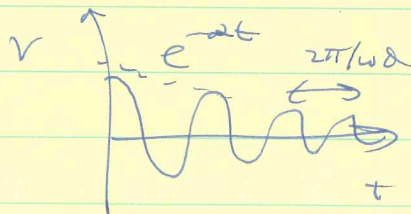
$$V(t) = e^{-\alpha t} (A_1 \cos \omega_d t + B_1 \sin \omega_d t)$$




To find A_1, A_2 need $v(0)$ and $\frac{dv}{dt} \Big|_{t=0}$

$v(0) = v_0$ known

$$(*) (*) \Rightarrow \frac{v_0}{R} + I_0 + C \frac{dv}{dt} \Big|_{t=0} = 0$$

$$\Rightarrow \frac{dv}{dt} \Big|_{t=0} = - \frac{(v_0 + RI_0)}{RC}$$

RLC step response

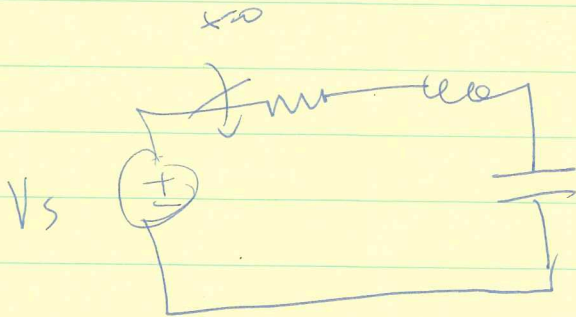

$$\text{KVL } L \frac{di}{dt} + Ri + v = V_s \quad t > 0$$

$$= 0 \quad t < 0$$

$$q = Cv \Rightarrow i = C \frac{dv}{dt}$$

$$\Rightarrow \frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{V_s}{LC} \quad t > 0$$

$$= 0 \quad t < 0$$

$$\Rightarrow \frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \omega^2 \frac{V_s}{LC} \quad \text{(later will be } \sin(\omega t))$$

$$\text{Soln. } v(t) = v_t(t) + v_{ss}(t)$$

transient steady state


$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \text{or}$$

$$(A_1 + A_2 t) e^{-\alpha t} \quad \text{with}$$


$$(A_1 (\cos \omega t + A_2 \sin \omega t)) e^{-\alpha t} \quad \text{under}$$

$$v_{ss}(t) = v(\infty) = V_s$$

Prove.

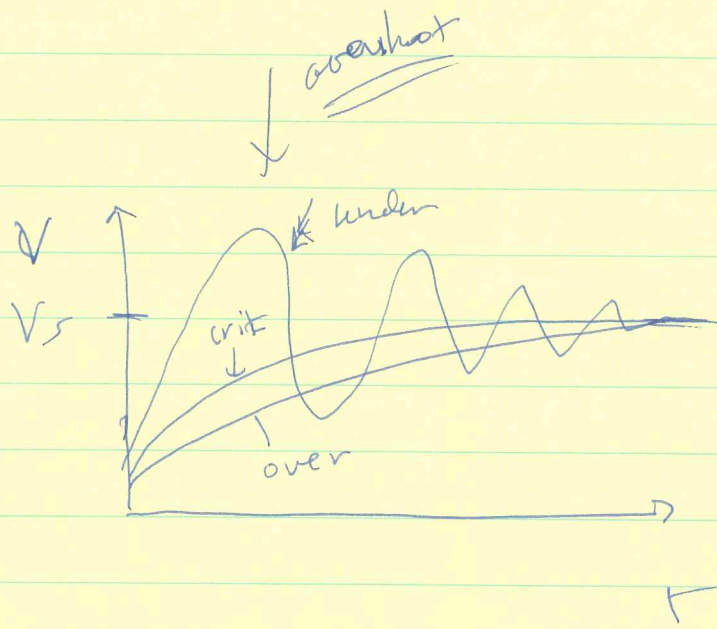

|| RLC step

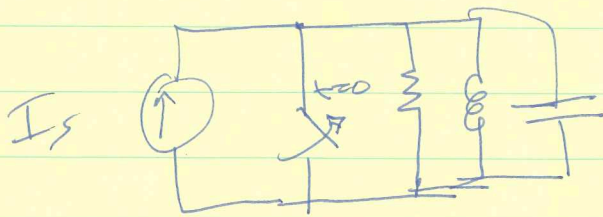

$$\text{KCL} \quad \frac{V}{R} + i + C \frac{dV}{dt} = I_s$$

$$\text{Using } V = L \frac{di}{dt}$$

$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC}$$

$$i(t) = i_t(t) + i_{ss}(t)$$

$$i(t) = I_{ss} + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \text{over}$$

$$i(t) = I_{ss} + (A_1 + A_2 t) e^{-\alpha t} \quad \text{crit}$$

$$i(t) = I_{ss} + (A_1 \cos \omega t + A_2 \sin \omega t) e^{-\alpha t} \quad \text{under}$$

TA will cover 2nd order RC circuits
+ RL circuits

eg. -

