


The 4th week

(1)

Thurs 2nd week

KCL $\sum_{n=1}^N i_n = 0$ Node
 KVL $\sum_{m=1}^M v_m = 0$ Loop

e.g. $\rightarrow i_1$

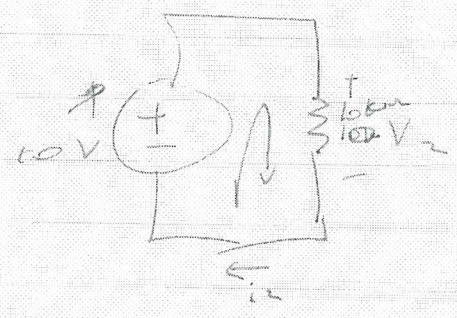

$V_m =$ voltage drop.
 As you go around loop if

Apply these + ohm's law
 to circuits \Rightarrow
 Find I, V everywhere.
 Note: Ch 2 ex. probs easy.
 Need method to do this (Ch 3)

2 nodes




KVL $-10V + V_2 = 0$
 $\Rightarrow V_2 = 10V$

KCL $\Rightarrow i_1 = i_2$

Ohm's law = $V_2 = i_2 R \Rightarrow i_2 = \frac{10V}{20k\Omega} = 1mA$


Done. Know I, V everywhere.

Absolute V vs relative?

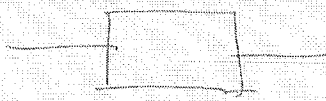


Stands for any circuit element (Resistor source)

2 circuit elements connected like this

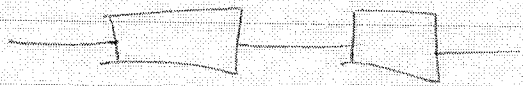


are said to be in series.

2 circuit elements connected like this

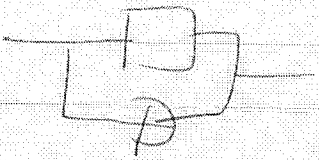

are said to be in parallel.

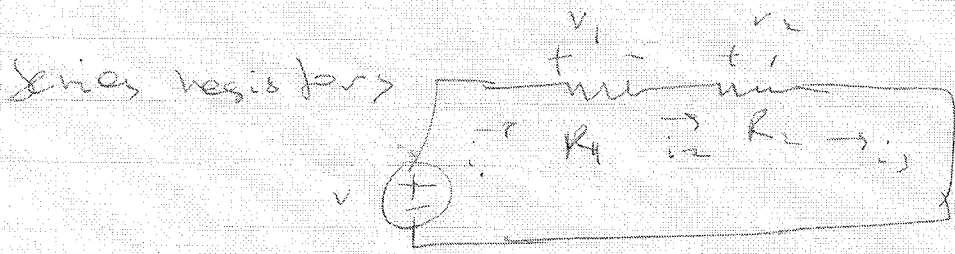

$i_1 = i_2 = i$ cell

$V_1 = iR_1$

$V_2 = iR_2$

$-V + V_1 + V_2 = 0$ KVL

R_1, R_2, V known
 i, V_1, V_2 not known

3 eqns, 3 unknown, general theorem
linear algebra

$i = \frac{V}{R_1 + R_2}$

$R_{eq} = R_1 + R_2$


$\Rightarrow \frac{R_1}{\parallel} \frac{R_2}{\parallel} = \frac{R_{eq}}{\parallel}$

N resistors in series $R_{eq} = \sum R_n$


Analogy voltage divider.
 Elaborate

(5)

Very important example

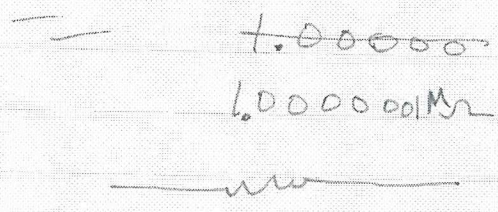

Be reasonable. Ignore 0.1Ω


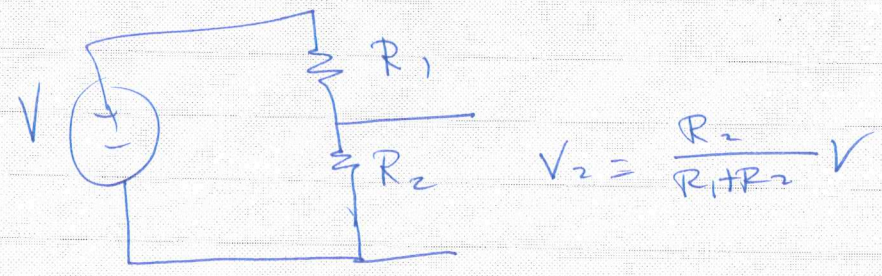


$$V_2 = \frac{R_2}{R_1 + R_2} V$$

"Voltage divider"

Voltage divider:

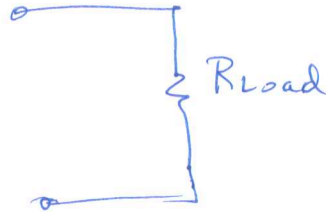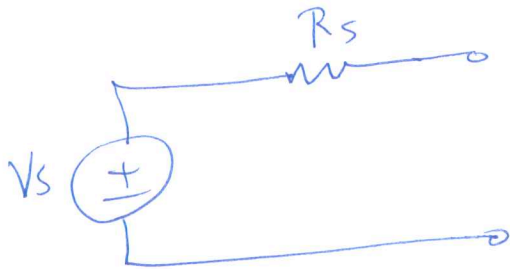Why important?
Want to connect 2 complex circuits: "Source" and "load"



Thevenin Thm:

Any circuit can be represented by this eq. circuit.

$S =$ "Source"

What is V_{load} ?
$$= \frac{R_{load}}{R_{load} + R_s} V_s$$


If $R_{load} \gg R_s \Rightarrow V_{load} = V_s$

If $R_{load} \ll R_s \Rightarrow V_{load} \rightarrow 0$

We say R_{load} "loads down" ~~power~~ ^{power} source. ~~supply~~ ^{supply}

(5)

Parallel resistors

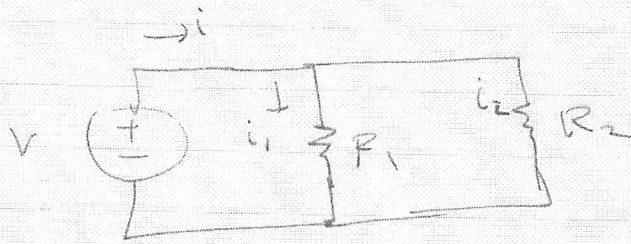

$$V = i_1 R_1 = i_2 R_2$$

$$i_1 = V/R_1 = \cancel{V/R_2} \quad i_2 = V/R_2$$


$$\text{KCL} \Rightarrow i = i_1 + i_2$$

$$i = \frac{V}{R_1} + \frac{V}{R_2} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V}{R_{eq}}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \Leftrightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

N in parallel

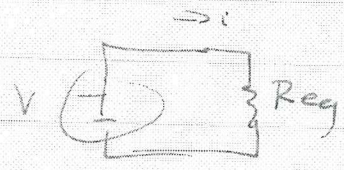
$$\frac{1}{R_{eq}} = \sum_n \frac{1}{R_n}$$




$R_1 \parallel R_2$ means
 R_1 in parallel with R_2

Current divider

eg.


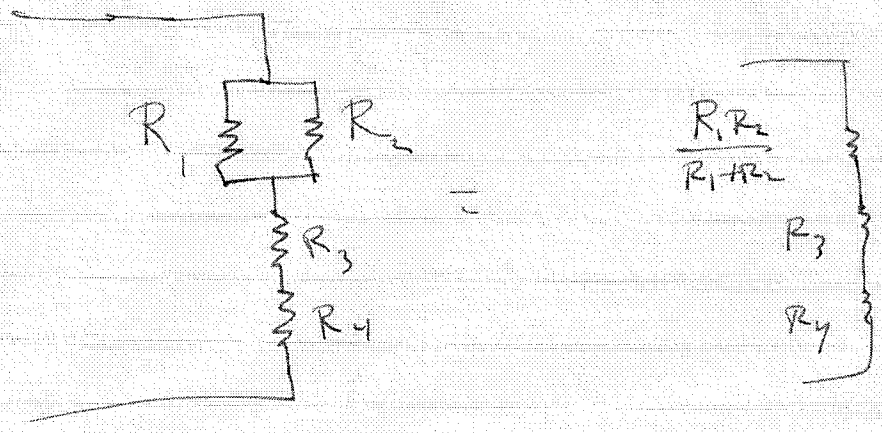


What is R_{eq} ?

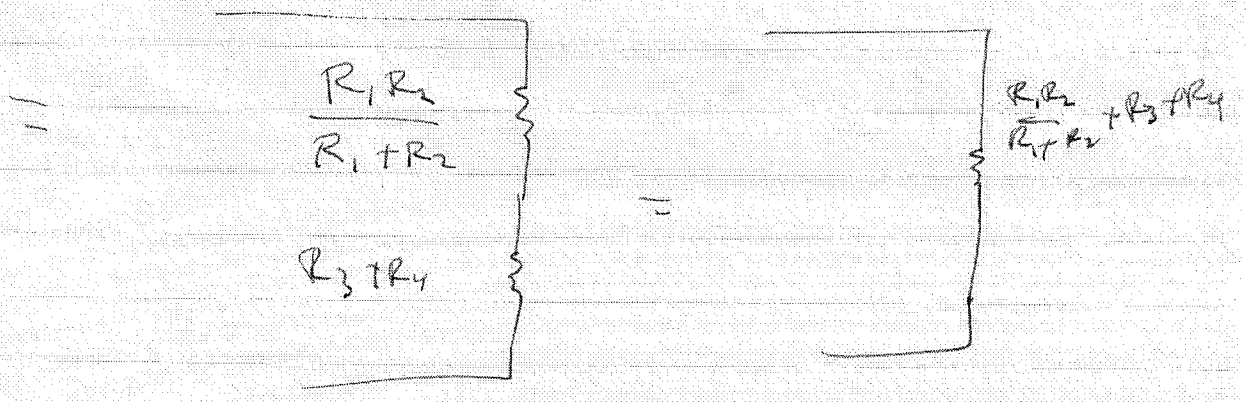




Important steps

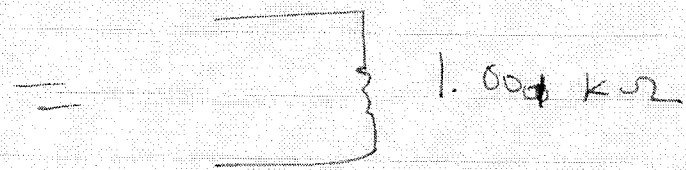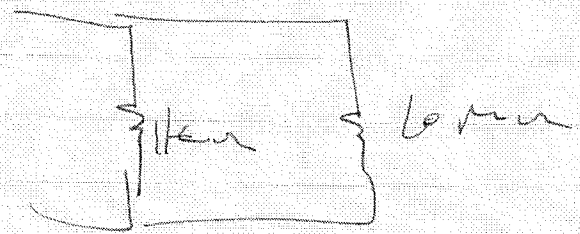


be reasonable. ignore 10 mV.


eg.

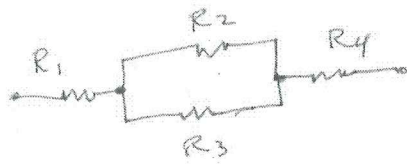

$$R_{eq} = ?$$

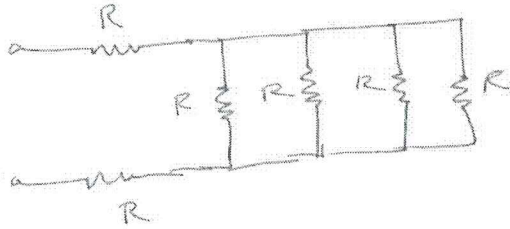


$$R_{eq} = ?$$

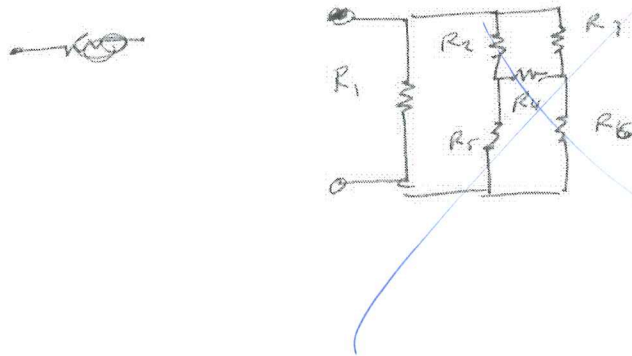

$$R_{eq} = ?$$

Teaser:

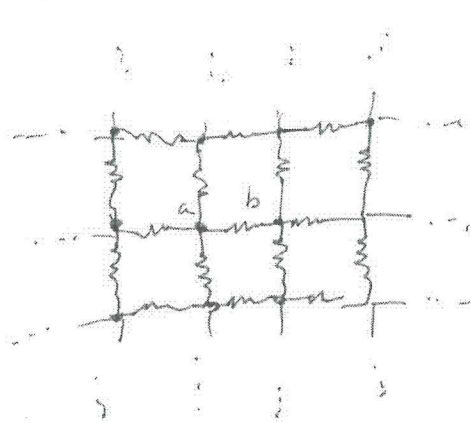

$$R_{ab} = ?$$

Dover