

A capacitor consists of 2 metal plates separated by an insulator (dielectric).



$$q = CV$$

Capacitance is the ratio of the charge on one plate of a capacitor to the voltage difference between the two plates, measured in Farad (F).

$$1 \text{ Farad} = 1 \text{ Coulomb} / 1 \text{ Volt}$$

$$C = \frac{KEA}{d}$$

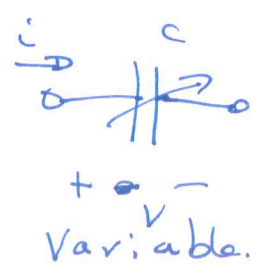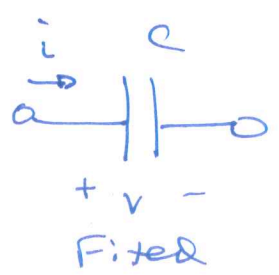Vacuum $\Rightarrow k=1$ "High k" $\Rightarrow k > 10$
 $\epsilon = 8.85 \times 10^{-12} \text{ F/m}$
 Constant of nature.



Applications




Filters (all communication equipment)

Smooth out voltage spikes on power lines
 (Power supply board should be)







Memory (Picture?)

1) Capacitor is an open circuit at dc.

eg. amplifier "block"

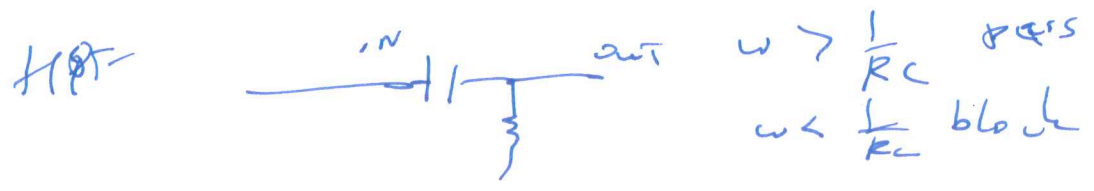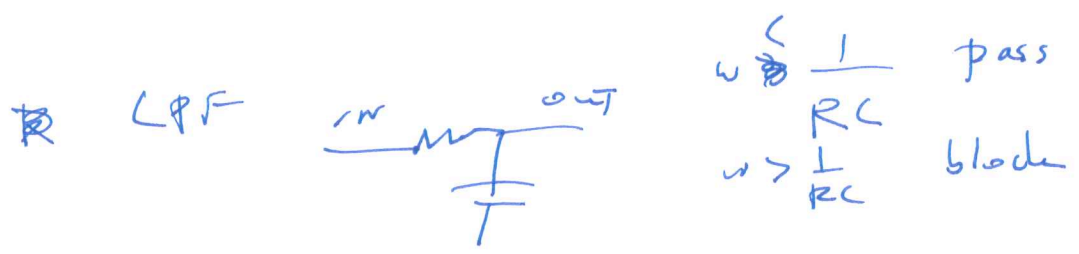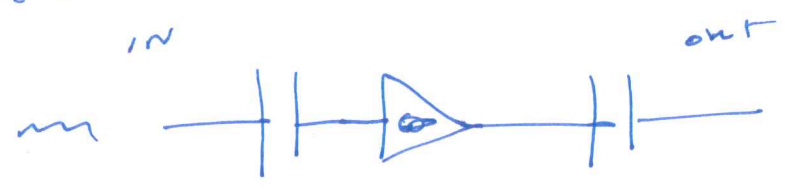

1bit Memory

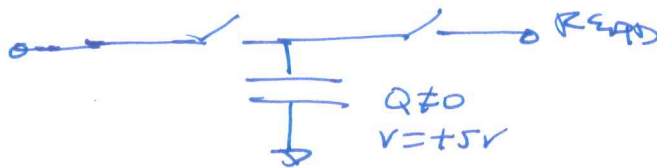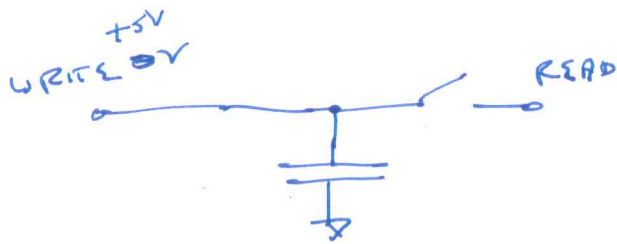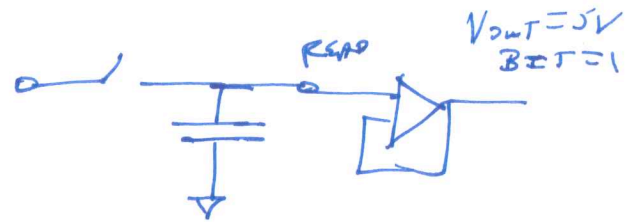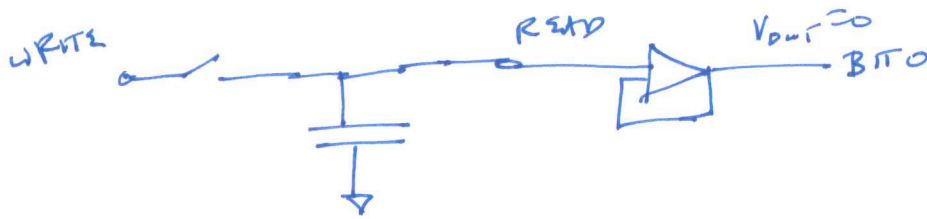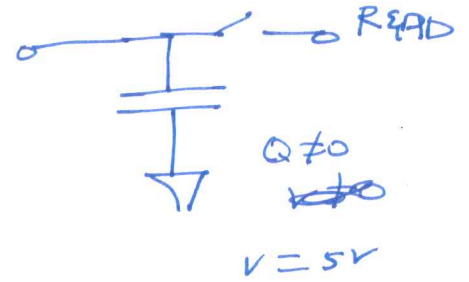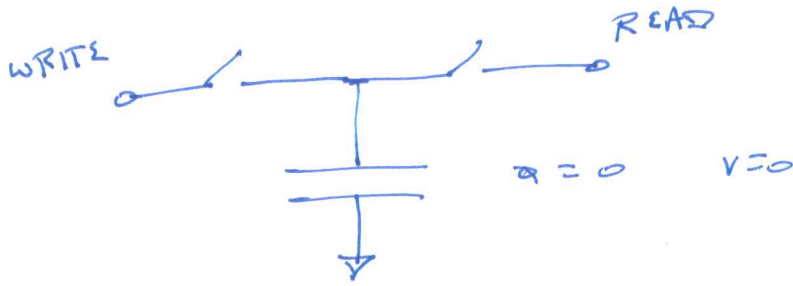

$$q = CV$$

$$i = \frac{dq}{dt} = C \frac{dV}{dt}$$

The voltage on a capacitor cannot change abruptly.

Because the $\frac{dV}{dt} \rightarrow \infty \Rightarrow i \rightarrow \infty$ not physical.

$C = \frac{\epsilon_0 A}{d}$
C is time independent.

q, v, i ^{can} depend on time i.e.

$$q(t) \quad v(t) \quad i(t)$$


$$q(t) = C v(t)$$

$$i(t) = C \frac{dv(t)}{dt}$$


$$\Rightarrow v(t) = \frac{1}{C} \int i(t) dt$$

$$\Rightarrow q(t) = \int i(t) dt$$

Example

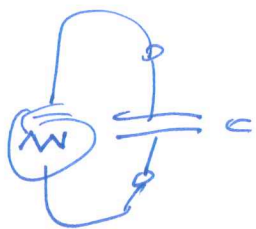


$V(t)$

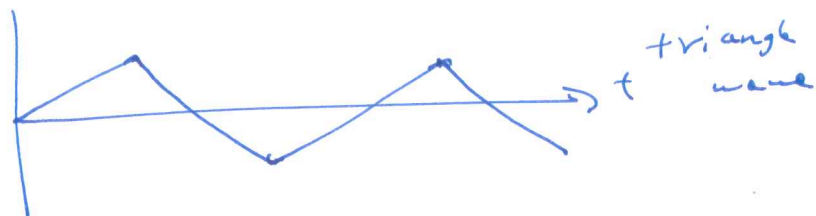


What is $i(t)$, $q(t)$?


$$i(t) = C \frac{dV(t)}{dt}$$

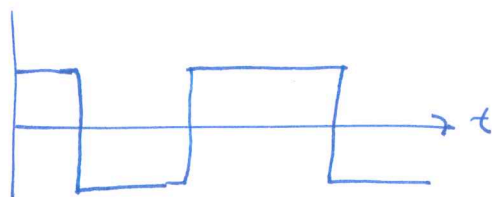

$$q(t) = \int i(t) dt$$

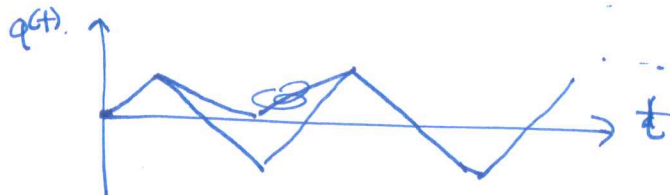



one bit memory write:

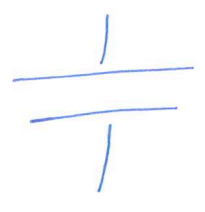

$$q = CV$$

$$V = \frac{q}{C} = 5V$$

$$\Rightarrow q = C \cdot 5V$$

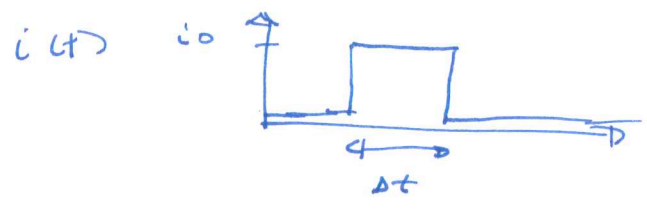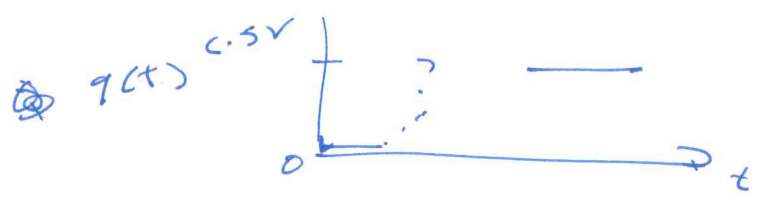

$$i_0 \Delta t = C \cdot 5V$$

Tells you how long, how much current to apply.

↓ In this time I to V to \Rightarrow power ~~dis~~ dissipated.

Stored in capacitor


$$W = \int p dt = \int i v dt = \int C \frac{dv}{dt} v dt$$

$$= C \int v dv = \boxed{\frac{1}{2} C V^2 = W}$$

Energy / Power

(7)


For a resistor

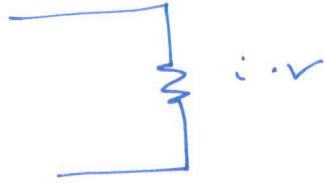

$$P = i \cdot v$$
$$\Rightarrow \text{heat}$$

(cannot recover)

Capacitor

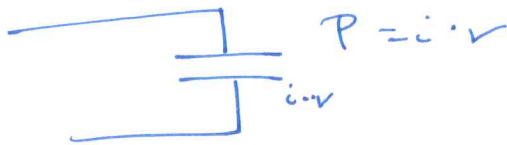

$$P = i \cdot v$$


electrical energy

can recover.

(will see how later.)

|| (Parallel) Capacitors

②

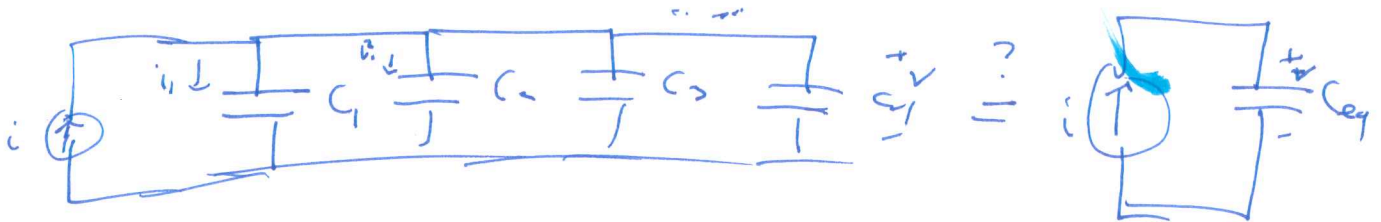

$$i = i_1 + i_2 + \dots + i_n$$

$$i = C_{eq} \frac{dv}{dt}$$

$$i_1 = C_1 \frac{dv}{dt}$$

$$i_2 = C_2 \frac{dv}{dt} \quad (\text{same } v)$$

$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \dots + C_n \frac{dv}{dt}$$

$$= \sum_{k=1}^n C_k \frac{dv}{dt} = C_{eq} \frac{dv}{dt}$$

$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_n$$

Series Capacitors

(9)



$$V = V_1 + V_2 + V_3 + \dots + V_n$$

$$V_1 = \frac{1}{C_1} \int i(t) dt$$

$$V_2 = \frac{1}{C_2} \int i(t) dt \quad \text{same } i$$


$$V = \frac{1}{C_1} \int i(t) dt + \frac{1}{C_2} \int i(t) dt + \dots + \frac{1}{C_n} \int i(t) dt$$

$$\Rightarrow = \frac{1}{C_{eq}} \int i(t) dt = \frac{1}{C_{eq}}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_n}$$

Inductors

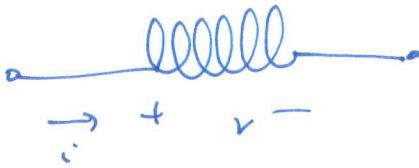An inductor consists of a coil of conducting wire.



$$V = L \frac{di}{dt}$$

$$L = \frac{N^2 \mu A}{l}$$

$$\mu = 4\pi \times 10^{-6} \text{ H/m}$$

vacuum.

larger for magnetic materials.

L time independent

V , $\frac{di}{dt}$ time dependent i.e.

$$V(t) = \frac{d(\text{flux})}{dt}$$

(1)

$$V = L \frac{di}{dt} \Rightarrow i(t) = \frac{1}{L} \int V(t) dt$$

$$V \neq 0 \quad i \neq 0 \Rightarrow \text{power } P = iV \neq 0$$

$$W = \int P dt = \int iV dt$$

$$= \int i \frac{di}{dt} L dt = \frac{1}{2} LI^2$$

stored energy.





An inductor acts like a short circuit ∞ Ω

The current through an inductor cannot change instantaneously.

R.C. then $\frac{di}{dt} \rightarrow \infty \Rightarrow V \rightarrow \infty$ not physical.

Series Inductors

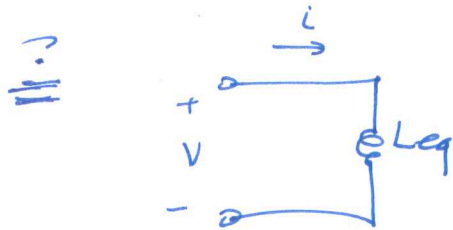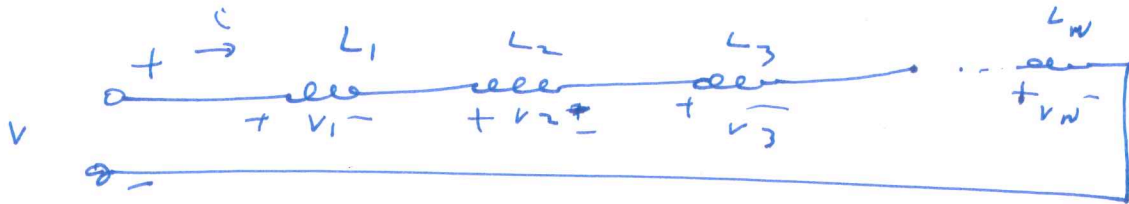

$$V = V_1 + V_2 + V_3 + \dots + V_n$$

$$V_1 = L_1 \frac{di}{dt}$$



$$V_2 = L_2 \frac{di}{dt} \quad \text{same;}$$

$$V = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_n \frac{di}{dt}$$

$$= (L_1 + L_2 + \dots + L_n) \frac{di}{dt}$$

$$\Rightarrow L_{eq} = L_1 + L_2 + L_3 + \dots + L_n$$

|| Ind.

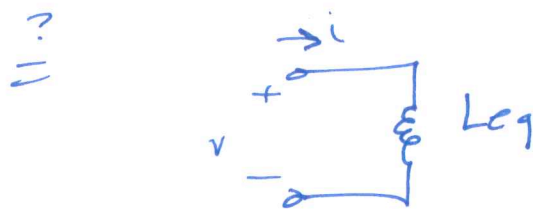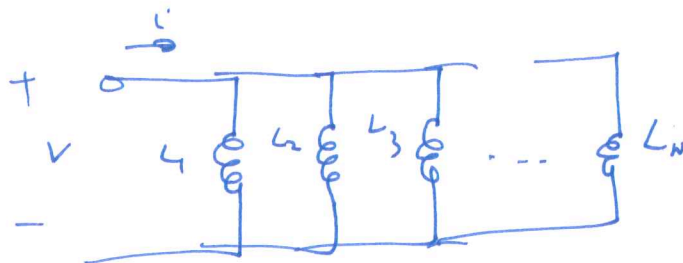

$$i = i_1 + i_2 + \dots + i_N$$

$$i_1 = \frac{1}{L_1} \int v dt$$

$$i_2 = \frac{1}{L_2} \int v dt \quad \text{Same } v$$

⋮


$$i = \frac{1}{L_1} \int v dt + \frac{1}{L_2} \int v dt + \dots + \frac{1}{L_N} \int v dt$$

$$= \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right) \int v dt$$

$$\Rightarrow \boxed{\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}}$$

(14)


HPF

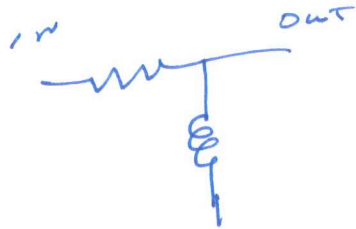

$$\omega > \frac{R}{L} \Rightarrow \text{PASS}$$

$$\omega < \frac{R}{L} \Rightarrow \text{NO PASS}$$


LPF

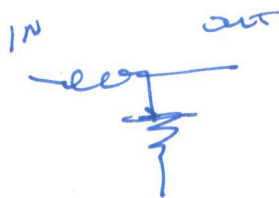

$$\omega < \frac{L}{R} \Rightarrow \text{PASS}$$

$$\omega > \frac{L}{R} \Rightarrow \text{NO PASS}$$

RLC Filter

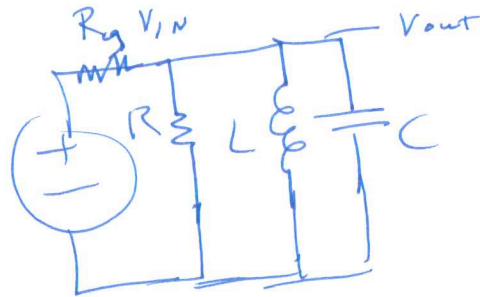


$$R \parallel i\omega L \parallel \frac{1}{i\omega C}$$

DC \Rightarrow L short circuit $\Rightarrow V_{out} = 0$

F \uparrow \Rightarrow C short circuit $\Rightarrow V_{out} = 0$
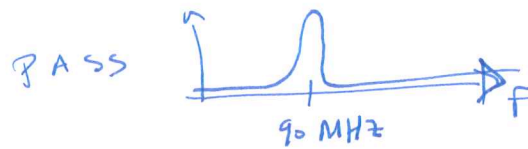
$$f = \frac{1}{2\pi\sqrt{LC}} \quad \underline{\text{PASS}}$$




"Tune" knob



SIMPLE RADIO USE

SLOW SPECTRUM

Integrator

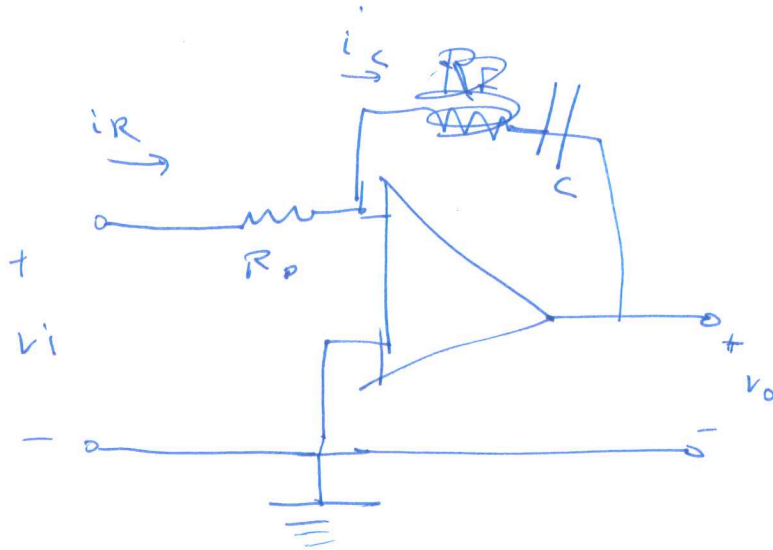


$$i_R = i_C$$

$$i_R = \frac{v_i}{R} \quad i_C = -C \frac{dv_o}{dt}$$

$$\frac{v_i}{R} = -C \frac{dv_o}{dt}$$

$$\Rightarrow v_o = -\frac{1}{RC} \int v_i(t) dt$$

Differentiator

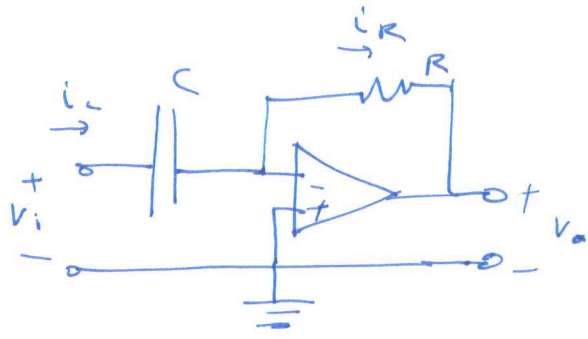

$$i_c = C \frac{dv_i}{dt}$$

$$i_R = -\frac{v_o}{R}$$

$$\Rightarrow v_o = -RC \frac{dv_i}{dt}$$

Have done :

- +
-
- integrate
- differentiate

What about $x, \frac{1}{x}$??? Not Linear.

R, L, C are all linear.
can not do.