

D

1ST ORDER CIRCUITS

RC no source

with dc source


RL no source

with dc source

What if



Source Free RC

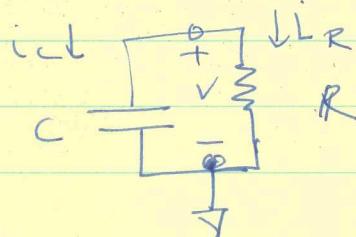

$$t=0 \quad V(t=0) \equiv V_0$$

As current flows thru R,

 q on C \downarrow

$$\Rightarrow V \text{ on } C = q/C \downarrow$$

$$\Rightarrow i \downarrow$$

Eventually $q=0$ $V=0$ $i=0$ The capacitor is discharged.

How long does it take?

 \Rightarrow ~~Re~~ Turnout RC.

$$KCL \quad i_C + i_R = 0$$

$$i_C = \frac{dq}{dt} = C \frac{dv}{dt} \quad i_R = V/R$$

$$\Rightarrow C \frac{dv}{dt} + \frac{V}{R} = 0$$

$$\Rightarrow \frac{dv}{dt} + \frac{V}{RC} = 0$$

1ST ORDER DIFF EQ.Define $I = Re$

$$\frac{dv(t)}{dt} + \frac{1}{I} v(t) = 0$$

(2)

D/P eqns in the physical world:

If you can find a solution

$V(t)$ that

1) Solves D.E.

2) Solves initial values

it is (correct) unique.

There are many mathematical methods

to solve them.

1) Guess
2) Know We will focus on using easiest method.

3) Integrate

$$\frac{dV}{dt} + \frac{1}{C} V = 0$$

$$\Rightarrow \int \frac{dV}{V} = \int \frac{1}{C} dt$$

$$\ln V = -\frac{t}{C} + \ln A \quad A = \text{constant}$$

~~$\ln \frac{V}{A}$~~ $\ln V - \ln A = \ln \frac{V}{A} = -\frac{t}{C}$

~~$\Rightarrow V(t) = A e^{-t/C}$~~

$$e^{\ln V/A} = e^{-t/C}$$

$$= \frac{V}{A}$$

$$\Rightarrow V(t) = A e^{-t/C}$$

(3)


Check

$$\frac{dV}{dt} = \frac{d}{dt} A e^{-t/\tau} = -\frac{A}{\tau} e^{-t/\tau} = -\frac{1}{\tau} A e^{-t/\tau}$$

$$= -\frac{1}{\tau} V \quad \checkmark$$

$$V(t=0) = A e^{-0/\tau} = A \quad \text{since } e^0 = 1$$

$$\Rightarrow V(t) = V_0 e^{-t/\tau}$$

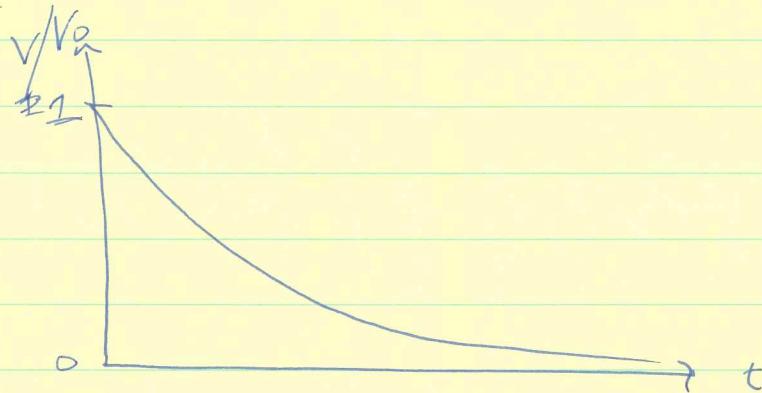

After time τ V falls to $\frac{1}{e} V_0 = 0.37 V_0$


$$e = 2.718$$

$$2\tau \quad V \text{ falls to } \frac{1}{e^2} V_0 = 0.135 V_0$$

τ is a characteristic time for capacitor to discharge

(4)

RL circuit

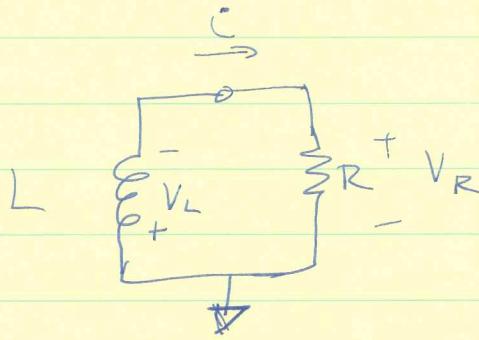

$$KVL \quad V_L = V_R$$

 τ

$$L \frac{di}{dt} = iR \quad \Rightarrow \quad \frac{di}{dt} + \frac{1}{L}i = 0 \quad \tau = L/R$$


Same as before: D.E.

$$f(t) + \frac{i}{\tau}$$

$$\frac{d}{dt} f(t) + \frac{1}{\tau} f(t) = 0 \quad -\frac{t}{\tau}$$

$$\text{Always } f(t) = A e^{-t/\tau}$$

$$i(t) = I_0 e^{-t/\tau}$$

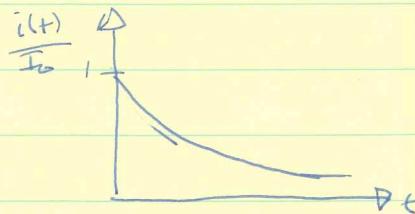

Eq RC



B



$t = 0$ open switch

Find voltage across cap vs time.

Before opening switch,

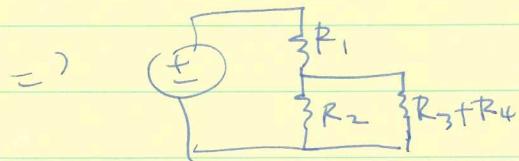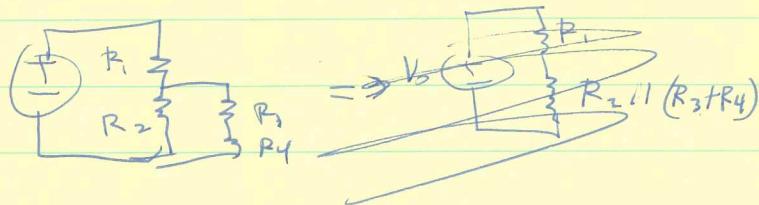


$$= \frac{R_2(R_3 + R_4)}{R_2 + (R_3 + R_4)}$$

$$V_o \Rightarrow V_{cap} = V_a \cdot \frac{\frac{R_4}{R_1 + \frac{R_2(R_3 + R_4)}{R_3 + R_4}}}{\frac{R_4}{R_1 + \frac{R_2(R_3 + R_4)}{R_3 + R_4}}}$$

$$= \underline{\underline{V_o}}$$


Q

After switch open here:

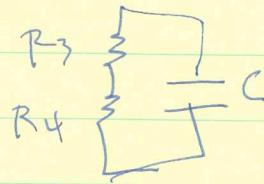

V_o as given

II

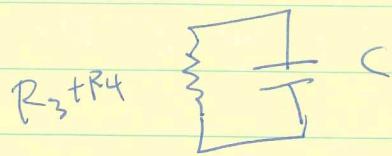

$$V(t) = V_o e^{-\frac{t}{\tau_I}} \quad \tau_I = (R_3 + R_4)C$$



$$V_R =$$

RL can be done similarly


(P)

g RL
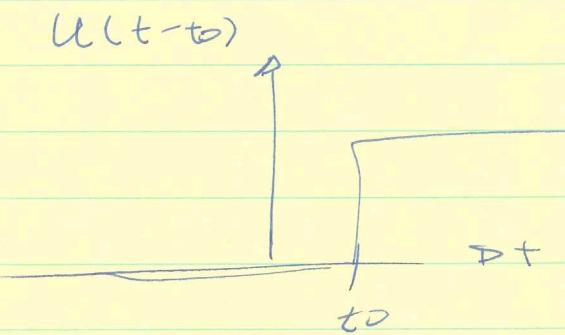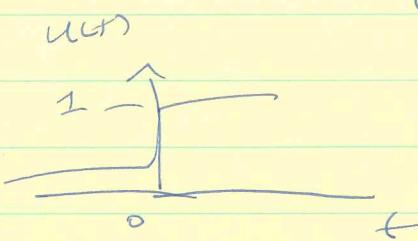
$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t \geq 0 \end{cases}$$



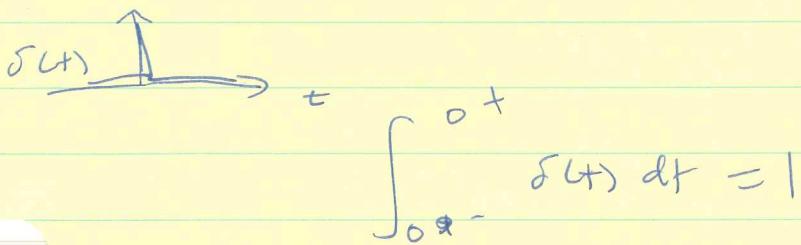
$$\delta(t) = \frac{d}{dt} u(t) = \begin{cases} 0 & t < 0 \\ \text{undefined} & t = 0 \\ 0 & t > 0 \end{cases}$$



$$\int_{-\infty}^b f(t) \delta(t-t_0) dt = f(t_0)$$


Why?

$f(t) \sim$

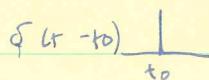

(8)

$$f(t) \delta(t - t_0)$$

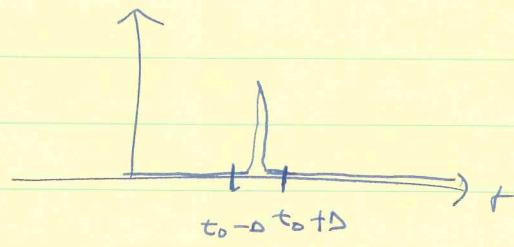

$$\int_{-\infty}^{\infty} f(t) \delta(t - t_0) dt = \int_{t_0 - \Delta}^{t_0 + \Delta} f(t) \delta(t - t_0) dt$$


$$\approx f(t_0) \int_{t_0 - \Delta}^{t_0 + \Delta} \delta(t - t_0) dt$$

↓
by defn of δ (ct)




$$= f(t_0)$$

(9)

Step response

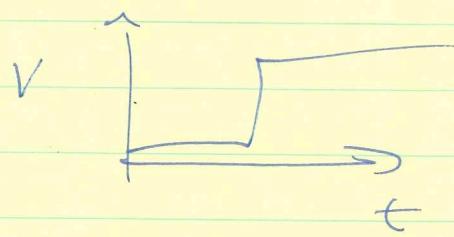

Laten wir annehmen Sinuswelle

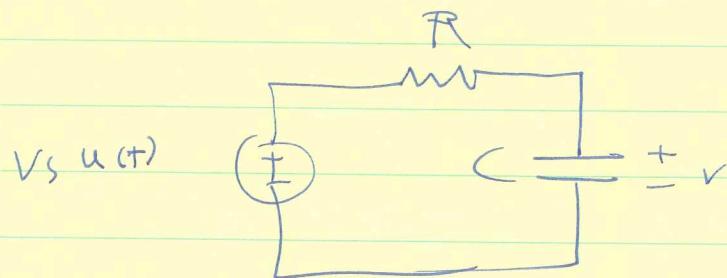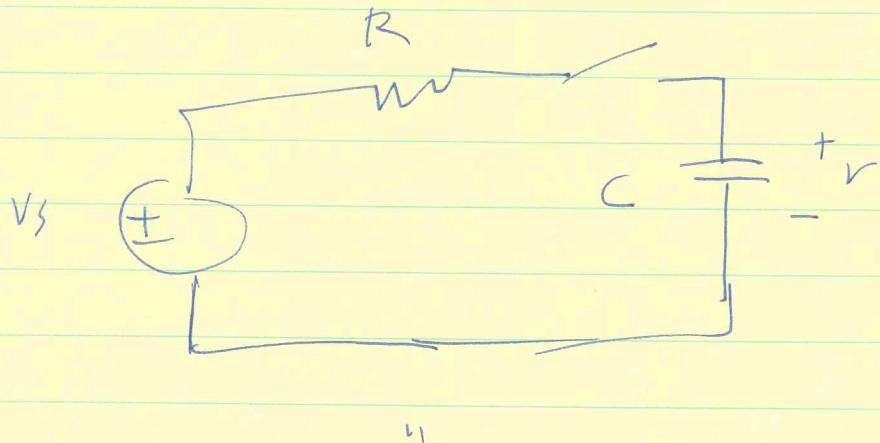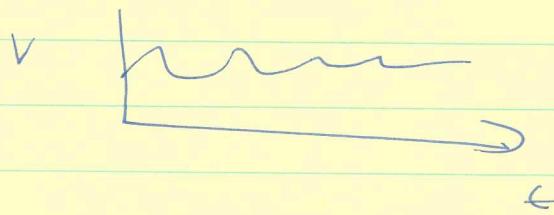

Before closing switch $v = V_0$
 $v(0^-) = V(0^+) = V_0$

(D)

$$KCL \quad C \frac{dV}{dt} + \frac{V - V_s u(+)}{R} = 0$$

$$\Rightarrow \frac{dV}{dt} + \frac{V}{RC} = \frac{V_s}{RC} u(+)$$

$$t > 0 \Rightarrow$$

$$\frac{dV}{dt} + \frac{V}{RC} = \frac{V_s}{RC}$$

$$\frac{dV}{dt} = -\frac{V - V_s}{RC}$$

$$\int_{V_0}^{V(t)} \frac{dV}{V - V_s} = - \int_0^t \frac{dt}{RC}$$

$$\ln(V - V_s) \Big|_{V_0}^{V(t)} = -\frac{t}{RC} \Big|_0^t$$

$$\ln(V(t) - V_s) - \ln(V_0 - V_s) = -\frac{t}{RC}$$

$$\ln \frac{V(t) - V_s}{V_0 - V_s} = -\frac{t}{RC}$$

$$e^{LHS} = e^{RHS}$$

$$V(t) \frac{V - V_s}{V_0 - V_s} = e^{-t/\tau} \quad \tau = RC$$

(n)

$$V(t) = V_s + \underbrace{(V_0 - V_s)}_{\substack{\text{steady state} \\ (\text{always there})}} e^{-t/\tau}$$

(TRANSIENT DISSES AS $t \rightarrow \infty$)

$$\Rightarrow V(t) = \begin{cases} V_0 & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

(and also writes

$$V(t) = V(t=\infty) + (V(t_0) - V(t=\infty)) e^{-\frac{t-t_0}{\tau}}$$


DR

$$V(t) = \underbrace{V_0 e^{-t/\tau}}_{\substack{\text{natural} \\ \text{response}}} + \underbrace{V_s (1 - e^{-t/\tau})}_{\substack{\text{Forced response} \\ \text{what happens if} \\ \text{there is a source.}}}$$

what happens if
there is no
source

(12)

Example RC w/ source

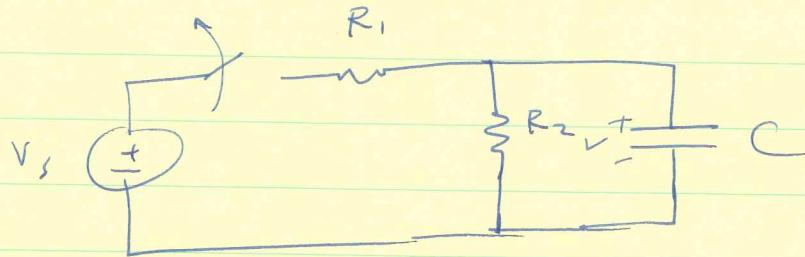Initial voltage V_0 across capacitor.Find $V(t)$ after switch closes,Switch opens at $t=0$.

Was closed a long time.

Find $V(t)$

After opens looks like



$$-t/R_2 C$$

$$V(t) = V(t=0) e^{-t/R_2 C}$$


$$V(t=0) = ?$$

$$V_s \frac{R_2}{R_1 + R_2}$$


$$\Rightarrow V(t) = V_s \frac{R_2}{R_1 + R_2} e^{-t/R_2 C}$$

(13)

RL

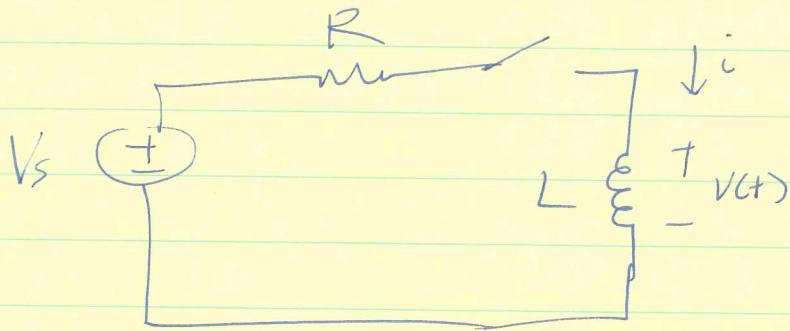

A

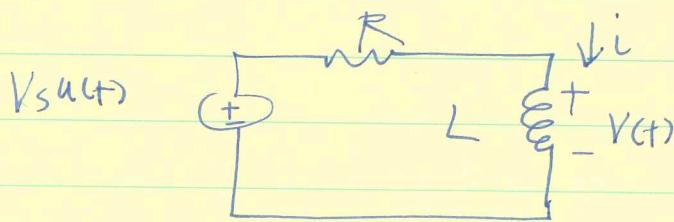

$$i = i_t + i_{ss}$$

i_{ss} constant

$$i_t = A e^{-t/\tau}$$

$$i_{ss} = \frac{V_s}{R} \Rightarrow i(t) = A e^{-t/\tau} + \frac{V_s}{R}$$


$$i(0^+) = i(0^-) = I_0$$

~~$$i(0) = A + \frac{V_s}{R} = I_0 \Rightarrow A = I_0 - \frac{V_s}{R}$$~~


$$\Rightarrow i(t) = (I_0 - \frac{V_s}{R}) e^{-t/\tau} + \frac{V_s}{R}$$

Chapter 7, Problem 53.

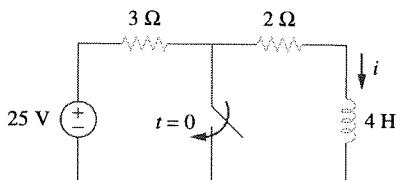Determine the inductor current $i(t)$ for both $t < 0$ and $t > 0$ for each of the circuits in Fig. 7.119.



(a)

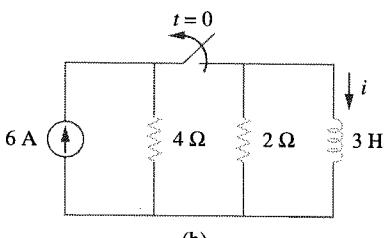

(b)

Figure 7.119
For Prob. 7.53.

Chapter 7, Solution 53.

(a) Before $t = 0$, $i = \frac{25}{3+2} = \underline{\underline{5 \text{ A}}}$

After $t = 0$, $i(t) = i(0)e^{-t/\tau}$

$$\tau = \frac{L}{R} = \frac{4}{2} = 2, \quad i(0) = 5$$
$$i(t) = \underline{\underline{5e^{-t/2} u(t)A}}$$

- (b) Before $t = 0$, the inductor acts as a short circuit so that the 2Ω and 4Ω resistors are short-circuited.

$$i(t) = \underline{\underline{6 \text{ A}}}$$

After $t = 0$, we have an RL circuit.

$$i(t) = i(0)e^{-t/\tau}, \quad \tau = \frac{L}{R} = \frac{3}{2}$$
$$i(t) = \underline{\underline{6e^{-2t/3} u(t)A}}$$

Chapter 7, Problem 63.

Obtain $v(t)$ and $i(t)$ in the circuit of Fig. 7.128.

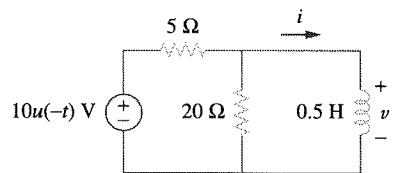


Figure 7.128
For Prob. 7.63.

Chapter 7, Solution 63.

$$\text{For } t < 0, \quad u(-t) = 1, \quad i(0) = \frac{10}{5} = 2$$

$$\text{For } t > 0, \quad u(-t) = 0, \quad i(\infty) = 0$$

$$R_{th} = 5 \parallel 20 = 4 \Omega, \quad \tau = \frac{L}{R_{th}} = \frac{0.5}{4} = \frac{1}{8}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$i(t) = \underline{2 e^{-8t} u(t) A}$$

$$v(t) = L \frac{di}{dt} = \left(\frac{1}{2}\right)(-8)(2)e^{-8t}$$

$$v(t) = \underline{-8 e^{-8t} u(t) V}$$