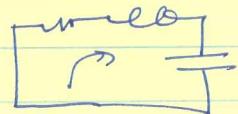


Initial Values

 $i(t=0) = i(0)$ inductor $V(t=0) = V(0)$ capacitor

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$



Solution has 2 unknown constants.

378
4370

E.g. underdamped

$$i(t) = e^{-\alpha t} [\beta_1 \cos(\omega_0 t) + \beta_2 \sin(\omega_0 t)]$$

α , ω_0 defined
 β_1, β_2 constants in terms of RLC

To find β_1, β_2 for a particular problem, needto know $i(t=0)$ & $\frac{di}{dt} \Big|_{t=0}$ Because: $i(t=0) = \beta_1$

$$\frac{di}{dt} \Big|_{t=0} = \omega_0 \beta_2$$

~~Similar~~ Similar calc. can be done for undamped.What if you are given $I_0 = i(t=0)$ and $V_0 = V_{cap}(t=0)$?

$$KVL \Big|_{t=0} \quad i(t=0) R + L \frac{di}{dt} \Big|_{t=0} + V_{cap}(t=0) = 0$$

$$\Rightarrow I_0 R + L \frac{di}{dt} \Big|_{t=0} + V_0 = 0$$

$$\Rightarrow \frac{di}{dt} \Big|_{t=0} = -\frac{1}{L} (R I_0 + V_0) \leftarrow$$

(2)

II RLC



$$\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0$$

Soln. has 2 unknown constants.

(Free & any 2nd order ODE)

Eg undamped

$$V(t) = e^{-\frac{at}{2}} [B_1 \cos(\omega t) + B_2 \sin(\omega t)]$$

$$V(t=0) = B_1$$

$$\left. \frac{dV}{dt} \right|_{t=0} = \omega B_2$$


What if you are given $V(t=0) = V_0$ and $I_0 = i_{\text{ind}}(t=0)$?

$$\text{KCL} \Big|_{t=0} \Rightarrow \frac{V_0}{R} + I_0 + \left. \frac{dV}{dt} \right|_{t=0} = 0$$

$$\Rightarrow \left. \frac{dV}{dt} \right|_{t=0} = - \frac{V_0 + I_0 R}{R C}$$

(11)

RLC Step response

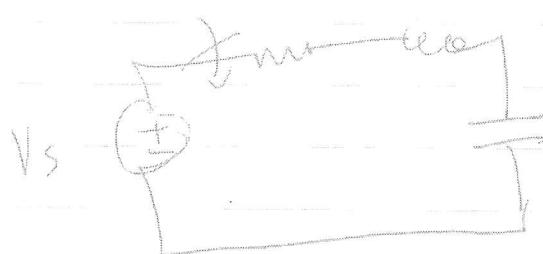

$$\text{KVL} \quad L \frac{di}{dt} + Ri + V = V_s \quad t > 0$$

$$= 0 \quad t < 0$$

$$q = CV \Rightarrow i = C \frac{dV}{dt}$$

$$\Rightarrow \frac{d^2V}{dt^2} + \frac{R}{L} \frac{dV}{dt} + \frac{V}{LC} = \frac{V_s}{LC} \quad t > 0$$

$$= 0 \quad t < 0$$

$$\Rightarrow \frac{d^2V}{dt^2} + \frac{R}{L} \frac{dV}{dt} + \frac{V}{LC} = -u(t) \quad \begin{matrix} \text{Initial} \\ \text{voltage} \\ \text{sinus} \end{matrix}$$

$$\text{Solu. } V(t) = V_t(t) + V_{ss}(t)$$

transient steady state
 \rightarrow constant

$$V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \begin{matrix} \text{as} \\ \text{if} \\ \text{under} \end{matrix}$$


$$(A_1 + A_2 t) e^{-s_1 t}$$

$$(A_1 (\cos s_1 t + A_2 \sin s_1 t)) e^{-s_1 t}$$

$$V_s(t) = V(\infty) = V_s$$

Prove.

(12)

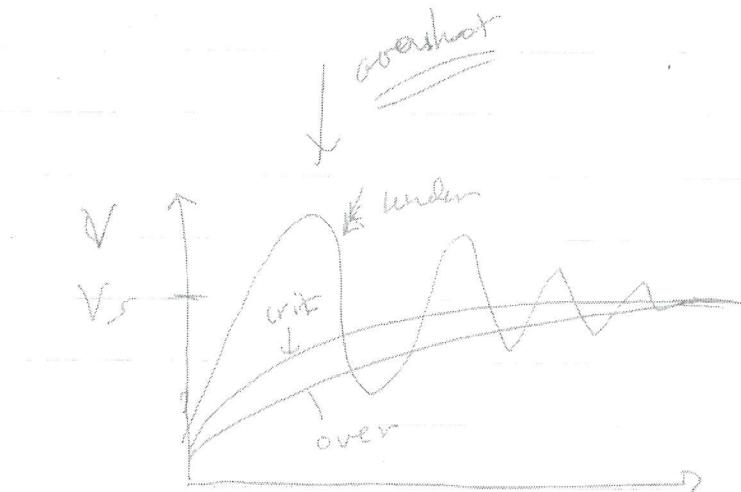

5

Applications:



Car ignition system

Battery 12V

Need $\sim 10,000V$ momentarily across
spark plug


Use RLC overshoot and switch to generate
the large voltage.

Smoothing

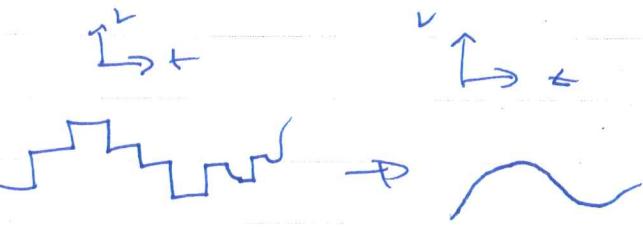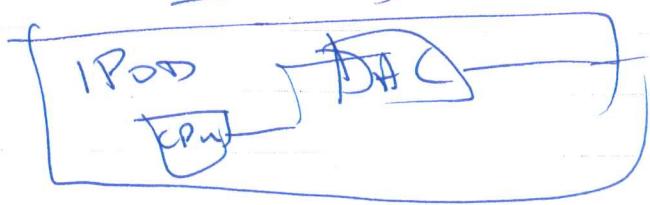

(13)

II RLC Step

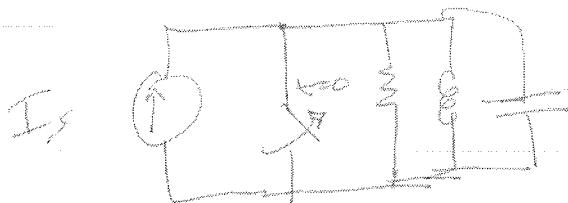

$$KCL \quad \frac{V}{R} + i - C \frac{dV}{dt} = I_s$$

$$\text{Using } V = L di/dt$$

$$\frac{d^2i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC}$$

$$i(t) = i_f(t) + i_{ss}(t)$$

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \text{over}$$

$$i(t) = I_{ss} + (A_1 + A_2 t) e^{-\alpha t} \quad \text{crit}$$


$$i(t) = I_{ss} + (A_1 \cos \omega t + A_2 \sin \omega t) e^{-\alpha t} \quad \text{under}$$

TF will have 3rd order RL circuits
+ RL currents


e.g.



④


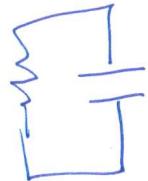
To date

RLC

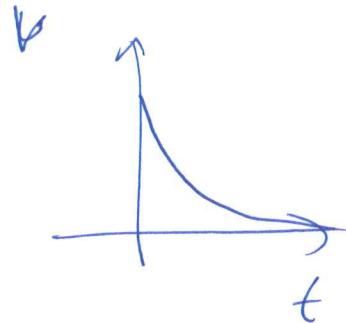

RL similar

In general:
RLC, RLC with switches

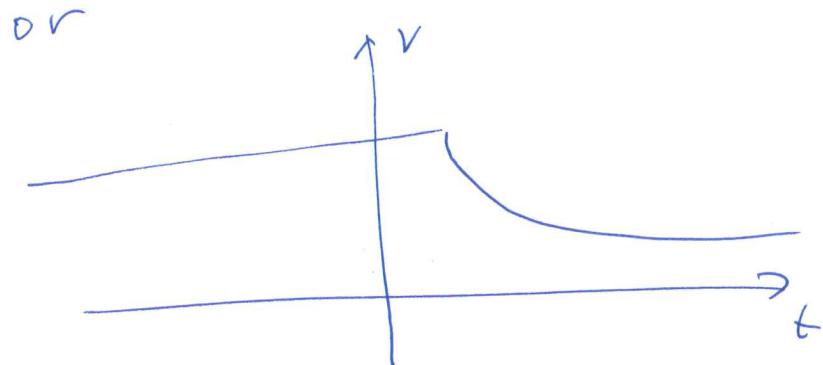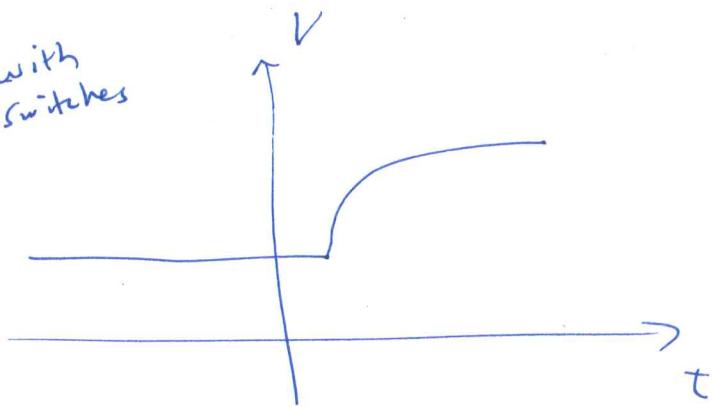

$$\text{Wt } V = iR$$

$$\rightarrow \text{I} = C V \quad i = C \frac{dV}{dt}$$

$$\text{else } V = L \frac{di}{dt}$$

No overshoot to final destination.

RLC has overshoot. Why?