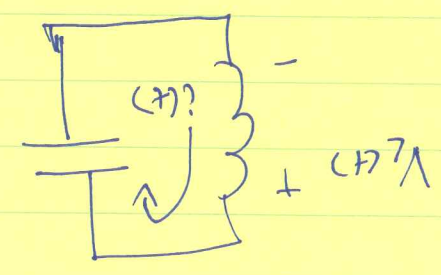


N.B. (1) First ...


②

KVL  $\Rightarrow V_2(t) = V_C(t)$  just call  $V_C(t) = -L \frac{di}{dt}$  by def. of:





Initially  $i = 0$   $V > 0$   
 $\frac{1}{2} LI^2$   $\frac{1}{2} CV^2$   
 Energy

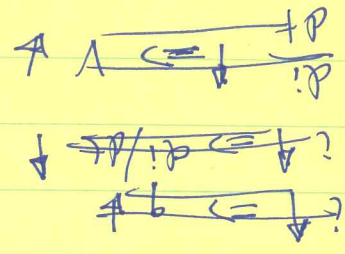$V \neq 0 \Rightarrow i = 0$  b.c.  $V = L \frac{di}{dt}$   
 Slope of:  $V = -L \frac{di}{dt}$



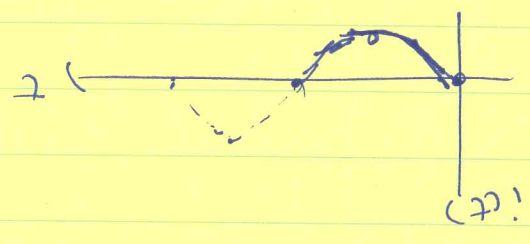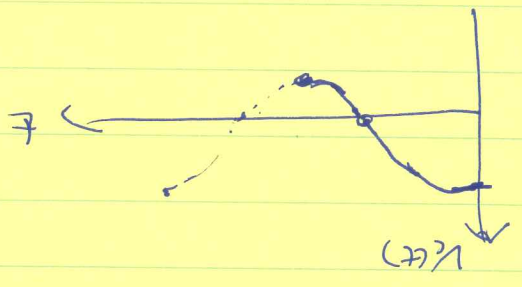$\Rightarrow i < 0 \Rightarrow V_C(t) > 0$  b.c.  $q \text{ (doubt) } \Rightarrow q = CV$   
 $V_C(t) > 0 \Rightarrow -L \frac{di}{dt} > 0$  slope becomes less



Then  $i \neq 0 \Rightarrow V = 0$   
 $i \neq 0 \Rightarrow V = 0$   
 $i < 0 \Rightarrow V < 0$   
 $i > 0 \Rightarrow V > 0$   
 Energy  $\frac{1}{2} LI^2$   
 Energy  $\frac{1}{2} CV^2$

$i < 0 \Rightarrow V < 0$  as above  
 $\Rightarrow V < 0 \Rightarrow -L \frac{di}{dt} < 0 \Rightarrow \frac{di}{dt} > 0 \Rightarrow i \uparrow$

$i \downarrow \Rightarrow \frac{di}{dt} < 0$  becomes less negative

b.c.  $i$  also negative  $\Rightarrow$  charge flows slower of (comp)

Energy goes back and forth between  $L$  &  $C$   
 Frequency is  $\frac{1}{\sqrt{LC}}$  (will prove)

If  $R$  in there, still lose energy.

Rate

B.c.  $IR = 0$  in resistor  $\rightarrow$  heat = lost energy to environment  
 $\Rightarrow$  eventually  $i = 0, V = 0$

Rate  $i^2 R \sim \frac{1}{L}$

So compare  $R \frac{1}{L}$  to  $\frac{1}{\sqrt{LC}}$

over damped vs. underdamped.

Equations

$\Rightarrow$  KVL  $\left\{ \begin{aligned} \frac{d}{dt} \\ -L \frac{d}{dt} \end{aligned} \right\} V = V$   
 $V_L(t) = V(t)$

$-L \frac{d^2 i}{dt^2} = \frac{dV}{dt} = \frac{c}{t} ?$

$q = cv$   
 $i = \frac{dq}{dt} = c \frac{dv}{dt}$

$\Rightarrow \frac{d^2 i}{dt^2} = -\frac{1}{LC} i$

2nd order D.E.

Soln

Note: Chs. 9, 14 deal with A, B, w, math of sin, cos  $B=0$   
 $i(t) = A \sin(\omega t) + B \cos(\omega t)$  works. Assume  $B=0$   
 for now.  $w = ??$

$\frac{d^2 i}{dt^2} = -\omega^2 A \sin(\omega t) = -\frac{1}{LC} A \sin(\omega t)$

$\Rightarrow \omega = \sqrt{\frac{1}{LC}}$



$\Rightarrow i(t) = A \sin\left(\frac{1}{\sqrt{LC}} t\right)$

$V = -L \frac{di}{dt} \Rightarrow$

$V(t) = -L \frac{d}{dt} \left[ A \cos\left(\frac{1}{\sqrt{LC}} t\right) \right] = -A \sqrt{\frac{L}{C}} \cos\left(\frac{1}{\sqrt{LC}} t\right)$

$i(t), v(t)$  said to be out of phase.


$\Rightarrow$  Damping

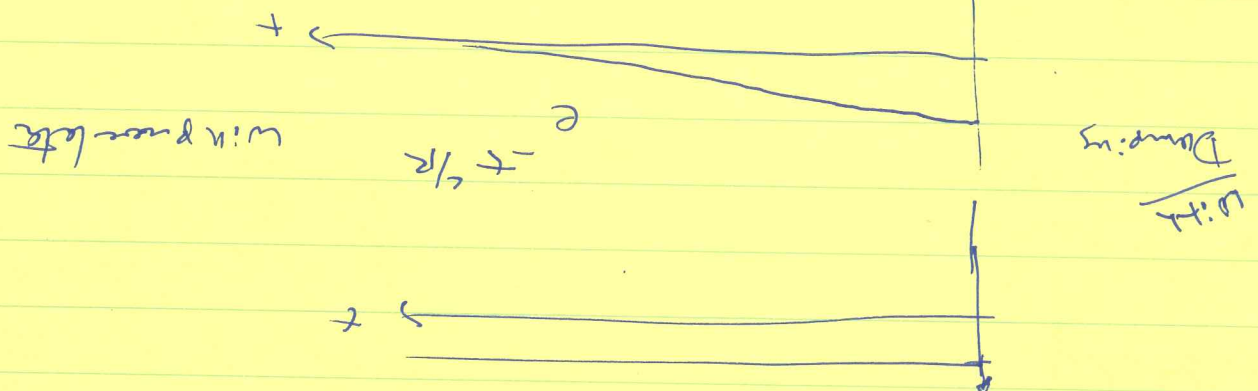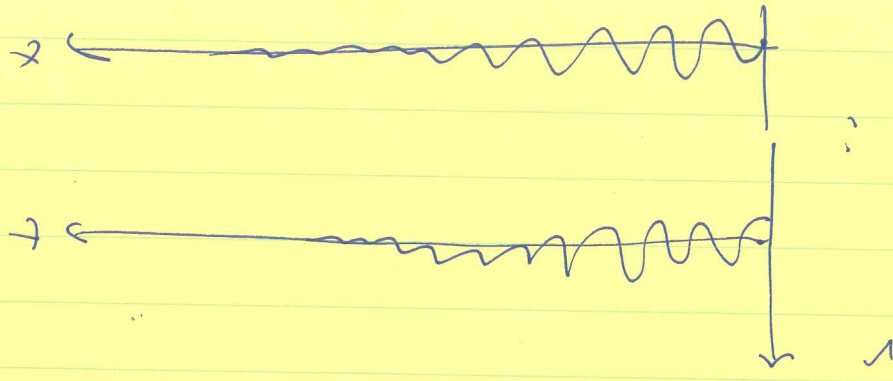

with more late


$$e^{-t^2/R}$$

with Damping

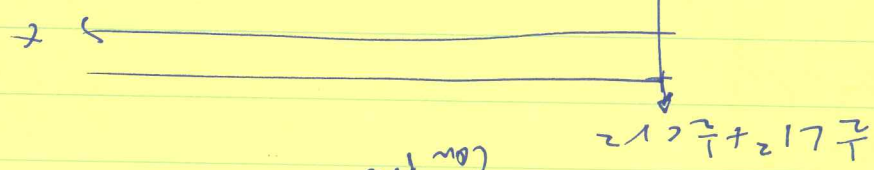

Can prove how? Show...



$$\frac{1}{2}L^2 + \frac{1}{2}C^2$$

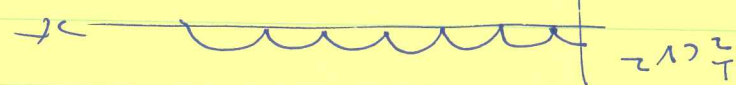

$$\frac{1}{2}C^2$$




$$\frac{1}{2}L^2$$

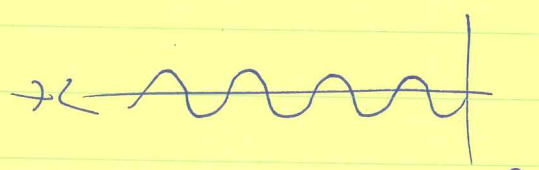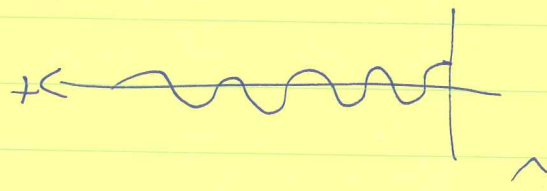

9

~~It~~ Sometimes damping same

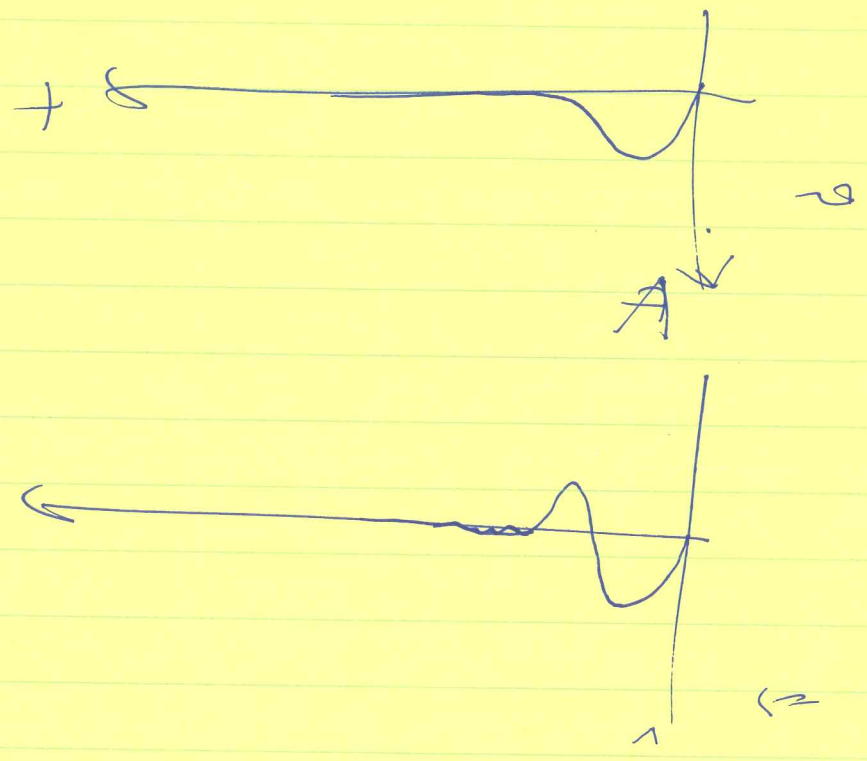

Damping same if

$$\left(\frac{R}{L}\right)^2 > \frac{1}{LC}$$

Found  $i(t) = A \sin\left(\sqrt{\frac{1}{LC}}t\right)$  no damping

want to find  $i(t)$  with damping.

will be  $i(t) \approx A e^{-\alpha t} \sin\left(\sqrt{\frac{1}{LC}}t\right)$

want exact soln.

Need math