
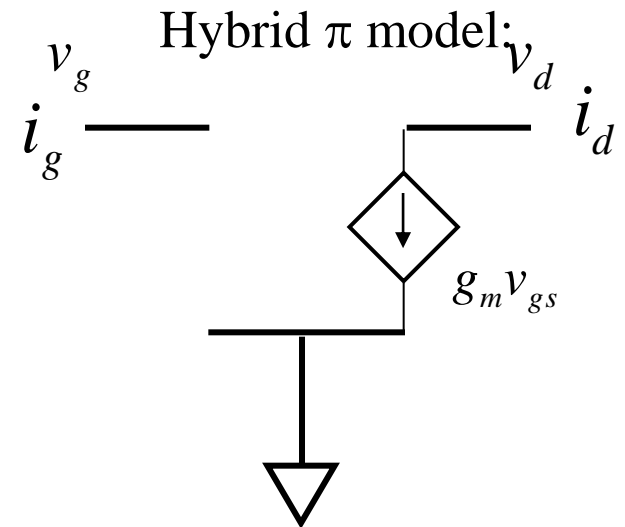


RF CMOS

EECS 277A
Fall 2010

AC equivalent circuit:

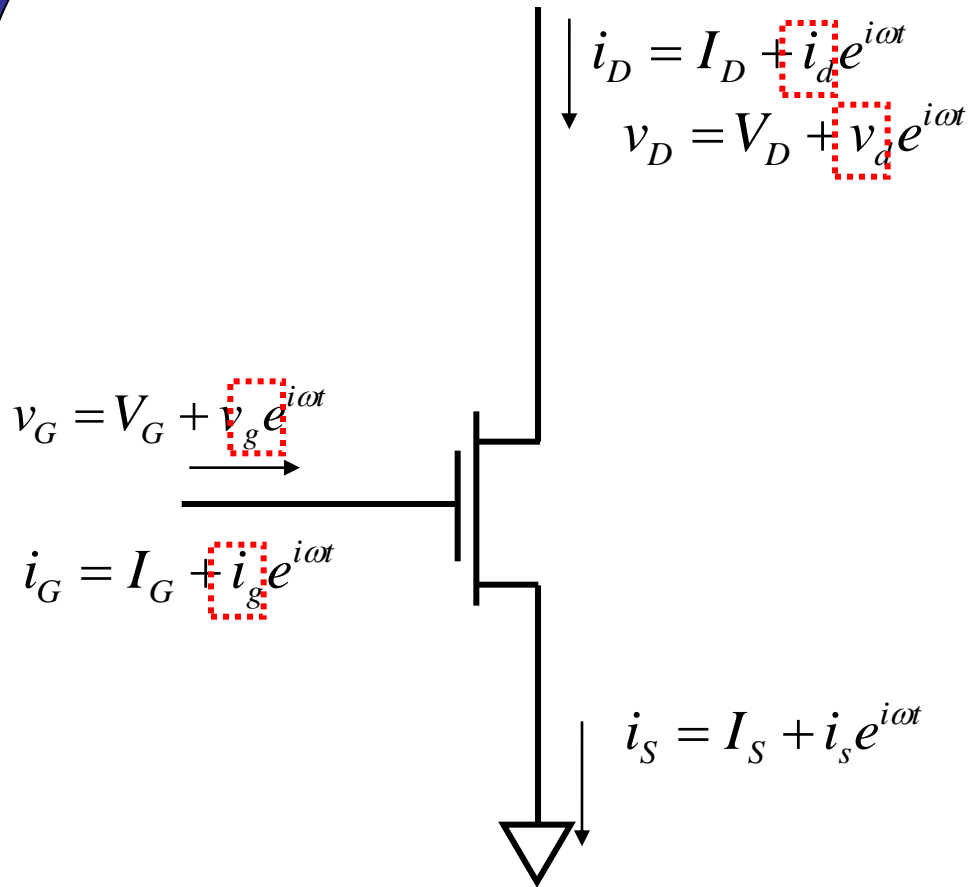

$$\begin{pmatrix} i_g \\ i_d \end{pmatrix} = \begin{pmatrix} 0 & 0 \\ g_m & 0 \end{pmatrix} \begin{pmatrix} v_g \\ v_d \end{pmatrix}$$

This is the common-source Y-matrix. You can get all the matrices from it.

Rules for ac analysis

- From complete circuit, calculate dc currents and voltages
- For ac analysis only:
 - dc voltage source -> short circuit
 - dc current source -> open circuit
- Replace transistor with π or T-model
- Now solve (simplified) ac circuit

Next

- Generalized y-parameters
- not just common emitters
- Capacitances
- y-parameters from doping profile
- Definition of f_T


General admittance matrix

Last lecture, we had emitter grounded.
Called common emitter configuration:

$$\begin{pmatrix} i_b \\ i_c \end{pmatrix} = \begin{pmatrix} \frac{g_m}{\beta} & 0 \\ \frac{eI_C}{kT} & 0 \end{pmatrix} \begin{pmatrix} v_{be} \\ v_c \end{pmatrix}$$

In general:
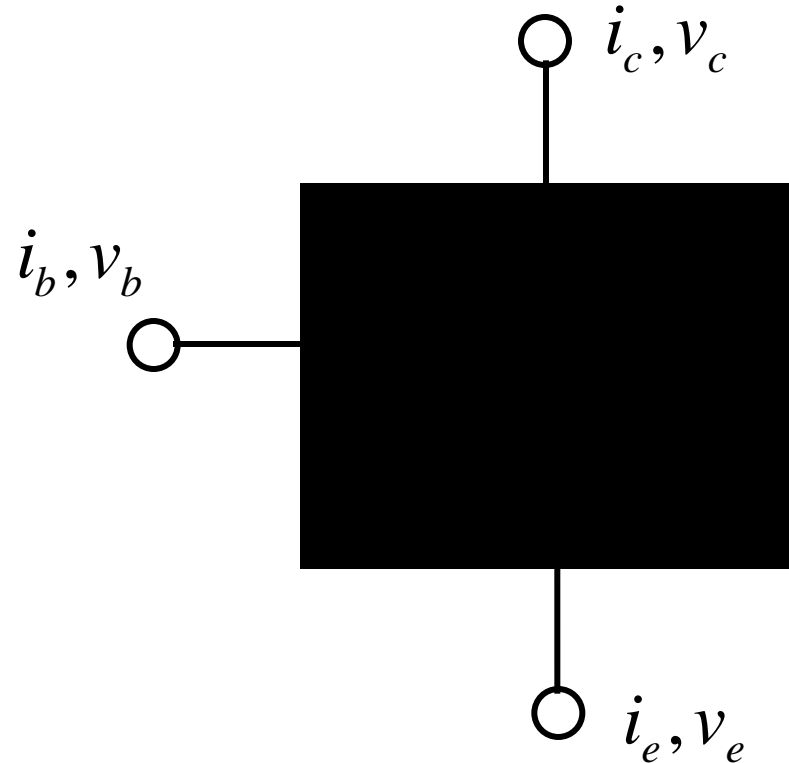
$$\begin{pmatrix} i_e \\ i_b \\ i_c \end{pmatrix} = \begin{pmatrix} \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \end{pmatrix} \begin{pmatrix} v_e \\ v_b \\ v_c \end{pmatrix}$$



Y-matrix has 9 elements, but once you know 4 you know them all because:

$$i_e = i_b + i_c$$

and: $v_{cb} + v_{be} = v_{ce}$

See book about details procedure to get 9 parameters from only 4.

Three configurations:

Common emitter configuration ($v_e=0$):

$$\begin{pmatrix} i_b \\ i_c \end{pmatrix} = \begin{pmatrix} y_{bb} & y_{bc} \\ y_{cb} & y_{cc} \end{pmatrix} \begin{pmatrix} v_b \\ v_c \end{pmatrix} = [y]_e \begin{pmatrix} v_b \\ v_c \end{pmatrix}$$

Common base configuration ($v_b=0$):

$$\begin{pmatrix} i_e \\ i_c \end{pmatrix} = \begin{pmatrix} y_{ee} & y_{ec} \\ y_{ce} & y_{cc} \end{pmatrix} \begin{pmatrix} v_e \\ v_c \end{pmatrix} = [y]_b \begin{pmatrix} v_e \\ v_c \end{pmatrix}$$



Easiest to
calculate from
doping profile.


Common collector configuration ($v_c=0$):

$$\begin{pmatrix} i_b \\ i_e \end{pmatrix} = \begin{pmatrix} y_{bb} & y_{be} \\ y_{eb} & y_{ee} \end{pmatrix} \begin{pmatrix} v_b \\ v_e \end{pmatrix} = [y]_c \begin{pmatrix} v_b \\ v_e \end{pmatrix}$$

Generalized π model:

Regardless of which configuration you use, the following π model applies:
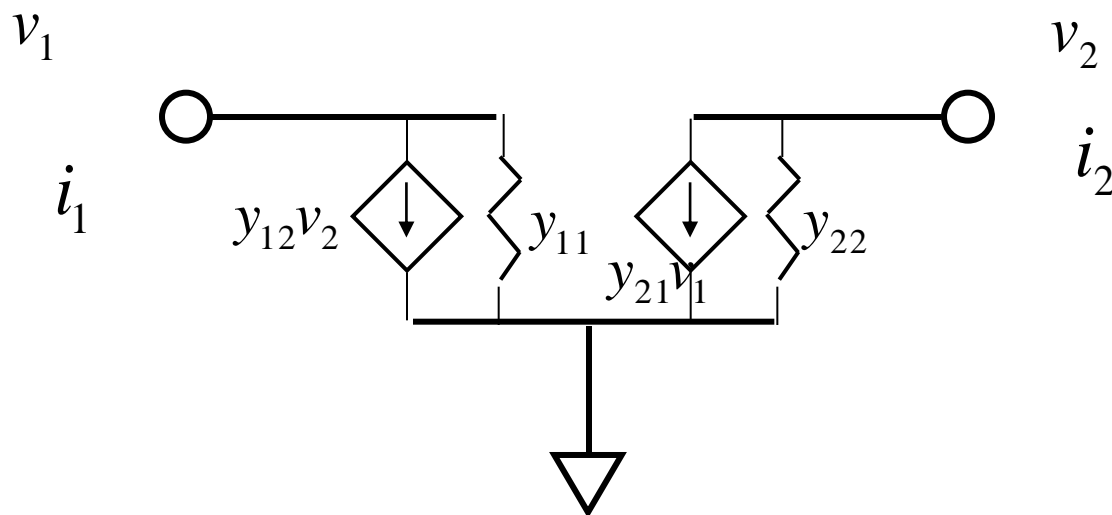
$$\begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \end{pmatrix}$$



Common emitter: 1=base, 2=collector


Common base: 1=emitter, 2=collector

Common collector: 1=base, 2=emitter

You might be used to
 $V=IR$

General impedance matrix
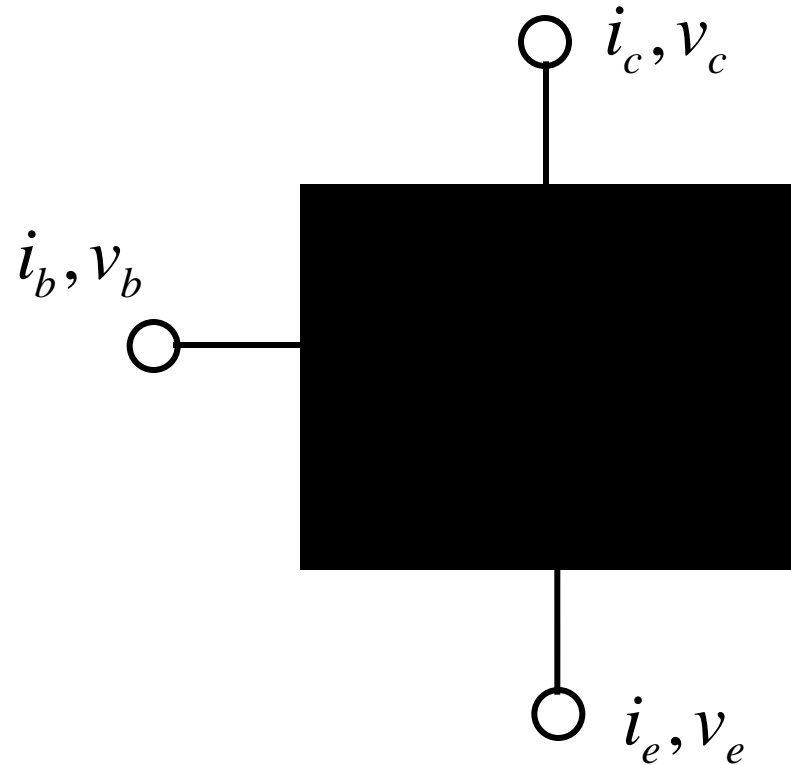
$$\begin{pmatrix} v_e \\ v_b \\ v_c \end{pmatrix} = \begin{pmatrix} \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \end{pmatrix} \begin{pmatrix} i_e \\ i_b \\ i_c \end{pmatrix}$$



Y-matrix has 9 elements, but once you know 4 you know them all because:

h matrix:

$$\begin{pmatrix} v_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{pmatrix} \begin{pmatrix} i_1 \\ v_2 \end{pmatrix}$$

Common emitter: 1=base, 2=collector

Common base: 1=emitter, 2=collector

Common collector: 1=base, 2= emitter

Note: In general, matrix elements depend on dc currents, dc voltages, and frequency. Spec. sheet (or model) will provide the matrix elements as a table vs. frequency, usually for only one bias current.

Common emitter h matrix:

$$\begin{pmatrix} v_b \\ i_c \end{pmatrix} = \begin{pmatrix} h_{11e} & h_{12e} \\ h_{21e} & h_{22e} \end{pmatrix} \begin{pmatrix} i_b \\ v_c \end{pmatrix}$$

- Early effect:

Collector voltage changes current gain (β).


- β depends on frequency *and* collector voltage.
- How do we define frequency at which $\beta = 1$?
- At $v_c=0$. This *is* h_{21e}

$$i_c = h_{21e}i_b + h_{22e}v_c \rightarrow h_{21e}i_b$$

- We define f_T such that:

$$|h_{21e}|(f_T) = 1$$

S-matrix

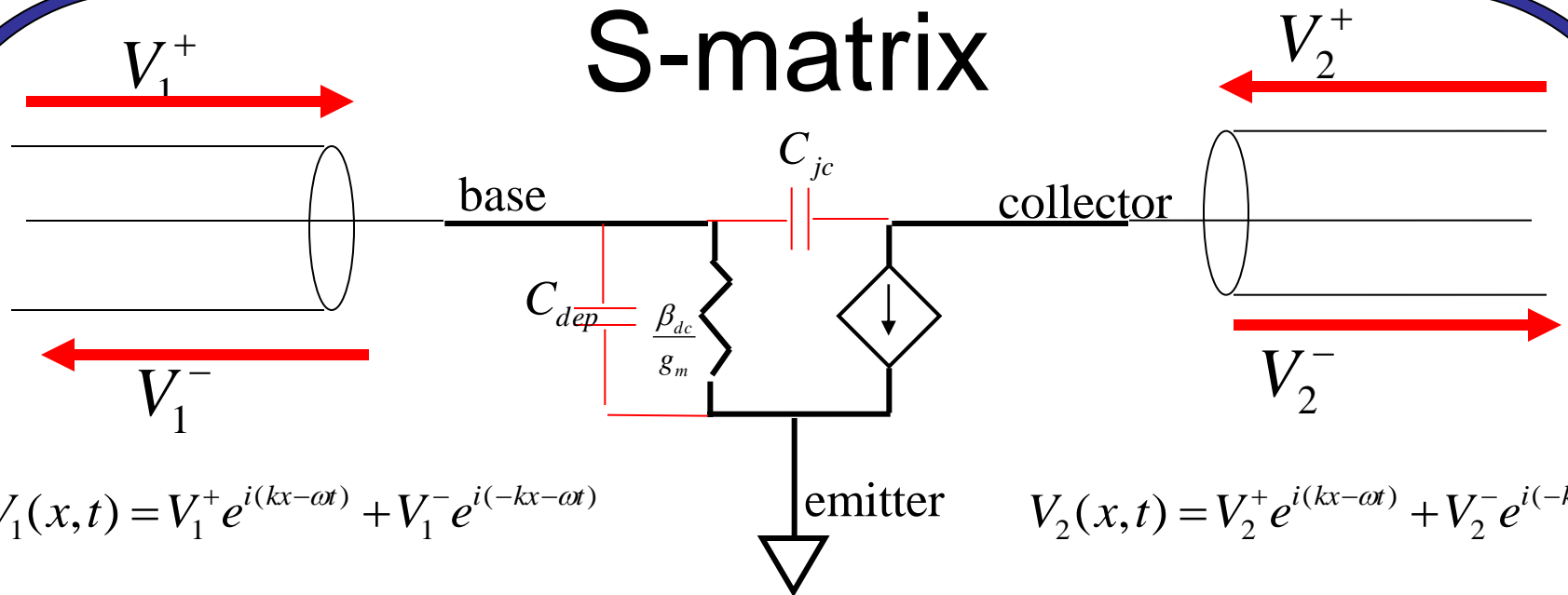

$$\begin{pmatrix} V_1^- \\ V_2^- \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} V_1^+ \\ V_2^+ \end{pmatrix}$$

$$V_1^- = S_{11} V_1^+ + S_{12} V_2^+$$

$$V_2^- = S_{21} V_1^+ + S_{22} V_2^+$$


S-parameters

TOSHIBA


2SA1245

This is what you see on data sheets.
Related to input impedance, output impedance
and gain vs. frequency.
=> Need to discuss ac performance.

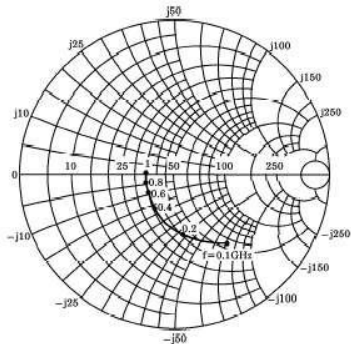
S_{11e}
 $V_{CE} = -5V$
 $I_C = -10mA$
 $T_a = 25^\circ C$
(UNIT : Ω)



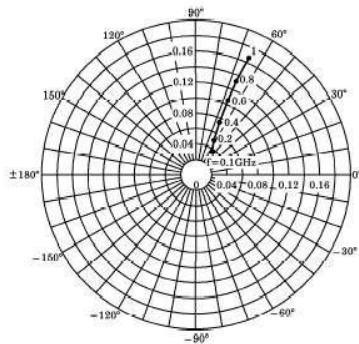
S_{12e}
 $V_{CE} = -5V$
 $I_C = -10mA$
 $T_a = 25^\circ C$



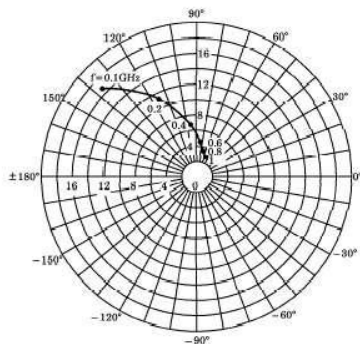S_{21e}
 $V_{CE} = -5V$
 $I_C = -10mA$
 $T_a = 25^\circ C$



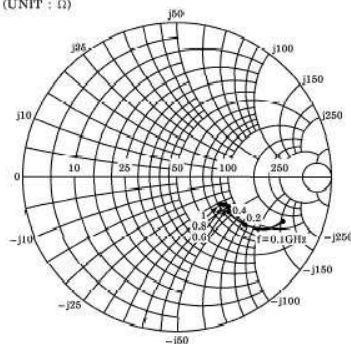S_{22e}
 $V_{CE} = -5V$
 $I_C = -10mA$
 $T_a = 25^\circ C$
(UNIT : Ω)




Summary of parameters

- Impedance matrix ($V=IR \rightarrow V=IZ$)
- Admittance matrix ($I=YV$)
- h-matrix (combination)
- ABCD matrix (combination)
- S-matrix (microwave reflections and transmissions)


“If you know one, then you know them all...”

See Liu, page 249 for conversions.

Measurement techniques

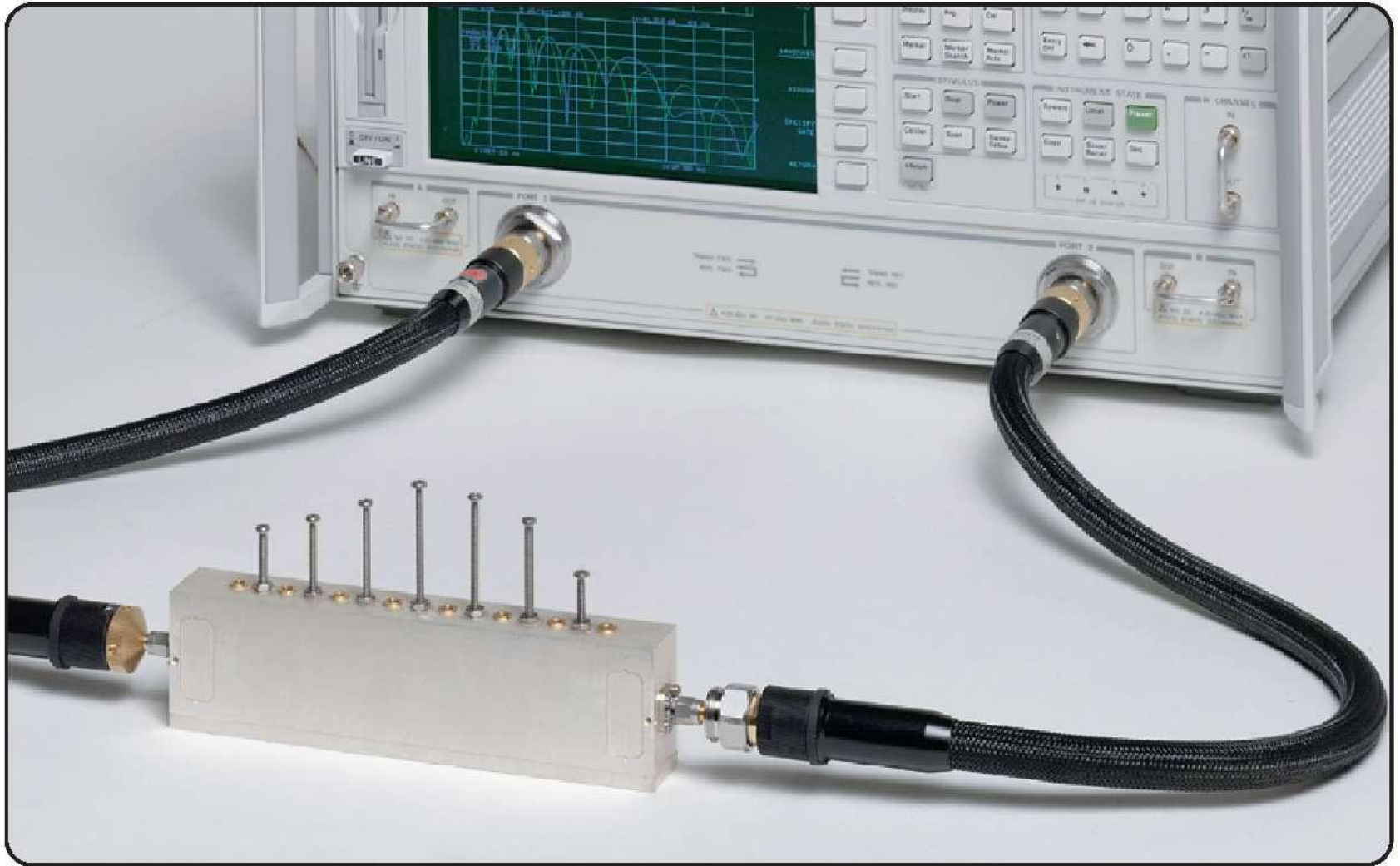

Measurement techniques

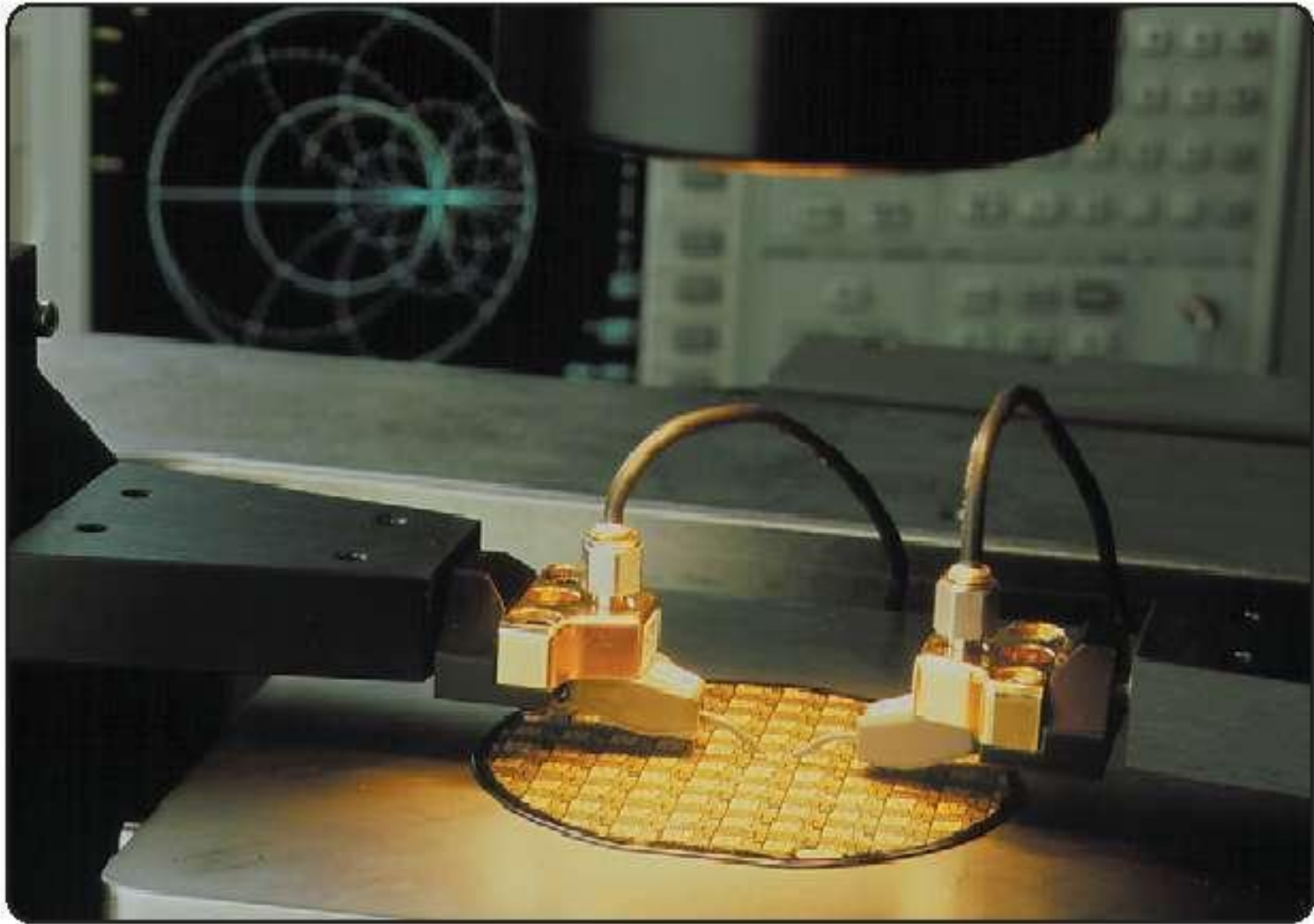



Cost (*rough* estimates)

- 10 GHz: \$50,000
- 20 GHz: \$70,000
- 40 GHz: \$90,000
- 110 GHz: \$250,000
- > 110 GHz: very expensive

For cost and difficulty reasons, parameters of transistor not always measure all the way up to f_T , but extrapolated.

These are only estimates. Contact vendor for actual prices.

AC equivalent circuit:

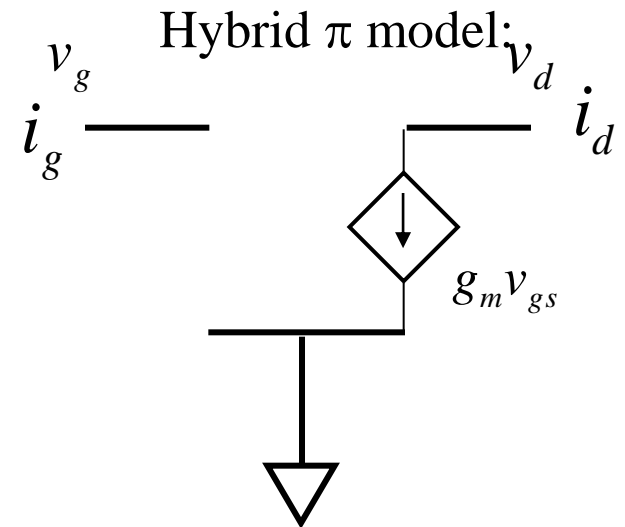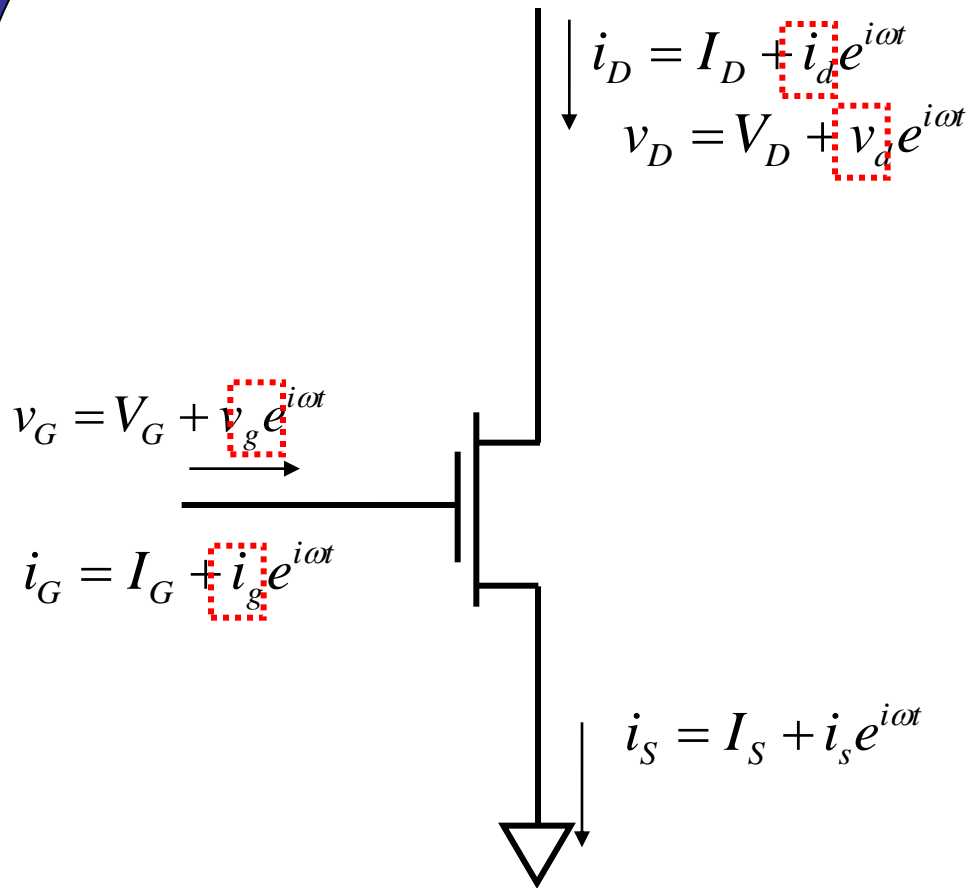


$$\begin{pmatrix} i_g \\ i_d \end{pmatrix} = \begin{pmatrix} 0 & 0 \\ g_m & 0 \end{pmatrix} \begin{pmatrix} v_g \\ v_d \end{pmatrix}$$

This is the common-source Y-matrix. You can get all the matrices from it.

$$f_T$$

Hybrid π model:

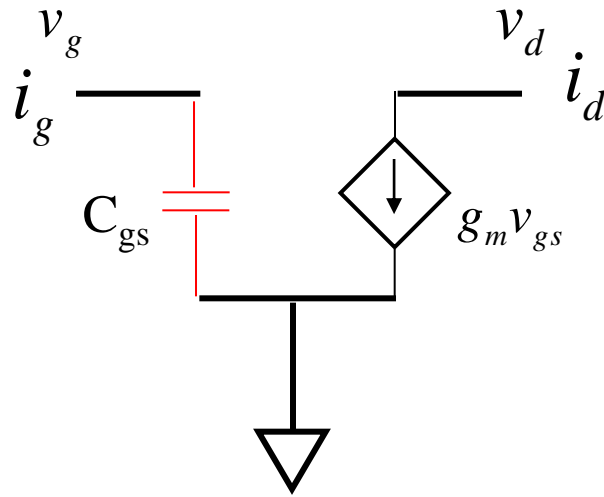


When current flowing through capacitor is equal to $g_m v_{gs}$ then the frequency is f_T .

$$i_g = v_{gs}(\omega C_{gs}) \quad i_d = g_M v_{gs}$$

$$\text{At } f_T \quad g_M v_{gs} = v_{gs}(\omega_T C_{gs})$$

$$\Rightarrow \omega_T = \frac{g_M}{C_{gs}} \Rightarrow f_T = \frac{g_M}{2\pi C_{gs}}$$

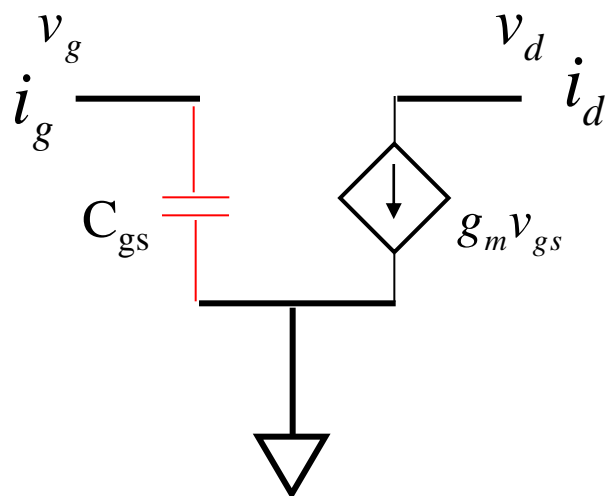
 f_T

$$f_T = \frac{g_M}{2\pi C_{gs}}$$

In HW#6, you will prove for the long-channel device:

$$g_M = \frac{W\mu C'_{ox}}{L} (V_{GS} - V_T)$$

$$C'_{ox} \sim C_{gs} / (LW)$$

$$f_T \rightarrow \frac{1}{2\pi} \frac{\mu(V_{GS} - V_T)}{L^2}$$

For a short-channel device,

$$g_M = v_{sat} WC'_{ox}$$

$$f_T \rightarrow \frac{v_{sat}}{2\pi L} = \frac{1}{2\pi\tau_{tr}}$$

Note:

(Intrinsic)

In saturation,


$$C_{gs} = (2/3) C_{ox} WL$$

$$C_{gd} = 0$$


$$C_{sd} = 0$$

So book model is only good for frequencies much less than f_T .

AC equivalent circuit:

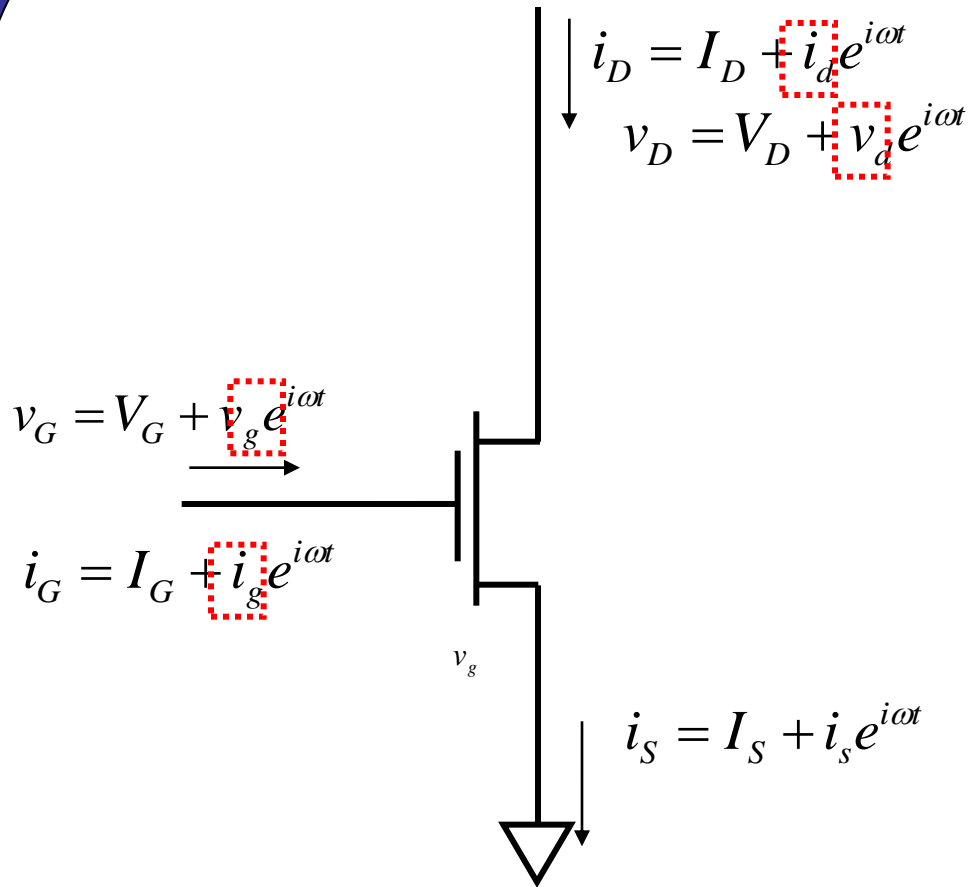


Hybrid π model:

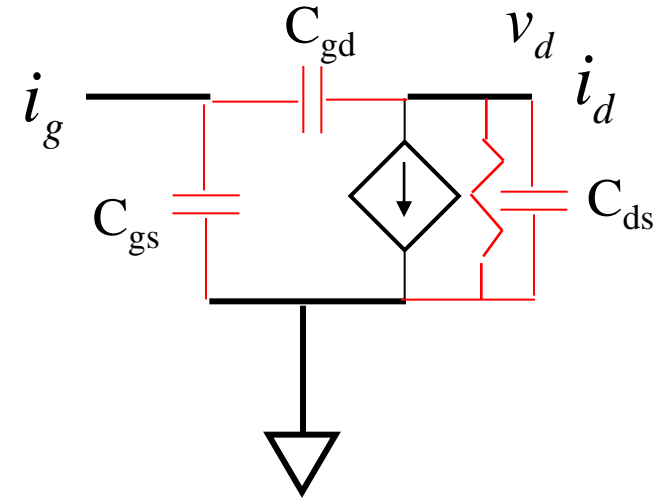

C_{gs} dominates.


Non-quasi static model:

Hybrid π model:

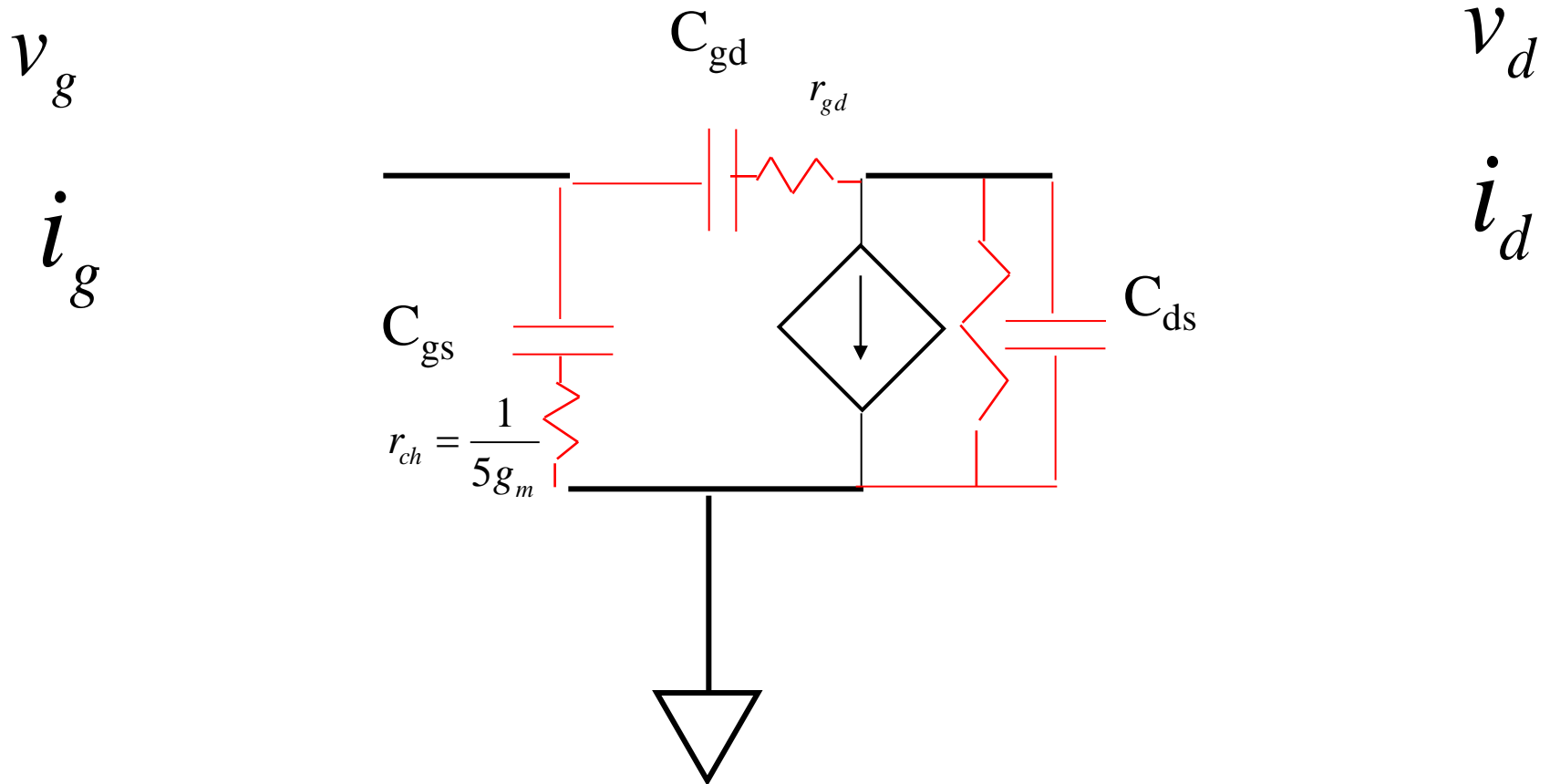

Parasitics: Gate resistance:

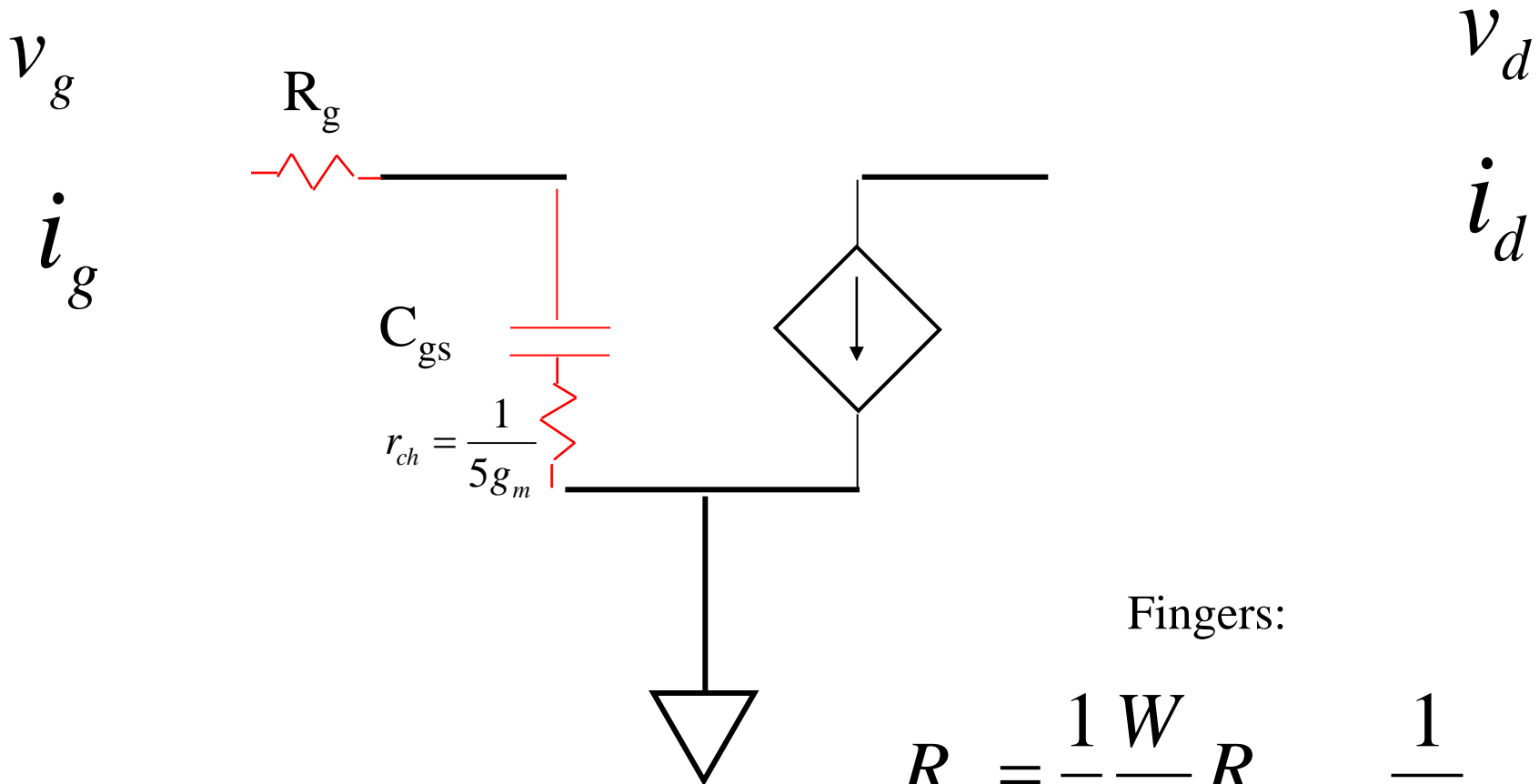
$$R_g = \frac{1}{3} \frac{W}{L} R_{square}$$



Fingers:


$$R_g = \frac{1}{3} \frac{W}{L} R_{square} \frac{1}{N}$$

Parasitics: Source/Drain resistance:

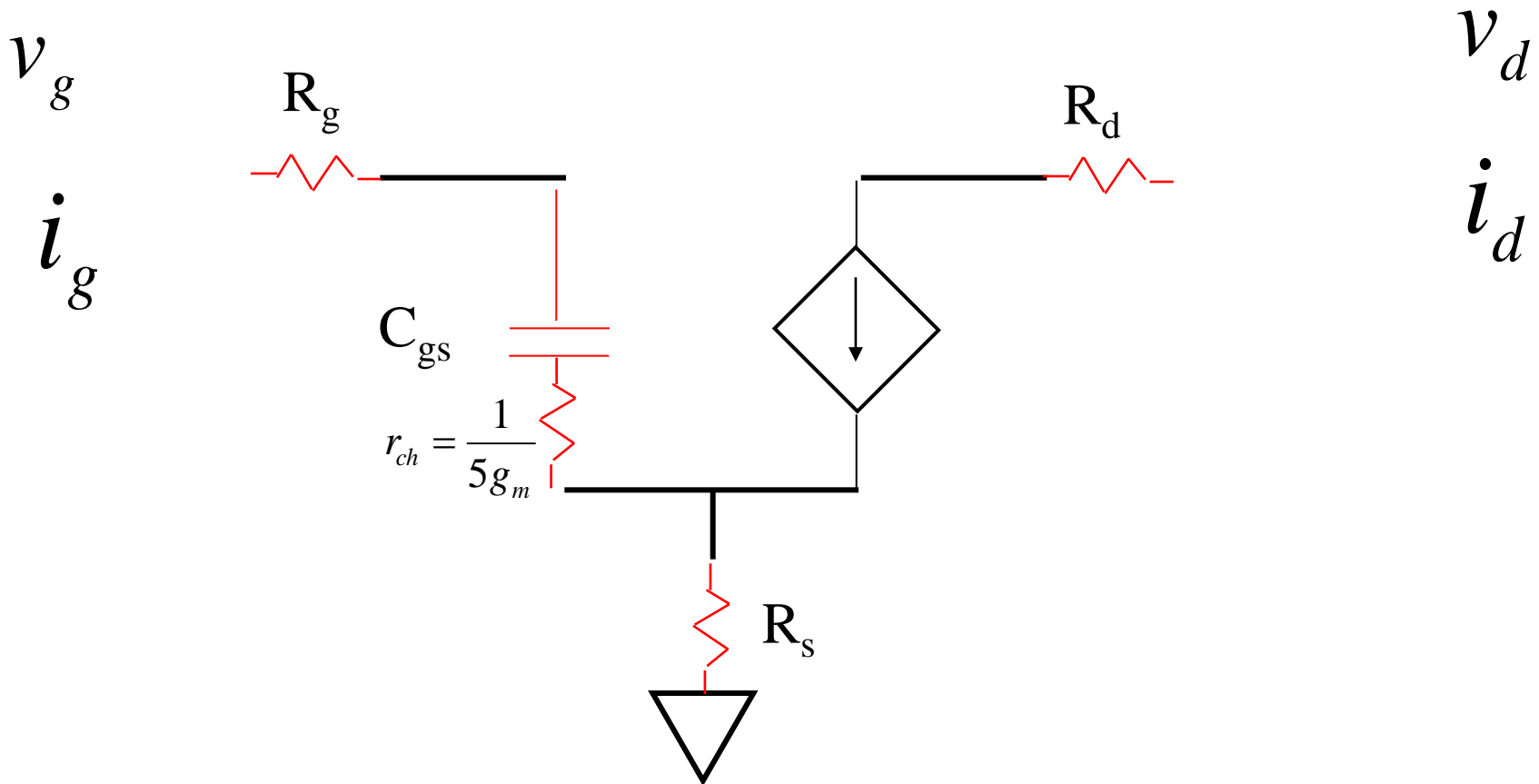

f_T
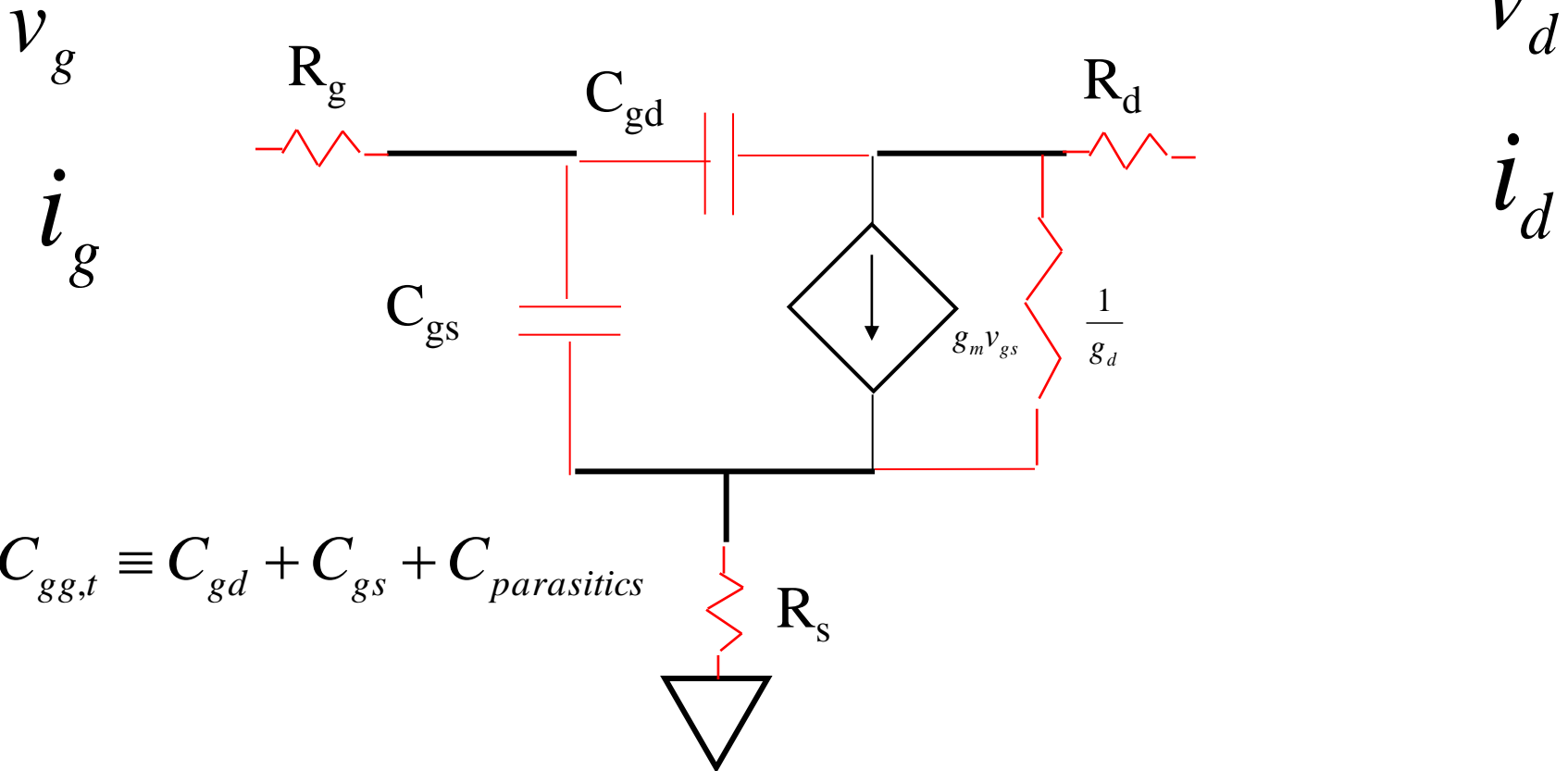
$$\frac{1}{2\pi f_T} = \frac{C_{gg,t}}{g_m} + \frac{C_{gg,t}}{g_m} (R_S + R_D) g_d + (R_S + R_D) C_{gd,t}$$



f_{\max} :

In real circuits, we do not want to short circuit the output!

Unilateral power gain: if impedance matching network is set up so that there is no reverse transmission ($S_{12}=0$), in that case the power gain is called the *unilateral power gain*.

“It can be shown that...”

$$U = \frac{|z_{21} - z_{12}|^2}{4[\operatorname{Re}(z_{11}) \operatorname{Re}(z_{22}) - \operatorname{Re}(z_{12}) \operatorname{Re}(z_{21})]}$$

“It can be shown that...”

$$f_{\max} = \sqrt{\frac{f_T}{8\pi r_g C_{gd}}}$$

Note r_{gate} dependence.

OR:

$$f_{\max} = \frac{1}{2} f_T \sqrt{\frac{r_o}{r_g}}$$

f_{MAX}

$$f_{MAX} = \sqrt{\frac{f_T}{8\pi R_G C_{gd,t} \left[1 + \left(\frac{2\pi f_T}{C_{gd,t}} \right) \Psi \right]}}$$

$$\Psi \equiv (R_S + R_D) \frac{C_{gg,t}^2 g_d^2}{g_m^2} + (R_S + R_D) \frac{C_{gd,t} C_{gg,t} g_d}{g_m} + \frac{C_{gg,t}^2 g_d}{g_m^2}$$

f_{max} helped by fingers.

f_T not helped by fingers.

f_{MAX} sometimes larger, sometimes smaller than f_T .

Example

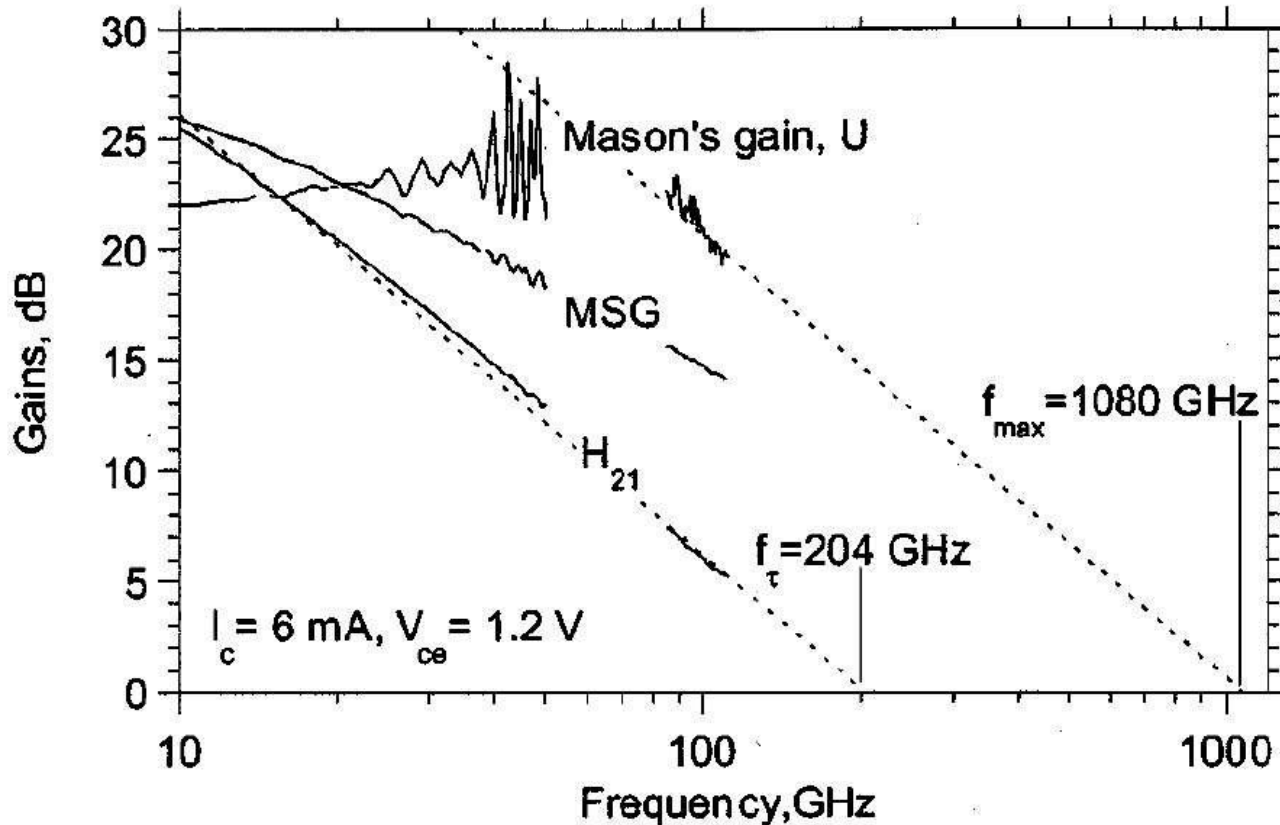


Fig. 14. Gains of a $0.4 \mu\text{m} \times 6 \mu\text{m}$ emitter and $0.7 \mu\text{m} \times 10 \mu\text{m}$ collector HBT fabricated using electron-beam lithography. Theoretical -20 dB/decade (H_{21} , U) gain slopes are indicated. The device exhibits an *extrapolated* 1.08 THz f_{max} .

From Rodwell, et al, TRANSACTIONS ON ELECTRON DEVICES 48 (11): 2606-2624 IEEE NOV 2001

RF/AMS

Table RFAMS1 RF and Analog Mixed-Signal CMOS Technology Requirements

Year of Production	2009	2010	2011	2012	2013	2014	2015	2016	2017	2018	2019	2020	2021	2022	2023	2024
<i>Performance RF/Analog [1]</i>																
Supply voltage (V) [2]	1.1	1.05	1.05	1.05	1	0.95	0.95	0.95	0.85	0.85	0.85	0.85	0.75	0.75	0.75	0.75
T_{ox} (nm) [2]	1.2	1.2	1.2	1.2	1.10	1.10	1.10	1.10	1.10	1.00	1.00	0.90	0.90	0.80	0.80	0.70
Gate Length (nm) [2]	38	38	32	29	27	22	18	17	15	14	13	12	11	9.7	8.9	8.1
g_m/g_{ds} at $5 \cdot L_{min-digital}$ [3]	30	30	30	30	30	30	30	30	30	30	30	30	30	30	30	30
1/f-noise ($\mu V^2 \cdot \mu m^2 / Hz$) [4]	100	90	80	70	70	60	50	50	40	40	40	30	30	30	20	20
σV_{th} matching ($mV \cdot \mu m$) [5]	5	5	5	5	5	5	5	5	5	5	5	4	4	4	4	4
I_{ds} ($\mu A / \mu m$) [6]	9	9	8	7	7	6	5	4	4	3	3	3	2	2	2	2
Peak F_t (GHz) [7]	240	240	280	310	340	400	480	520	570	630	680	750	820	890	970	1060
Peak F_{max} (GHz) [8]	290	290	340	380	420	510	610	670	740	820	900	990	1090	1200	1320	1450
NF _{min} (dB) [9]	0.2	<0.2	<0.2	<0.2	<0.2	<0.2	<0.2	<0.2	<0.2	<0.2	<0.2	<0.2	<0.2	<0.2	<0.2	<0.2
<i>Precision Analog/RF Driver [1]</i>																
Supply voltage (V)	2.5	1.8	1.8	1.8	1.8	1.8	1.8	1.8	1.8	1.8	1.5	1.5	1.5	1.5	1.5	1.5
T_{ox} (nm) [10]	5	3	3	3	3	3	3	3	3	3	2.6	2.6	2.6	2.6	2.6	2.6
Gate Length (nm) [10]	250	180	180	180	180	180	180	180	180	180	130	130	130	130	130	130
g_m/g_{ds} at $10 \cdot L_{min-digital}$ [11]	220	160	160	160	160	160	160	160	160	160	110	110	110	110	110	110
1/f Noise ($\mu V^2 \cdot \mu m^2 / Hz$) [4]	1000	360	360	360	360	360	360	360	360	360	270	270	270	270	270	270
σV_{th} matching ($mV \cdot \mu m$)	9	6	6	6	6	6	6	6	6	6	5	5	5	5	5	5
Peak F_t (GHz) [7]	40	50	50	50	50	50	50	50	50	50	70	70	70	70	70	70
Peak F_{max} (GHz) [8]	70	90	90	90	90	90	90	90	90	90	120	120	120	120	120	120
Availability of optional analog / High-voltage FETs	limited	limited	common	common	wide	wide	wide	wide	wide	wide	wide	wide	wide	wide	wide	wide

switch to UTB FD or

RF CMOS


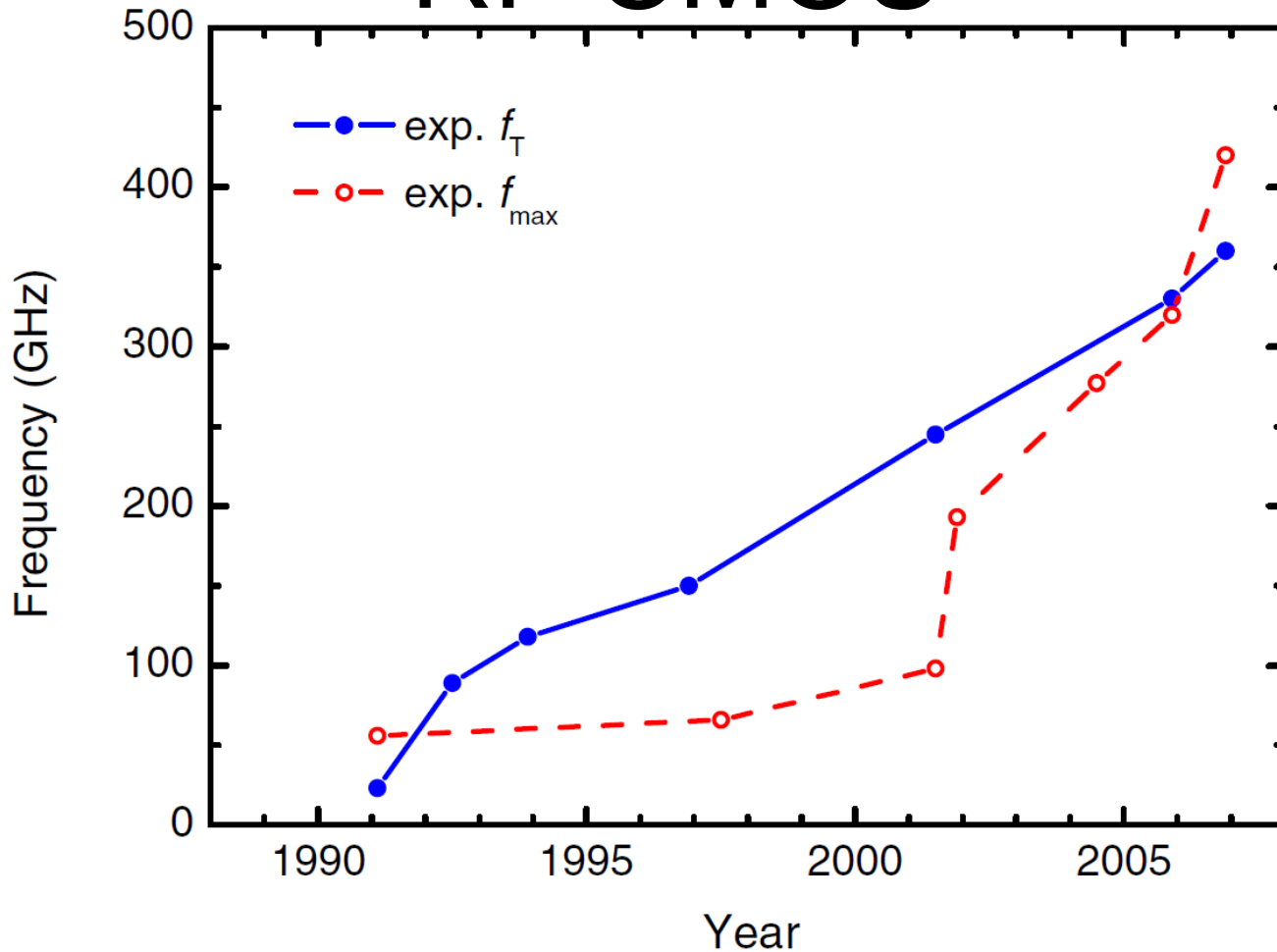


Fig. 1. Evolution of the record cutoff frequency f_T and the record maximum frequency of oscillation f_{max} of RF Si MOSFETs versus time.


F. Schwierz and J. J. Liou, "RF Transistors: Recent Developments and Roadmap toward Terahertz Applications", *Solid-State Electronics*, **51**, 1079-1091, (2007).

Cutoff frequency (f_T)

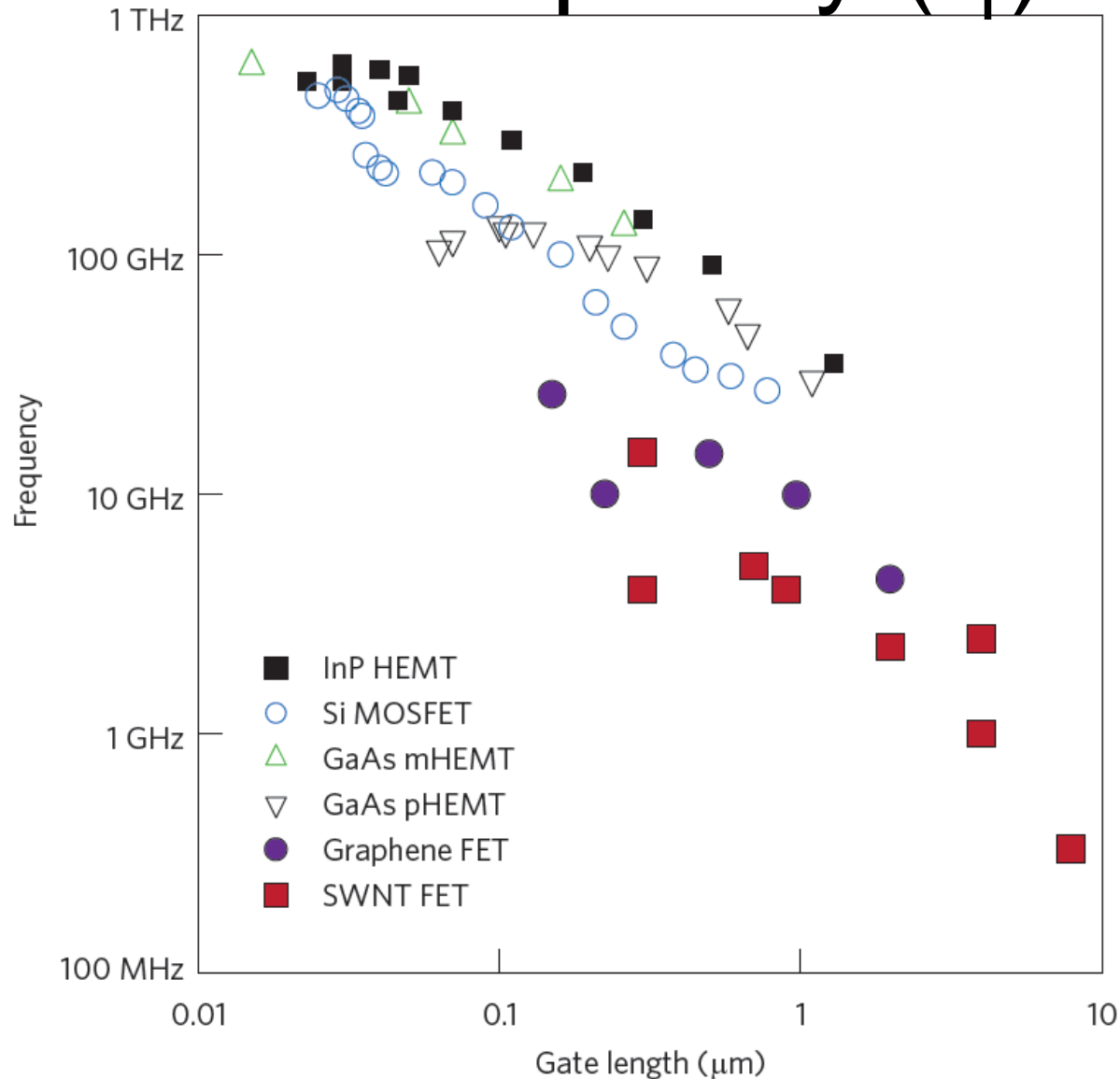


C. Rutherglen, D. Jain and P. Burke, "Nanotube Electronics for Radiofrequency Applications", *Nature Nanotechnology*, **4**, 811-819, (2009).

III-V f_{Max}

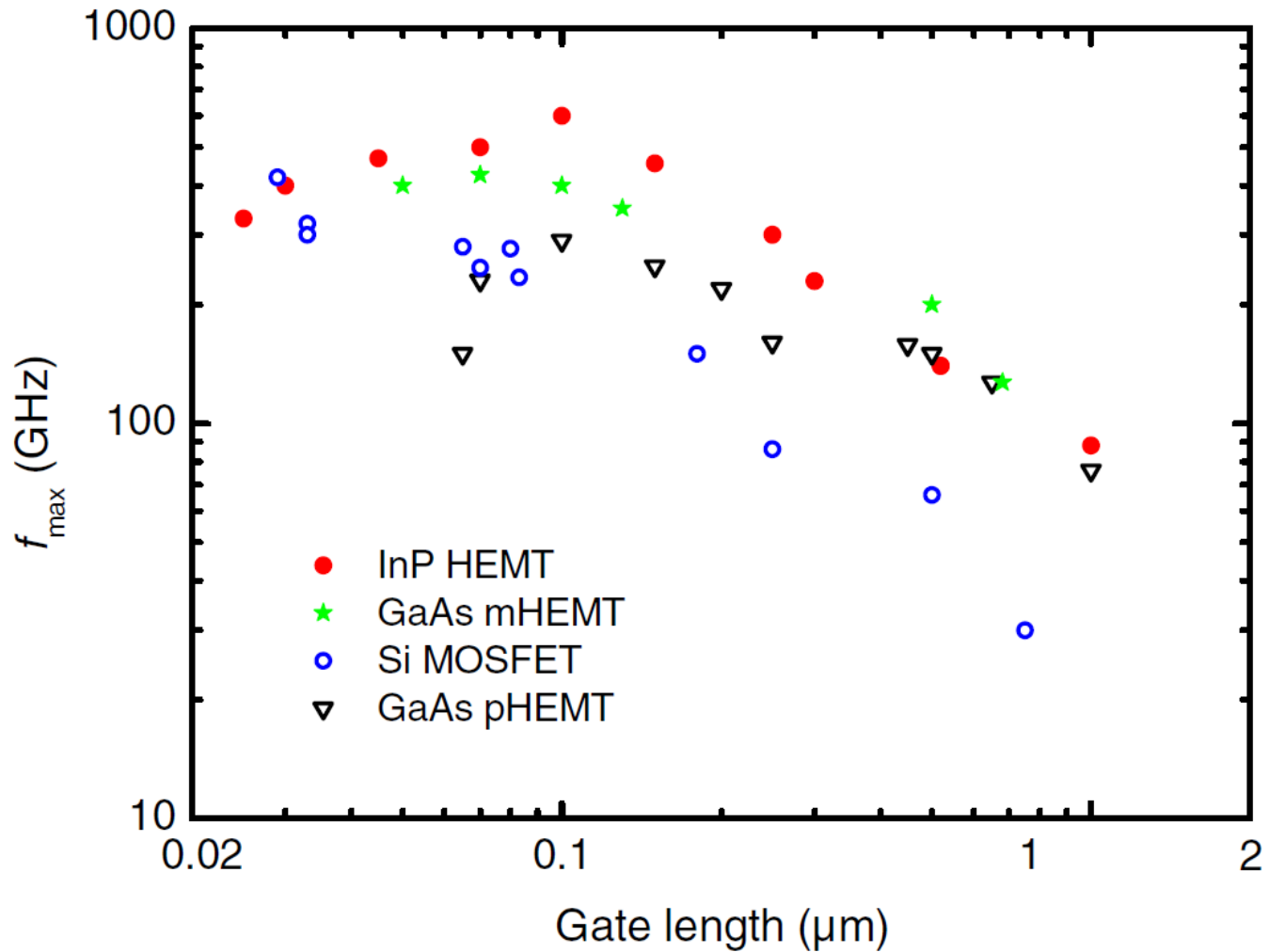

F. Schwierz and J. J. Liou, "RF Transistors: Recent Developments and Roadmap toward Terahertz Applications", *Solid-State Electronics*, **51**, 1079-1091, (2007).

f_T vs f_{Max}

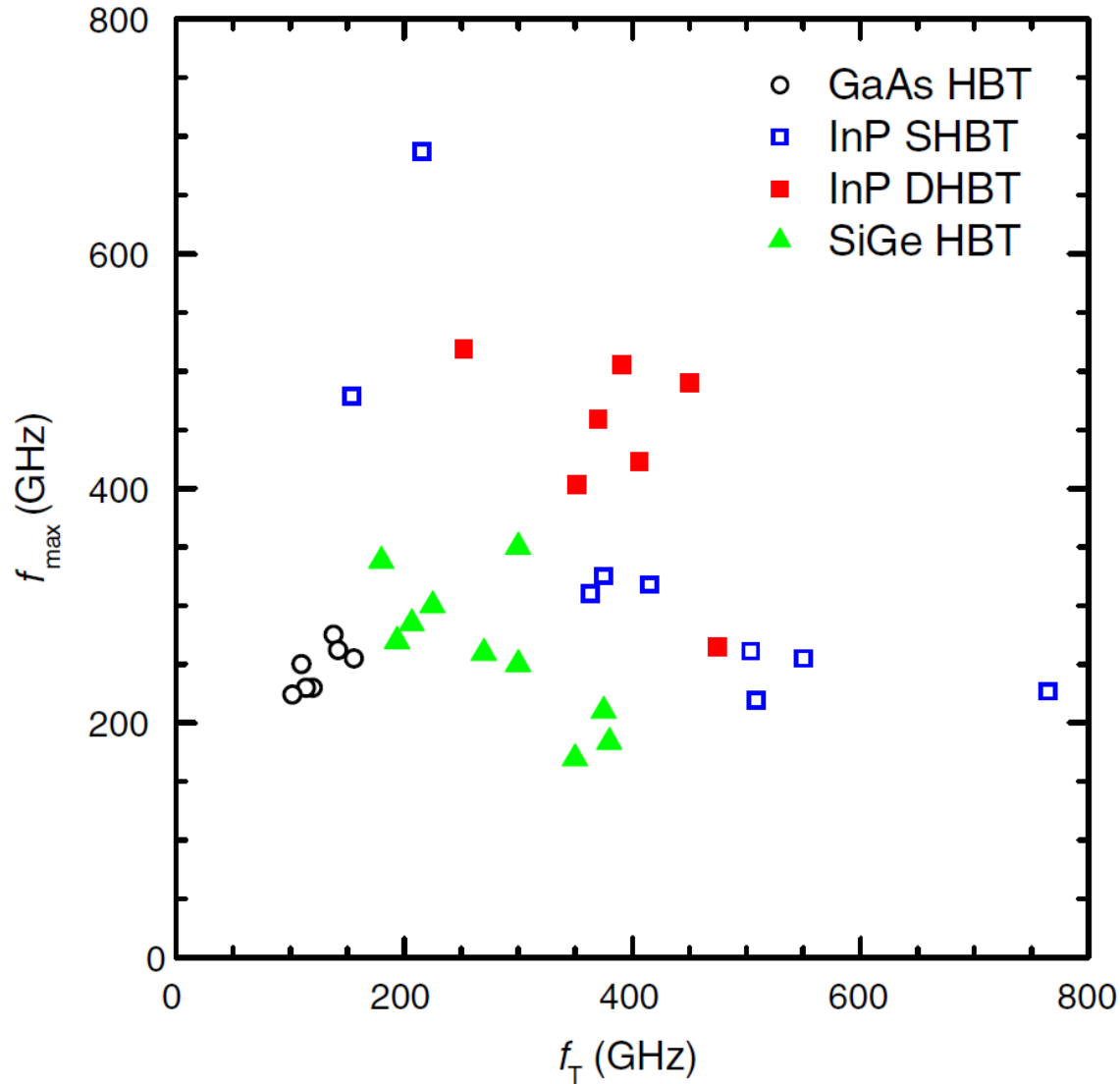

F. Schwierz and J. J. Liou, "RF Transistors: Recent Developments and Roadmap toward Terahertz Applications", *Solid-State Electronics*, **51**, 1079-1091, (2007).