

EECS70A Spring 2010 Midterm Exam #2  
5/20/2010 8:00 to 9:20 am  
Professor Peter Burke


Name: Solutions  
ID no.: \_\_\_\_\_

1	2	3	4	5	Total
/20	/20	/20	/20	/20	/100

**DO NOT BEGIN THE EXAM  
UNTIL YOU ARE TOLD TO  
DO SO.**

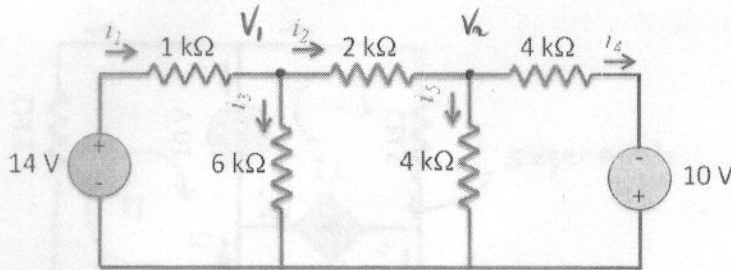**PROBLEM ONE:**

Using nodal analysis, find the nodal voltages and all the currents ( $i_1$ - $i_5$ ) in this circuit.



$$\frac{V_1}{6k\Omega} + \frac{V_1 - 14}{1k\Omega} + \frac{V_1 - V_2}{2k\Omega} = 0$$

$$V_1 + 6V_1 - 84 + 3V_1 - 3V_2 = 0$$

$$10V_1 - 3V_2 = 84$$

$$10(2V_2 + 5) - 3V_2 = 84$$

$$20V_2 + 50 - 3V_2 = 84$$

$$V_2 = \frac{34}{17} = 2V$$

$$\frac{V_2}{4k\Omega} + \frac{V_2 + 10}{4k\Omega} + \frac{V_2 - V_1}{2k\Omega} = 0$$

$$V_2 + V_2 + 10 + 2V_2 - 2V_1 = 0$$

$$4V_2 - 2V_1 = -10$$

$$2V_2 - V_1 = -5$$

$$V_1 = 5 + 2V_2$$

$$V_1 = 5 + 4 = 9V$$

$$i_1 = \frac{14 - 9}{1k} = \boxed{5mA}$$

$$i_2 = \frac{9 - 2}{2k\Omega} = \boxed{3.5mA}$$


$$i_3 = \frac{9}{6k\Omega} = \boxed{1.5mA}$$

$$i_4 = \frac{2 + 10}{4k\Omega} = \boxed{3mA}$$

$$i_5 = \frac{2}{4k\Omega} = \boxed{0.5mA}$$

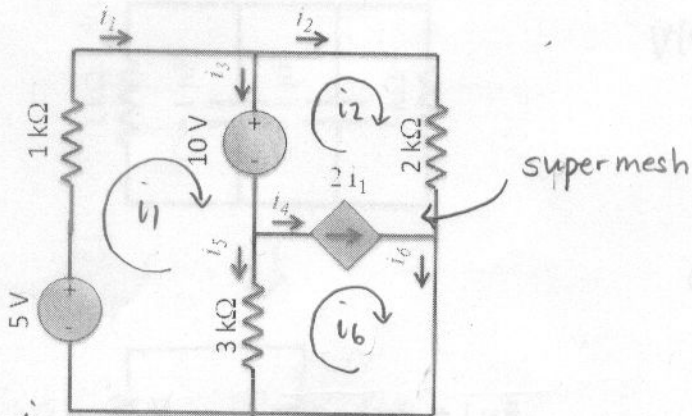**PROBLEM TWO:**

Use mesh analysis to find the currents  $i_1$ - $i_6$ , then find the power dissipated in the  $2k\Omega$  resistor.



power dissipated in  $2k\Omega$  resistor:

$$P = I^2 R = (5mA)^2 \cdot 2k\Omega = 50mW$$

Supermesh:  $i_6 - i_2 = 2i_1$

Mesh 1:  $-5 + 1k\Omega(i_1) + 10 + 3k(i_1 - i_6) = 0$   
 $4k\Omega i_1 - 3ki_6 = -5$

$4k\Omega i_1 - 3k(2i_1 + i_2) = -5$   
 $2k\Omega i_1 - 3ki_2 = -5$   
 $i_1 = \frac{5 - 3ki_2}{2k}$

Mesh 2:  $3k(i_6 - i_1) - 10 + 2k(i_2) = 0$

$2ki_2 + 3ki_6 - 3ki_1 = 10$   
 $2ki_2 + 3k(2i_1 + i_2) - 3ki_1 = 10$   
 $5ki_2 + 3ki_1 = 10$

$5ki_2 + 3k\left(\frac{5 - 3ki_2}{2k}\right) = 10$   
 $5ki_2 + \frac{15 - 9ki_2}{2k} = 10$

$10ki_2 + 15 - 9ki_2 = 20$   
 $i_2 = 5mA$

$i_5 = i_4 - i_6 = -5 - -5 = 0mA$

$i_3 = i_1 - i_2 = -5mA - 5mA = -10mA = i_3$

$i_1 = \frac{5 - 3k(5mA)}{2k} = \frac{-10}{2k} = -5mA = i_1$




$i_6 = 2i_1 + i_2 = -10mA + 5mA = -5mA = i_6$

$i_4 = 2i_1 = -10mA = i_4$



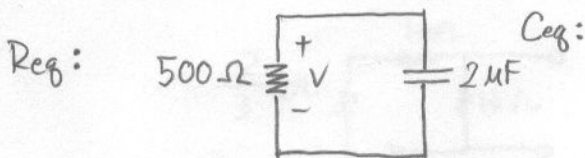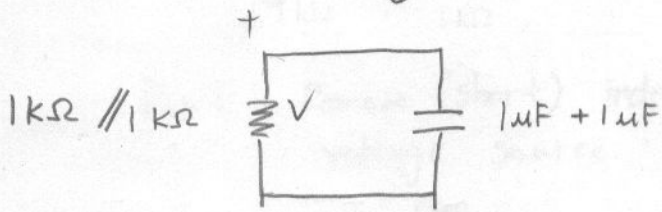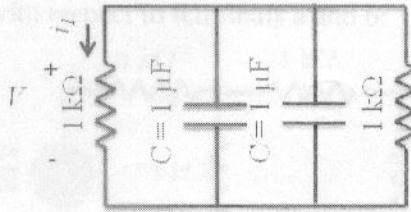**PROBLEM THREE:**

Find  $V(t)$ ,  $i_1(t)$ , given that  $V(t=0) = 5$  V.



$$V(t) = V(0) e^{-\frac{t}{RC}} \text{ V}$$

$$V(t=0) = V(0) = 5$$

$$R_{eq} = 500 \Omega$$

$$C_{eq} = 2 \mu\text{F}$$

$$\tau = RC = 500 \cdot 2 \cdot 10^{-6} = 0.001$$

$$V(t) = 5 e^{-\frac{t}{0.001}}$$


$$V(t) = 5 e^{-1000t} \text{ V}$$

$$i_1(t) = \frac{V(t)}{1000 \Omega}$$



$$i_1(t) = 0.005 e^{-1000t} \text{ A}$$

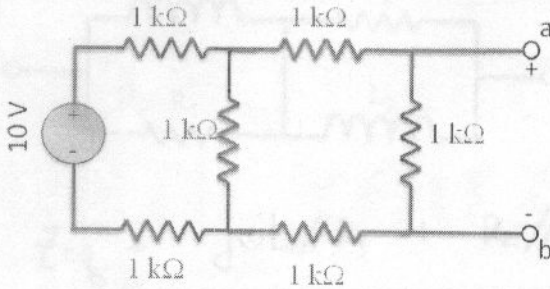**PROBLEM FOUR:**

Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:



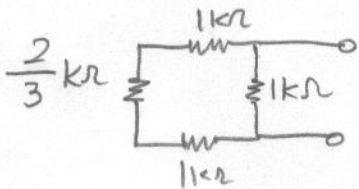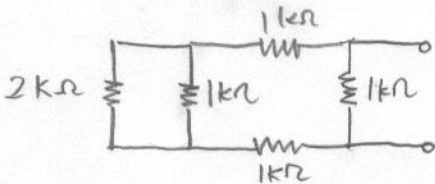
$R_{th}$ : Remove (short) independent voltage source




$$\frac{8}{3} \parallel 1 = \frac{\frac{8}{3} \cdot 1}{\frac{8}{3} + 1} = \frac{\frac{8}{3}}{\frac{8}{3} + \frac{3}{3}} = \frac{8}{11} \text{ k}\Omega = R_{th}$$

$$\frac{8}{11} \text{ k}\Omega = R_N$$



$\frac{8}{11} \text{ k}\Omega$

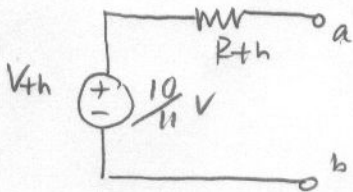

← Thevenin

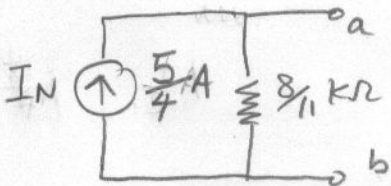


$V_{th} = V_{oc}$

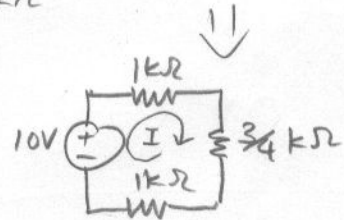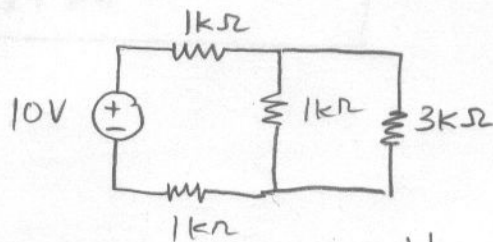

$$I = \frac{10}{2 \text{ k}\Omega + \frac{3}{4} \text{ k}\Omega} = \frac{40}{11} \text{ mA}$$

$$\left(\frac{40}{11} \text{ mA}\right) \left(\frac{3}{4} \text{ k}\Omega\right) = \frac{30}{11} \text{ V}$$


So, new ckt:

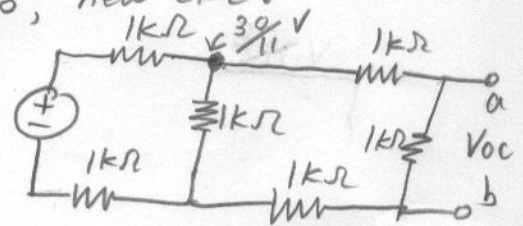

$$V_{oc} = \frac{30}{11} / 3 = \frac{10}{11} \text{ V}$$

$$V_{th} = \frac{10}{11} \text{ V}$$

$$I_N = \frac{V_{th}}{R_{th}} = \frac{10}{8} = \frac{5}{4} \text{ A}$$

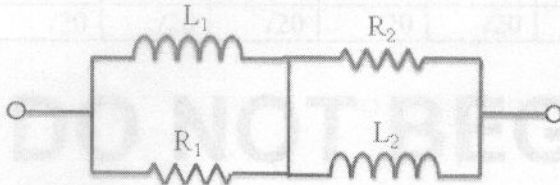**PROBLEM FIVE:**Find  $Z_{eq}$  for this circuit:

$$Z_{eq} = j\omega L_1 // R_1 + R_2 // j\omega L_2$$

$$Z_{eq} = \frac{j\omega L_1 \cdot R_1}{j\omega L_1 + R_1} + \frac{j\omega L_2 \cdot R_2}{j\omega L_2 + R_2} \quad \Omega$$