

# EECS 70A: Network Analysis


Homework #3

Due in discussion section,  
Wednesday, May 5, 2010.

Problem 1:

-Use nodal analysis to find all node voltages.

-Find  $i_x$ .

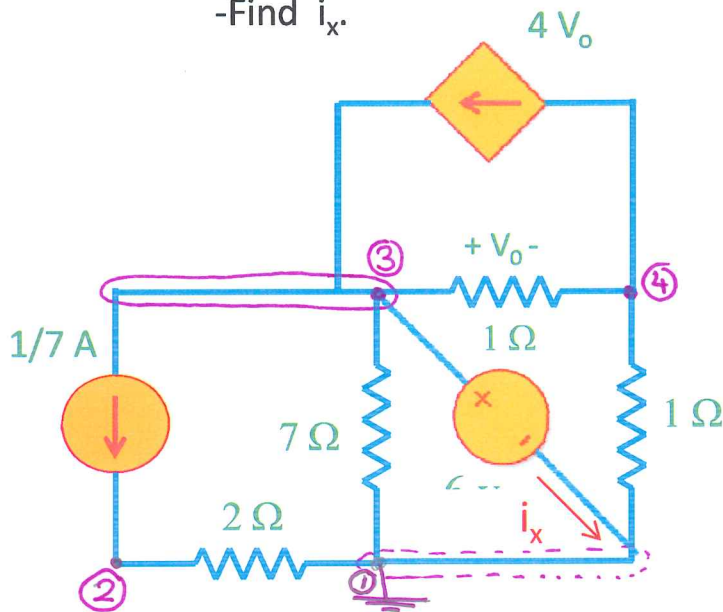

↳ node 1 is the voltage ref.  
so  $v_1 = 0$  by definition

## Problem 1)

- ① Define the reference node  
You can choose any of the 4 nodes for the reference, if you choose node 1 or 3, one of the terminals of the voltage source is grounded and analysis will be easier. If you have chosen a reference other than node 1, your node voltage values might be different than this solution, but you should still get the same voltage drop across all elements and the same values for all currents.

There are 3 unknowns:  $V_2, V_3$  and  $V_4 \Rightarrow$  We need 3 independent equations.

- ② Apply KCL + Ohm's law to nodes:

$$\begin{aligned} \text{@ node 4: } \quad & \left. \begin{aligned} \frac{V_4 - V_3}{1\Omega} + \frac{V_4 - V_1}{1\Omega} + 4V_0 = 0 \\ V_0 = V_3 - V_4 \end{aligned} \right\} \begin{aligned} V_4 - V_3 + V_4 + 4(V_3 - V_4) &= 0 \\ V_3(-1 + 4) + V_4(1 + 1 - 4) &= 0 \\ \underline{3V_3 - 2V_4 = 0} & \text{ (eq. 1)} \end{aligned} \end{aligned}$$

$$\begin{aligned} \text{@ node 2: } \quad & \left. \begin{aligned} \frac{V_2 - V_1}{2\Omega} - \frac{1}{7}A = 0 \\ V_1 = 0 \end{aligned} \right\} \Rightarrow \underline{V_2 = \frac{2}{7}V} \text{ (eq. 2)} \end{aligned}$$

- ③ Apply KVL to voltage source:  $V_3 = 6V$  (eq. 3)

- ④ Now that we have the 3 equations, solve them for  $V_2, V_3$  and  $V_4$ :

$$\begin{aligned} \text{Plug } V_3 \text{ in equation 1: } \quad & 3(6V) - 2V_4 = 0 \\ & V_4 = \frac{18V}{2} = 9V \end{aligned}$$

$$\begin{cases} V_2 = \frac{2}{7}V \\ V_3 = 6V \\ V_4 = 9V \end{cases}$$

Prob.1

- Find  $i_x$ .

To find  $i_x$ , write a KCL at node 3:


$$\frac{1}{7}A + \frac{V_3}{7\Omega} + i_x + \frac{V_3 - V_4}{1\Omega} - 4V_0 = 0$$

$$\frac{1}{7}A + \frac{6V}{1\Omega} + i_x + \frac{6V - 9V}{1\Omega} - 4\left[\frac{6V}{V}\right](6V - 9V) = 0$$

$$1A + i_x - 3A + 12A = 0$$

$$\underline{i_x = -10A}$$

Problem 2: Solve for node voltages.

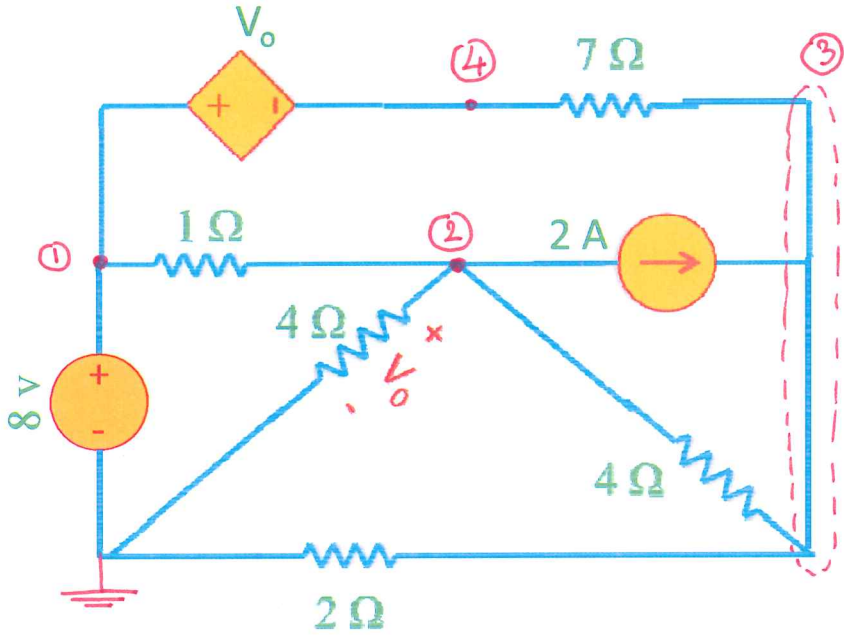

Problem 2)

$V_1, V_2, V_3$  and  $V_4$  are the unknowns  $\Rightarrow$  We have to write 4 independent equations.

at node 1 :  $V_1 = 8V$  (eq. 1)

KCL + Ohm @ node 2 :  $\frac{V_2 - V_1}{1\Omega} + \frac{V_2}{4\Omega} + \frac{V_2 - V_3}{4\Omega} + 2A = 0$

$\times 4$   $\left\{ \begin{array}{l} -V_1 + V_2(1 + \frac{1}{4} + \frac{1}{4}) - \frac{V_3}{4} = -2 \\ \hline -4V_1 + 6V_2 - V_3 = -8 \quad \text{(eq. 2)} \end{array} \right.$

KCL + Ohm @ node 3 :  $\frac{V_3 - V_4}{7\Omega} + \frac{V_3 - V_2}{4\Omega} + \frac{V_3}{2\Omega} - 2A = 0$

$\times 28$   $\left\{ \begin{array}{l} -\frac{V_2}{4\Omega} + V_3(\frac{1}{7\Omega} + \frac{1}{4\Omega} + \frac{1}{2\Omega}) - \frac{V_4}{7\Omega} = 2A \\ \hline -7V_2 + 25V_3 - 4V_4 = 56 \quad \text{(eq. 3)} \end{array} \right.$

KVL for the VCVS :  $\left. \begin{array}{l} V_1 - V_4 = V_0 \\ V_0 = V_2 \end{array} \right\} \Rightarrow V_1 - V_4 = V_2 \rightarrow V_1 - V_2 - V_4 = 0 \quad \text{(eq. 4)}$

Replace  $V_1 = 8V$  in eq. 2 & eq. 4 :

(eq. 2)  $\rightarrow -4 \times 8 + 6V_2 - V_3 = -8 \Rightarrow 6V_2 - V_3 = 24 \quad \text{(eq. 2*)}$

(eq. 4)  $\rightarrow V_1 - V_2 - V_4 = 0 \rightarrow 8 - V_2 - V_4 = 0 \Rightarrow V_2 + V_4 = 8V \quad \text{(eq. 4*)}$

(Prob. 2)

Solve equations 4, 2 and 3 using Cramer's method:

$$\begin{array}{l} \text{(eq 4)} \\ \text{(eq 2)} \\ \text{(eq 3)} \end{array} \begin{bmatrix} 1 & 0 & 1 \\ 6 & -1 & 0 \\ -7 & 25 & -4 \end{bmatrix} \begin{bmatrix} V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 8 \\ 24 \\ 56 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 1 & 0 & 1 \\ 6 & -1 & 0 \\ -7 & 25 & -4 \end{vmatrix} = 1 \times \begin{vmatrix} -1 & 0 \\ 25 & -4 \end{vmatrix} + 0 \times \begin{vmatrix} 6 & 0 \\ -7 & -4 \end{vmatrix} + 1 \times \begin{vmatrix} 6 & -1 \\ -7 & 25 \end{vmatrix}$$
$$= 1 \times (4 - 0) + 0 + 1 \times (6 \times 25 - 7) = 147$$

$$\Delta_1 = \begin{vmatrix} 8 & 0 & 1 \\ 24 & -1 & 0 \\ 56 & 25 & -4 \end{vmatrix} = 688$$

$$\Delta_2 = \begin{vmatrix} 1 & 8 & 1 \\ 6 & 24 & 0 \\ -7 & 56 & -4 \end{vmatrix} = 600$$

$$\Delta_3 = \begin{vmatrix} 1 & 0 & 8 \\ 6 & -1 & 24 \\ -7 & 25 & 56 \end{vmatrix} = 488$$

$$V_2 = \frac{\Delta_1}{\Delta} = \frac{688}{147} = 4.68 \text{ v}$$

$$V_3 = \frac{\Delta_2}{\Delta} = \frac{600}{147} = 4.08 \text{ v}$$

$$V_4 = \frac{\Delta_3}{\Delta} = \frac{488}{147} = 3.319 \text{ v}$$





(Prob. 3.)

Write equations 2\*, 3\* & 4 in Matrix Form:

$$\begin{array}{l} 2* \\ 3* \\ 4 \end{array} \begin{bmatrix} 1 & -2 & 0 \\ 0 & 11 & -5 \\ 1 & 2 & -5 \end{bmatrix} \begin{bmatrix} V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} -20 \\ 20 \\ 6 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 1 & -2 & 0 \\ 0 & 11 & -5 \\ 1 & 2 & -5 \end{vmatrix} = -35$$

$$\Delta_1 = \begin{vmatrix} -20 & -2 & 0 \\ 20 & 11 & -5 \\ 6 & 2 & -5 \end{vmatrix} = 760$$

$$\Delta_2 = \begin{vmatrix} 1 & -20 & 0 \\ 0 & 20 & -5 \\ 1 & 6 & -5 \end{vmatrix} = 30$$

$$\Delta_3 = \begin{vmatrix} 1 & -2 & -20 \\ 0 & 11 & 20 \\ 1 & 2 & 6 \end{vmatrix} = 206$$

$$V_2 = \frac{\Delta_1}{\Delta} = \frac{760}{-35} = -21.7 \text{ v}$$

$$V_3 = \frac{\Delta_2}{\Delta} = \frac{30}{-35} = -0.857 \text{ v}$$

$$V_4 = \frac{\Delta_3}{\Delta} = \frac{206}{-35} = -5.88 \text{ v}$$

Find the current supplied by the VCCS:

$$P = V_x I = V_o \left(-\frac{3}{2} V_2\right)$$

$$V_o = V_1 - V_3 = 10 - (-0.857) = 10.857 \text{ v}$$

$$V_x = V_4 - V_3 = -5.88 - (-0.857) = -5.03 \text{ v}$$

$$P = (10.857) \left(-\frac{3}{2} \times -5.03\right) = 81.91 \text{ W}$$

### Problem 3)

@ node 1:  $V_1 = 10 \text{ V}$  (eq. 1)

@ node 2:  $V_2 = -2V_0$   
 $V_0 = V_1 - V_3$  }  $\Rightarrow V_2 = -2(V_1 - V_3) \rightarrow -2V_1 - V_2 + 2V_3 = 0$  (eq. 2)

KCL + Ohm @ node 3:

$$\left. \begin{aligned} -\frac{3}{2}V_1 + \frac{V_3 - V_1}{1\Omega} + \frac{V_3 - V_4}{1\Omega} + \frac{V_3}{0.5\Omega} = 0 \\ V_1 = V_4 - V_3 \end{aligned} \right\} \Rightarrow -V_1 + V_3\left(\frac{3}{2} + 1 + 1 + 2\right) - V_4\left(\frac{3}{2} + 1\right) = 0$$

$$\Rightarrow -V_1 + \frac{11}{2}V_3 - \frac{5}{2}V_4 = 0 \xrightarrow{\times 2} \underline{-2V_1 + 11V_3 - 5V_4 = 0} \text{ (eq. 3)}$$

KCL + Ohm @ node 4:

$$\frac{V_4 - V_3}{1\Omega} + \frac{V_4}{1\Omega} + \frac{V_4 - V_2}{2\Omega} + 3\text{A} = 0$$

$$-\frac{V_2}{2\Omega} - \frac{V_3}{1\Omega} + V_4\left(\frac{1}{1\Omega} + \frac{1}{1\Omega} + \frac{1}{2\Omega}\right) = -3\text{A} \Rightarrow -\frac{V_2}{2} - V_3 + \frac{5}{2}V_4 = -3$$


$$\xrightarrow{\times (-2)} \underline{V_2 + 2V_3 - 5V_4 = 6} \text{ (eq. 4)}$$

Replace equation 1 ( $V_1 = 10\text{V}$ ) in eq. 3 and eq. 2:

eq. 2:  $-2 \times 10 - V_2 + 2V_3 = 0 \rightarrow V_2 - 2V_3 = -20$  (eq. 2\*)

eq. 3:  $-2 \times 10 + 11V_3 - 5V_4 = 0 \rightarrow 11V_3 - 5V_4 = 20$  (eq. 3\*)

Problem 4: Write the node-voltage equations and put them in matrix form.

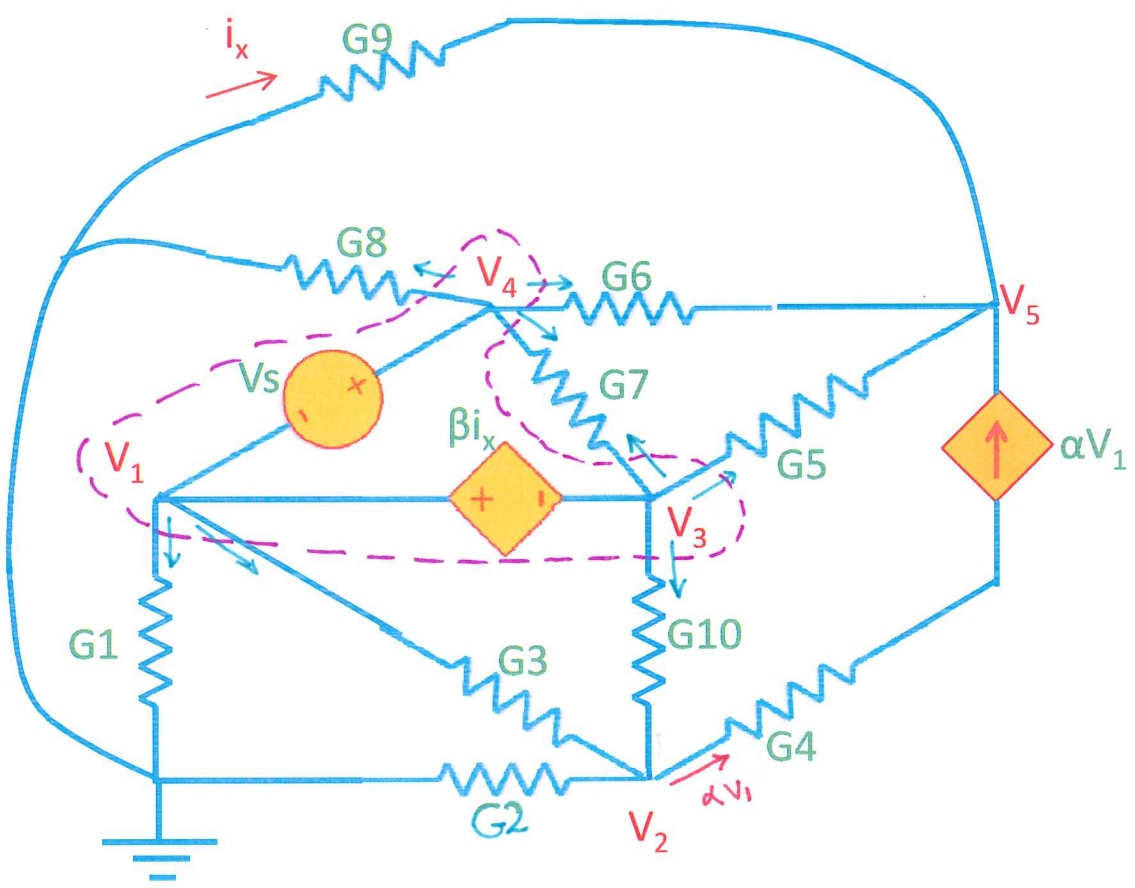

Problem 4) 5 unknowns  $\Rightarrow$  need 5 equations

KCL + Ohm @ node 2:

$$G_2 V_2 + G_3 (V_2 - V_1) + G_{10} (V_2 - V_3) + \alpha V_1 = 0$$

$$(\alpha - G_3) V_1 + (G_2 + G_3 + G_{10}) V_2 - G_{10} V_3 = 0 \quad (\text{eq. 1})$$

KCL + Ohm @ node 5:

$$G_9 V_5 + G_6 (V_5 - V_4) + G_5 (V_5 - V_3) - \alpha V_1 = 0$$

$$-\alpha V_1 - G_5 V_3 - G_6 V_4 + (G_9 + G_6 + G_5) V_5 = 0 \quad (\text{eq. 2})$$

KCL + Ohm @ supernode :

$$\underbrace{G_1 V_1 + G_3 (V_1 - V_2)}_{\text{node 1}} + \underbrace{G_{10} (V_3 - V_2) + G_5 (V_3 - V_5) + G_7 (V_3 - V_4) + G_7 (V_4 - V_3)}_{\text{node 3}} + \underbrace{G_6 (V_4 - V_5) + G_8 V_4}_{\text{node 4}} = 0$$

These two terms cancel out  $\rightarrow G_7$  could have been part of the supernode.

$$(G_1 + G_3) V_1 + V_2 (-G_3 - G_{10}) + V_3 (G_{10} + G_5) + V_4 (G_6 + G_8) + V_5 (-G_5 - G_6) = 0 \quad (\text{eq. 3})$$

We still need 2 more equations  $\Rightarrow$  write 2 KVLs at the supernode:

$$V_4 - V_1 = V_s \quad (\text{eq. 4})$$


$$\left. \begin{array}{l} V_1 - V_3 = \beta i_x \\ i_x = -G_9 V_5 \end{array} \right\} \Rightarrow V_1 - V_3 = -G_9 \beta V_5 \Rightarrow V_1 - V_3 + G_9 \beta V_5 = 0 \quad (\text{eq. 5})$$

(Prob. 4)

Now write the equations in matrix form:

$$\begin{bmatrix} \alpha - G_3 & G_2 + G_3 + G_{10} & -G_{10} & 0 & 0 \\ -\alpha & 0 & -G_5 & -G_6 & G_7 + G_6 + G_5 \\ G_1 + G_3 & -G_3 - G_{10} & G_{10} + G_5 & G_6 + G_8 & -G_5 - G_6 \\ 1 & 0 & -1 & 0 & \beta G_7 \\ -1 & 0 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ v_5 \end{bmatrix}$$

Problem 5: Solve for mesh currents.

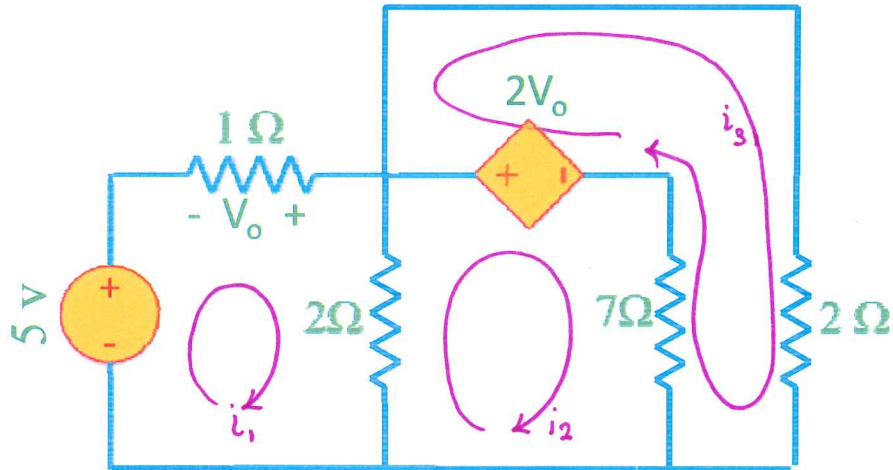

### Problem 5)

$$\text{KVL @ mesh 1: } -5 + (1\Omega)(i_1) + (2\Omega)(i_1 - i_2) = 0$$

$$i_1(1+2) - 2i_2 = 5$$

$$\underline{3i_1 - 2i_2 = 5 \quad (\text{eq.1})}$$

$$\left. \begin{array}{l} \text{KVL @ mesh 2: } 2(i_2 - i_1) + 2V_0 + 7(i_2 - i_3) \\ V_0 = (1\Omega)(-i_1) = -i_1 \end{array} \right\} \Rightarrow \underline{4i_1 + 9i_2 - 7i_3 = 0 \quad (\text{eq.2})}$$

$$\left. \begin{array}{l} \text{KVL @ mesh 3: } -2V_0 + 2i_3 + 7(i_3 - i_2) = 0 \\ V_0 = -i_1 \end{array} \right\} \Rightarrow \underline{2i_1 - 7i_2 + 9i_3 = 0 \quad (\text{eq.3})}$$

$$\begin{array}{l} \text{eq.1} \\ \text{eq.2} \\ \text{eq.3} \end{array} \begin{bmatrix} 3 & -2 & 0 \\ -4 & 9 & -7 \\ 2 & -7 & 9 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = 52$$

$$\Delta_1 = 160$$

$$\Delta_2 = 110$$

$$\Delta_3 = 50$$



$$i_1 = \frac{\Delta_1}{\Delta} = \frac{160}{52} = 3.077 \text{ A}$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{110}{52} = 2.12 \text{ A}$$

$$i_3 = \frac{\Delta_3}{\Delta} = \frac{50}{52} = 0.96 \text{ A}$$

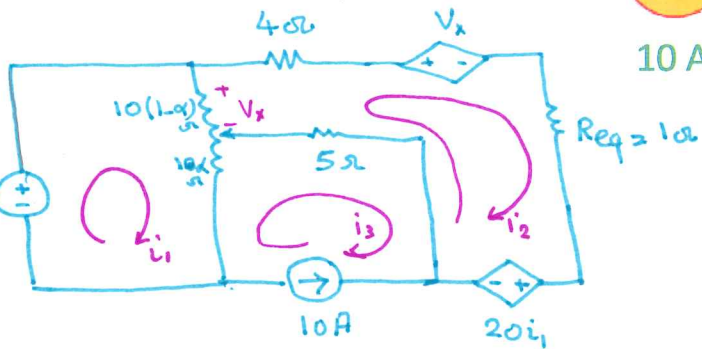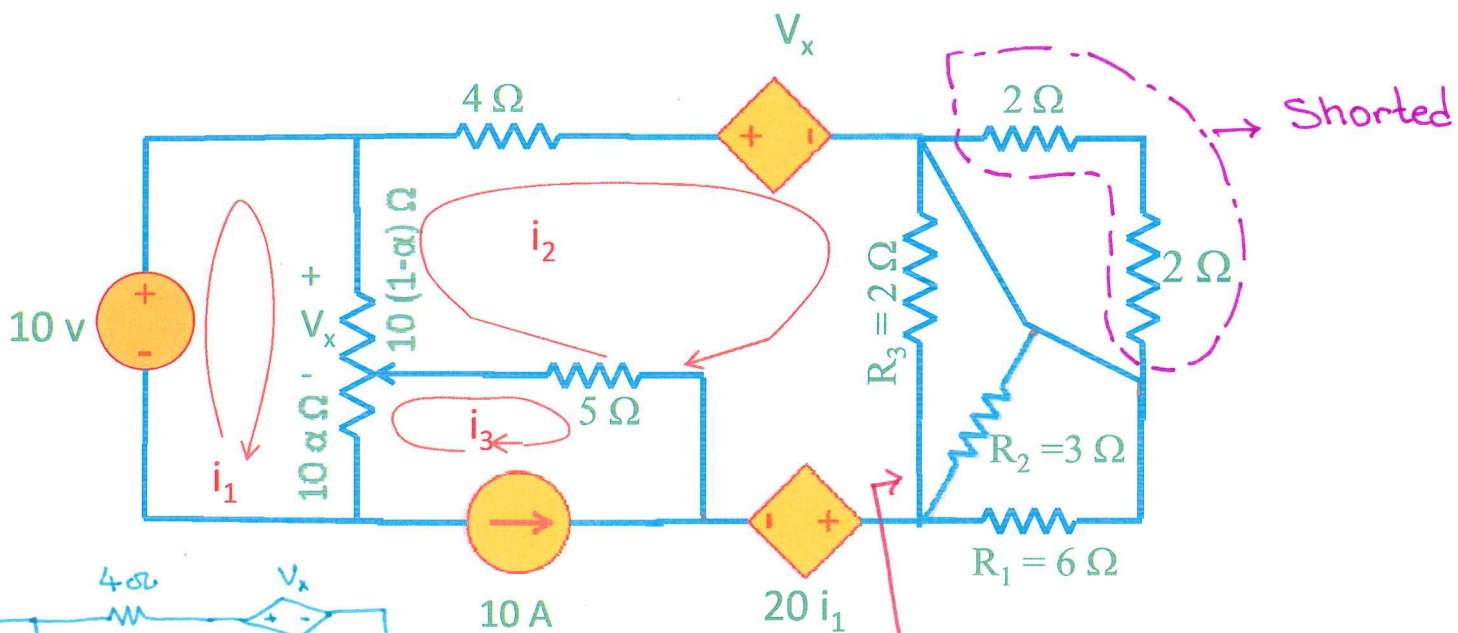Problem 6:

- Obtain mesh currents  $i_1$  through  $i_3$  (in terms of  $\alpha$ ).
- Find the total power dissipated in  $R_1$ ,  $R_2$  and  $R_3$  ( $P_1 + P_2 + P_3$  in terms of  $\alpha$ ).



$$\begin{aligned}
 R_{eq} &= R_1 \parallel R_2 \parallel R_3 \\
 &= 6\Omega \parallel 3\Omega \parallel 2\Omega \\
 &= \frac{6 \times 3}{6+3} \Omega \parallel 2\Omega \\
 &= 2\Omega \parallel 2\Omega = 1\Omega
 \end{aligned}$$



## Problem 6)

KVL @ mesh 1:

$$-10 + 10(1-\alpha)(i_1 - i_2) + 10\alpha(i_1 - i_3) = 0$$

$$10i_1 - 10(1-\alpha)i_2 - 10\alpha i_3 = 10 \xrightarrow{\div 10} \underline{i_1 + (\alpha-1)i_2 - \alpha i_3 = 1} \quad (\text{eq. 1})$$

KVL @ mesh 2:

$$-\cancel{V_x} + 4i_2 + \cancel{V_x} + \overset{10\alpha}{R_{eq}} i_2 + 20i_1 + 5(i_2 - i_3) = 0$$

$$20i_1 + (4+1+5)i_2 - 5i_3 = 0$$

$$20i_1 + 10i_2 - 5i_3 = 0 \xrightarrow{\div 5} \underline{4i_1 + 2i_2 - i_3 = 0} \quad (\text{eq. 2})$$

@ mesh 3:  $i_3 = -10A$

replace  $i_3$  by  $(-10)$  in eq. 1 & eq. 2:

$$\text{eq. 1} \rightarrow i_1 + (\alpha-1)i_2 - 10\alpha = 1 \Rightarrow i_1 + (\alpha-1)i_2 = 1 + 10\alpha \quad (\text{eq. 1*})$$

$$\text{eq. 2} \rightarrow 4i_1 + 2i_2 - 10 = 0 \xrightarrow{\div 2} 2i_1 + i_2 = 5 \quad (\text{eq. 2*})$$

$$\begin{cases} i_1 + (\alpha-1)i_2 = 1 + 10\alpha \\ 2i_1 + i_2 = 5 \end{cases} \xrightarrow{\times 2} \begin{cases} 2i_1 + 2(\alpha-1)i_2 = 2 + 20\alpha \\ 2i_1 + i_2 = 5 \end{cases}$$

---

$$2(\alpha-1)i_2 - i_2 = 2 + 20\alpha - 5$$

$$(2\alpha-3)i_2 = 20\alpha-3 \Rightarrow i_2 = \frac{20\alpha-3}{2\alpha-3} \quad A$$

(Prob. b)

$$2i_1 + i_2 = 5 \rightarrow i_1 = \frac{5 - i_2}{2}$$

$$i_1 = \frac{1}{2} \left( 5 - \frac{20\alpha - 3}{2\alpha - 3} \right) = \frac{1}{2} \left( \frac{10\alpha - 15 - 20\alpha + 3}{2\alpha - 3} \right)$$

$$i_1 = \frac{-10\alpha - 12}{2(2\alpha - 3)} = \frac{-(5\alpha + 6)}{(2\alpha - 3)} \text{ A}$$


- Find the total power absorbed in  $R_1, R_2$  &  $R_3$  :

$$P_{R_1} + P_{R_2} + P_{R_3} = P_{\text{Req}}$$

$$P = V \cdot I = (IR) \cdot I = I^2 R$$

$$P_{\text{Req}} = i_2^2 \cdot R_{\text{eq}} = \left( \frac{-(5\alpha + 6)}{2\alpha - 3} \right)^2 \cdot 1\Omega = \left( \frac{5\alpha + 6}{2\alpha - 3} \right)^2 \text{ W}$$

Problem 7: Solve for mesh currents.

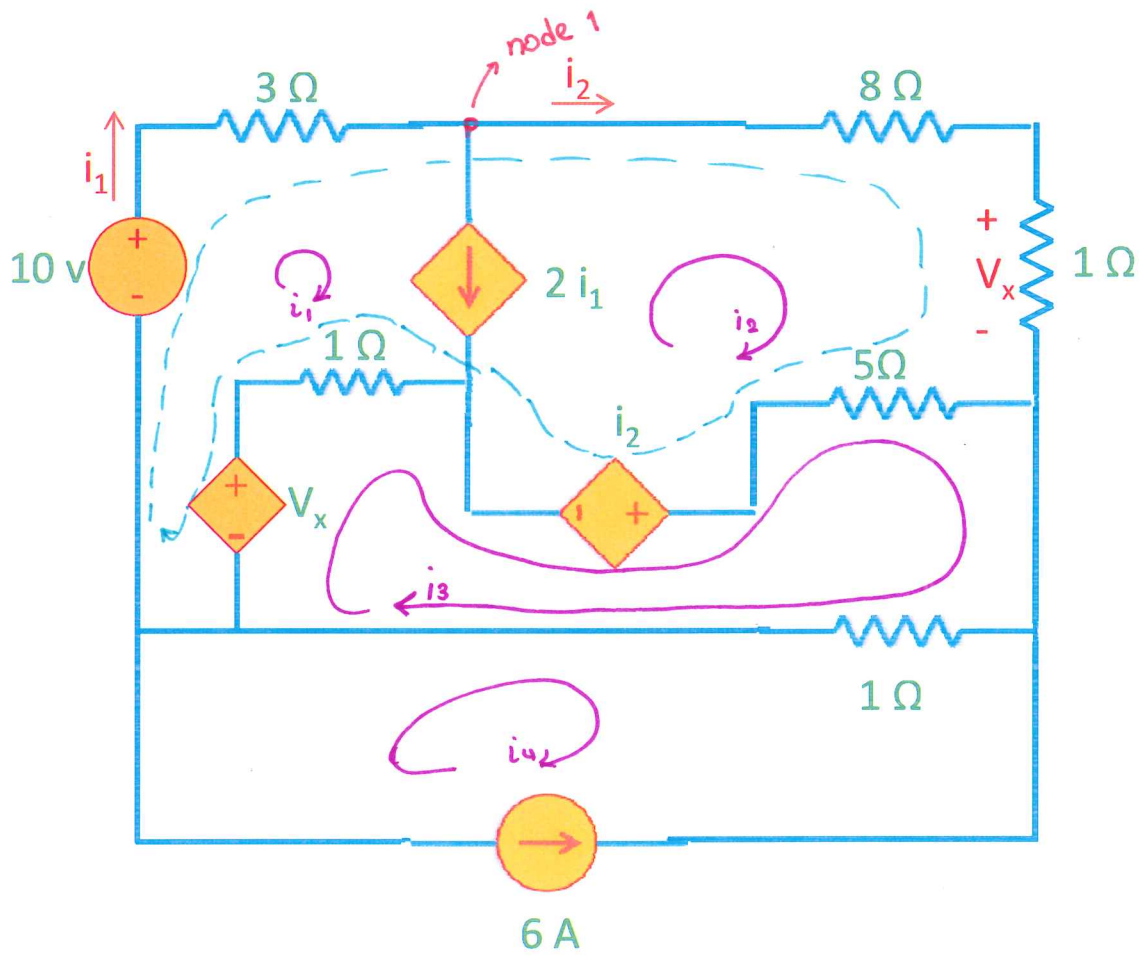

## Problem 7)

@ mesh 4:  $i_4 = -6A$  (eq. 1)

KVL @ mesh 3:  $-V_x + 100(i_3 - i_1) - i_2 + 500(i_3 - i_2) + 100(i_3 - i_4) = 0$

$$V_x = 100 \times i_2 = i_2$$

$$-i_2 + i_3 - i_1 - i_2 + 5i_3 - 5i_2 + i_3 - i_4 = 0$$

$$-i_1 - i_2(1+1+5) + i_3(1+5+1) - i_4 = 0$$

$$-i_1 - 7i_2 + 7i_3 - i_4 = 0 \quad (\text{eq. 2})$$

KVL @ supermesh:

$$-10 + 3i_1 + 8i_2 + 1i_2 + 5(i_2 - i_3) + i_2 + 1(i_1 - i_3) + V_x = 0$$

$$V_x = 100 \times i_2 = i_2$$

$$i_1(3+1) + i_2(8+1+5+1+1) + i_3(-5-1) = 10$$

$$4i_1 + 16i_2 - 6i_3 = 10 \xrightarrow{\div 2} 2i_1 + 8i_2 - 3i_3 = 5 \quad (\text{eq. 3})$$

KCL @ supermesh (node 1):  $i_1 - i_2 = 2i_1 \Rightarrow i_1 + i_2 = 0$  (eq. 4)

Replace equation 1 in equation 2:

$$-i_1 - 7i_2 + 7i_3 - (-6) = 0 \rightarrow -i_1 - 7i_2 + 7i_3 = -6 \quad (\text{eq. 2*})$$

Solving with Cramer's rule:

$$\begin{array}{l} \text{eq 4} \\ \text{eq 3} \\ \text{eq 2*} \end{array} \begin{bmatrix} 1 & 1 & 0 \\ 2 & 8 & -3 \\ -1 & -7 & 7 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 5 \\ -6 \end{bmatrix}$$

$$\Delta = 24$$

$$\Delta_1 = -17$$

$$\Delta_2 = 17$$


$$\Delta_3 = -6$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{-17}{24} = -0.7 \text{ A}$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{17}{24} = 0.7 \text{ A}$$

$$i_3 = \frac{\Delta_3}{\Delta} = \frac{-6}{24} = -0.25 \text{ A}$$

Problem 8: Solve for mesh currents.

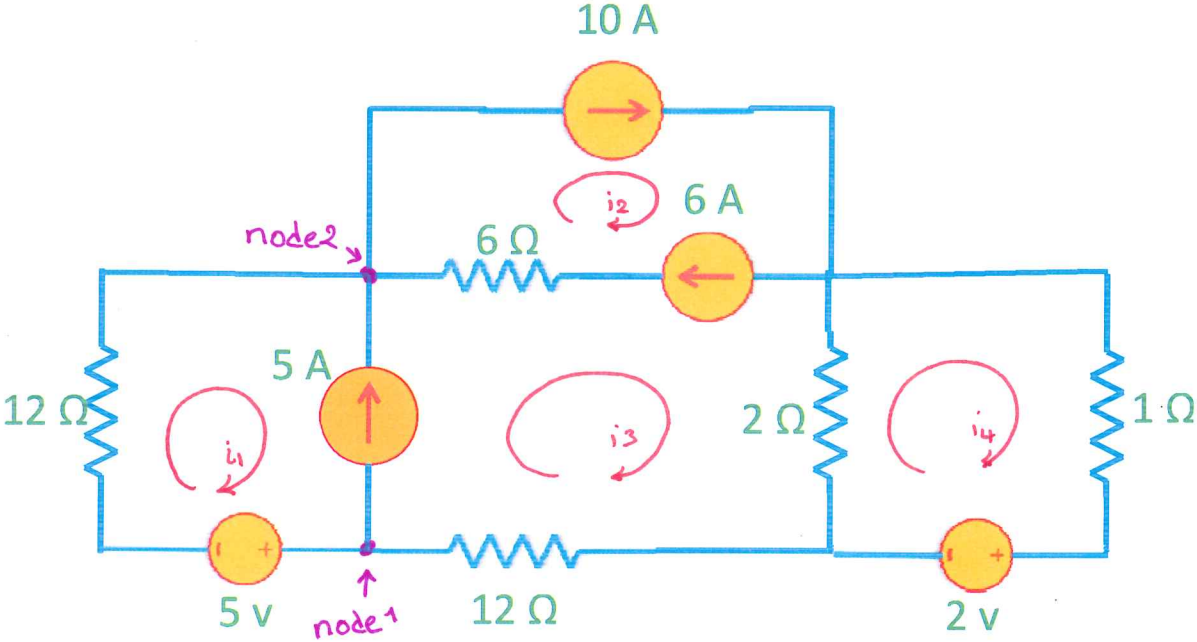

## Problem 8)

$$\text{@ mesh 2: } \underline{i_2 = 10A} \quad (\text{eq. 1})$$

$$\begin{aligned} \text{KVL @ mesh 4: } \quad 2(i_4 - i_3) + i_4 + 2 &= 0 \\ 3i_4 - 2i_3 &= -2 \quad (\text{eq. 2}) \end{aligned}$$

There are 4 unknowns;  $i_1, i_2, i_3$  and  $i_4$  so we need 4 eq.s. We have got two equations so far, and must write two more. We can not write any KVL equations for mesh 1, mesh 2, mesh 3 or any of the supermeshes, so we have to write two KCL equations.

$$\text{KCL @ node 1: } i_3 - i_1 = 5A \quad (\text{eq. 3})$$

$$\text{KCL @ node 2: } i_1 + 6A + 5A = 10A \Rightarrow \underline{i_1 = -1A} \quad (\text{eq. 4})$$


$$\text{Replace } i_1 \text{ by } -1A \text{ in eq. 3} \Rightarrow i_3 - (-1A) = 5A \Rightarrow \underline{i_3 = 4A}$$

$$\text{Replace } i_3 \text{ by } 4A \text{ in eq. 2} \Rightarrow 3i_4 - 2(4A) = -2$$

$$i_4 = \frac{8-2}{3} = \frac{6}{3}$$

$$\underline{i_4 = 2A}$$

Problem 9: Use your circuit analysis skills to find the ratio of the power absorbed by  $R_L$  to the power supplied by  $V_s$ .

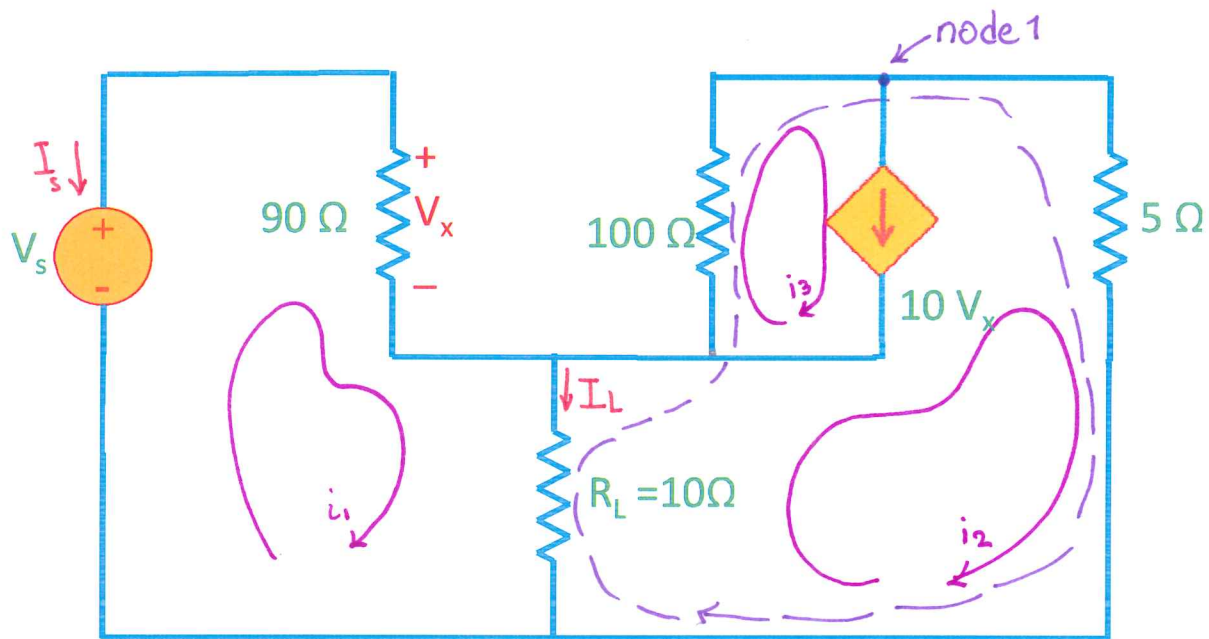



Problem 9)

To find the power ratio, we must first find  $I_s$  and  $I_L$ . You can use nodal or mesh analysis. Here mesh analysis has been used:

$$\begin{aligned} \text{KVL @ mesh 1: } -V_s + 90i_1 + 10(i_1 - i_2) &= 0 \\ 100i_1 - 10i_2 &= V_s \quad (\text{eq. 1}) \end{aligned}$$

$$\begin{aligned} \text{KVL @ supermesh: } 10(i_2 - i_1) + 100i_3 + 5i_2 &= 0 \\ -10i_1 + 15i_2 + 100i_3 &= 0 \\ \xrightarrow{\div 5} -2i_1 + 3i_2 + 20i_3 &= 0 \quad (\text{eq. 2}) \end{aligned}$$

$$\begin{aligned} \text{KCL @ supermesh, node 1: } i_3 - i_2 = 10 V_x \\ V_x = 90i_1 \end{aligned} \quad \Rightarrow \quad i_3 - i_2 = 10(90i_1)$$

$$\Rightarrow 900i_1 + i_2 - i_3 = 0 \quad (\text{eq. 3})$$

Solving the equations:

$$\begin{bmatrix} 100 & -10 & 0 \\ -2 & 3 & 20 \\ 900 & 1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \\ 0 \end{bmatrix}$$

(Prob. 9)

$$\Delta = -182280$$

$$\Delta_1 = \begin{vmatrix} V_s & -10 & 0 \\ 0 & 3 & 20 \\ 0 & 1 & -1 \end{vmatrix} = V_s \begin{vmatrix} 3 & 20 \\ 1 & -1 \end{vmatrix} + 10 \begin{vmatrix} 0 & 20 \\ 0 & -1 \end{vmatrix} + 0 \begin{vmatrix} 0 & 3 \\ 0 & 1 \end{vmatrix}$$
$$= V_s(-3-20) = -23V_s$$

$$\Delta_2 = \begin{vmatrix} 100 & V_s & 0 \\ -2 & 0 & 20 \\ 900 & 0 & -1 \end{vmatrix} = 100 \begin{vmatrix} 0 & 20 \\ 0 & -1 \end{vmatrix} - V_s \begin{vmatrix} -2 & 20 \\ 900 & -1 \end{vmatrix} + 0$$
$$= -V_s(2 - 20 \times 900) = 17998V_s$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{-23V_s}{-182280} = 1.26 \times 10^{-4} V_s \Rightarrow P_{\text{source}} = V_s \cdot I_s = V_s \cdot (-i_1) = V_s \cdot (-1.26 \times 10^{-4} V_s)$$
$$\Rightarrow P_{\text{source}} = -1.26 \times 10^{-4} V_s^2 \text{ [W]}$$
$$= -0.126 V_s^2 \text{ [mW]}$$


$$i_2 = \frac{\Delta_2}{\Delta} = \frac{17998V_s}{-182280} \approx -0.1 V_s \therefore P_{R_L} = (I_L)^2 \cdot R_L = (i_1 - i_2)^2 \cdot R_L$$

$$P_{R_L} = \underbrace{(1.26 \times 10^{-4} + 0.1)^2}_{\approx 0.1} V_s^2 \cdot 10 \Omega \approx 0.1 V_s^2 \text{ [W]}$$

$$P_{R_L} \approx 100 V_s^2 \text{ [mW]}$$

$$\Rightarrow \frac{P_{R_L}}{P_{\text{source}}} = \frac{100 V_s^2}{-0.126 V_s^2} = -793.6$$

Problem 10: Find  $i_0$ .

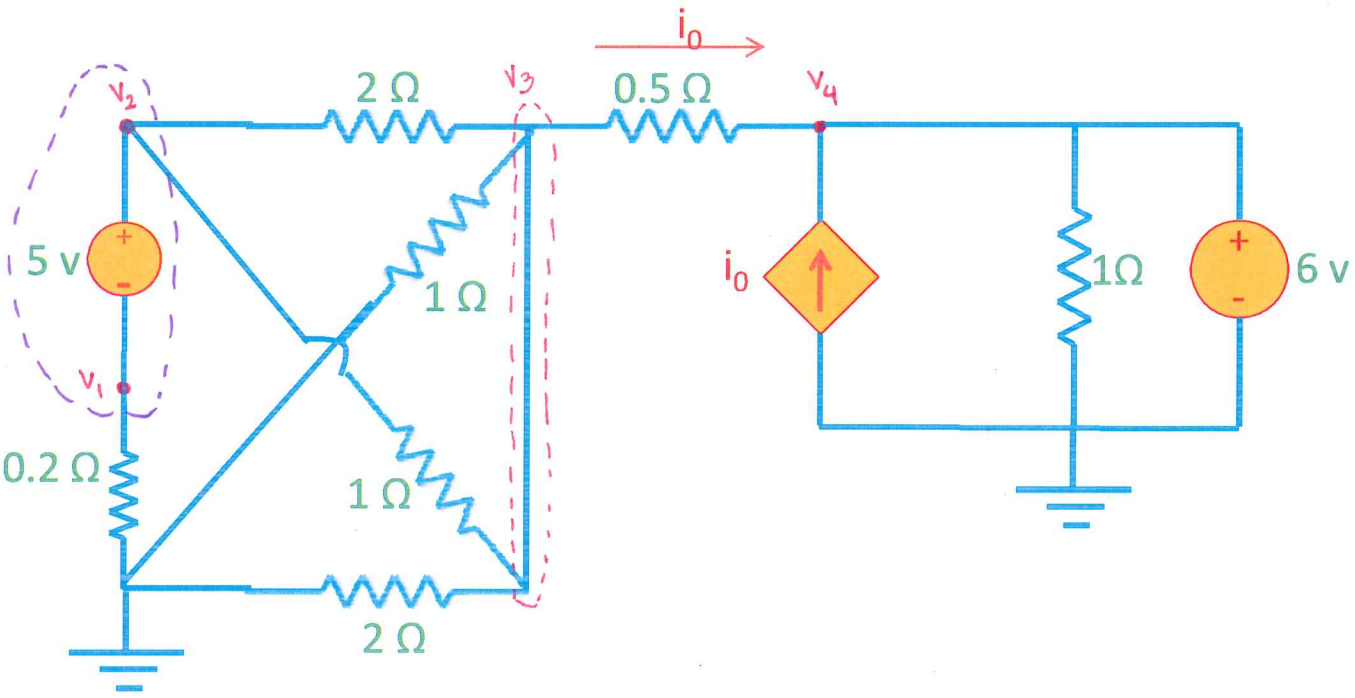

## Problem 10)

Because of the way this circuit looks, it is easier to do nodal analysis.  
To find  $i_o$ , first we have to obtain  $V_3$  and  $V_4$

KCL + Ohm @ node 3:

$$\frac{V_3 - V_2}{2.5\Omega} + \frac{V_3}{1\Omega} + \frac{V_3 - V_2}{1\Omega} + \frac{V_3}{2\Omega} + \frac{V_3 - V_4}{0.5\Omega} = 0$$

$$-V_2 \left( \frac{1}{2} + 1 \right) + V_3 \left( \frac{1}{2} + 1 + 1 + \frac{1}{2} + 2 \right) - 2V_4 = 0$$

$$-\frac{3}{2}V_2 + 5V_3 - 2V_4 = 0 \quad \xrightarrow{\times 2} \quad -3V_2 + 10V_3 - 4V_4 = 0 \quad (\text{eq. 1})$$

KCL + Ohm @ the supernode:

$$\frac{V_1}{0.2\Omega} + \frac{V_2 - V_3}{2\Omega} + \frac{V_2 - V_3}{1\Omega} = 0$$

$$5V_1 + \frac{3}{2}V_2 - \frac{3}{2}V_3 = 0 \quad \xrightarrow{\times 2} \quad 10V_1 + 3V_2 - 3V_3 = 0 \quad (\text{eq. 2})$$

@ node 4:  $V_4 = 6V$  (eq. 3)

KVL @ supernode:  $V_2 - V_1 = 5V \rightarrow -V_1 + V_2 = 5V$  (eq. 4)


Replace  $V_4$  from eq. 2 in eq. 1:

$$-3V_2 + 10V_3 = 24 \quad (\text{eq. 1*})$$

$$\begin{bmatrix} 0 & -3 & 10 \\ 10 & 3 & -3 \\ -1 & 1 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 24 \\ 0 \\ 5 \end{bmatrix} \rightarrow V_3 = \frac{\Delta_3}{\Delta} = \frac{\begin{vmatrix} 0 & -3 & 24 \\ 10 & 3 & 0 \\ -1 & 1 & 5 \end{vmatrix}}{\begin{vmatrix} 0 & -3 & 10 \\ 10 & 3 & -3 \\ -1 & 1 & 0 \end{vmatrix}} = \frac{462}{121} = 3.8V$$

$$i_o = \frac{V_3 - V_4}{0.5\Omega} = \frac{3.8V - 6V}{0.5\Omega} = -4.36A$$

Problem 11: Find node voltages and currents.

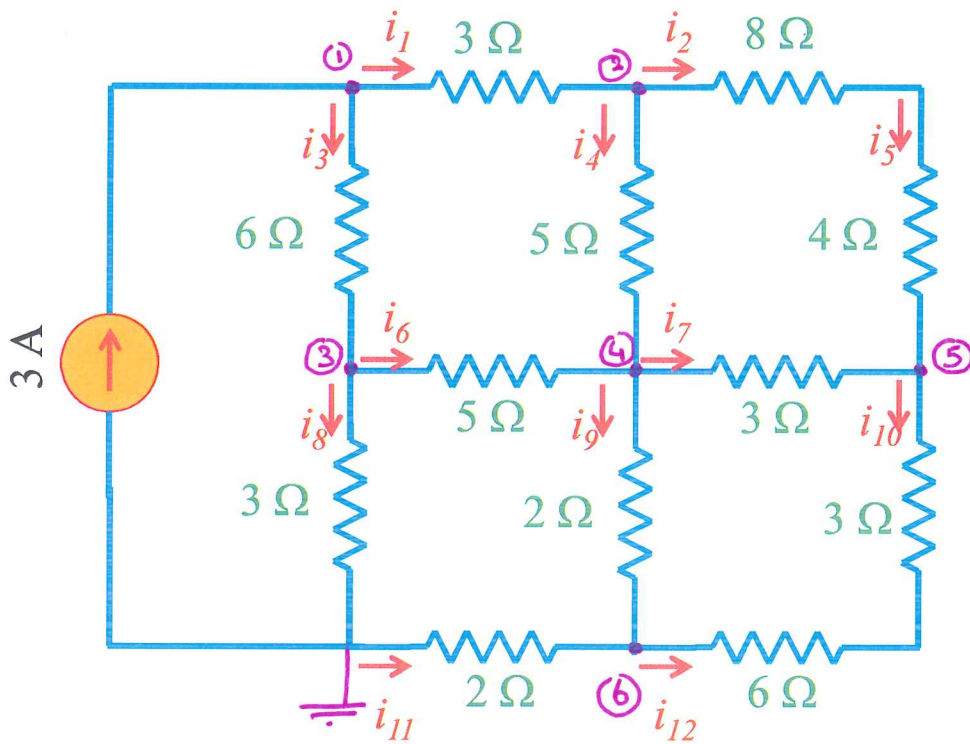

Problem 11)

KCL + Ohm's law @

$$\text{node 1: } \frac{V_1 - V_3}{6} + \frac{V_1 - V_2}{3} = 3 \text{ A} \Rightarrow V_1 \left( \frac{1}{6} + \frac{1}{3} \right) - \frac{V_3}{6} - \frac{V_2}{3} = 3$$

$$\xrightarrow{\times 6} 3V_1 - V_3 - 2V_2 = 18 \quad (\text{eq. 1})$$

$$\text{node 2: } \frac{V_2 - V_1}{3\Omega} + \frac{V_2 - V_4}{5\Omega} + \frac{V_2 - V_5}{8\Omega + 4\Omega} = 0 \Rightarrow \frac{-V_1}{3} + V_2 \left( \frac{1}{3} + \frac{1}{5} + \frac{1}{12} \right) - \frac{V_4}{5} - \frac{V_5}{12} = 0$$

$$\xrightarrow{\times 60} -20V_1 + 37V_2 - 12V_4 - 5V_5 = 0 \quad (\text{eq. 2})$$

$$\text{node 3: } \frac{V_3 - V_1}{6\Omega} + \frac{V_3 - V_4}{5\Omega} + \frac{V_3}{3\Omega} = 0 \Rightarrow \frac{-V_1}{6} + V_3 \left( \frac{1}{6} + \frac{1}{5} + \frac{1}{3} \right) - \frac{V_4}{5} = 0$$

$$\xrightarrow{\times 30} -5V_1 + 21V_3 - 6V_4 = 0 \quad (\text{eq. 3})$$

$$\text{node 4: } \frac{V_4 - V_3}{5\Omega} + \frac{V_4 - V_2}{5\Omega} + \frac{V_4 - V_5}{3\Omega} + \frac{V_4 - V_6}{2\Omega} = 0$$

$$-\frac{V_2}{5} - \frac{V_3}{5} + V_4 \left( \frac{1}{5} + \frac{1}{5} + \frac{1}{3} + \frac{1}{2} \right) - \frac{V_5}{3} - \frac{V_6}{2} = 0$$

$$\xrightarrow{\times 30} -6V_2 - 6V_3 + V_4(6+6+10+15) - 10V_5 - 15V_6 = 0$$

$$-6V_2 - 6V_3 + 37V_4 - 10V_5 - 15V_6 = 0 \quad (\text{eq. 4})$$

$$\text{node 5: } \frac{V_5 - V_2}{8\Omega + 4\Omega} + \frac{V_5 - V_4}{3\Omega} + \frac{V_5 - V_6}{3\Omega + 6\Omega} = 0$$

$$-\frac{V_2}{12} - \frac{V_4}{3} + V_5 \left( \frac{1}{12} + \frac{1}{3} + \frac{1}{9} \right) - \frac{V_6}{9} = 0 \xrightarrow{\times 36} -3V_2 - 12V_4 + 19V_5 - 4V_6 = 0 \quad (\text{eq. 5})$$

$$\text{node 6: } \frac{V_6 - V_5}{6\Omega + 3\Omega} + \frac{V_6 - V_4}{2\Omega} + \frac{V_6}{2\Omega} = 0 \Rightarrow \frac{-V_4}{2} - \frac{V_5}{9} + V_6 \left( \frac{1}{9} + \frac{1}{2} + \frac{1}{2} \right) = 0$$

$$\xrightarrow{\times 18} -9V_4 - 2V_5 + 20V_6 = 0 \quad (\text{eq. 6})$$

(Prob. 11)

$$\begin{bmatrix} 3 & -2 & -1 & 0 & 0 & 0 \\ -20 & 37 & 0 & -12 & -5 & 0 \\ -5 & 0 & 21 & -6 & 0 & 0 \\ 0 & -6 & -6 & 37 & -10 & -15 \\ 0 & -3 & 0 & -12 & 19 & -4 \\ 0 & 0 & 0 & -9 & -2 & 20 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \end{bmatrix} = \begin{bmatrix} 18 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \end{bmatrix} = \begin{bmatrix} 14.33 \text{ v} \\ 10.08 \text{ v} \\ 4.83 \text{ v} \\ 4.98 \text{ v} \\ 5.32 \text{ v} \\ 2.77 \text{ v} \end{bmatrix}$$

$$i_1 = \frac{V_1 - V_2}{3\Omega} = \frac{14.33 - 10.08 \text{ v}}{3\Omega} = 1.416 \text{ A}$$

$$i_2 = \frac{V_2 - V_5}{8\Omega + 4\Omega} = \frac{(10.08 - 5.32) \text{ v}}{12\Omega} = 0.37 \text{ A}$$

$$i_3 = \frac{V_1 - V_3}{6\Omega} = \frac{(14.33 - 4.83) \text{ v}}{6\Omega} = 1.58 \text{ A}$$

$$i_4 = \frac{V_2 - V_4}{5\Omega} = \frac{(10.08 - 4.98) \text{ v}}{5\Omega} = 1.02 \text{ A}$$

$$i_5 = i_2 = 0.37 \text{ A}$$

$$i_6 = \frac{V_3 - V_4}{5\Omega} = \frac{(4.83 - 4.98) \text{ v}}{5\Omega} = -0.03 \text{ A}$$

$$i_7 = \frac{V_4 - V_5}{3\Omega} = \frac{(4.98 - 5.32) \text{ v}}{3\Omega} = -0.113 \text{ A}$$

$$i_8 = \frac{V_3}{3\Omega} = \frac{4.83 \text{ v}}{3\Omega} = 1.61 \text{ A}$$

$$i_9 = \frac{V_4 - V_6}{2\Omega} = \frac{(4.98 - 2.77) \text{ v}}{2\Omega} = 1.105 \text{ A}$$

$$i_{10} = \frac{V_5 - V_6}{3\Omega + 6\Omega} = \frac{(5.32 - 2.77) \text{ v}}{9\Omega} = 0.28 \text{ A}$$

$$i_{11} = \frac{-V_6}{2\Omega} = \frac{-2.77 \text{ v}}{2\Omega} = -1.385 \text{ A}$$

$$i_{12} = -i_{10} = -0.28 \text{ A}$$

To solve the 6 simultaneous equations, you can use the elimination method or Cramer's rule to solve it by hand, or use a calculator or a software like MATLAB.

Here the equations have been solved by MATLAB. To do so, first enter the 6x6 matrix for voltage coefficients- Let's call it matrix G- using the following command:

$G = [3 \ -2 \ -1 \ 0 \ 0 \ 0; -20 \ 37 \ 0 \ -12 \ -5 \ 0; -5 \ 0 \ 21 \ -6 \ 0 \ 0; 0 \ -6 \ -6 \ 37 \ -10 \ -15; 0 \ -3 \ 0 \ -12 \ 19 \ -4; 0 \ 0 \ 0 \ -9 \ -2 \ 20]$

Also enter the 6x1 matrix on the right (I), If we call the 6x1 matrix for voltages V, Then the simultaneous equations in matrix form is:  $GxV=I$

If both sides of the above equation are multiplied by the inverse of matrix G, i.e.  $G^{-1}$  we get  $G^{-1}xGxV=G^{-1}xI$ , or  $V=G^{-1}xI$

after you have defined G and I, use the following command to find V:

$V=(G^{-1})xI$