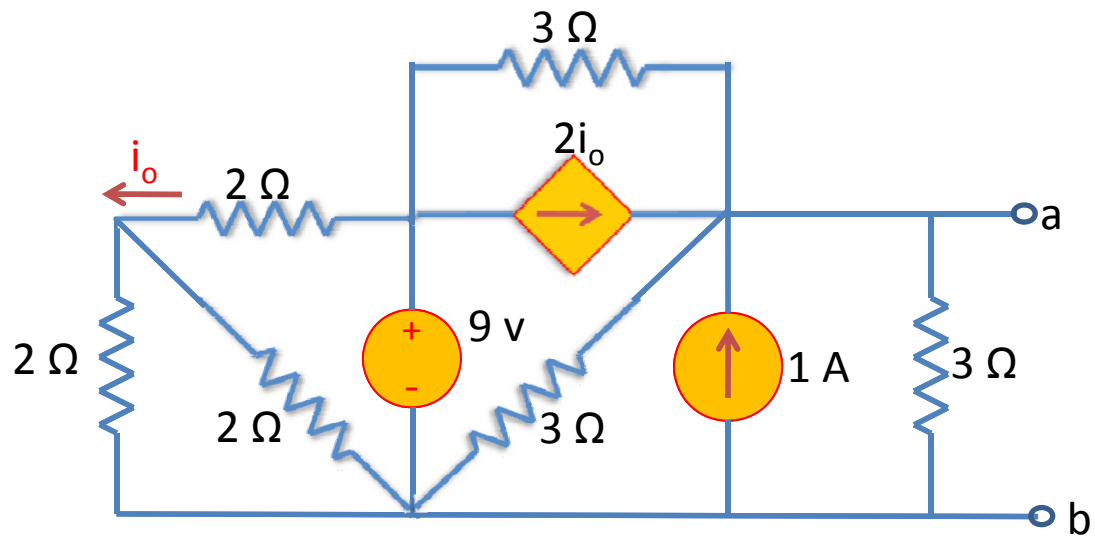


EECS 70A: Network Analysis


Homework #4

Due Friday, May 14, 2010.


Problem1) Obtain the Thevenin and Norton equivalent as seen from a-b terminals:




Problem2) Determine the relationship between V_o and I_o .

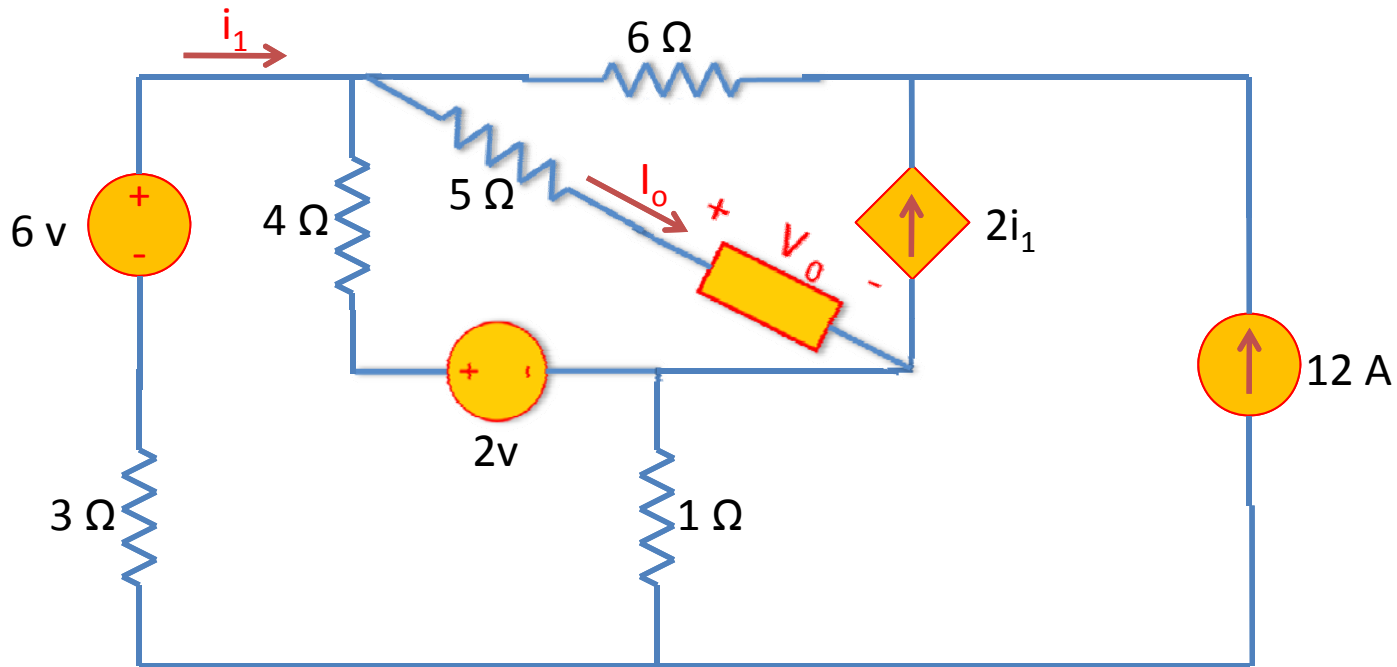


Problem3) Obtain the Norton equivalent.

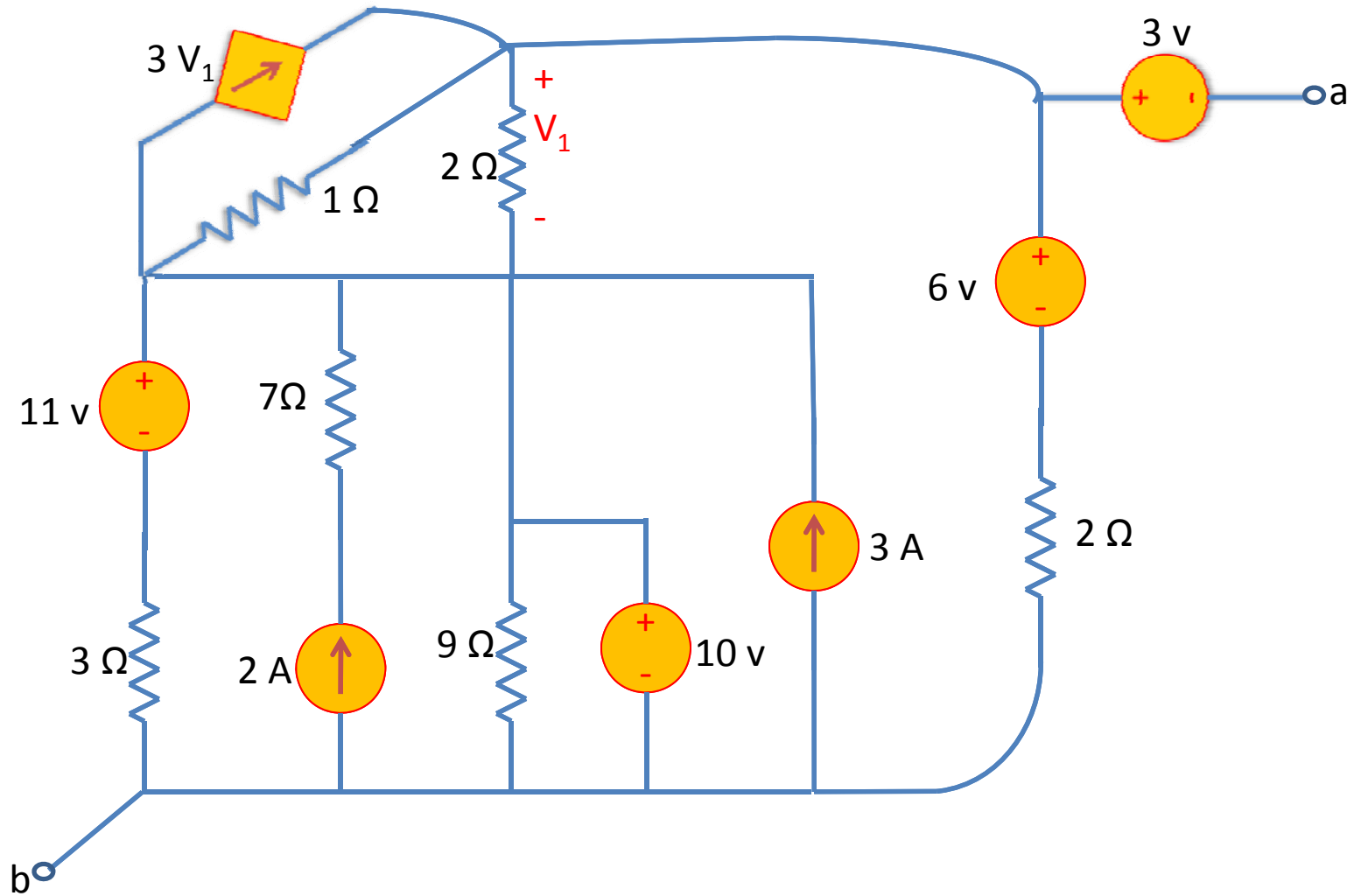


Problem4) Find the value for α , such that the power transferred to R_L is maximum.
 What is the value for the maximum power.

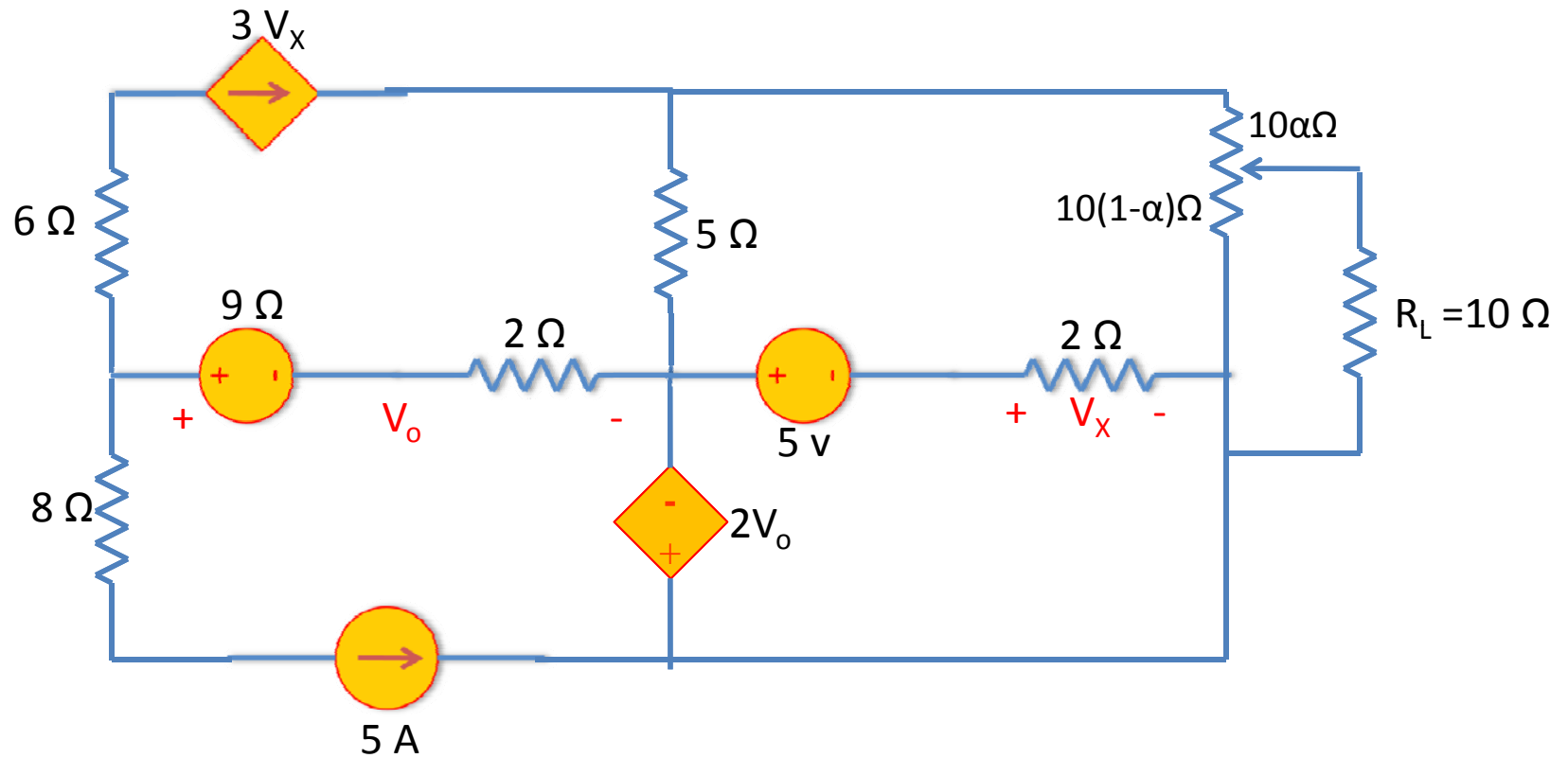


Problem 5) Find the maximum power transferred to R_L . [S]=[1/Ω] is the unit for conductance.

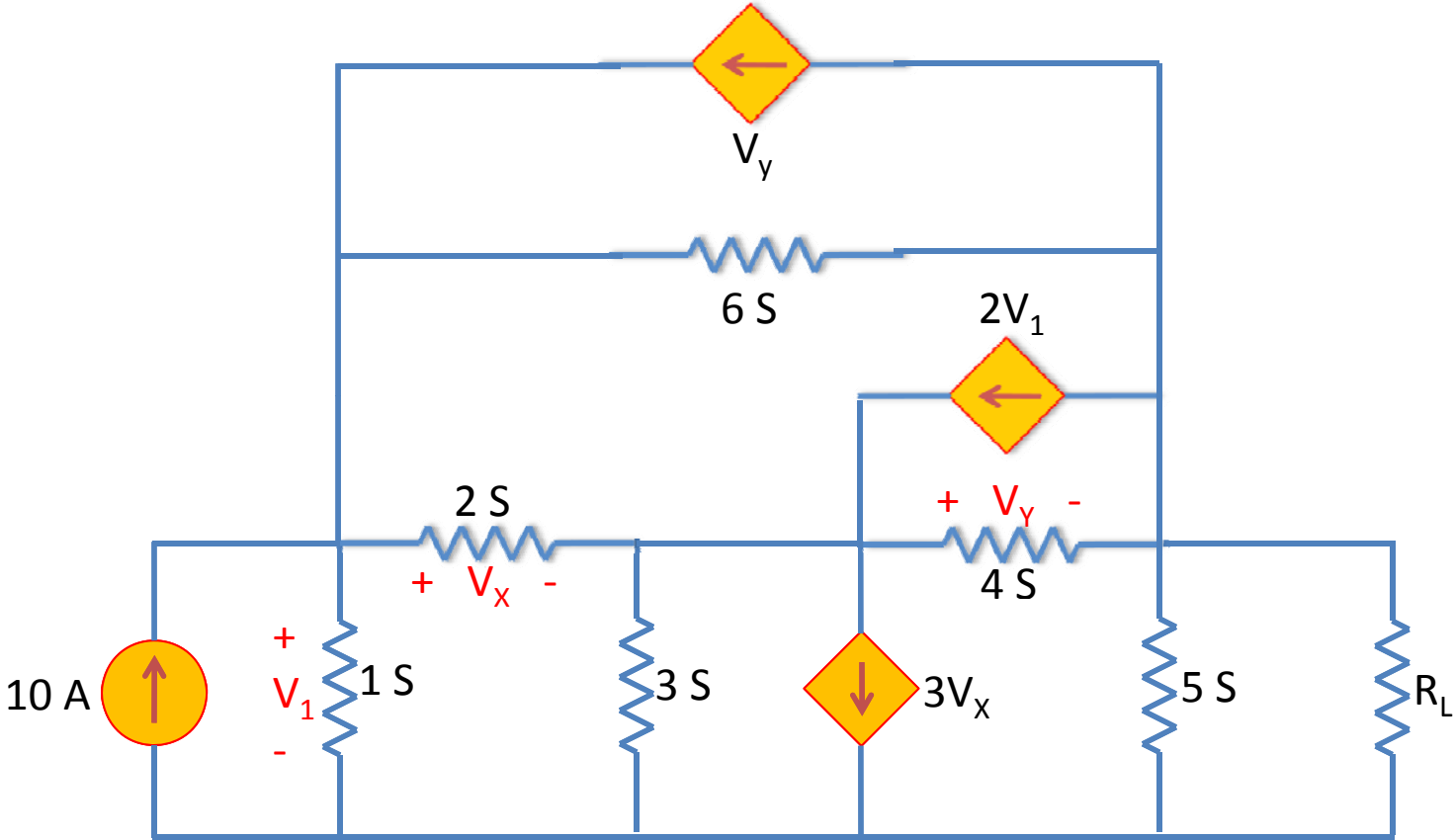


Problem6) Find the voltage across C_2 .

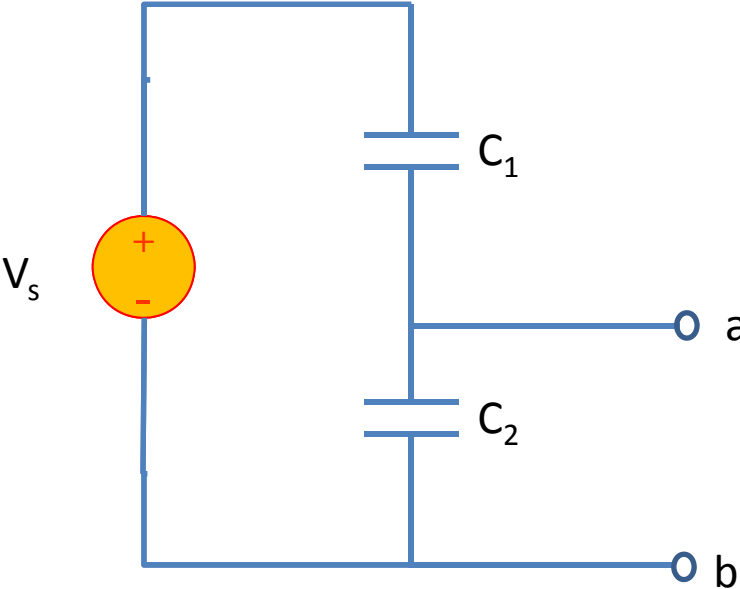

Problem 7) Find the equivalent capacitance. All capacitors have the value of 1mF.

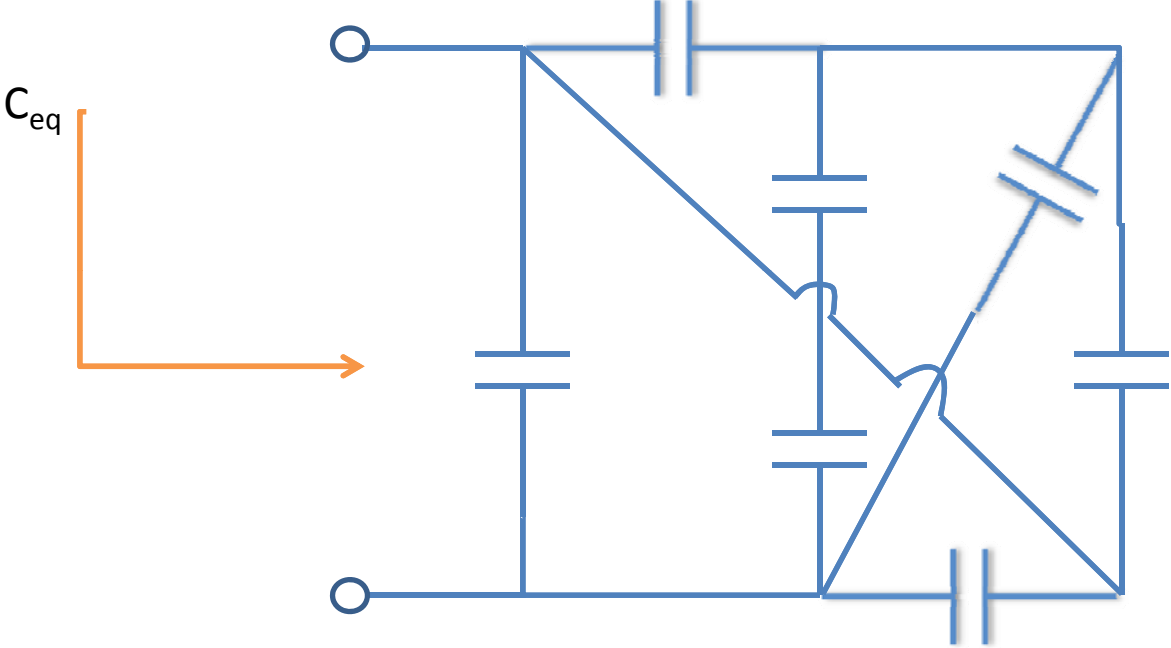


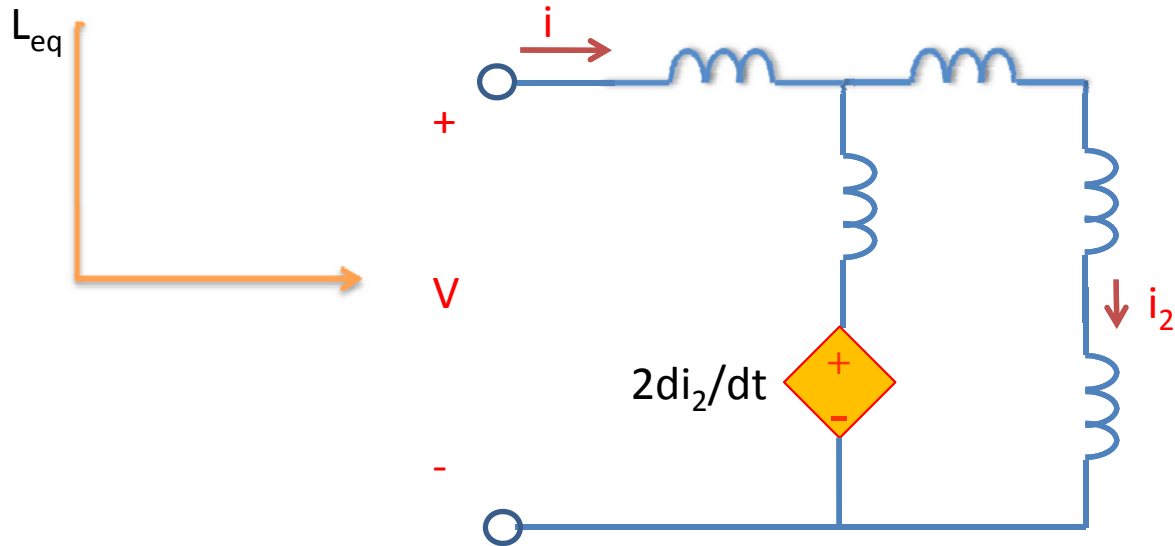Problem8) Find the equivalent inductance. All inductors are 1H.




Hint: $V=L_{eq} di/dt$


Problem 9) Switch opens at $t=0$, Find $V(t)$ for $t>0$.

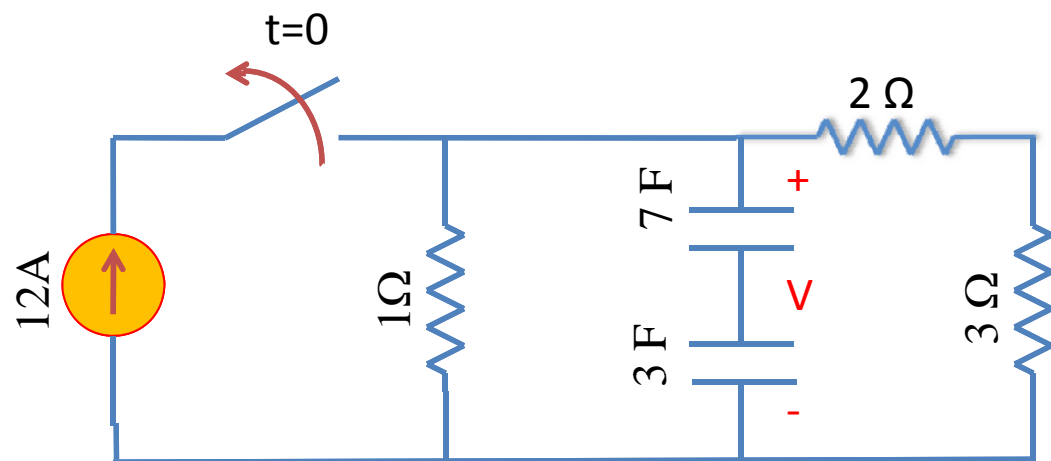

Problem 10) Switch opens at $t=0$. Find the inductor current.

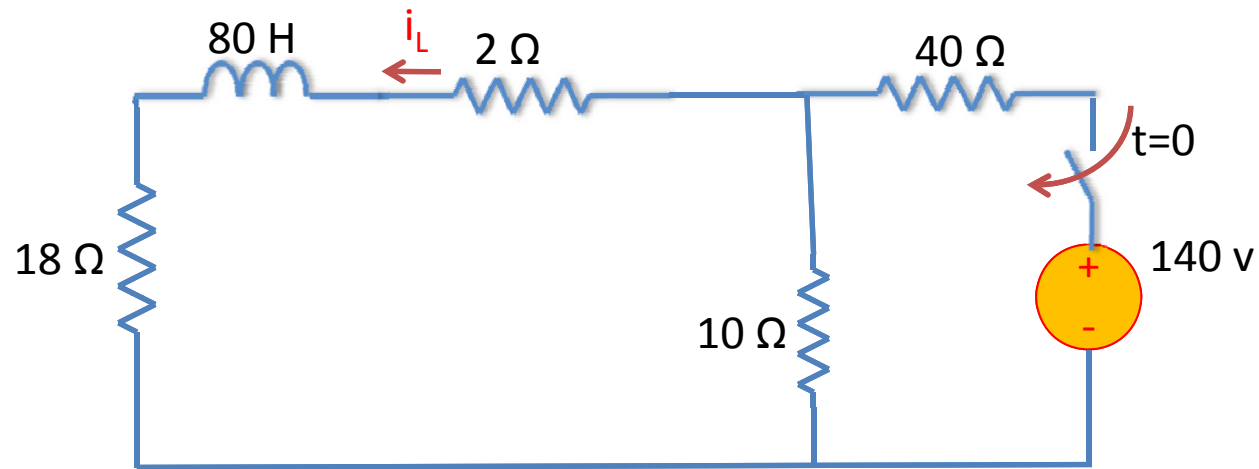

Problem 11) Find $V(t)$.

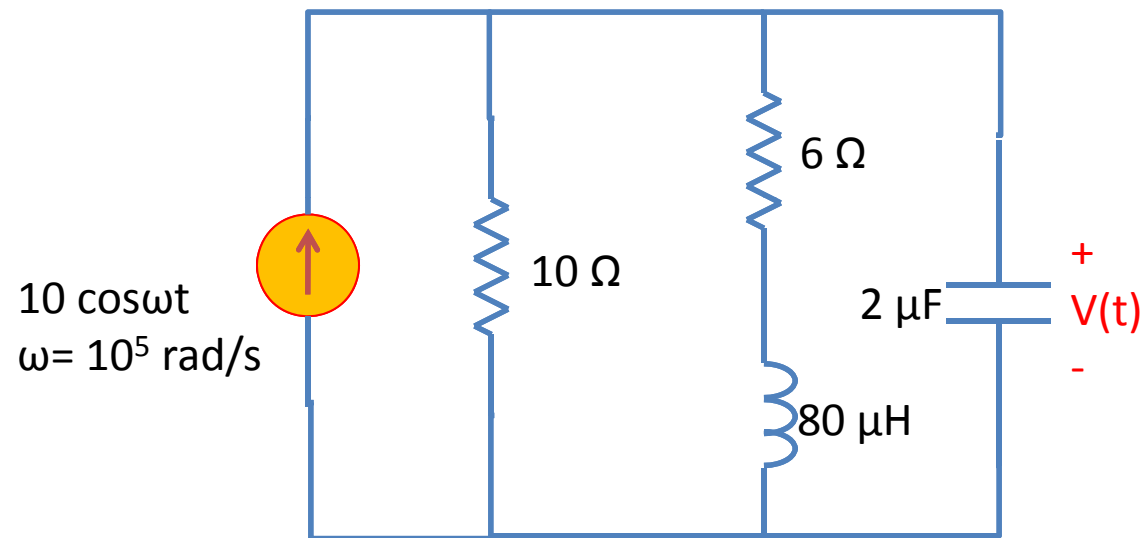

(Monster problem-Extra credit: Part 2): Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:

