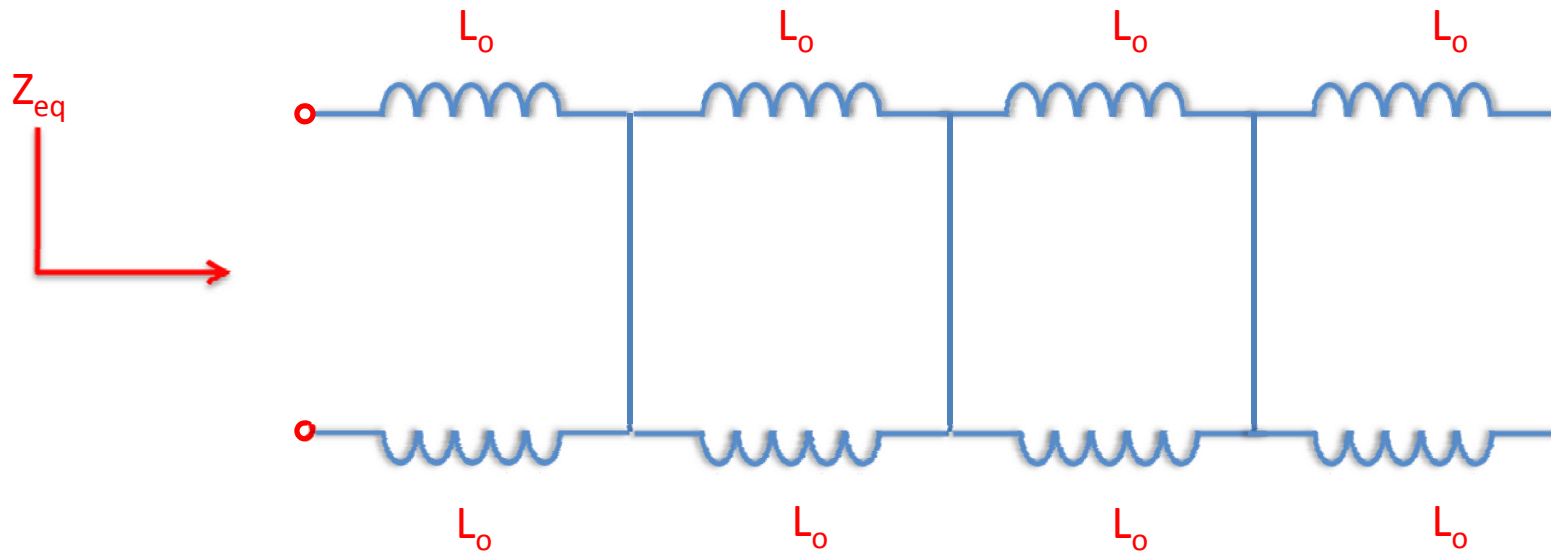


EECS 70A: Network Analysis


Homework #5

Due in discussion section,
Wednesday, May 19, 2010.


Problem1: Solve for Z_{eq} .



Problem2: Solve for Z_{eq} .

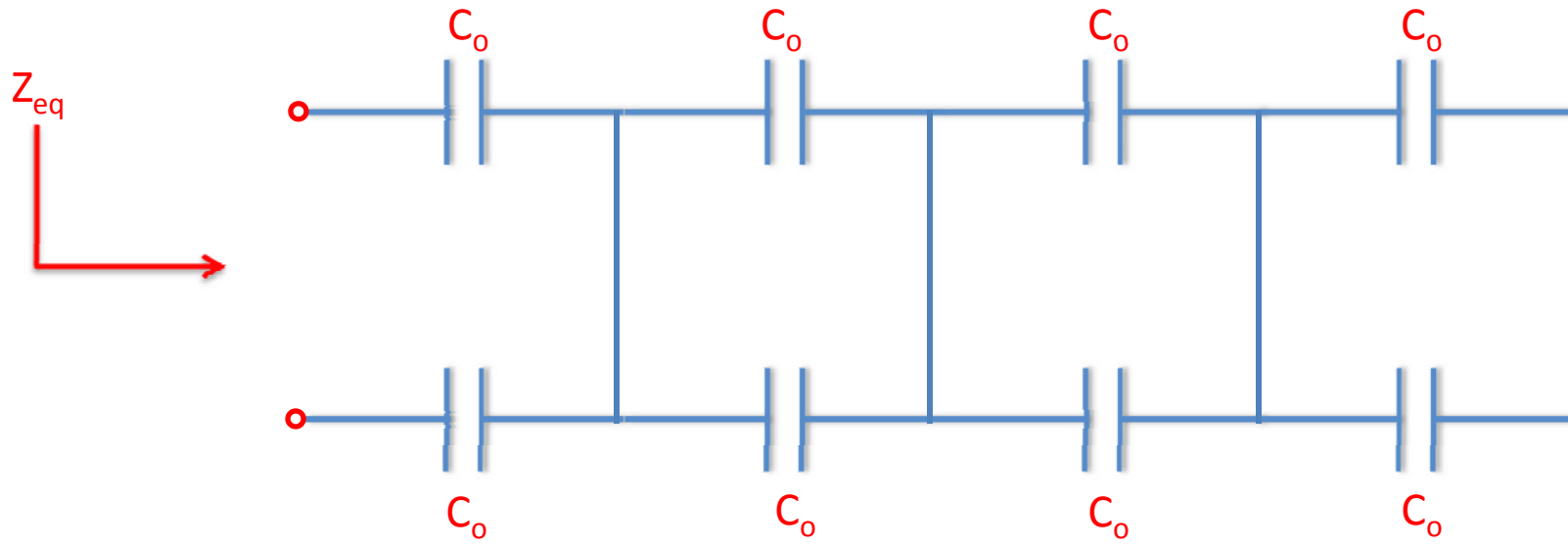

Problem3) Solve for Z_{eq} . All capacitors have same value C_o .

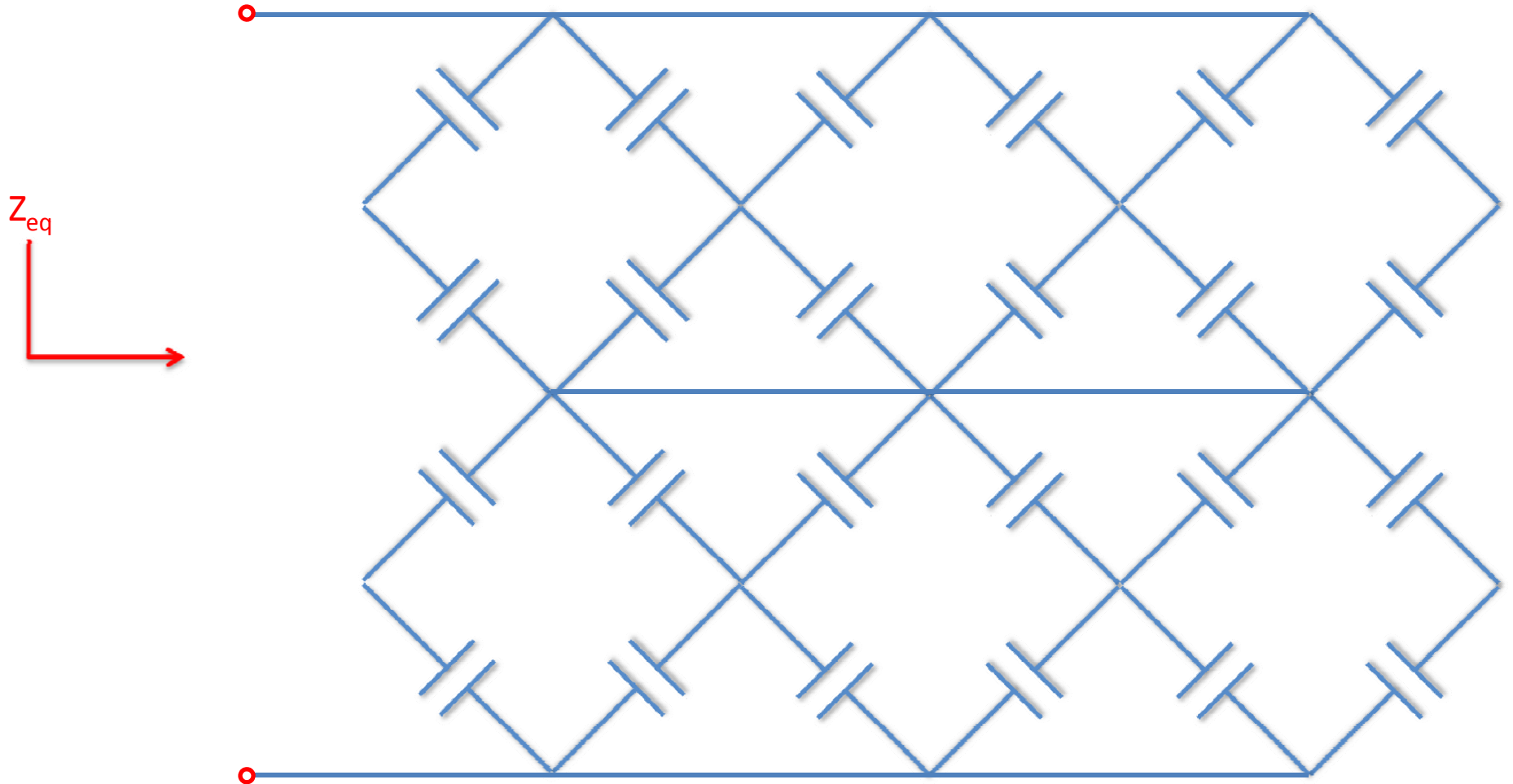

Problem4) Solve for Z_{eq} . All inductors have same value L_o .

