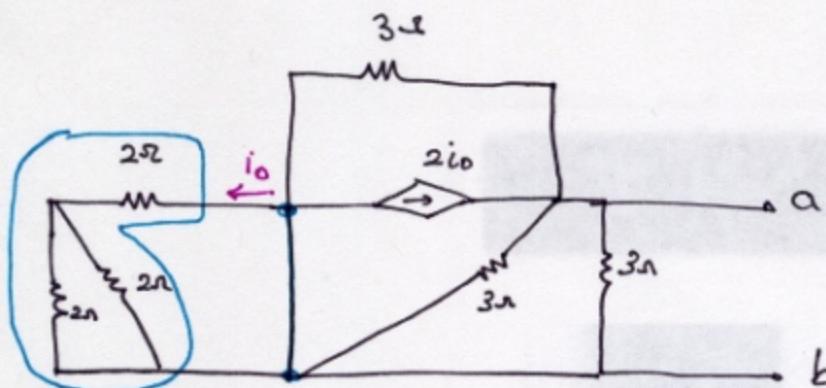


Problem 1)


(1. dobit)

isom neqas seft bno d-p nqo , nV bnič at.



To find  $R_{th}$ , turn off all independent sources:



Shorted  $\Rightarrow i_0 = 0$

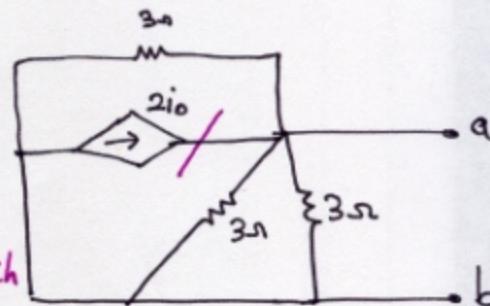

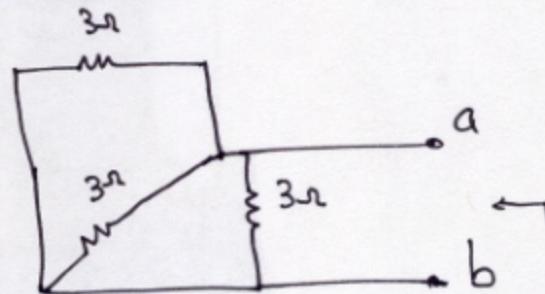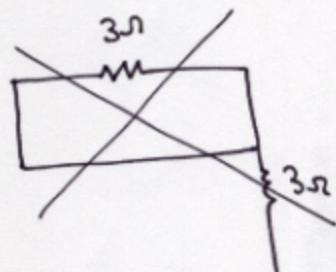$i_0 = 0 \Rightarrow 2i_0 = 0$   
⇒ no current  
in this branch  
⇒ open





$$R_{th} = 3\Omega \parallel 3\Omega \parallel 3\Omega$$

$$R_{th} = 1\Omega$$

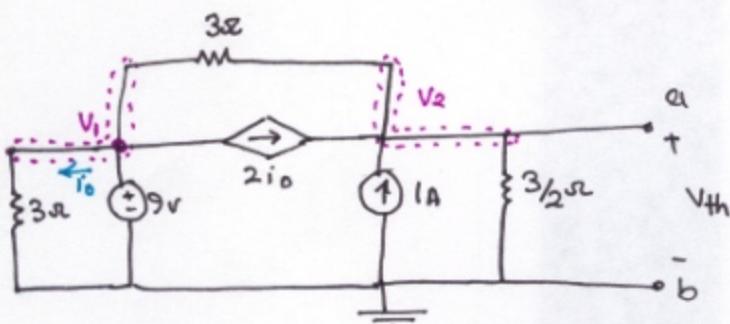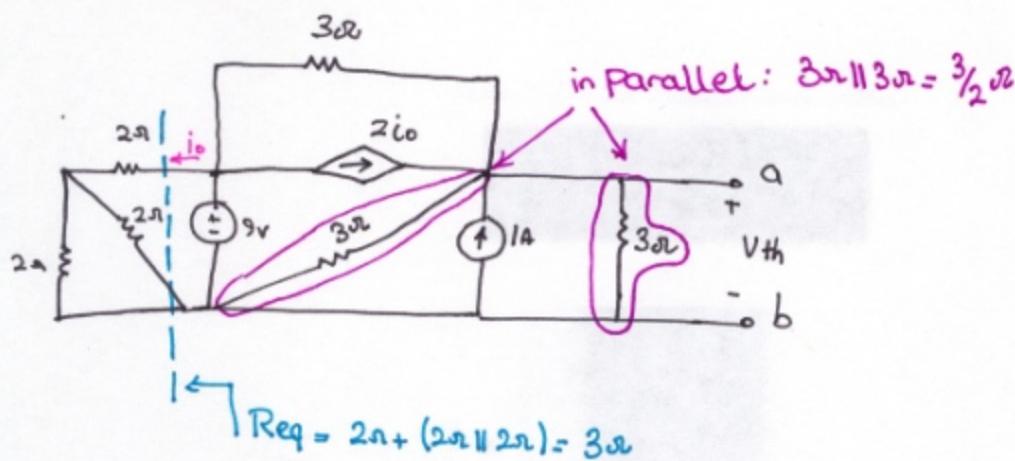(problem 1)

to find  $V_{th}$ , find the open-circuit voltage between terminals a-b.  
to make analysis easier, you can first simplify the circuit as much as possible.



nodal analysis:

$$V_{th} = V_{ab} = V_2$$

$$@ \text{node 1: } V_1 = 9_v \quad (\text{eq. 1})$$

$$@ \text{node 2: } \frac{V_2 - V_1}{3\Omega} + (-2i_o) + (-1A) + \frac{V_2 - 0}{\frac{3}{2}\Omega} = 0 \quad (\text{eq. 2})$$

$$\text{to find } i_o : i_o = \frac{V_1}{3\Omega} = \frac{9_v}{3\Omega} = 3A$$

Replace  $i_o$  and  $V_1$  in with (3A) and (9<sub>v</sub>) in equation 2:


$$\frac{V_2 - 9}{3} + (-2 \times 3) - 1 + \frac{V_2}{\frac{3}{2}} = 0$$

(Prob.1)

$$\frac{V_2}{3} - 3 - 6 - 1 + \frac{2V_2}{3} = 0 \Rightarrow V_2 = 10 \text{ V}$$

$$V_{th} = 10 \text{ V}$$


Therenin equivalent

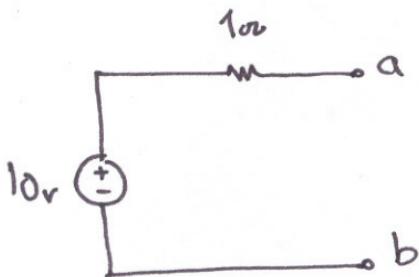


Norton equivalent :

$$R_n = R_{th} = 1\Omega$$

$$I_n = \frac{V_{th}}{R_{th}} = \frac{10 \text{ V}}{1\Omega} = 10 \text{ A}$$

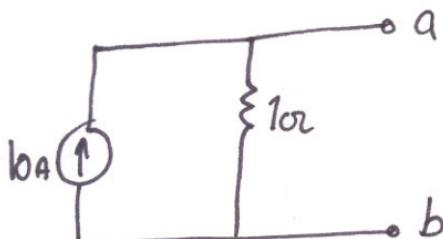

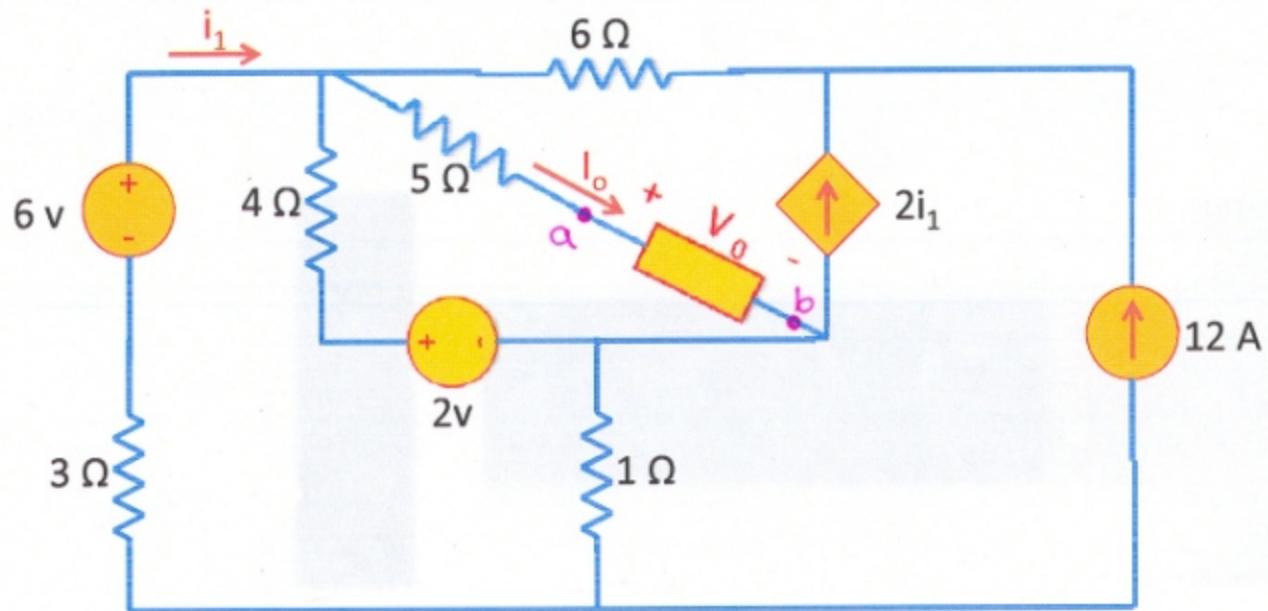
Problem2) Determine the relationship between  $V_o$  and  $I_o$ .


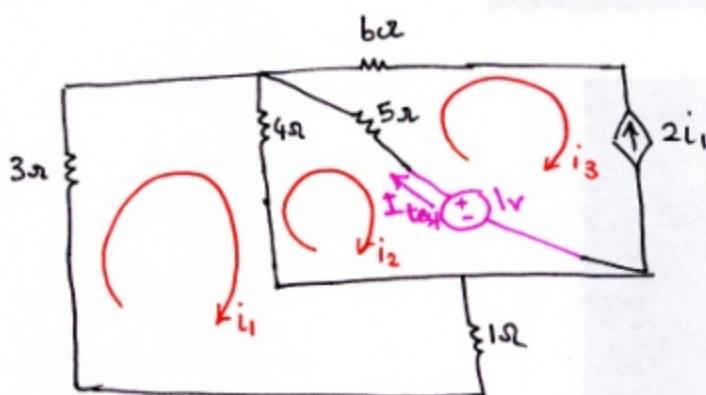
## Problem 2)

To find the relationship between  $V_o$  and  $I_o$ , first find the equivalent circuit seen by the unknown element; ie. the terminals a-b:

to find  $R_{th}$ , turn off the independent sources and apply a test source between a and b:



if we add a voltage source as the test source

$$R_{th} = \frac{V_{test}}{I_{test}} = \frac{1v}{\frac{1}{16}} = 16\Omega$$

mesh analysis:

$$\text{kvl @ mesh 1: } 3i_1 + 4(i_1 - i_2) + i_1 = 0 \\ 2i_1 - i_2 = 0 \quad (\text{eq. 1})$$

$$\text{kvl @ mesh 2: } 4(i_2 - i_1) + 5(i_2 - i_3) + 1 = 0 \\ -4i_1 + 9i_2 - 5i_3 = -1 \quad (\text{eq. 2})$$

$$\text{mesh 3: } i_3 = -2i_1 \quad (\text{eq. 3})$$


$$\left. \begin{array}{l} \text{eq. 2} \\ \text{eq. 3} \end{array} \right\} \Rightarrow -4i_1 + 9i_2 - 5(-2i_1) = -1 \\ 6i_1 + 9i_2 = -1 \quad \xrightarrow{\substack{\text{eq. 1} \rightarrow \\ 6i_1 + 9i_2 = -1 \\ 2i_1 - i_2 = 0}} \quad \Rightarrow \quad \begin{cases} i_2 = -\frac{1}{12} \text{ A} \\ i_1 = -\frac{1}{24} \text{ A} \\ i_3 = -2i_1 = \frac{1}{12} \text{ A} \end{cases}$$

$$I_{test} = i_3 - i_2 = \frac{1}{12} - \left(-\frac{1}{12}\right) = \frac{1}{6} \text{ A},$$

$$R_{th} = \frac{1v}{I_{test}} = \frac{1}{\frac{1}{6}} = 6\Omega$$

(Prob. 2)

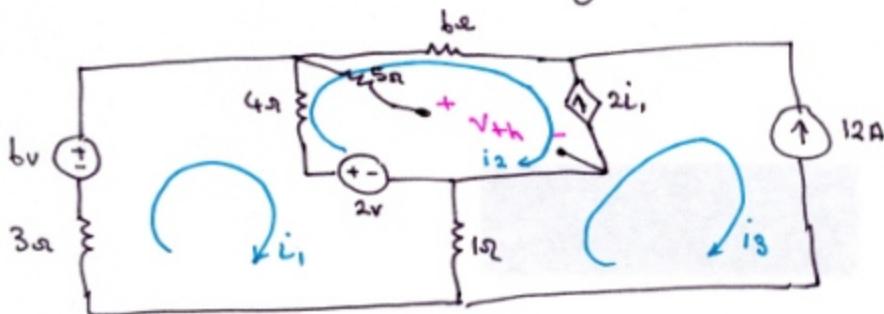$V_{th}$  : go back to the original circuit and find the open circuit voltage between a and b:



note that for the  $5\Omega$  resistor, since terminals a-b are open, there is no current flowing in the  $5\Omega$  resistor  $\Rightarrow$  can be neglected.  
and has no voltage drop

mesh analysis:

$$\text{mesh 3: } i_3 = -12 \text{ A} \quad (\text{eq. 1})$$

$$\text{KVL @ mesh 1: } 3i_1 - 6 + 4(i_1 - i_2) + 2 + 1(i_1 - i_3) = 0$$

$$8i_1 - 4i_2 - i_3 = 4$$

$$8i_1 - 4i_2 - (-12) = 4$$



$$8i_1 - 4i_2 = -8$$

$$2i_1 - i_2 = -2 \quad (\text{eq. 2})$$

$$@ \text{mesh 2: } i_2 = -2i_1 \quad (\text{eq. 3})$$


$$\text{replace } i_2 = -2i_1 \text{ (eq. 3)} \text{ in eq. 2: } 2i_1 - (-2i_1) = -2 \Rightarrow i_1 = -\frac{1}{2} \text{ A}$$

$$i_2 = -2i_1 = 1 \text{ A}$$

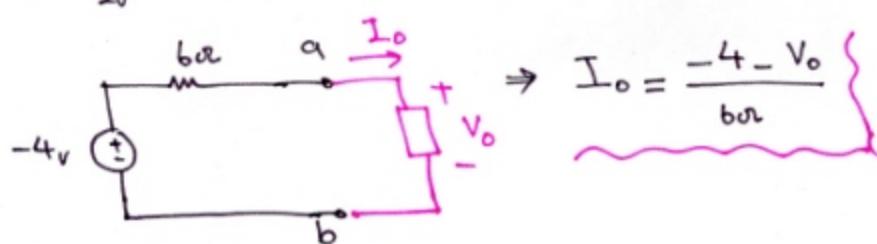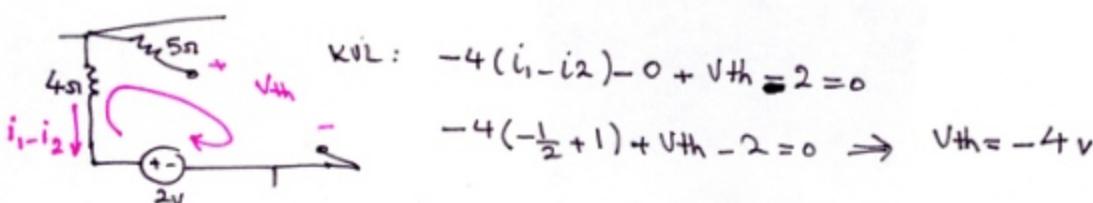

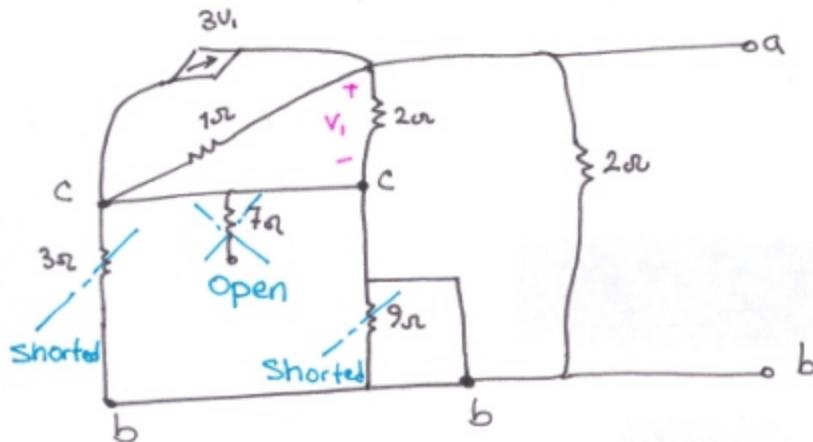
### Problem 3)

- $R_{th}$ : Turn off all independent sources, this is how the circuit looks:



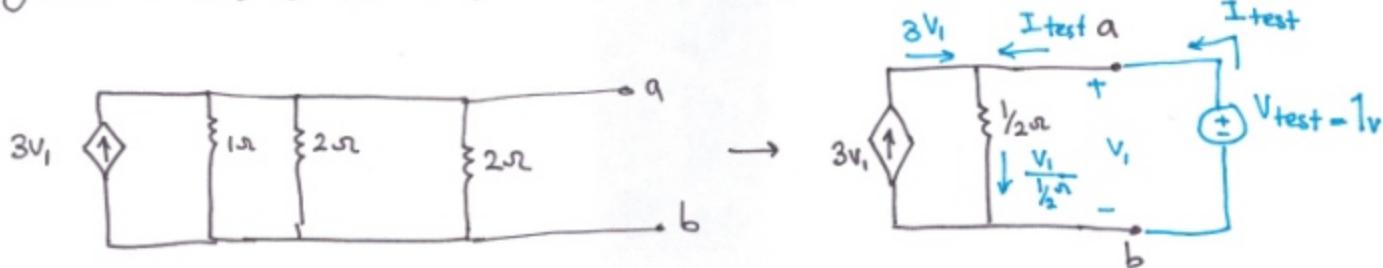As you can see, when the  $1\Omega$  voltage source is turned off, terminals nodes (b) and (c) are shorted, so the  $9\Omega$  and the  $3\Omega$  resistors can be ignored (they are shorted), the  $7\Omega$  resistor is open and can be ignored, this is the simplified circuit diagram:



$$KCL: 3V_1 + I_{test} \neq \frac{V_1}{\frac{1}{2}\Omega}$$


$$V_1 = V_{test} = 1V$$

$$3 + I_{test} = 2 \Rightarrow I_{test} = -1A, R_{th} = \frac{V_{test}}{I_{test}} = \frac{1V}{-1A} = -1\Omega$$

- $I_{sh}$ : Short a to b and find the short circuit current.

It is easier to do nodal analysis.

Since we are only interested in the short-circuit current, we can simplify the rest of the circuit as much as possible; all the elements in parallel with the  $1\Omega$  voltage source have no effect on  $I_{short-circuit}$ .

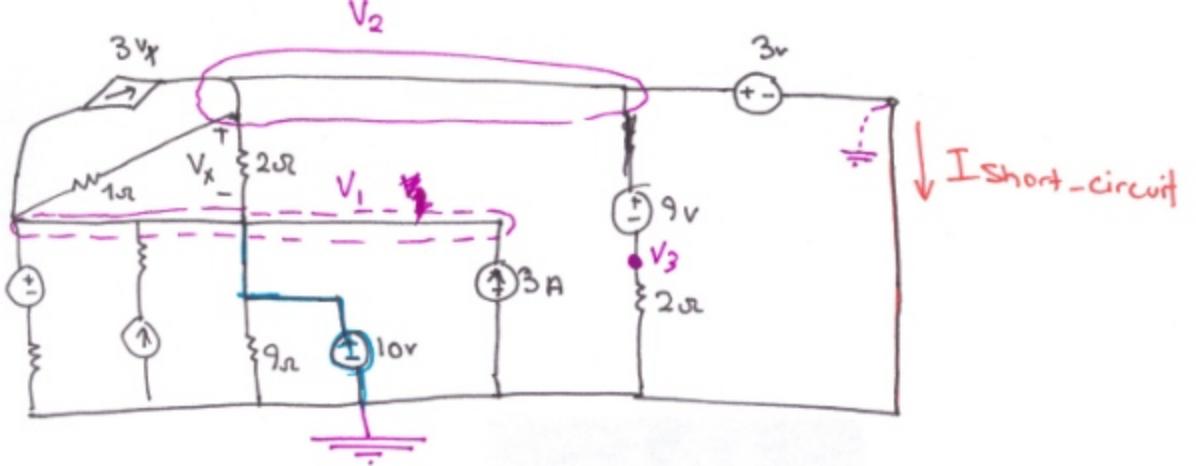


node 1:  $V_1 = 10V$  (because of the voltage source)

node 2:  $V_2 = 3V$

node 3:  $V_3 = V_2 - 9V = 3 - 9 = -6V$

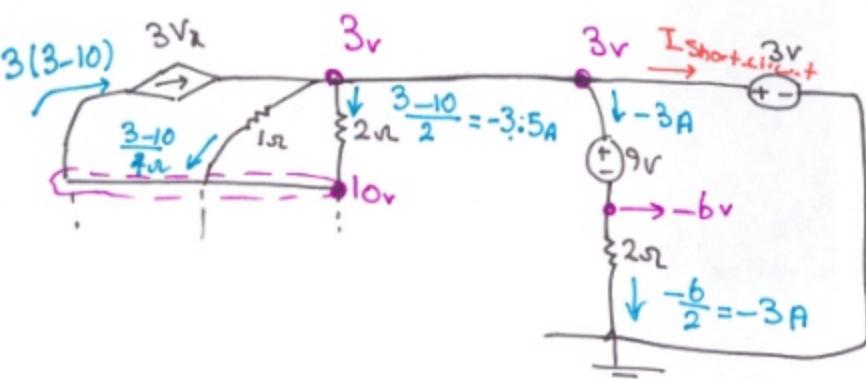We must write a KCL to find  $I_{\text{short-circuit}}$ :




$$3(3-10)V - \frac{(3-10)V}{2\Omega} - \frac{(3-10)V}{1\Omega} - \left(\frac{-6V}{2\Omega}\right) - I_{\text{short-circuit}} = 0$$


$$-21 + 3.5 + 7 + 3 = I_{\text{short-circuit}}$$

$$I_n = I_{\text{short-circuit}} = -21 + 13.5 = -7.5A$$

Norton equivalent:

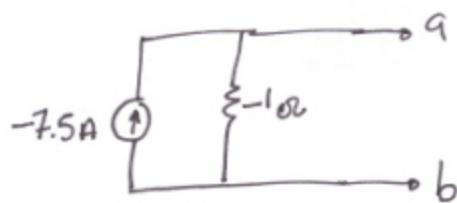


Problem4) Find the value for  $\alpha$ , such that the power transferred to  $R_L$  is maximum.  
 What is the value for the maximum power.

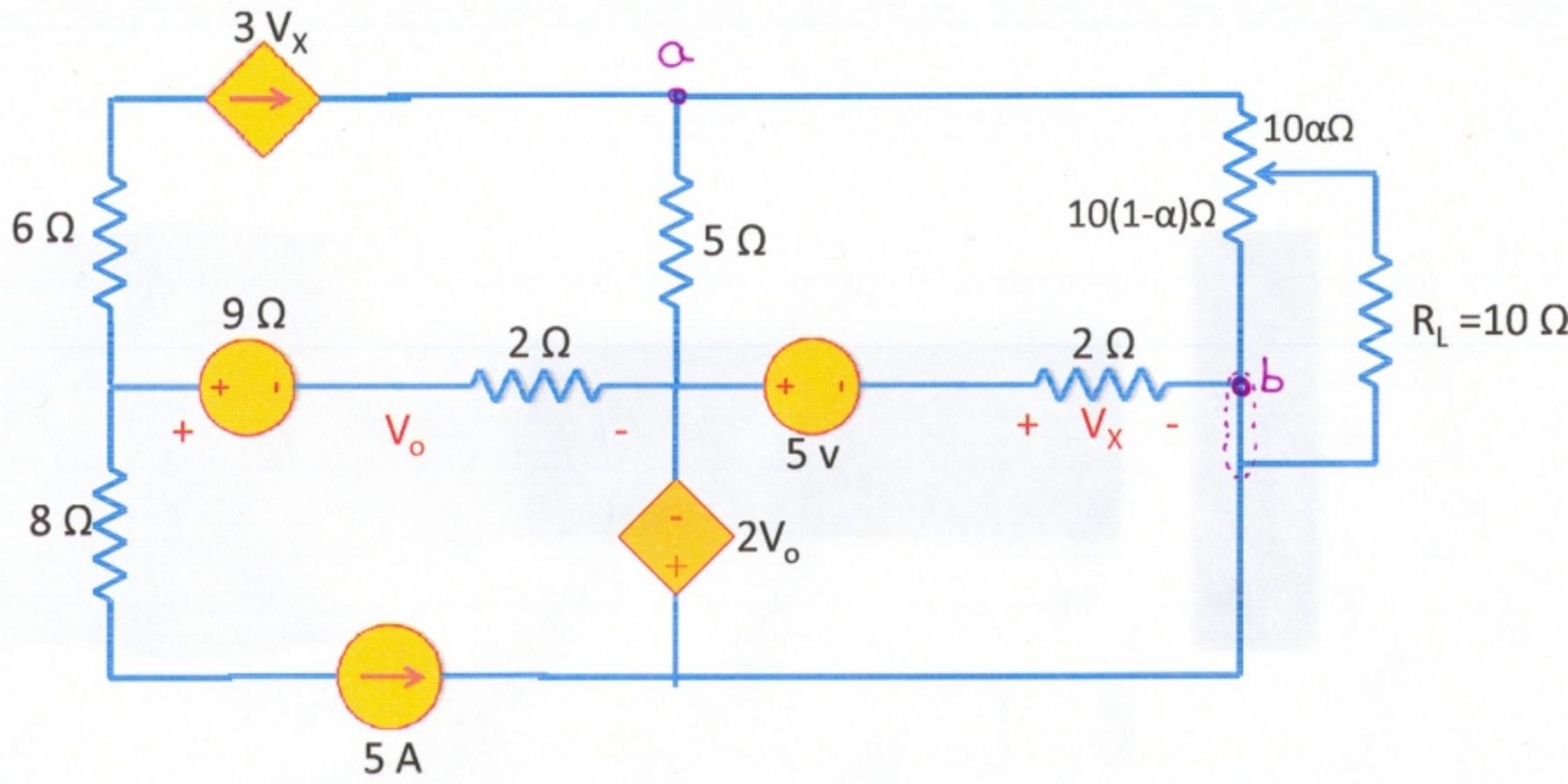

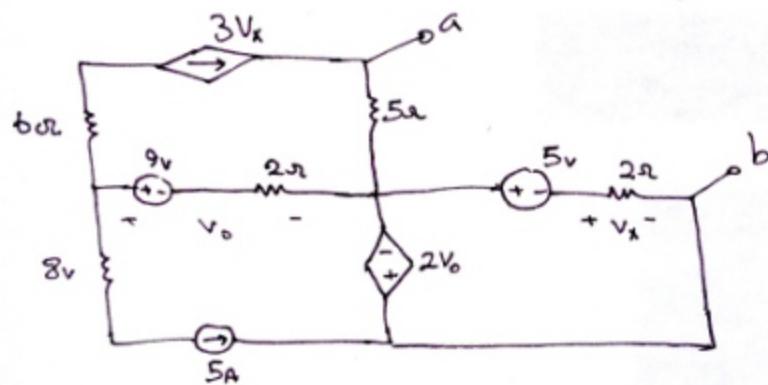
Problem 4)

To find the optimum value for  $\alpha$ , let's first find the equivalent circuit seen by  $R_L$ ; to make analysis easier, we can find the equivalent circuit in two steps.

First leave out the potentiometer and find the equivalent circuit from terminals a-b (shown on the diagram)



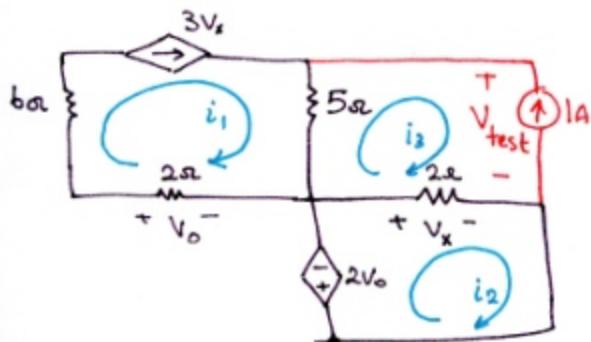- to find  $R_{th}$ , turn off all independent sources, and add the test source;



Here we can use nodal or mesh analysis to find  $V_{test}$ .

$$@ \text{mesh 3: } i_3 = -1 \text{ A} \quad (\text{eq. 1})$$


$$\begin{aligned} @ \text{mesh 1: } i_1 &= 3V_x \\ V_x &= 2(i_2 - i_3) \end{aligned} \quad \left. \begin{aligned} \Rightarrow i_1 &= 6(i_2 - i_3) \\ i_3 &= -1 \text{ A} \end{aligned} \right\} \Rightarrow i_1 = 6(i_2 + 1) \quad (\text{eq. 2})$$

$$\begin{aligned} \text{KVL @ mesh 2: } 2V_0 + 2(i_2 - i_3) &= 0 \\ V_0 &= -2i_1 \end{aligned} \quad \left. \begin{aligned} \Rightarrow (-2i_1) + (i_2 - i_3) &= 0 \\ -2i_1 + i_2 &= -1 \end{aligned} \right\} \quad (\text{eq. 3})$$

(problem 4)

$$\begin{aligned} \text{eq. 2} &\rightarrow i_1 - 6i_2 = 6 \\ \text{eq. 3} &\rightarrow -2i_1 + i_2 = -1 \end{aligned} \quad \left. \begin{array}{l} \times 2 \\ \hline \end{array} \right\} \begin{array}{l} 2i_1 - 12i_2 = 12 \\ -2i_1 + i_2 = -1 \\ \hline -11i_2 = 11 \end{array} \Rightarrow i_2 = -1 \text{ A}$$


$$i_1 = 6 + 6i_2 = 0 \text{ A}$$

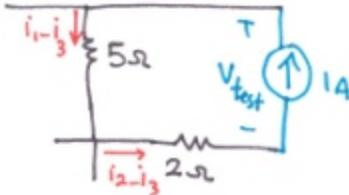

$$\begin{aligned} V_{test} &= 5\Omega \times (i_1 - i_3) + 2\Omega (i_2 - i_3) \\ &= 5\Omega (0 - (-1)) + 2\Omega (-1 - (-1)) \\ &= 5 \times 1 = 5V \end{aligned}$$

$$R_{th} = \frac{V_{test}}{I_{test}} = \frac{5V}{1A} = 5\Omega$$

\*  $V_{th}$

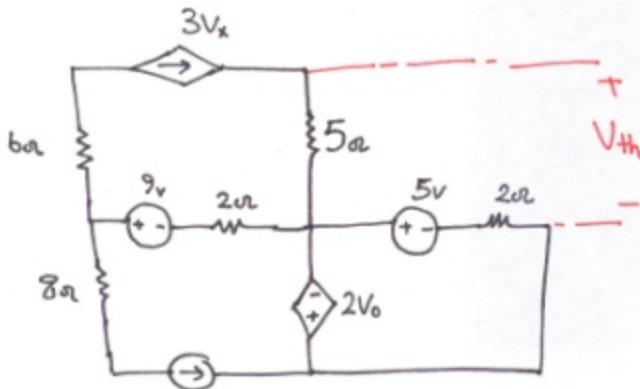

$$\text{at mesh 1: } \begin{cases} i_1 = 3V_x \\ V_x = 2\Omega \times i_3 \end{cases} \Rightarrow i_1 = 6i_3 \quad (\text{eq. 1})$$

$$@ \text{ mesh 2: } i_2 = -5 \text{ A} \quad (\text{eq. 2})$$

$$\begin{aligned} @ \text{ mesh 3: } 2V_0 + 5 + 2i_3 &= 0 \\ V_0 = 9 + 2\Omega (i_2 - i_1) & \end{aligned} \quad \left. \begin{array}{l} \Rightarrow 2(9 + 2i_2 - 2i_1) + 5 + 2i_3 = 0 \\ 18 + 4i_2 - 4i_1 + 5 + 2i_3 = 0 \\ -5A \end{array} \right.$$

$$18 - 20 - 4i_1 + 5 + 2i_3 = 0$$

$$-4i_1 + 2i_3 = -3 \quad (\text{eq. 3})$$

(Prob. 4)


resistor is by big current

$$\begin{aligned} \text{eq. 1} \rightarrow i_1 = 6i_3 \\ \text{eq. 3} \rightarrow -4i_1 + 2i_3 = -3 \end{aligned} \quad \left. \begin{array}{l} \\ \end{array} \right\} \Rightarrow -4(6i_3) + 2i_3 = -3 \\ -22i_3 = -3 \Rightarrow i_3 = \frac{3}{22} \text{ A}$$

$$i_1 = 6i_3 = \frac{18}{22} \text{ A}$$


$$V_{th} = 5i_1 + 5 + 2i_3 = 5 \cdot \frac{18}{22} + 5 + 2 \cdot \frac{3}{22} = 9.36 \text{ V}$$

This is the equivalent circuit from a-b:

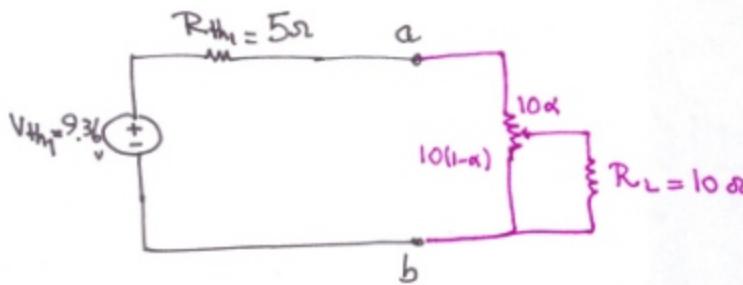

Step 2. Now we should find the equivalent circuit seen by  $R_L$ , we could have found this from the beginning, but it is easier to do it two steps:


$\cdot R_{th}$

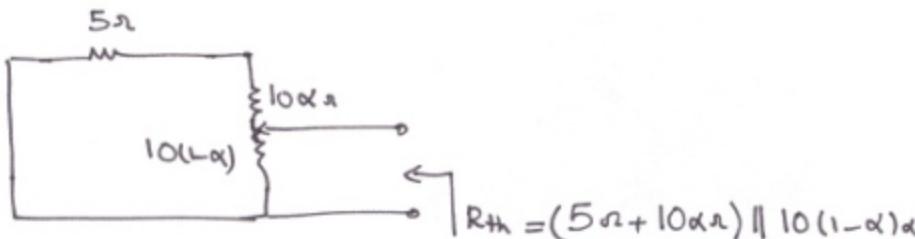

$$R_{th} = \frac{(5 + 10\alpha) \cdot 10(1-\alpha)}{5 + 10\alpha + 10(1-\alpha)}$$

$$= \frac{(5 + 10\alpha) 10(1-\alpha)}{15} = \frac{10(1+2\alpha)(1-\alpha)}{3} \Omega$$


(Prob. 4)

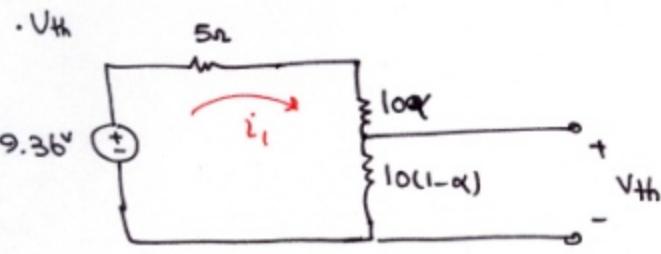

$$i_L = \frac{9.36v}{5\Omega + 10\alpha + 10(1-\alpha)} = \frac{9.36}{15} A$$

$$V_{th} = i_L \times 10(1-\alpha) = \frac{9.36}{15} \times 10(1-\alpha) = 6.24(1-\alpha)$$

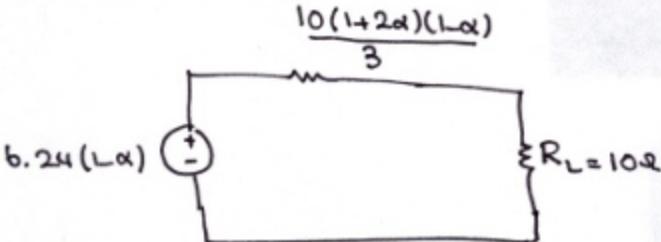Therefore the total equivalent circuit seen by  $R_L$  is:



$$P_L = i_L^2 \cdot R_L$$

$$P_L = i_L^2 \cdot 10\Omega$$

To maximize  $P_L$ , we have to maximize  $i_L$ :

$$i_L = \frac{\frac{6.24(1-\alpha)v}{3}}{\frac{10(1+2\alpha)(1-\alpha)}{3} + 10\Omega} = \frac{6.24 \times 3}{10} \cdot \frac{(1-\alpha)}{(1+2\alpha)(1-\alpha)+3} = \frac{6.24 \times 3}{10} \cdot \frac{1-\alpha}{(-2\alpha^2+\alpha+4)}$$

$$\frac{di_L}{dt} = \frac{6.24 \times 3}{10} \cdot \frac{-1(-2\alpha^2+\alpha+4) - (1-\alpha)(-4\alpha+1)}{(-2\alpha^2+\alpha+4)^2} = \frac{6.24 \times 3}{10} \cdot \frac{-2\alpha^2+4\alpha-4}{(-2\alpha^2+\alpha+4)^2}$$

$$\frac{di_L}{dt} = \left[ \frac{6.24 \times 3}{10} \right] \cdot \frac{\frac{(-2\alpha^2+4\alpha-4)}{(-2\alpha^2+\alpha+4)^2} \rightarrow <0}{\frac{(-2\alpha^2+\alpha+4)}{(-2\alpha^2+\alpha+4)^2} \rightarrow >0} \Rightarrow \frac{di_L}{dt} < 0 \Rightarrow \text{as } \alpha \text{ increases, } i_L \text{ decreases}$$

$\Rightarrow \text{to get maximum } i_L, \alpha \text{ should be minimum}$

$$\Rightarrow \underbrace{\alpha = 0}_{\text{optimum}}$$

$$\begin{aligned} \lim_{\alpha \rightarrow \infty} -2\alpha^2 + 4\alpha - 4 &= -\infty \\ -4\alpha + 4 &= 0 \Rightarrow \alpha = 1 \\ -2(1)^2 + 4(1) - 4 &= -2 < 0 \\ \Rightarrow -2\alpha^2 + 4\alpha - 4 &< 0 \end{aligned}$$


$$i_L \Big|_{\alpha=0} = \frac{6.24v}{10\Omega + \frac{10}{3}\Omega} = 0.468 A$$

$$P_L \Big|_{\max} = (0.468)^2 \times 10 = 2.19 W$$

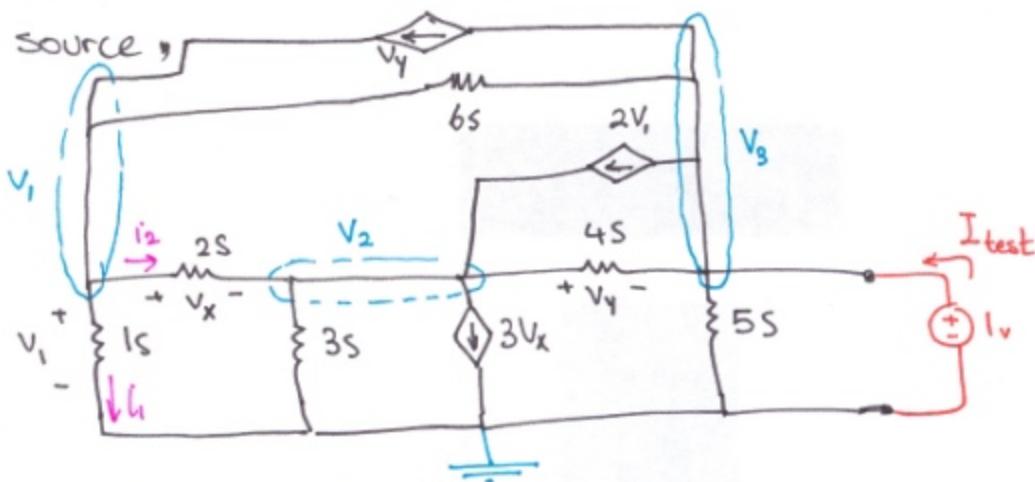(Problem 5)

First we must find the equivalent circuit seen by  $R_L$ :

- $R_{th}$ : turn off all independent sources and add a 1V test voltage



\* S is the unit for conductance ( $G$ ). So for example, the current flowing in the 1s conductance:

$$i_1 = \frac{V_1}{R} = G_1 V_1 \Rightarrow i_1 = (1S) V_1$$

$$\text{for the } 2s \text{ conductance: } i_2 = \frac{V_1 - V_2}{R} = G_2 (V_1 - V_2) = (2S) (V_1 - V_2)$$

at node 1:  $V_1 + 2(V_1 - V_2) + 6(V_1 - V_3) - \cancel{V_y} = 0$   
 $V_1 = V_2 - V_3$        $\cancel{V_y} = V_2 - V_3$

$$V_1 + 2V_1 - 2V_2 + 6V_1 - 6V_3 - V_2 + V_3 = 0$$

$$9V_1 - 3V_2 - 5V_3 = 0 \quad (\text{eq.1})$$

@ node 2:  $2(V_2 - V_1) + 3V_2 + 3V_x + 4(V_2 - V_3) - 2V_1 = 0$   
 $V_x = V_1 - V_2$

$$V_1(-2+3-2) + V_2(2-3+3+4) - 4V_3 = 0 \Rightarrow -V_1 + 6V_2 - 4V_3 = 0 \quad (\text{eq.2})$$

(Problem 5)

@ node 3:  $V_3 = I_v$

$$\text{eq.1} \rightarrow 9V_1 - 3V_2 - 5(1) = 0 \rightarrow 9V_1 - 3V_2 = 5 \xrightarrow{\lambda 2} \left\{ \begin{array}{l} 18V_1 - 6V_2 = 10 \\ -V_1 + 6V_2 = 4 \end{array} \right.$$

$$\text{eq.2} \rightarrow -V_1 + 6V_2 - 4(1) = 0 \Rightarrow -V_1 + 6V_2 = 4$$
$$\begin{array}{r} 18V_1 - 6V_2 = 10 \\ -V_1 + 6V_2 = 4 \\ \hline 17V_1 = 14 \\ V_1 = 0.82 \text{ V} \\ V_2 = \frac{4+V_1}{6} = 0.8 \text{ V} \end{array}$$

To find  $I_{test}$  write a KCL @ node 3:


$$V_y + 6(V_3 - V_1) + 2V_1 + 4(V_3 - V_2) + 5V_3 = I_{test}$$

$$V_2 - V_3 + 6V_3 - 6V_1 + 2V_1 + 4V_3 - 4V_2 + 5V_3 = I_{test}$$

$$\begin{aligned} I_{test} &= (-6+2)V_1 + (-4)V_2 + (-1+6+4+5)V_3 \\ &= -4 \times 0.82 - 3 \times 0.8 + 14 \times 1 = -3.28 - 2.4 + 14 = 8.32 \text{ A} \end{aligned}$$

$$R_{th} = \frac{V_{test}}{I_{test}} = \frac{I_v}{8.32 \text{ A}} = 0.12 \text{ } \Omega$$

to find  $V_{th}$ :

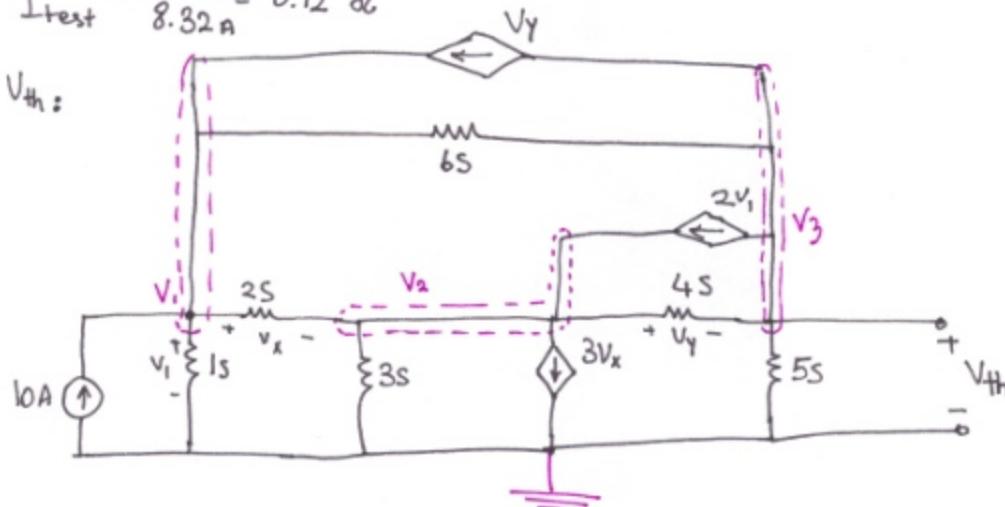

$$\text{Node 1: } 1 \cdot V_1 + 2(V_1 - V_2) + 6(V_1 - V_3) - V_y = 10 \text{ A}$$

$$9V_1 - 3V_2 - 5V_3 = 10 \quad (\text{eq. 1})$$

(Problem 5)

@ node 2:

$$3V_2 + 2(V_2 - V_1) + \underbrace{3V_x}_{V_1 - V_2} + 4(V_2 - V_3) - 2V_1 = 0$$

$$-V_1 + 6V_2 - 4V_3 = 0 \quad (\text{eq. 2})$$

@ node 3:

$$5V_3 + 4(V_3 - V_2) + 2V_1 + 6(V_3 - V_1) + \underbrace{V_y}_{V_2 - V_3} = 0$$


$$-4V_1 - 3V_2 + 14V_3 = 0 \quad (\text{eq. 3})$$

$$\begin{bmatrix} 9 & -3 & -5 \\ -1 & 6 & -4 \\ 4 & -3 & 14 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$

$$V_{th} = V_3 = \frac{\Delta_3}{\Delta} = \frac{\begin{vmatrix} 9 & -3 & 10 \\ -1 & 6 & 0 \\ 4 & -3 & 0 \end{vmatrix}}{\begin{vmatrix} 9 & -3 & -5 \\ -1 & 6 & -4 \\ 4 & -3 & 14 \end{vmatrix}}$$

$$V_{th} = \frac{270}{423} = 0.64 \text{ v}$$

$$R_{th} = 0.12 \Omega$$

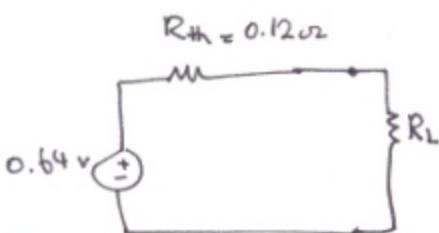

to get the maximum power transfer,

$$R_{th} = R_L \Rightarrow R_L = 0.12 \Omega$$


$$P_L = \frac{V_{th}^2}{4R} = \frac{(0.64)^2}{4 \times 0.12} = 0.85 \text{ w}$$

$$P_L = i_L^2 \cdot R_L$$

$$P_L = \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 \cdot R_L$$

$$R_L = R_{th} = R \Rightarrow P_L = \left( \frac{V_{th}}{R+R} \right)^2 \cdot R = \frac{V_{th}^2}{4R}$$

Problem 6) Find the voltage across  $C_2$ .

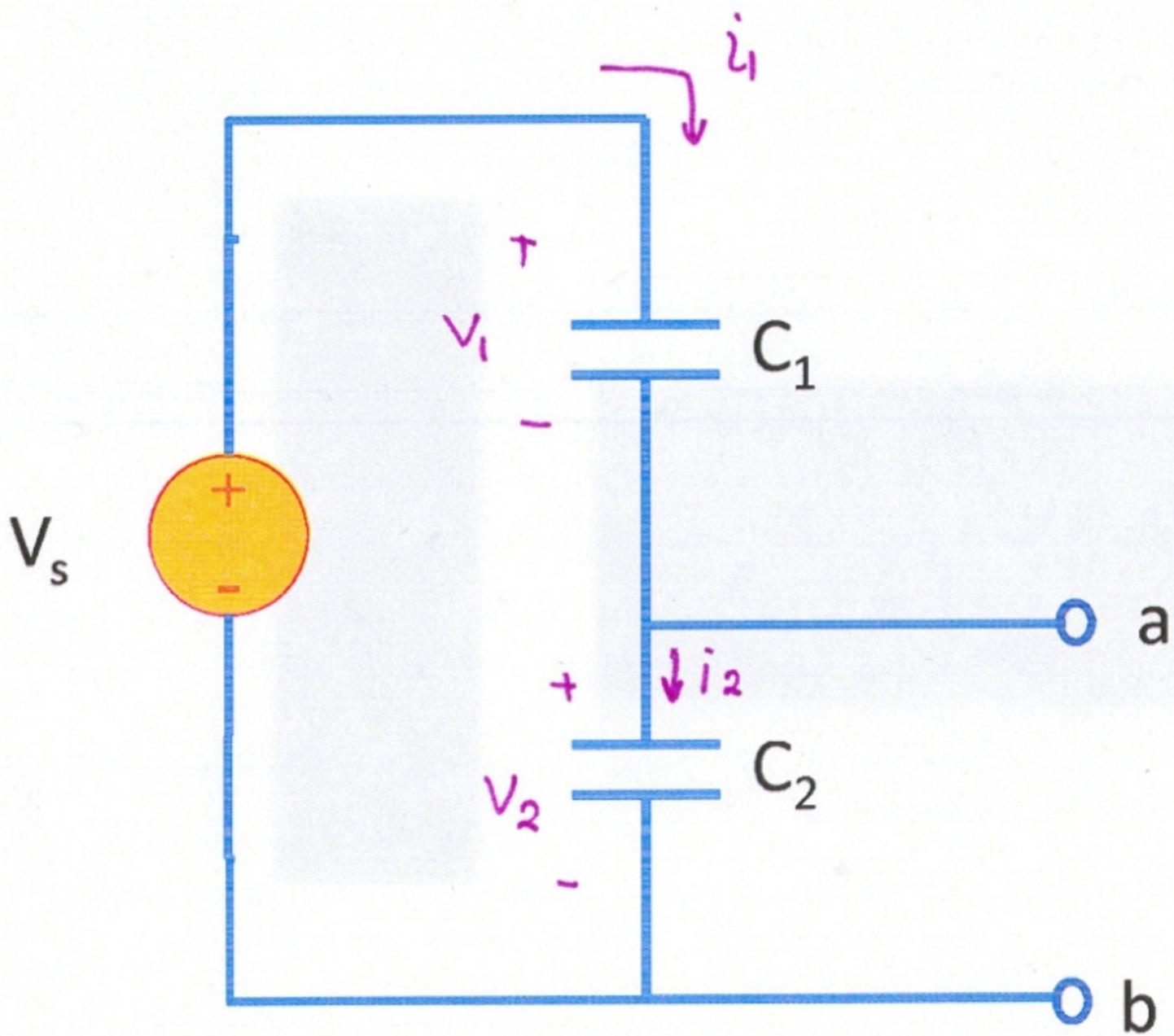

(Problem 6)

$C_1$  is in series with  $C_2 \Rightarrow i_1 = i_2 = i$

$$q = \int_0^t i(t) dt$$

charge stored in the capacitor

$$q_1 = \int i_1(t) dt = \int i(t) dt$$

$$q_2 = \int i_2(t) dt = \int i(t) dt \Rightarrow q_1 = q_2 = q$$

$$q_1 = C_1 V_1$$

$$q_2 = C_2 V_2$$


$$KVL \rightarrow V_s = V_1 + V_2$$

$$\left. \begin{array}{l} C_1 V_1 = C_2 V_2 \\ C_1 (V_s - V_2) = C_2 V_2 \end{array} \right\} \Rightarrow C_1 (V_s - V_2) = C_2 V_2$$



$$C_1 V_s = (C_1 + C_2) V_2$$

$$V_2 = \frac{C_1}{C_1 + C_2} V_s$$



Problem 7) Find the equivalent capacitance. All Capacitors have the value of 1mF.

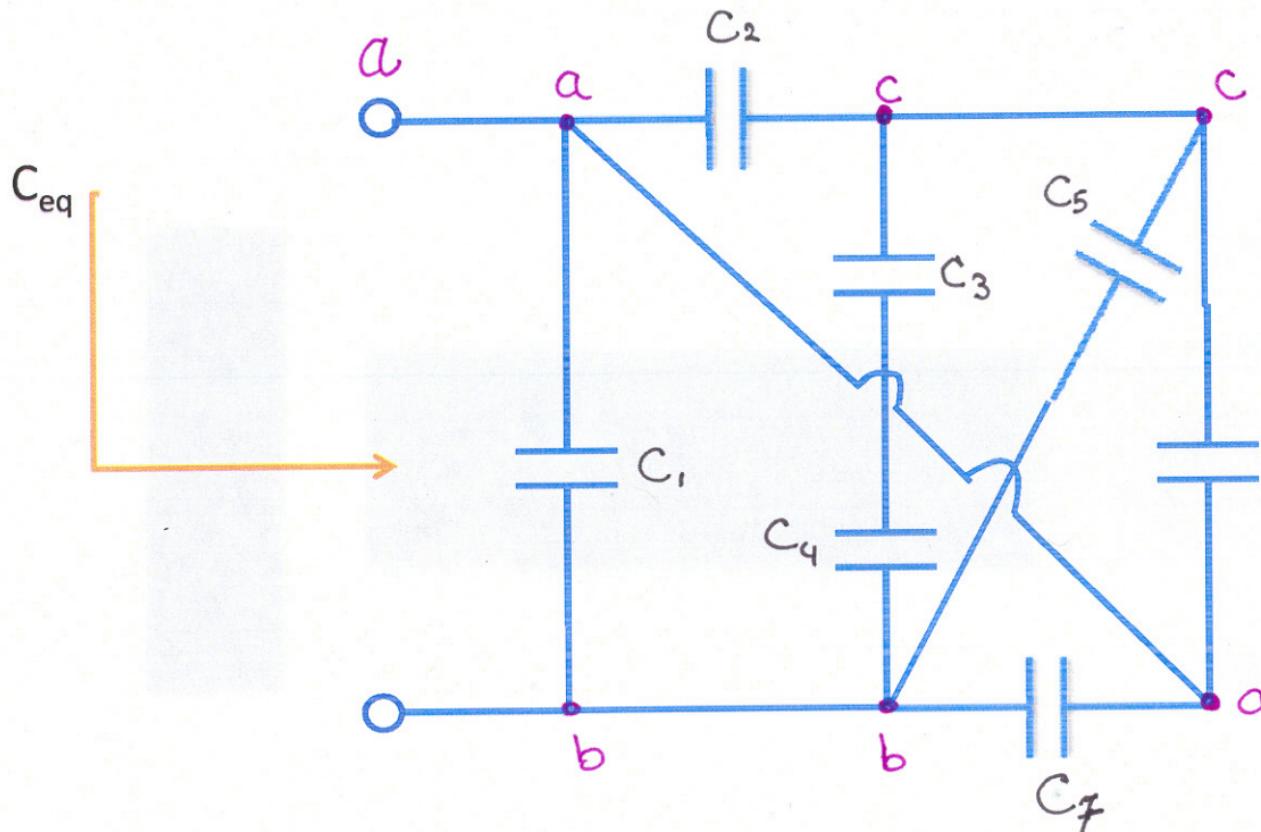

(Problem 7)

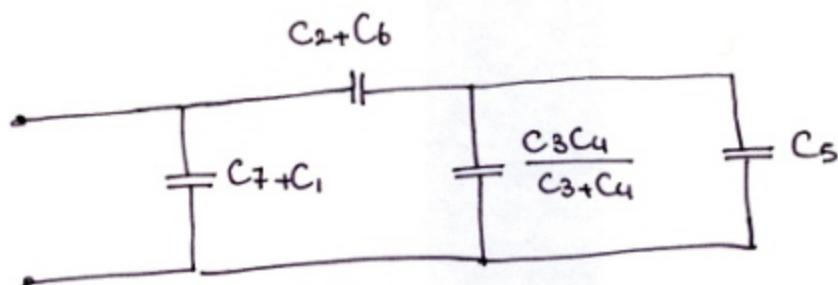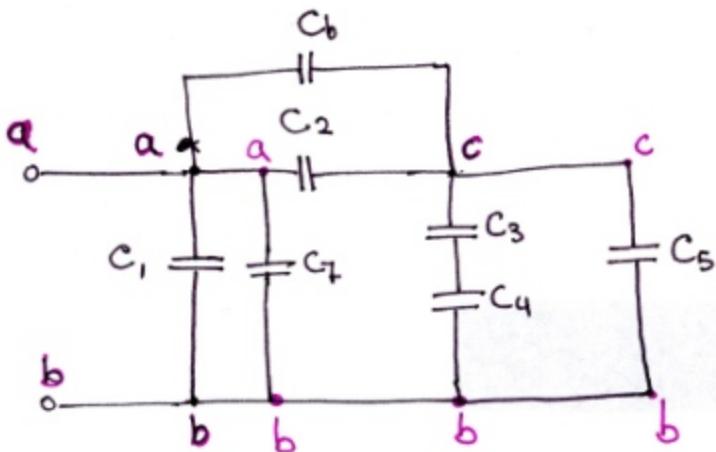

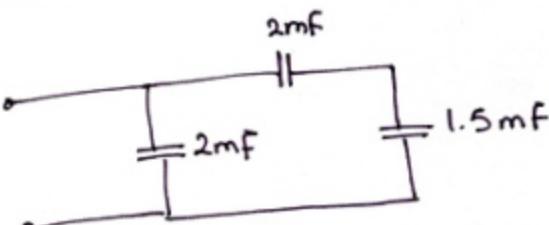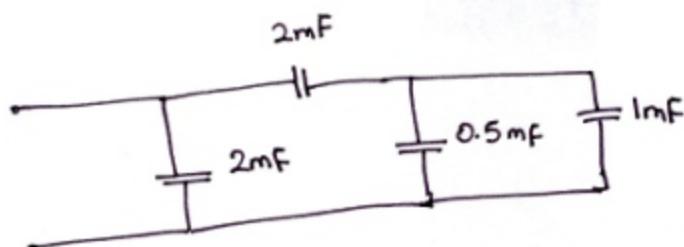
$$C_1 = C_2 = C_3 = C_4 = C_5 = C_6 = C_7 = 1 \text{ mF}$$



$$\frac{2\text{mF} \times 1.5\text{mF}}{2\text{mF} + 1.5\text{mF}} = \frac{6}{7} \text{ mF}$$

$$2\text{mF} + \frac{6}{7} \text{ mF} = \frac{20}{7} \text{ mF} \Rightarrow C_{eq} = \frac{20}{7} \text{ mF}$$

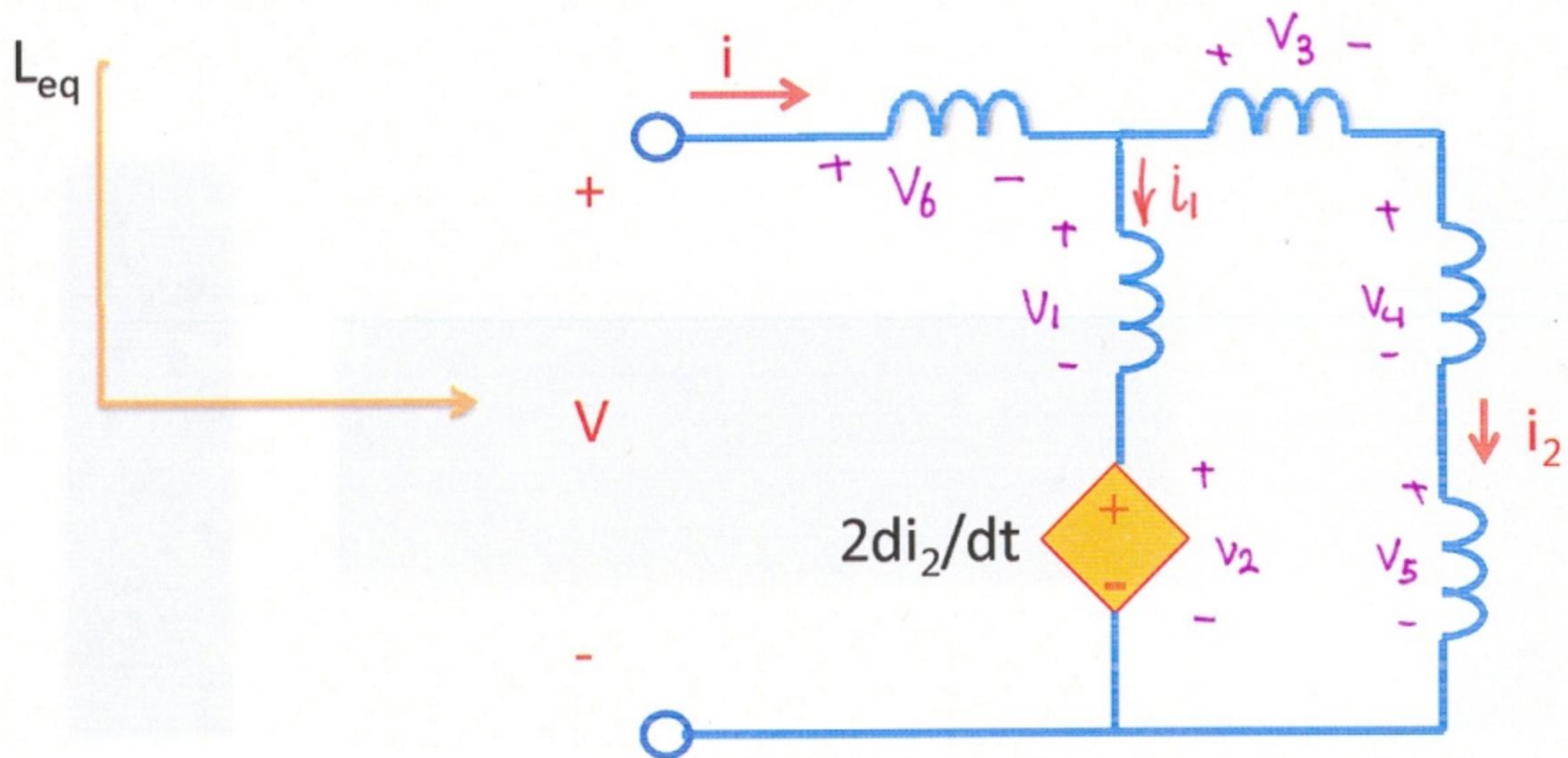Problem8) Find the equivalent inductance. All inductors are 1H



Hint:  $V = L_{eq} \frac{di}{dt}$

(Problem 8)

$$V = V_6 + V_1 + V_2 = L \frac{di}{dt} + L \frac{di_1}{dt} + 2 \frac{di_2}{dt} \quad (*)$$

$$V = \frac{di}{dt} + \frac{di_1}{dt} + 2 \frac{di_2}{dt}$$

KVL :  $V_1 + V_2 = V_3 + V_4 + V_5$

$$\frac{di_1}{dt} + 2 \frac{di_2}{dt} = \frac{di_2}{dt} + \frac{di_2}{dt} + \frac{di_2}{dt} \Rightarrow \frac{di_1}{dt} = \frac{di_2}{dt}$$

$$i_1 + i_2 = i \Rightarrow \frac{di_1}{dt} + \frac{di_2}{dt} = \frac{di}{dt} \Rightarrow \frac{di_1}{dt} = \frac{di_2}{dt} = \frac{1}{2} \frac{di}{dt}$$

$$\frac{di_1}{dt} = \frac{di_2}{dt} \quad \left\{ \Rightarrow \text{replace in } (*) \rightarrow V = \frac{di}{dt} + \frac{1}{2} \frac{di}{dt} + 2 \times \frac{1}{2} \frac{di}{dt}$$


$$V = \frac{5}{2} \frac{di}{dt} = L_{eq} \frac{di}{dt}$$

$$\Rightarrow L_{eq} = \frac{5}{2} H$$

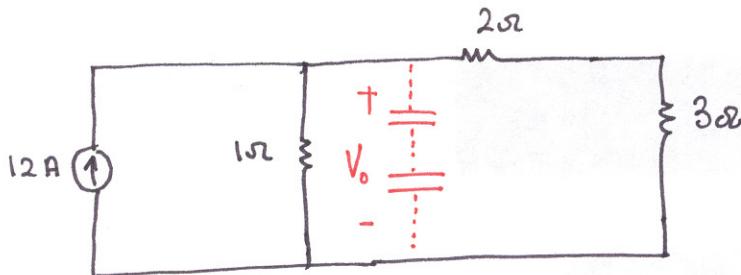Problem 9)

$$V(t) = V_0 e^{-t/RC}$$


before the switch opens: (Capacitors behave like open circuits)



$$V_0 = 12 \times R_{eq} = 12 \times (1\Omega \parallel (2\Omega + 3\Omega))$$

$$= 12 \times (1 \parallel 5) = 12 \times \frac{1 \times 5}{1+5} = 10V$$

after the switch opens:

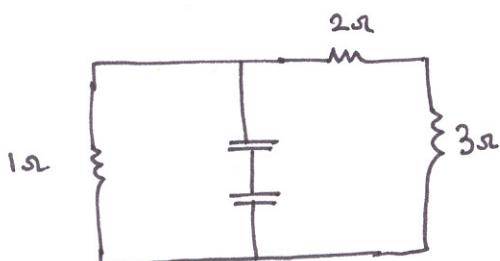

$$R_{eq} = 1\Omega \parallel (2\Omega + 3\Omega) = 5/6\Omega$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{3 \times 7}{3+7} F = 2.1 F$$


$$T = R_{eq} \cdot C_{eq} = \frac{5}{6} \times 2.1 = 1.75 \text{ s}$$

$$V(t) = 10 e^{-t/1.75} \quad (t > 0)$$

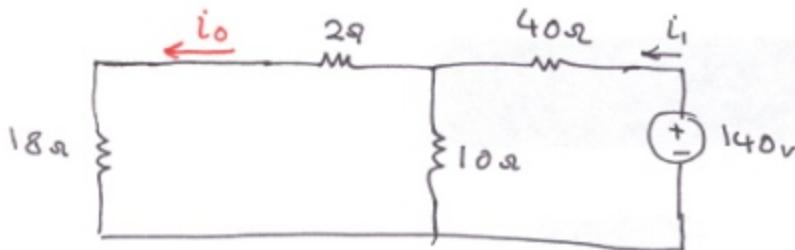(Problem 10)

$$i_L(t) = i_0 e^{-R_L t}$$



before switch opens : ( Inductor behaves like a short circuit )



$$i_1 = \frac{140\text{v}}{40\Omega + (10||2+18)\Omega} = \frac{140\text{v}}{(40+10||20)\Omega} = 3\text{ A}$$

$$i_0 = i_1 \times \frac{10\Omega}{10\Omega + 2\Omega + 18\Omega} = i_1 \times \frac{10}{30} = 1 \times \frac{1}{3} = 1\text{ A}$$

after the switch opens :

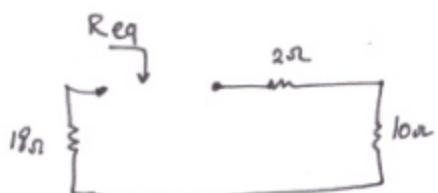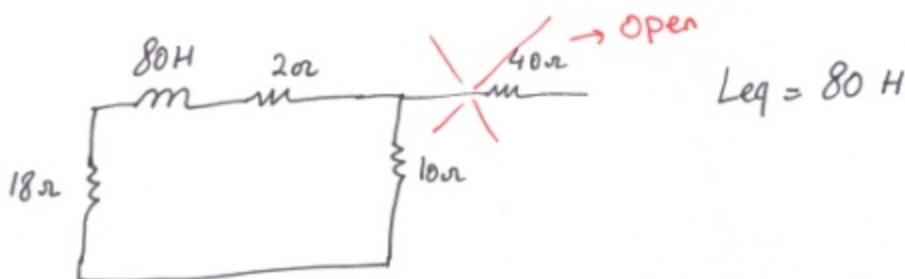

$$R_{eq} = 2\Omega + 8\Omega + 10\Omega = 20\Omega$$


$$i_L(t) = i_0 e^{-R_L t} = 1 \times e^{-\frac{20}{80}t} = e^{-t/4} \text{ A } (t > 0)$$

(Problem 11)

First we should find all impedances:

$$\text{For the capacitor: } Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 10^5 \times 2 \times 10^{-6}} = -5j \Omega$$
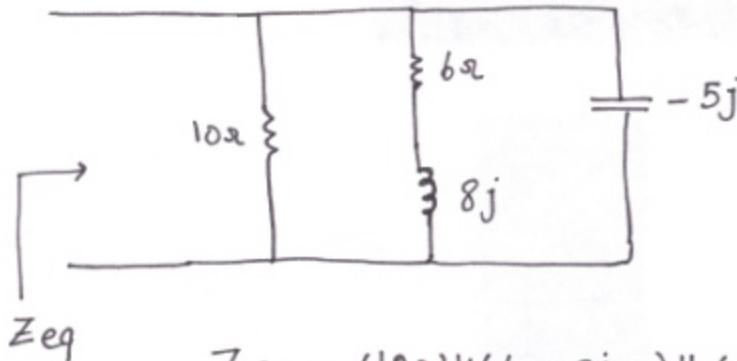
$$\text{~ ~ ~ Inductor: } Z_L = j\omega L = j \times 10^5 \times 80 \times 10^{-6} = 8j \Omega$$




$$Z_{eq} = (10\Omega) \parallel (6\Omega + 8j\Omega) \parallel (-5j\Omega)$$

$$\frac{1}{Z_{eq}} = \frac{1}{10\Omega} + \frac{1}{(6+8j)\Omega} + \frac{-1}{5j\Omega}$$

$$\frac{1}{Z_{eq}} = \frac{(j-2)(3+4j)+5j}{10j(3+4j)} = \frac{-10}{30j-40} = \frac{-1}{3j-4}$$

$$\Rightarrow Z_{eq} = 4 - 3j \Omega$$

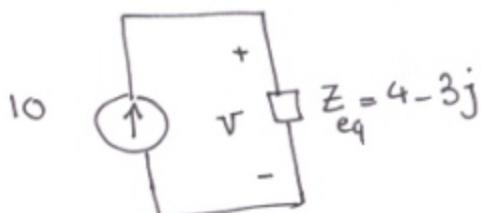

$$V = I \cdot Z_{eq} = 10(4 - 3j) = 10 \times 5 \angle -0.64^\circ$$

$$= 50 \angle -0.64^\circ$$

$$v(t) = 50 \cos(\omega t - 0.64) v$$