
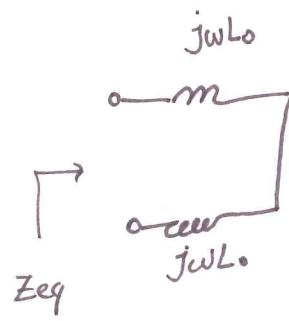


EECS 70A: Network Analysis

Homework #5
Due in discussion section,
Wednesday, May 19, 2010.

Problem1: Solve for Z_{eq} .


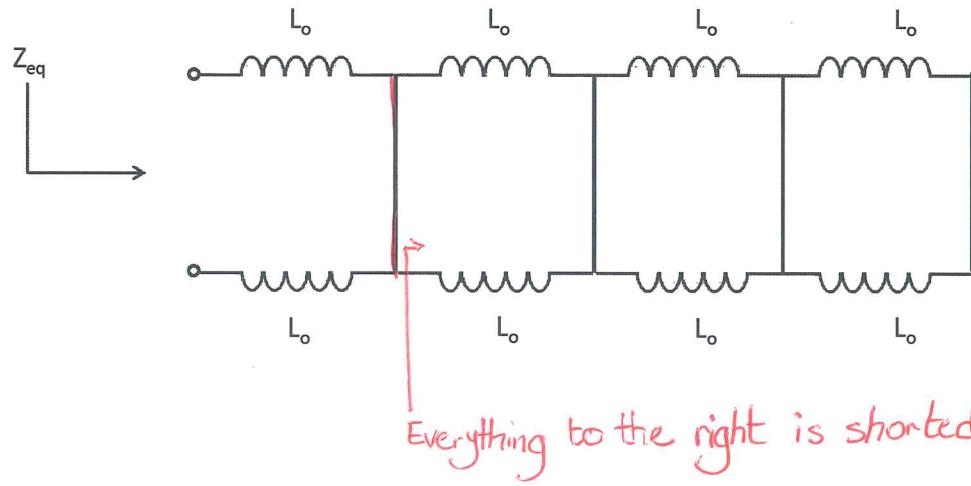


The two inductors are in series.

$$Z_{eq} = jwL_o + jwL_o$$


$$Z_{eq} = 2jwL_o$$

Problem2: Solve for Z_{eq} .

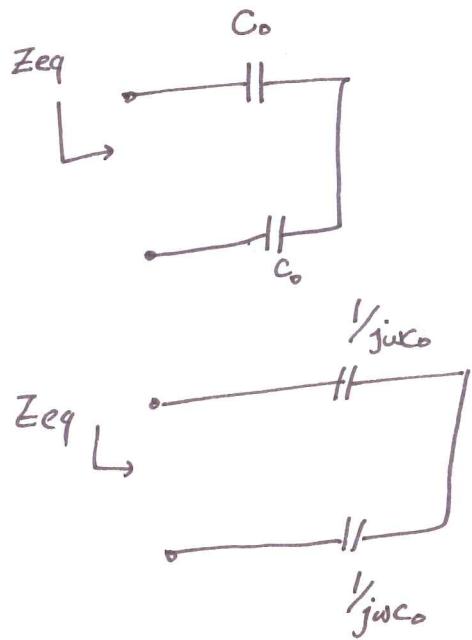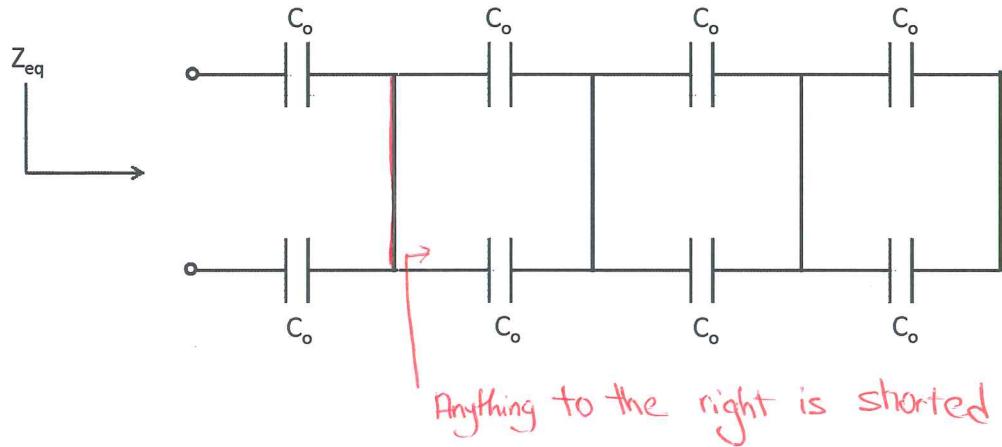


$$Z_{eq} = \frac{1}{jwC_o} + \frac{1}{jwC_o} = \frac{2}{jwC_o}$$


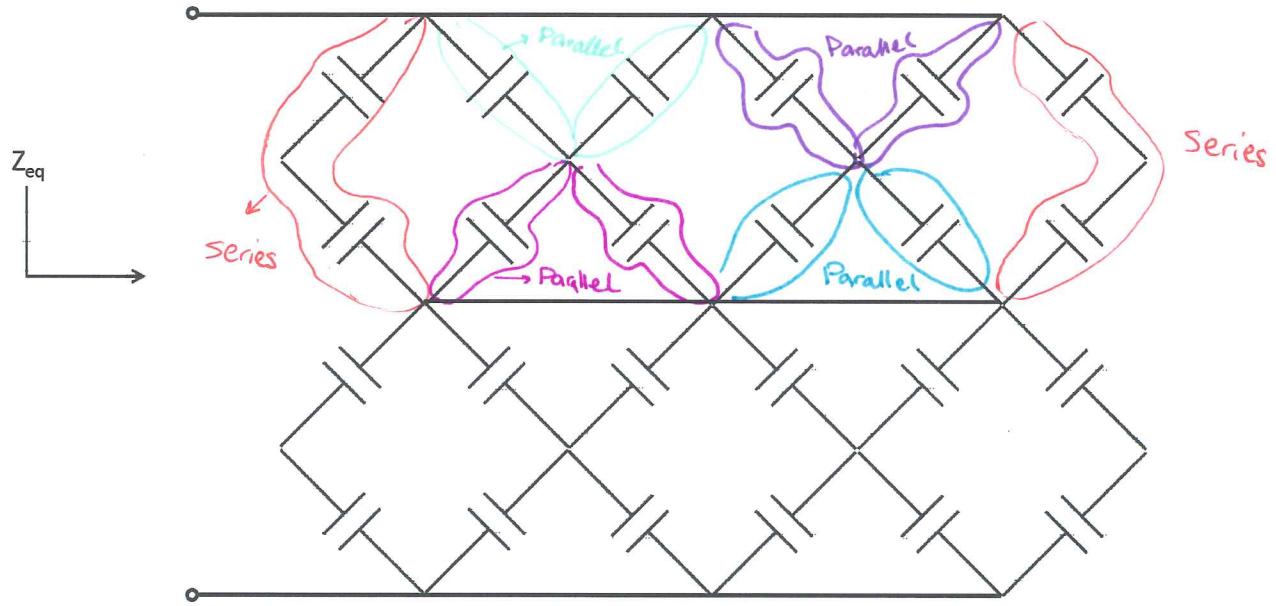
Problem3) Solve for Z_{eq} . All capacitors have same value C_0 .



The bottom part is similar to the top part. We replace the parallel capacitors with $2C_0$ and the series with $\frac{C_0}{2}$, and find each impedance:

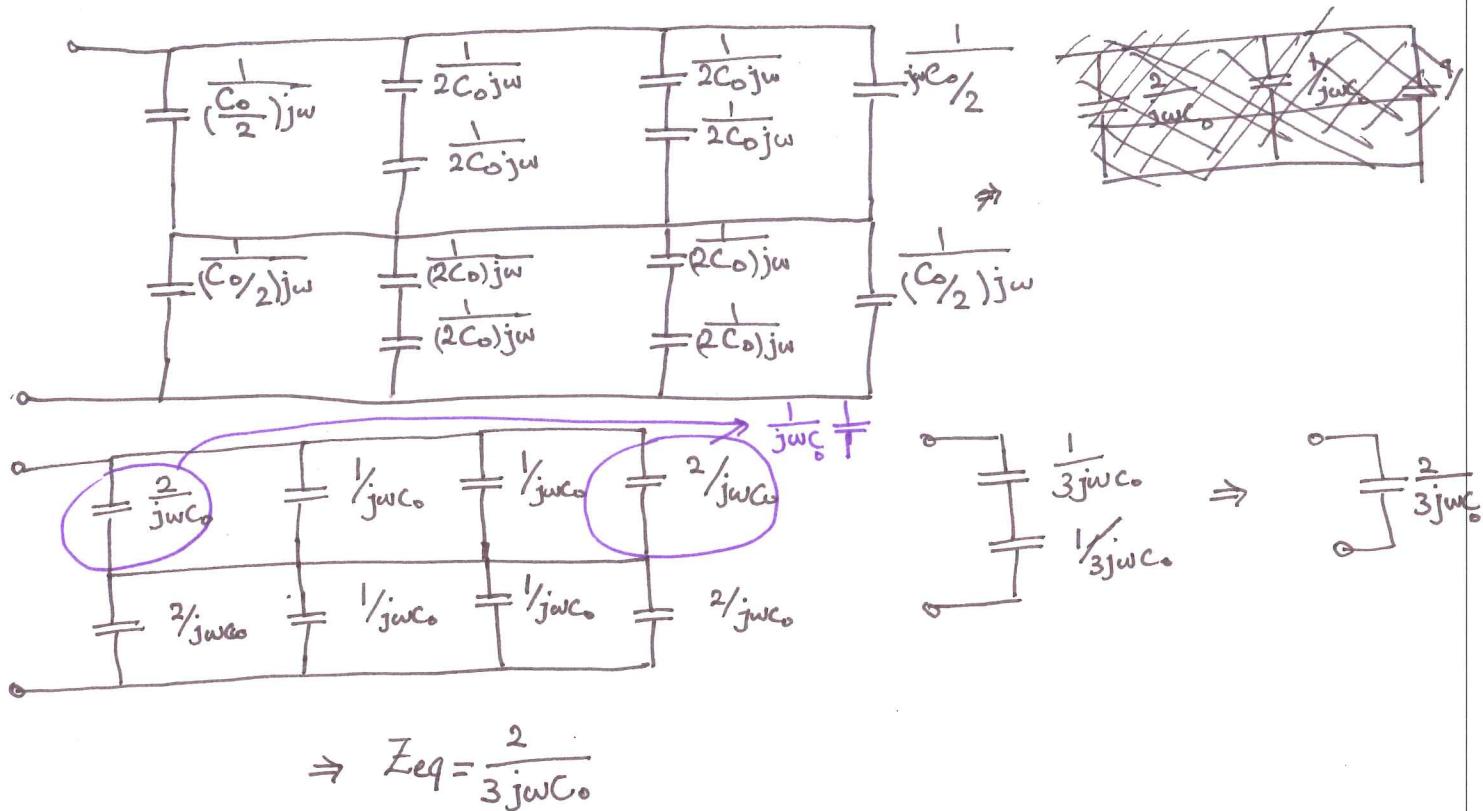

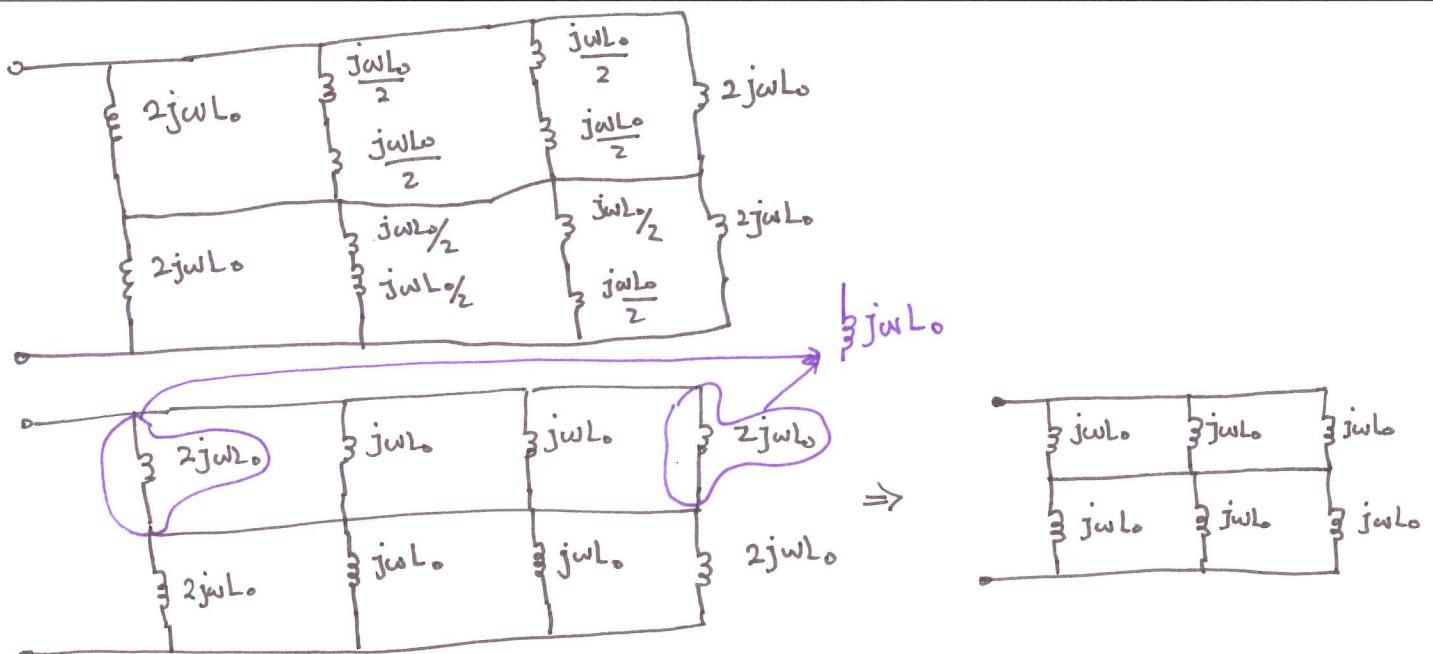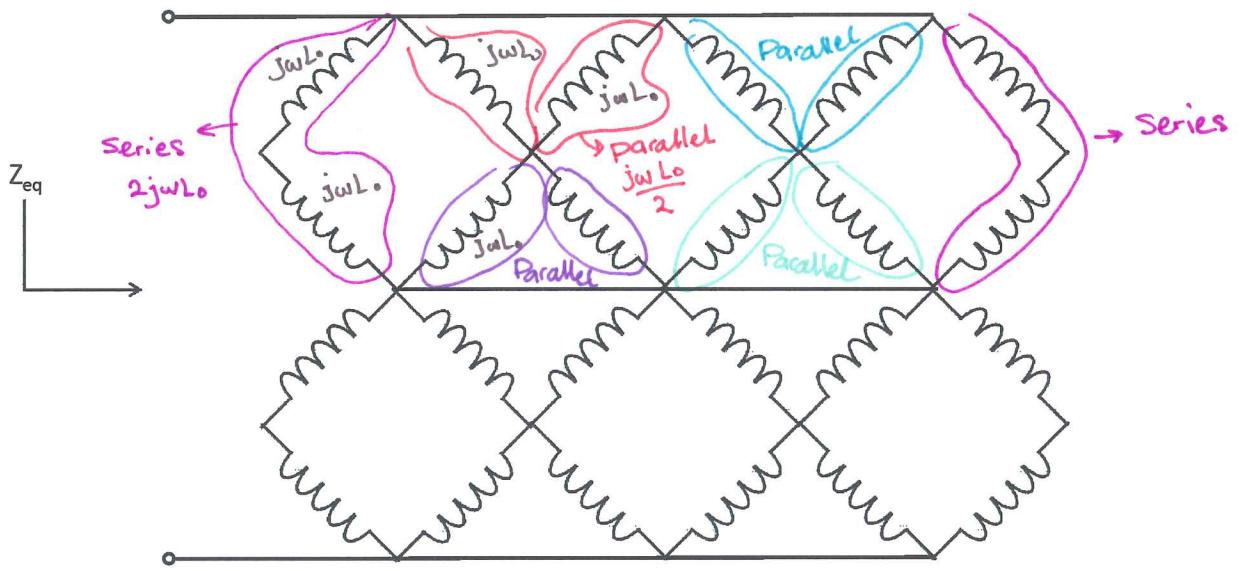Problem4) Solve for Z_{eq} . All inductors have same value L_0 .



$$Z_{eq} = \frac{2}{3} jwL_0$$