

# EECS 70A: Network Analysis

Homework #6


Due Friday, June 4, 2010.

# Problem 1:

## Time to frequency and back


- A) Given  $v(t) = 4 \cos(\omega t + \pi/4)$  find the phasor  $\mathbf{V}$  that represents  $v(t)$ .  
Express  $\mathbf{V}$  as  $x+jy$  and as  $re^{i\phi}$ .
- B) Given  $i(t) = 4 \sin(\omega t + \pi/2)$  find the phasor  $\mathbf{I}$  that represents  $i(t)$ .  
Express  $\mathbf{I}$  as  $x+jy$  and as  $re^{i\phi}$ .
- C) Given  $\mathbf{V} = 3 + j4$  find  $v(t)$ .
- D) Given  $\mathbf{I} = 1.5 e^{i\pi/3}$  find  $i(t)$ .

# Problem 2

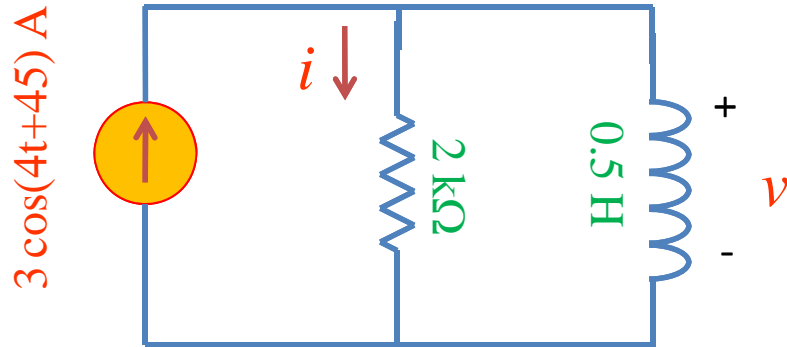


Find  $i(t)$  and  $v(t)$ . Hint: convert the current source into a phasor, then find the current and voltage phasors for the whole circuit, then convert back to the time dependent  $i(t)$ ,  $v(t)$ .

# Problem 3

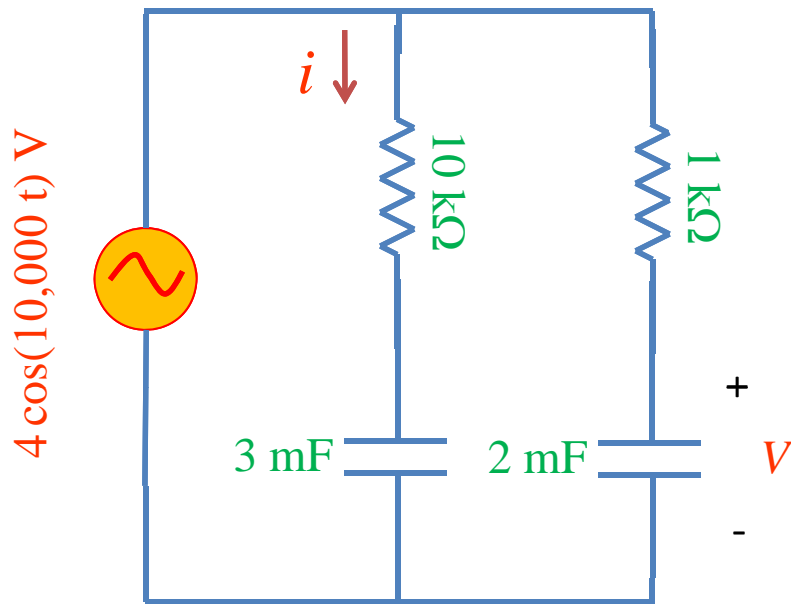


Find  $i(t)$  and  $v(t)$ . Hint: convert the voltage source into a phasor, then find the current and voltage phasors for the whole circuit, then convert back to the time dependent  $i(t)$ ,  $v(t)$ .

# Problem 4: Transfer function

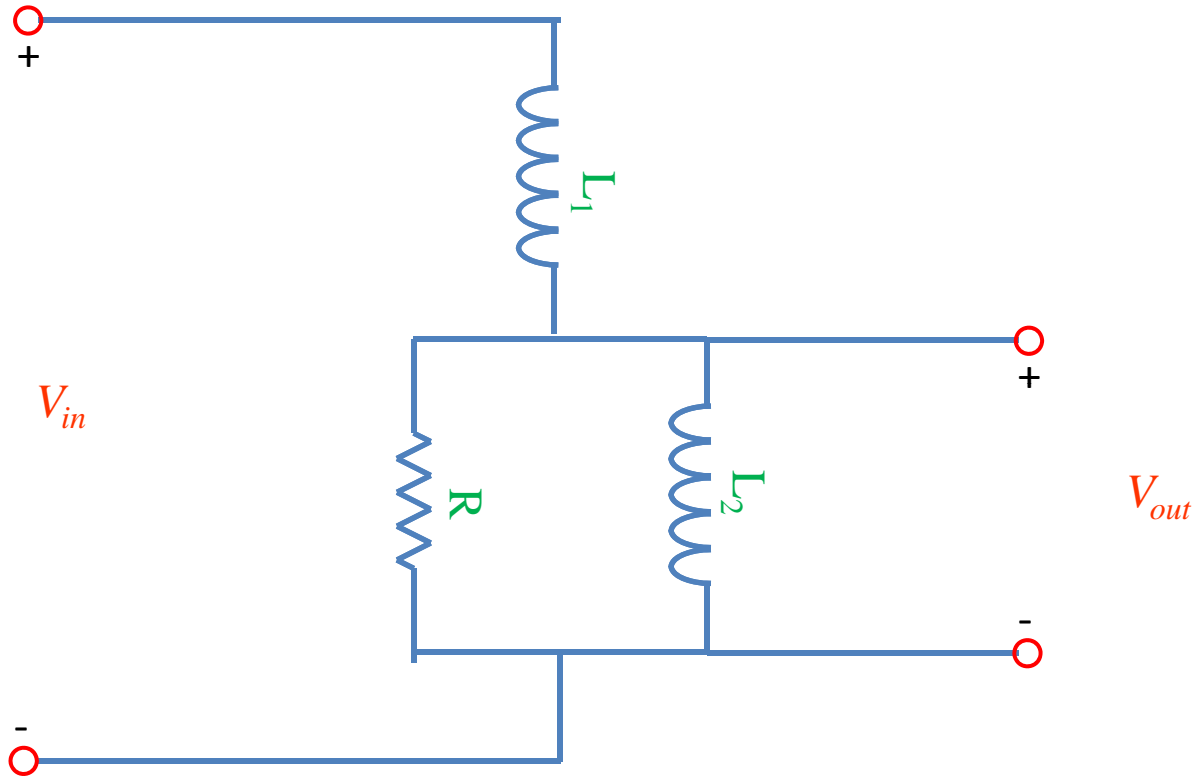


Calculate  $H(\omega)$  for this circuit. Sketch the magnitude of  $H(\omega)$  vs.  $\omega$ .

# Problem 5: Transfer function

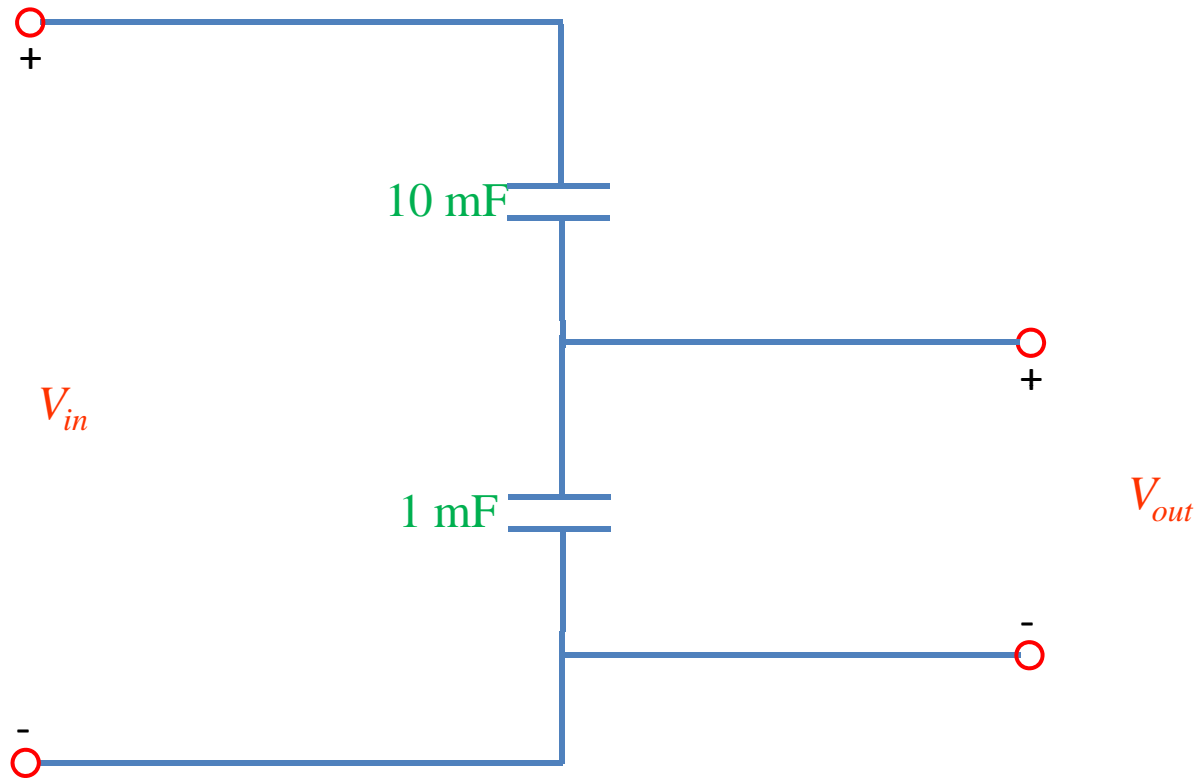

Calculate  $H(\omega)$  for this circuit. Sketch the magnitude of  $H(\omega)$  vs.  $\omega$ .

# Problem 6: Band stop filter

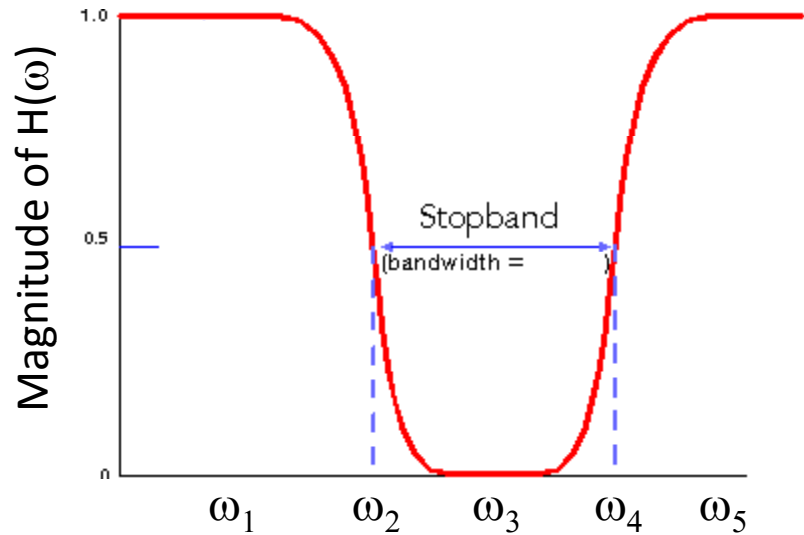

- A) Given  $v(t) = 4 \cos(\omega_1 t + \pi/4)$  find  $v_{\text{out}}(t)$ .
- B) Given  $v(t) = 3 \cos(\omega_2 t + \pi/2)$  find  $v_{\text{out}}(t)$ .
- C) Given  $v(t) = 2 \cos(\omega_3 t + \pi/3)$  find  $v_{\text{out}}(t)$ .
- D) Given  $v(t) = 2 \cos(\omega_4 t + \pi/2)$  find  $v_{\text{out}}(t)$ .
- E) Given  $v(t) = 2 \cos(\omega_5 t + \pi/4)$  find  $v_{\text{out}}(t)$ .

Note: You cannot determine the phase of  $v_{\text{out}}(t)$  so leave that as unknown in your answer.