

Problem 1:

Time to frequency and back

- A) Given $v(t) = 4 \cos(\omega t + \pi/4)$ find the phasor \mathbf{V} that represents $v(t)$.
Express \mathbf{V} as $x+jy$ and as $re^{j\phi}$.
- B) Given $i(t) = 4 \sin(\omega t + \pi/2)$ find the phasor \mathbf{I} that represents $i(t)$.
Express \mathbf{I} as $x+jy$ and as $re^{j\phi}$.
- C) Given $\mathbf{V} = 3 + j4$ find $v(t)$.
- D) Given $\mathbf{I} = 1.5 e^{j\pi/3}$ find $i(t)$.

$$\begin{aligned} \text{A) } v(t) = 4 \cos(\omega t + \frac{\pi}{4}) \text{ V} &\Rightarrow \mathbf{V} = 4e^{j\pi/4} = 4 \cos \frac{\pi}{4} + j \cdot 4 \sin \frac{\pi}{4} \\ &= 2\sqrt{2} + j \cdot 2\sqrt{2} \end{aligned}$$

$$\begin{aligned} \text{B) } i(t) &= 4 \sin(\omega t + \frac{\pi}{2}) \\ &= 4 \cos \omega t \quad \Rightarrow \mathbf{V} = 4e^{j0} = 4 \\ \mathbf{V} &= 4 (\cos 0 + j \sin 0) = 4 + j \cdot 0 = 4 \text{ V} \end{aligned}$$

$$\text{C) } \mathbf{V} = 3 + j4$$

$$|\mathbf{V}| = \sqrt{3^2 + 4^2} = \sqrt{9 + 16} = 5$$


$$\phi = \tan^{-1}\left(\frac{y}{x}\right) = \tan^{-1}\left(\frac{4}{3}\right) = 53^\circ \Rightarrow \phi = 0.927 \text{ rad}$$

$$\begin{aligned} v(t) &= \text{Re}(\mathbf{V}e^{j\omega t}) = \text{Re}(5e^{j \cdot 0.927} \cdot e^{j\omega t}) = 5 \cos(\omega t + 0.927 \text{ (rad)}) \\ &= 5 \cos(\omega t + 53^\circ) \text{ V} \end{aligned}$$

$$\text{D) } \mathbf{I} = 1.5 e^{j\pi/3}$$

$$\begin{aligned} i(t) &= \text{Re}(\mathbf{I}e^{j\omega t}) = \text{Re}(1.5e^{j\pi/3} \cdot e^{j\omega t}) = \text{Re}(1.5e^{j(\omega t + \pi/3)}) \\ &= 1.5 \cos(\omega t + \pi/3) \text{ A} \end{aligned}$$

Problem 2

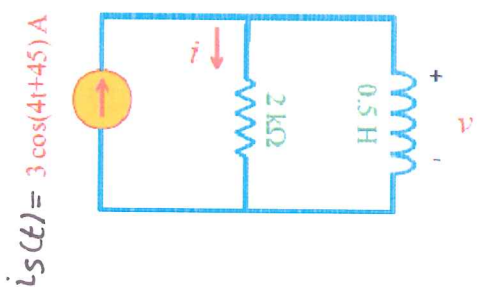


Find $i(t)$ and $v(t)$. Hint: convert the current source into a phasor, then find the current and voltage phasors for the whole circuit, then convert back to the time dependent $i(t)$, $v(t)$.

$$i_s(t) = 3 \cos(4t + 45^\circ) \text{ A} \quad 45^\circ = \pi/4 \text{ rad}$$

$$I_s = 3 e^{j\pi/4} = 3 \cos \frac{\pi}{4} + 3j \sin \frac{\pi}{4} = \frac{3\sqrt{2}}{2} (1+j) \text{ A}$$
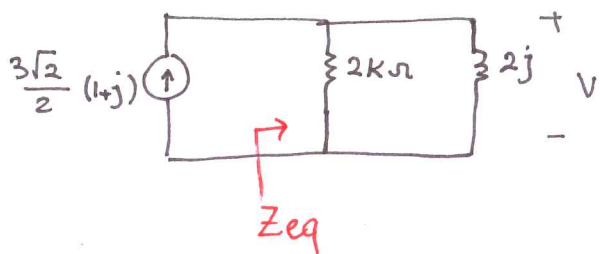
$$Z_L = j\omega L = j \times 4 \times \frac{1}{2} = 2j \Omega$$



$$v = I_s \cdot Z_{eq}$$

$$Z_{eq} = \frac{2k\Omega \cdot 2j \Omega}{2k\Omega + 2j\Omega} = \frac{2 \times 10^3 \times 2j}{2 \times 10^3 + 2j} \Omega$$

$$Z_{eq} = \frac{2j}{1 + 0.001j} \Omega$$

$$V = I_s \cdot Z_{eq} = \frac{3\sqrt{2}}{2} (1+j) \cdot \frac{2j}{1 + 0.001j} = \frac{3\sqrt{2}(-1+j)}{1 + 0.001j} \times \frac{1 - 0.001j}{1 - 0.001j}$$

$$= 3\sqrt{2} \frac{(-1+j)(1-0.001j)}{(1+10^{-6}) \approx 1} = 3\sqrt{2} \frac{-1 + 0.001j + j + 0.001}{1}$$

$$= 3\sqrt{2} (-0.999 + 1.001j) = -4.238 + 4.246j \text{ (V)} = 6 e^{j(2.35)} \text{ (V)}$$


$$v(t) = 6 \cos(4t + 2.35) \text{ (V)}$$

Problem 2.

$$I = \frac{V}{Z} = \frac{V}{R}$$

$$I = \frac{6e^{j(2.35)} \text{ V}}{2 \text{ k}\Omega} = 3e^{j(2.35)} \text{ mA} \Rightarrow i(t) = 3 \cos(4t + 2.35 \text{ rad}) \text{ mA}$$

Problem 3

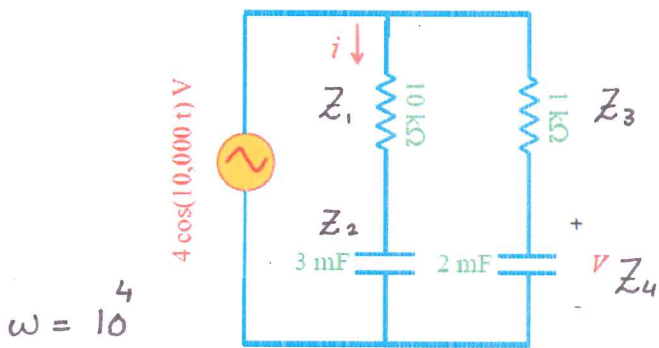

$$Z_1 = 10 \text{ k}\Omega$$


$$Z_2 = \frac{1}{j\omega C} = \frac{1}{j \times 10^4 \times 3 \times 10^{-3}} = \frac{1}{30j} = \frac{-j}{30} \Omega$$

$$Z_3 = 1 \text{ k}\Omega$$

$$Z_4 = \frac{1}{j\omega C} = \frac{1}{j \times 10^4 \times 2 \times 10^{-3}} = \frac{-j}{20} \Omega$$

Find $i(t)$ and $v(t)$. Hint: convert the voltage source into a phasor, then find the current and voltage phasors for the whole circuit, then convert back to the time dependent $i(t)$, $v(t)$.

$$V_s = 4 \angle 0^\circ \text{ V}$$

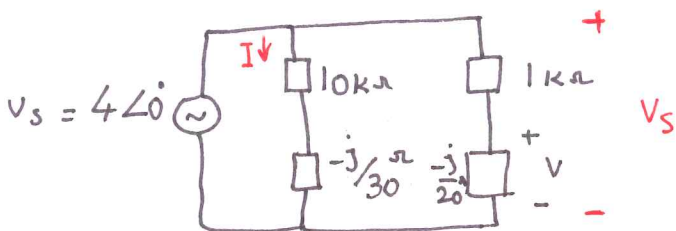

$$V = \frac{V_s \times Z_4}{Z_4 + Z_3}$$

$$V = \frac{4 \text{ V} \times \frac{-j}{20} \Omega}{1000 \Omega + \frac{-j}{20} \Omega} = \frac{4 \text{ V} \times \frac{-j}{20} \Omega}{1000 \Omega - \frac{j}{20} \Omega} = \frac{(j) \times 4}{(-5000 + \frac{j}{4}) \times 4} = \frac{4j}{-2000 + j}$$

$$V = \frac{4j}{-2000 + j} = \frac{4j(-2000 - j)}{(2000)^2 + 1^2} = \frac{-8000j + 4}{4000001 \approx 4000000} = \frac{-2000j + 1}{10^8} \text{ V}$$

-1.57 rad is almost equal to -90 degrees


$$V = \frac{2000 e^{-1.57j}}{10^8} \text{ V} = 0.2 e^{-1.57j} \text{ mV} \Rightarrow v(t) = 0.2 \cos(10^4 t - 1.57) \text{ mV}$$

$$I = \frac{V_s}{Z_1 + Z_2} = \frac{4 \text{ V}}{10 \text{ k}\Omega + \frac{-j}{30} \Omega} = \frac{4}{10^4 - \frac{j}{30}} \text{ A} = \frac{4(10^4 + \frac{j}{30})}{(10^4)^2 + (\frac{1}{30})^2} = \frac{4 \times 10^4 e^{j(3.33 \times 10^{-6})}}{10^8}$$

$$I = 0.4 e^{j(3.3 \times 10^{-6})} \text{ mA}$$

$$i(t) = 0.4 \cos(10^4 t + 3.3 \times 10^{-6}) \text{ mA}$$


Problem 4: Transfer function

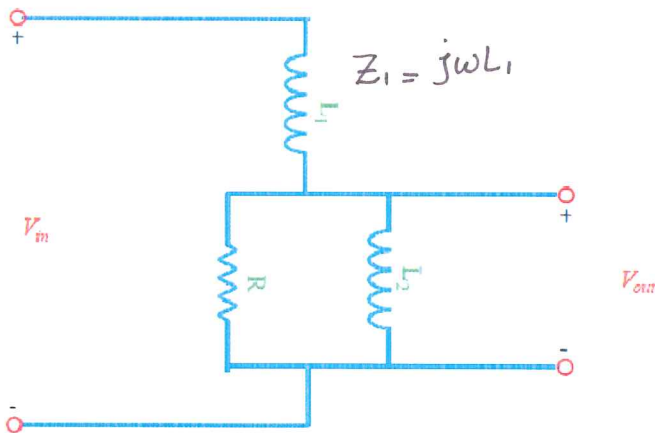

$$Z_2 = R \parallel j\omega L_2$$

$$Z_2 = \frac{R \cdot j\omega L_2}{R + j\omega L_2}$$

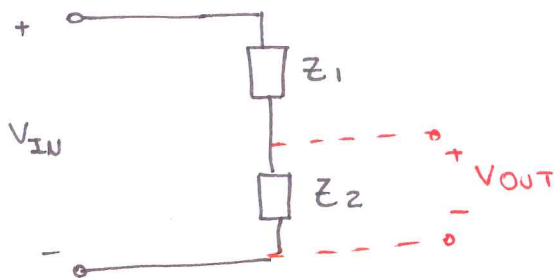Calculate $H(\omega)$ for this circuit. Sketch the magnitude of $H(\omega)$ vs. ω .



voltage divider :

$$V_{OUT} = \frac{V_{IN} \cdot Z_2}{Z_1 + Z_2}$$


$$V_{OUT} = \frac{V_{IN} \cdot \frac{R \cdot j\omega L_2}{R + j\omega L_2}}{\frac{R \cdot j\omega L_2}{R + j\omega L_2} + j\omega L_1} \Rightarrow \frac{V_{OUT}}{V_{IN}} = \frac{R \cdot j\omega L_2}{R \cdot j\omega L_2 + j\omega L_1 (R + j\omega L_2)}$$

$$H(\omega) = \frac{V_{OUT}}{V_{IN}} = \frac{j\omega R L_2}{j\omega R(L_2 + L_1) + j^2 \omega^2 L_1 L_2} = \frac{R L_2}{R(L_1 + L_2) + j\omega L_1 L_2}$$


$$|H(\omega)| = \left| \frac{R L_2}{R(L_1 + L_2) + j\omega L_1 L_2} \right| = \frac{R L_2}{\sqrt{R^2 (L_1 + L_2)^2 + \omega^2 L_1^2 L_2^2}}$$

$$\lim_{\omega \rightarrow 0} |H(\omega)| = \frac{R L_2}{R(L_1 + L_2)} = \frac{L_2}{L_1 + L_2} \Rightarrow \text{Low pass filter}$$

$$\lim_{\omega \rightarrow \infty} |H(\omega)| = 0$$

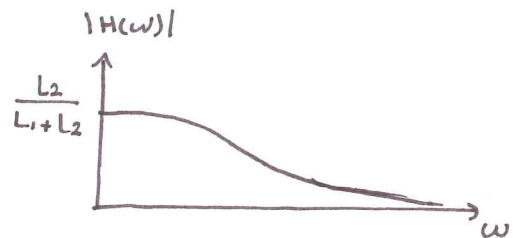

Problem 5: Transfer function

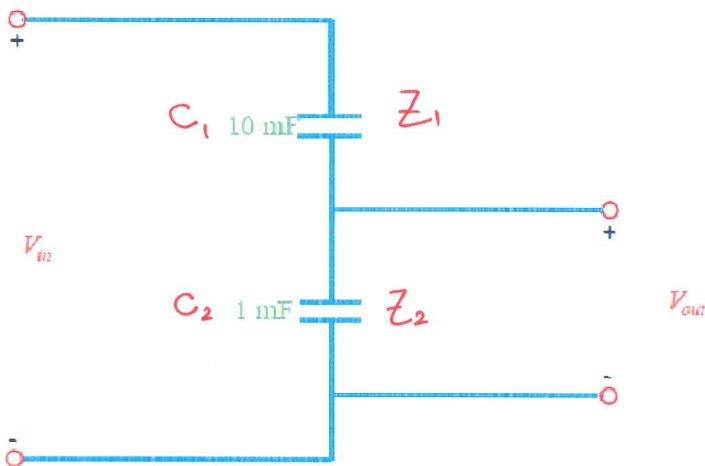


Calculate $H(\omega)$ for this circuit. Sketch the magnitude of $H(\omega)$ vs. ω .


$$V_{OUT} = \frac{V_{IN} \times Z_2}{Z_1 + Z_2}$$

$$H(\omega) = \frac{V_{OUT}}{V_{IN}} = \frac{Z_2}{Z_1 + Z_2} = \frac{\frac{1}{j\omega C_2}}{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}} = \frac{\frac{1}{C_2}}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{\frac{1}{1 \times 10^{-3}}}{\frac{1}{10 \times 10^{-3}} + \frac{1}{10^{-3}}} = \frac{10}{1 + 10}$$

$$H(\omega) = \frac{10}{11} \rightarrow |H(\omega)| = \frac{10}{11}$$

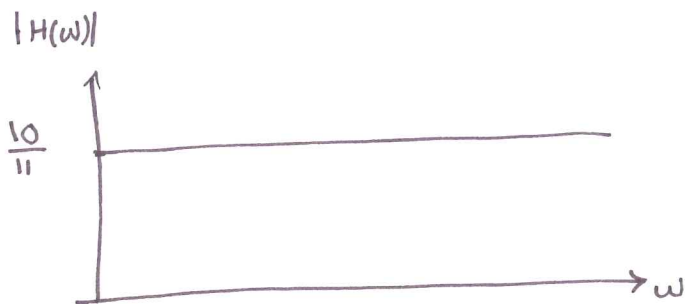

Problem 6: Band stop filter

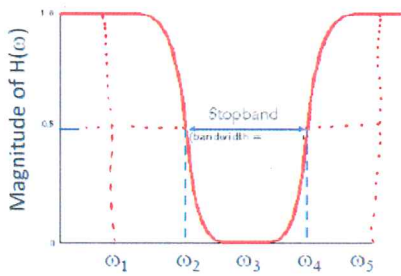

- A) Given $v(t) = 4 \cos(\omega_1 t + \pi/4)$ find $v_{out}(t)$.
 B) Given $v(t) = 3 \cos(\omega_2 t + \pi/2)$ find $v_{out}(t)$.
 C) Given $v(t) = 2 \cos(\omega_3 t + \pi/3)$ find $v_{out}(t)$.
 D) Given $v(t) = 2 \cos(\omega_4 t + \pi/2)$ find $v_{out}(t)$.
 E) Given $v(t) = 2 \cos(\omega_5 t + \pi/4)$ find $v_{out}(t)$.

Note: You cannot determine the phase of $v_{out}(t)$ so leave that as unknown in your answer.

$$A) \quad v(t) = 4 \cos(\omega_1 t + \pi/4) \Rightarrow \bar{V} = 4 e^{j\pi/4}$$

$$|H(\omega_1)| = 1 \Rightarrow \left| \frac{V_{out}}{V_{in}} \right|_{\omega=\omega_1} = 1 \Rightarrow |V_{out}| = |V_{in}| = 4$$

$$v_{out}(t) = 4 \cos(\omega_1 t + \phi) \quad (\phi \text{ is unknown})$$

$$B) \quad v(t) = 3 \cos(\omega_2 t + \frac{\pi}{2}) \Rightarrow \bar{V} = 3 e^{j\pi/2}$$

$$|V_{out}|_{\omega=\omega_2} = |H(\omega_2)| |V_{in}| = 0.5 \times 3 = 1.5 \Rightarrow v_{out}(t) = 1.5 \cos(\omega_2 t + \phi_2)$$

$$C) \quad v(t) = 2 \cos(\omega_3 t + \pi/3) \Rightarrow \bar{V} = 2 e^{j\pi/3}$$

$$|H(\omega_3)| = 0 \Rightarrow \frac{|V_{out}|}{|V_{in}|} = 0 \Rightarrow |V_{out}| = 0 \Rightarrow v_{out}(t) = 0$$

$$D) \quad v(t) = 2 \cos(\omega_4 t + \pi/2) \Rightarrow \bar{V} = 2 e^{j\pi/2}$$

$$|H(\omega_4)| = 0.5 \Rightarrow |V_{out}| = |H(\omega_4)| \cdot |V_{in}| = 0.5 \times 2 = 1$$

$$v_{out}(t) = \cos(\omega_4 t + \phi_3)$$

$$E) \quad v(t) = 2 \cos(\omega_5 t + \pi/4) \Rightarrow \bar{V} = 2 e^{j\pi/4}, \quad |H(\omega_5)| = 1 \Rightarrow |V_{out}| = 2$$

$$v_{out}(t) = 2 \cos(\omega_5 t + \phi_4)$$

