

# EECS 70A: Network Analysis

## Lecture 1

# Northeast Blackout 2003


What:

- 256 power plants down
- 55 million people affected

How did this happen?


ISAT GeoStar 45  
23:15 EST 14 Aug. 2003

# Power Networks

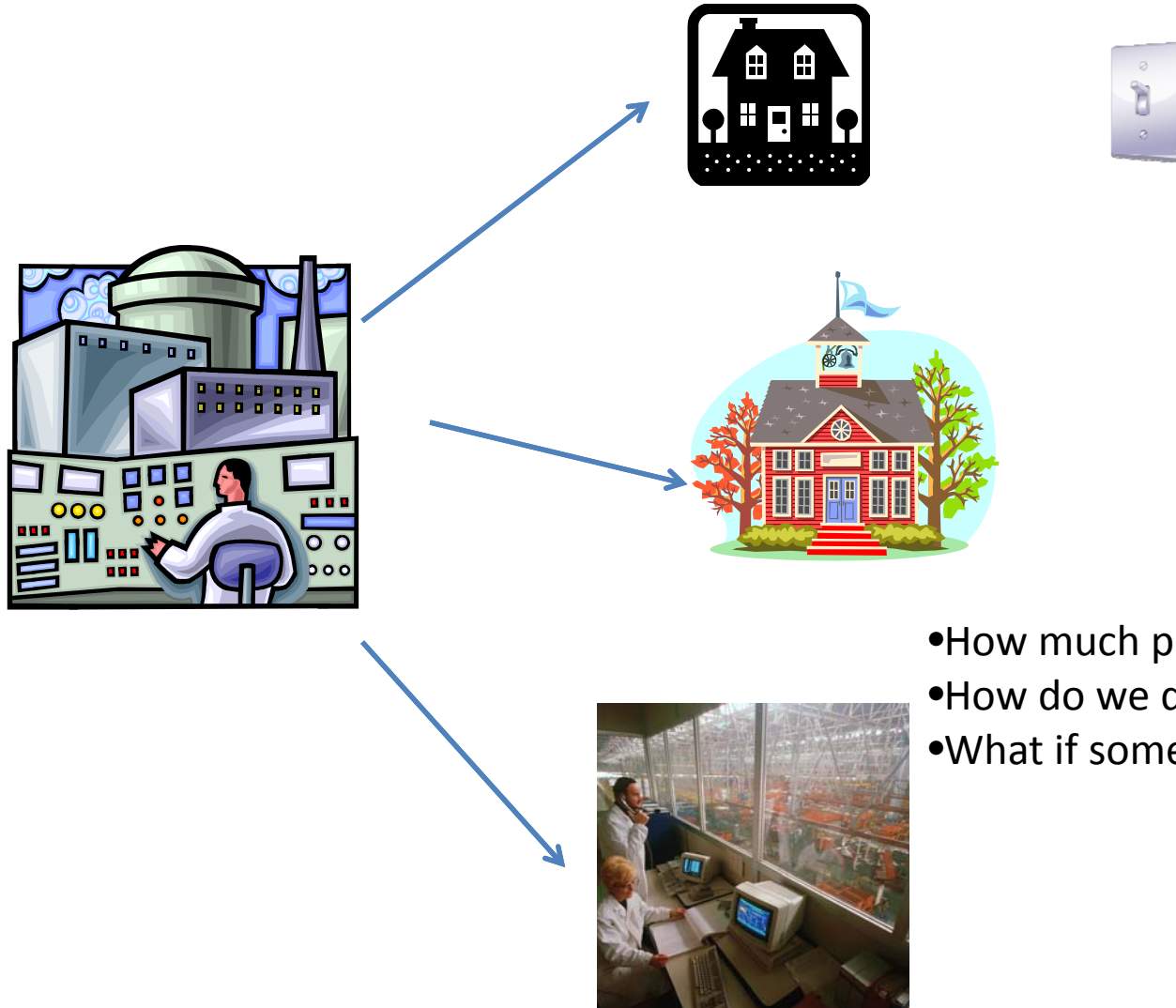

- How much power used?
- How do we quantify power?
- What if someone turns on one light?

# Digital circuits

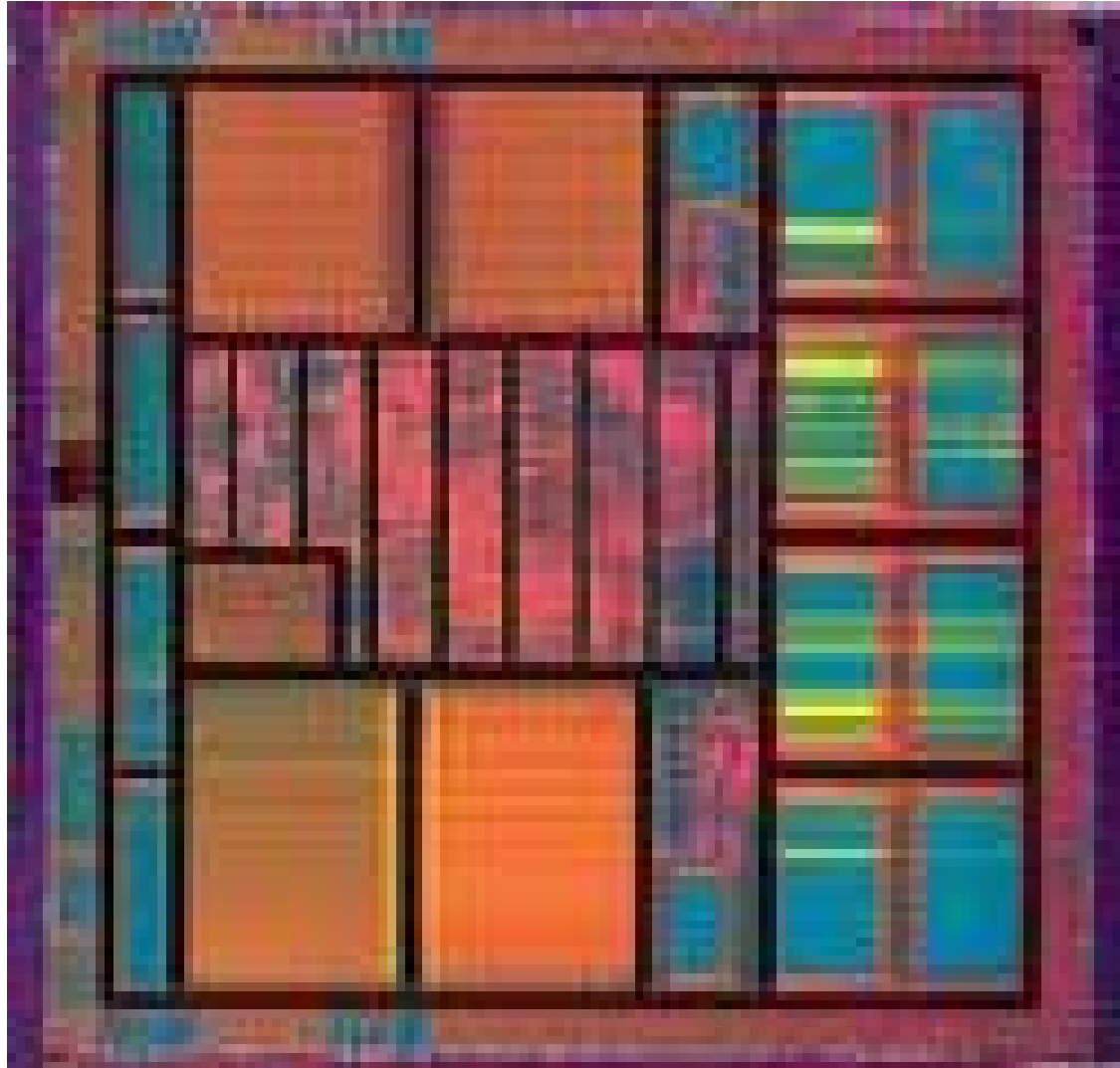

- How do we understand what every transistor is doing?
- There are *hundreds of millions...*

# Simplifications

Leon Charles Thevenin  
1857–1926



Edward Lawry Norton  
1898–1983



Ultimate problem solvers: Take a complex system, break it into its component parts:

***Network analysis***

# Current

*DEMO...*

Charge of an electron:


$$e = -1.6 \times 10^{-19} \text{ Coulomb [C]}$$

Current is flow of charge.

In a wire, charges are free electrons.

$$i = dq/dt$$
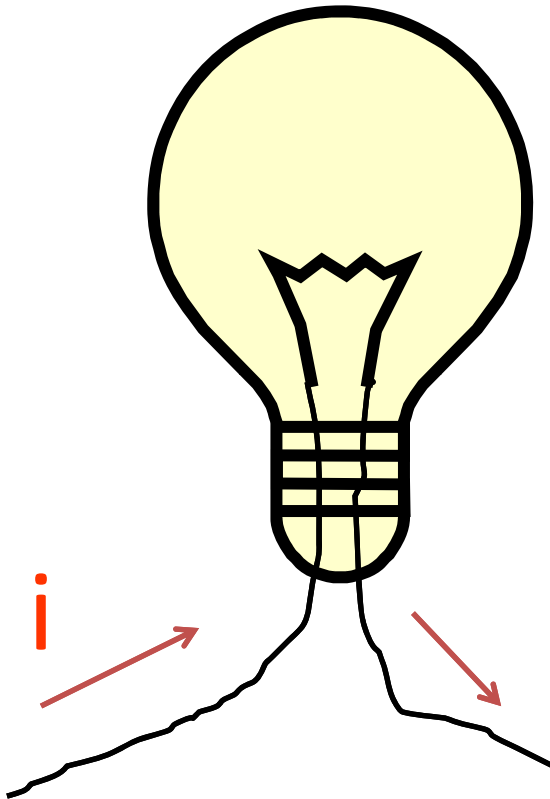
$$\text{Amperes [A]} = \text{Coulombs/second [C]/[s]}$$



# Examples


1 electron per second flows past a plane.

What is the current? (instructor)

10 A of current flows.


How many electrons per second flow past a plane? (students)

# Demo circuit: Current source

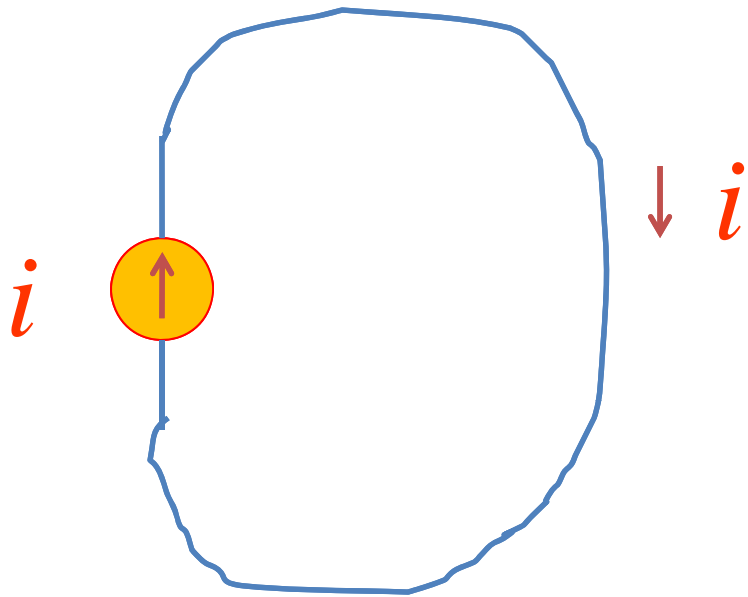

*DEMO...*

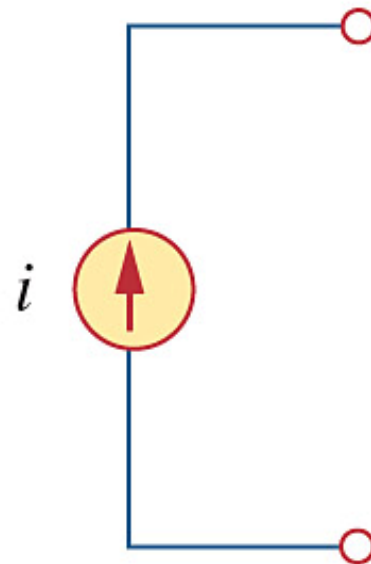Our first circuit element:  
*Current source*






# Voltage

Physically, how do we get electrons to move? Apply a force.

$$F = eE$$

$$\int_a^b E dx = V_{ab} = V_a - V_b = \Delta V$$

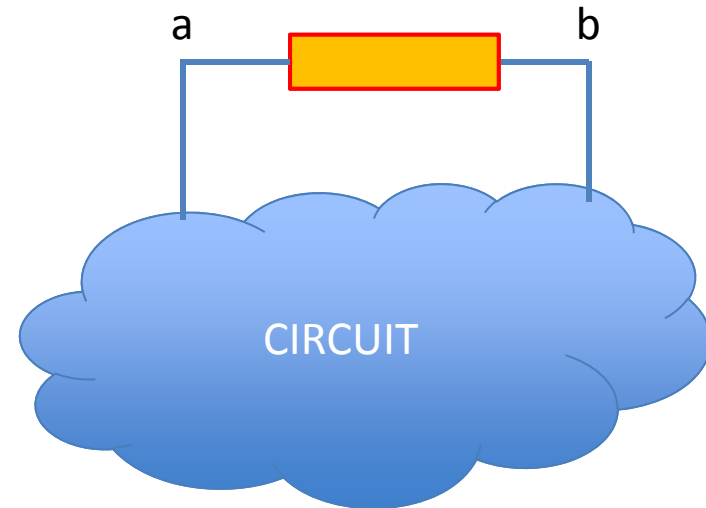$V_{ab} \neq 0 \Rightarrow$  electrons pushed  $a$  to  $b$ ,  
causing current to flow




E electric field: Volts/meter [V/m]

V voltage (aka potential difference): Volts [V]

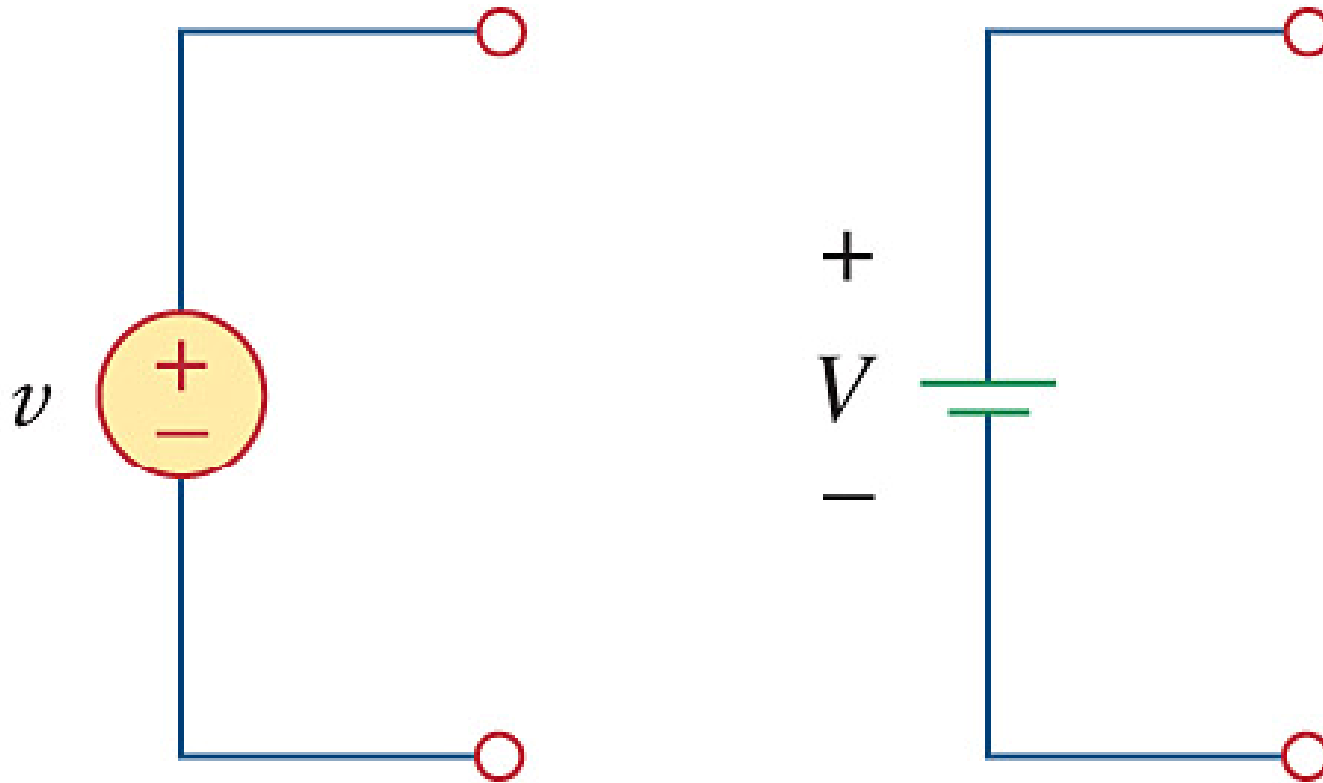
# Voltage source

Our next circuit element:  
*Voltage source*




Makes  $V_{ab}$  constant, regardless of how much current flows through it.

# Dependent sources

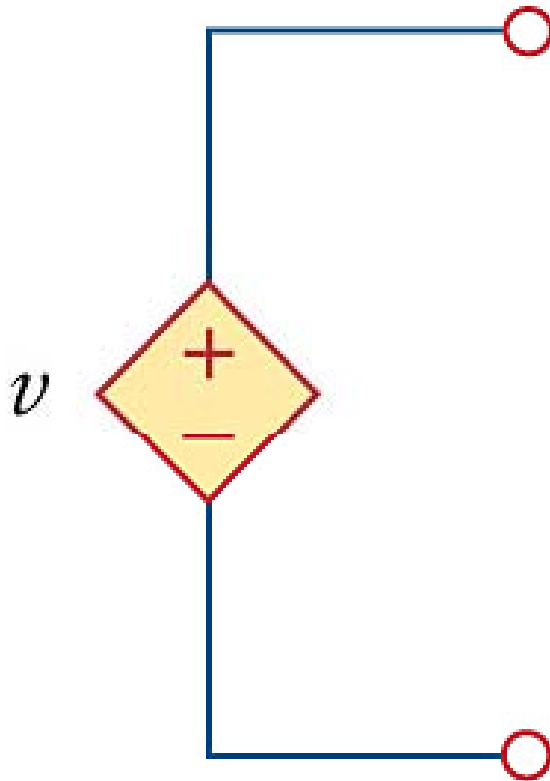


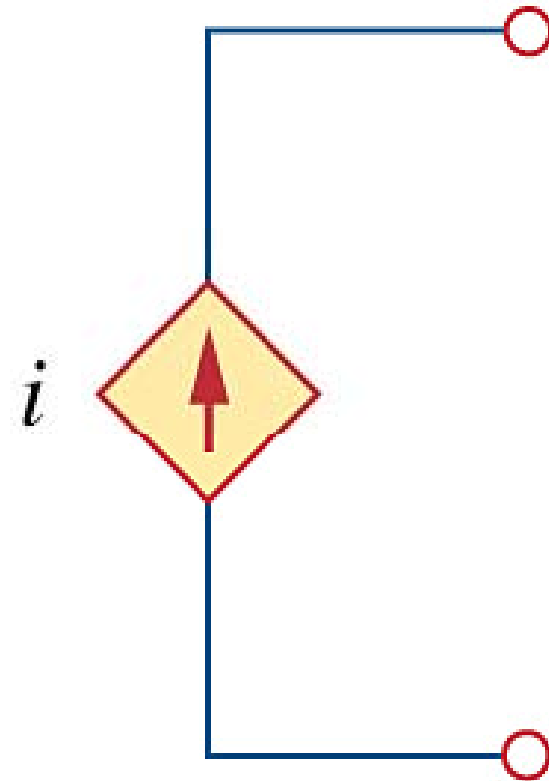Value of voltage is determined by something somewhere else in circuit.



Value of current is determined by something somewhere else in circuit.

# Circuit elements

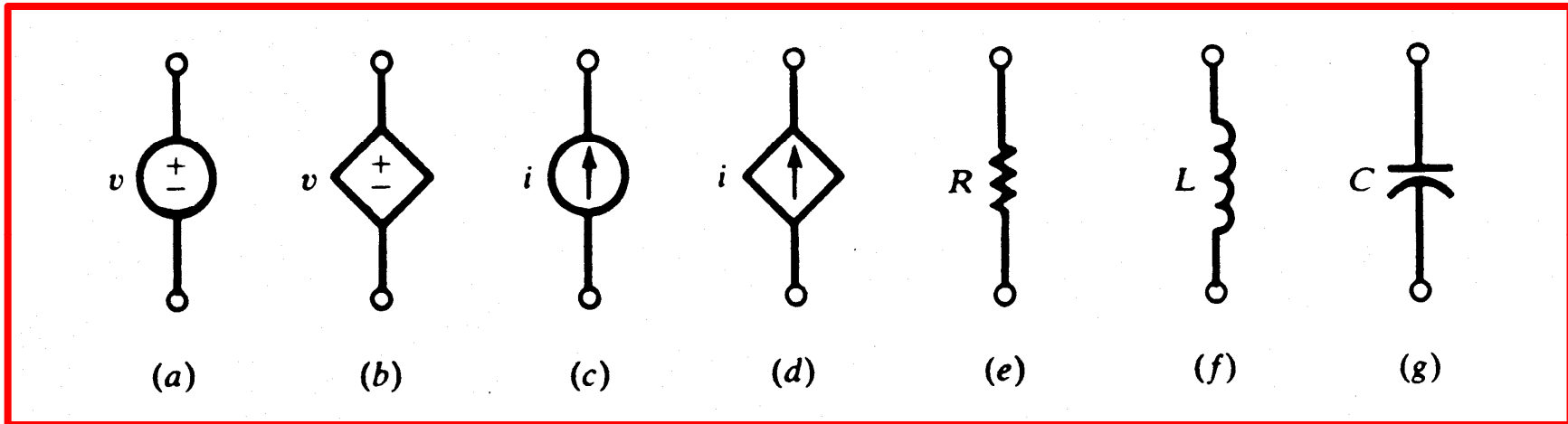


Independent sources

Dependent sources

- A dependent source is an active element in which the source quantity is controlled by another voltage or current.
- They have four different types: VCVS, CCVS, VCCS, CCCS. Keep in mind the signs of dependent sources.

# Power

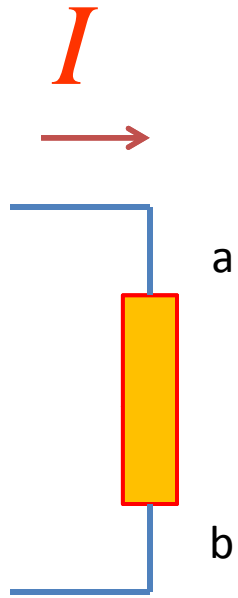


$$I \times V_{ab} = \text{power}$$

Watts [W] = Volt Amp [V-A]


Note: MKSA unit system:  
*Meters Kilogram Second Amp*

# Examples

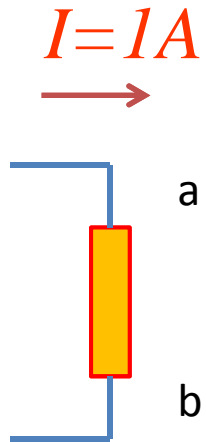

$$V_{ab} = 100 \text{ Volts}$$

$$P = ? \quad (\text{instructor})$$

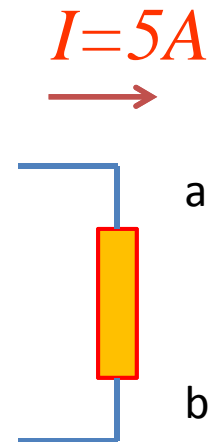


$$P = 10 \text{ W}$$

$$V_{ab} = ?$$

(students)

# Sign convention

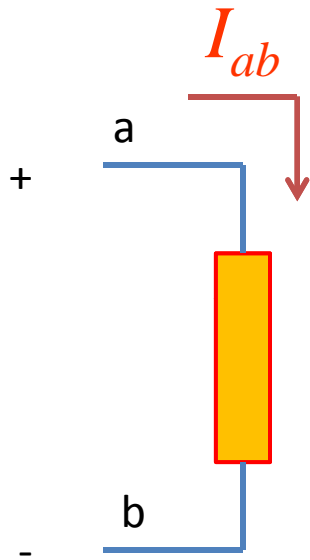

$V_{ab}$  positive  $\Rightarrow V_a > V_b$

$I_{ab}$  positive  $\Rightarrow$  current flows from a to b

$V_{ab}$  negative  $\Rightarrow V_a < V_b$

$I_{ab}$  negative  $\Rightarrow$  current flows from b to a

Define convention first, then solve problem.

$P > 0$  means power flowing into element (e.g. resistor)

$P < 0$  means power flowing out of element (e.g. battery)

# Example

$V = 120\text{ V}$  @ socket (assume DC).


Cost of electricity is 10 cents/kW-h

Day nothing, night 10 light bulbs on (100 W bulbs) for 1 hr.

What is monthly electric bill?  
(instructor)




# Topology

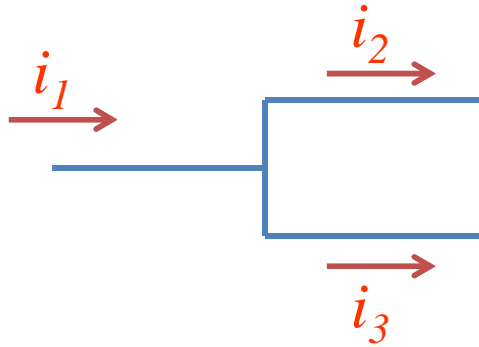


$$i_1 = i_2 + i_3$$

*Like water in a river...*

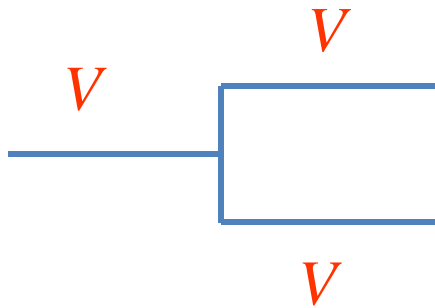

*Voltage same everywhere....  
Concept of a node*

# Example

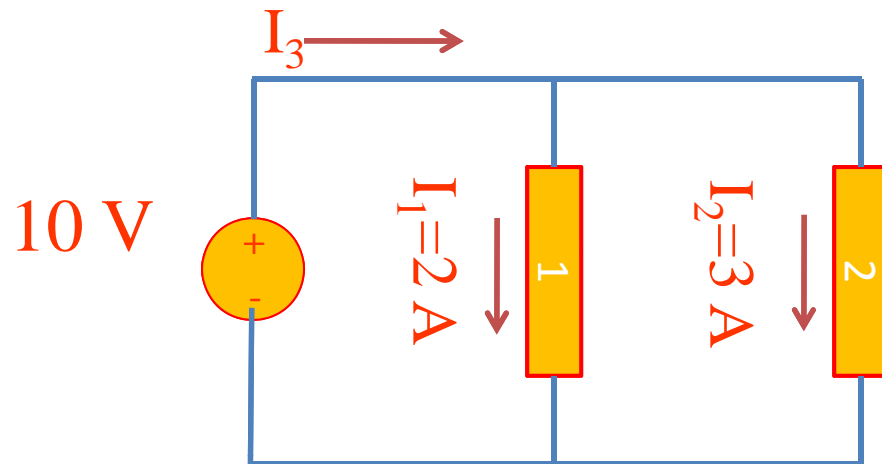

$$I_3 = ?$$


$$V_{\text{element 1}} = ?$$

$$V_{\text{element 2}} = ?$$

$$\text{Power supplied by source} = ?$$

(instructor)

# Example

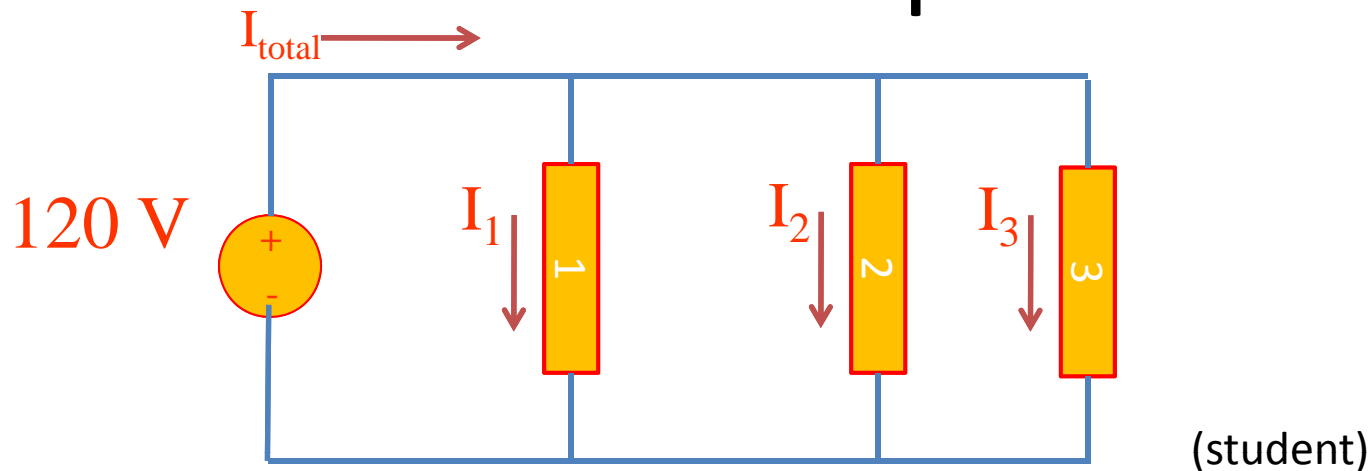


Three light bulbs (100 W each) on 1 hour/night. 120 V @ socket.

What is I per bulb?

What is  $I_{total}$  from supply?

What is bill?

# Power failure example

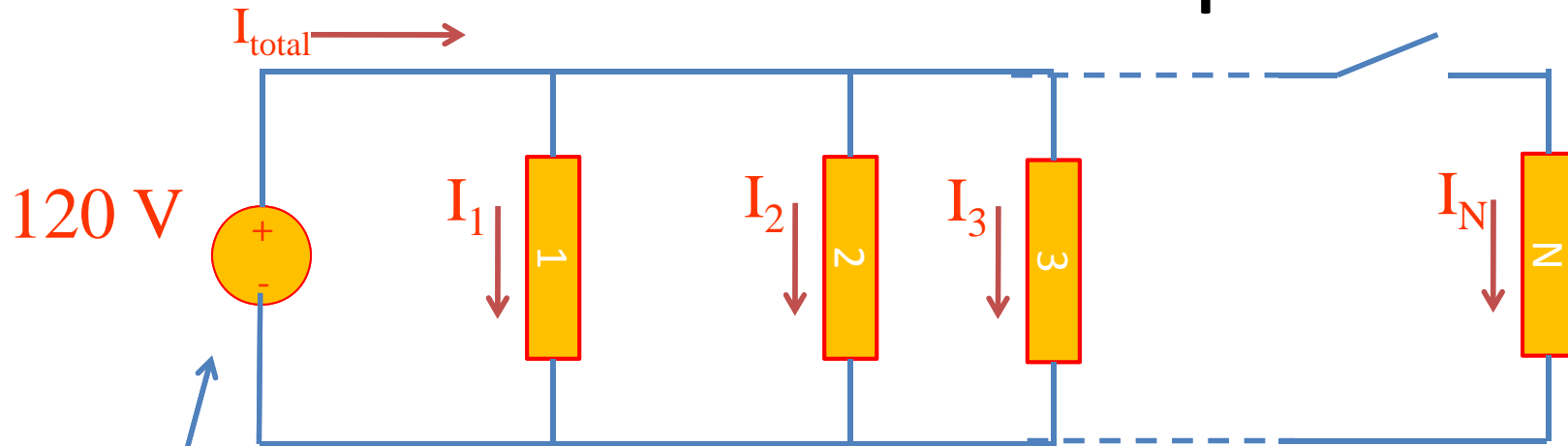

*DEMO...*

Generator will fail of power required  $> 1$  MW

How many light bulbs need to be turned on to damage the generator?