


Announcements:

1. PSpice is installed in ECT 123 and EH 1131.

EECS 70A: Network Analysis

Lecture 10

Capacitors

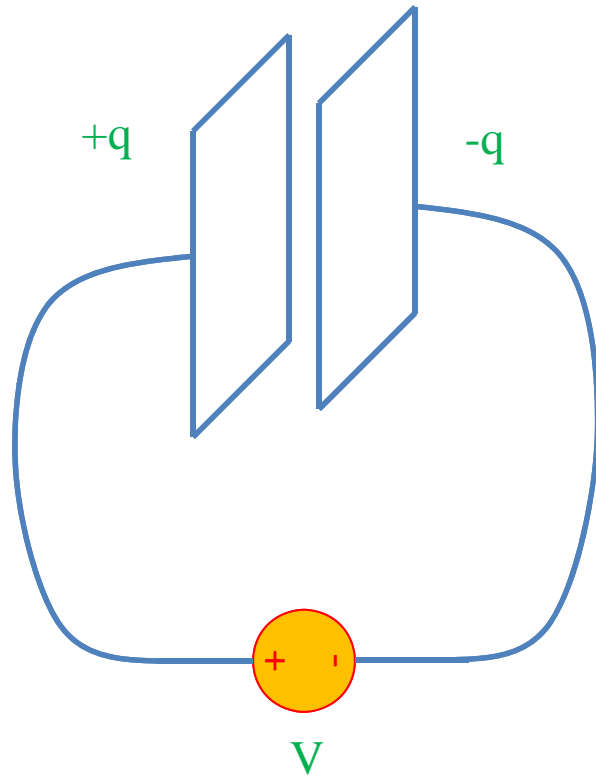

$$q = CV$$

$$C = \frac{\epsilon A}{d}$$

A=area
d=plate separation

Farads[F] = Coulombs/Volt [C]/[V]


$$\epsilon_0 = 8.85 \times 10^{-12} \text{ F / m}$$

$$\epsilon = \kappa \epsilon_0$$

Dielectric constant:



$$\kappa = 3.9 \text{ SiO}_2$$

$$\kappa = 25 \text{ HfO}_2$$

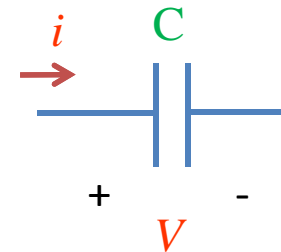

“High-K Dielectric”

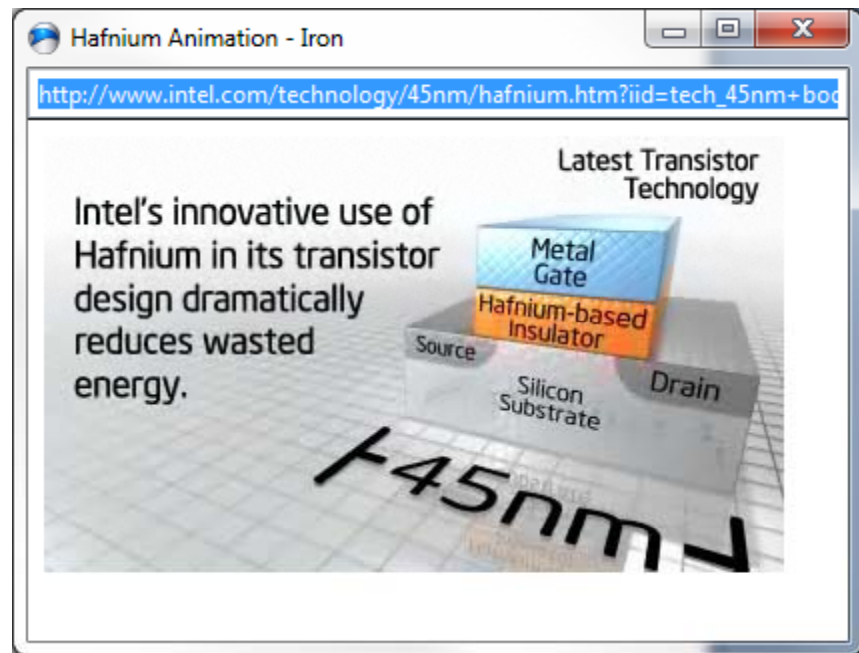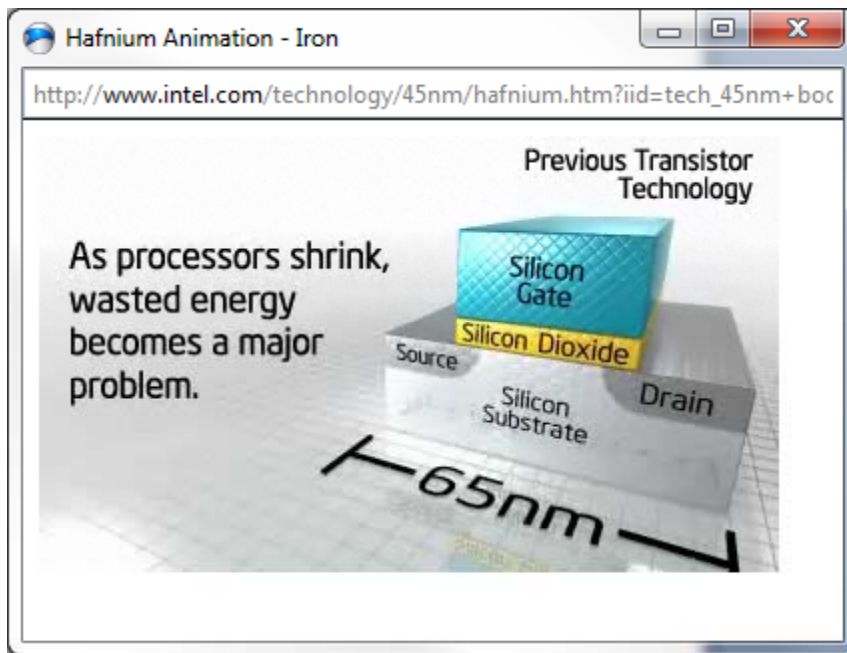http://www.intel.com/technology/45nm/hafnium.htm?iid=tech_45nm+body_animation_hafnium



Time dependence

$$q = CV \quad i = \frac{dq}{dt} = C \frac{dV}{dt}$$

q, V, i can depend on time !

Implicit:


$$q(t) = CV(t) \quad i(t) = \frac{dq(t)}{dt} = C \frac{dV(t)}{dt}$$

Will not always write (t), but it is assumed from now on.



$$i(t) = C \frac{dV(t)}{dt} \Rightarrow V(t) = \frac{1}{C} \int i(t) dt$$
$$\Rightarrow q(t) = \int i(t) dt$$

Example Capacitor Problem

Find $V(t)$, $q(t)$

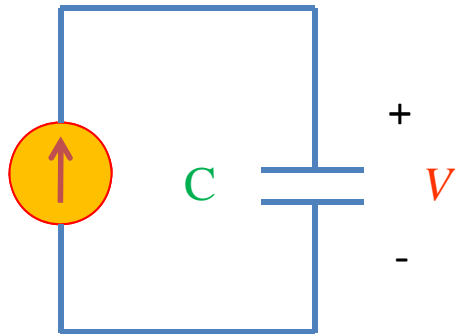


One-bit memory

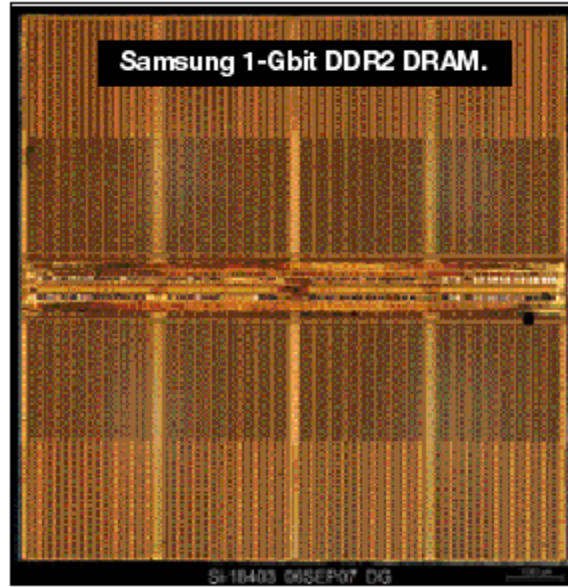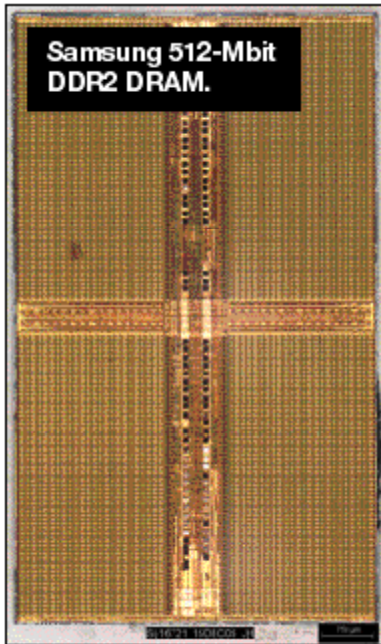

Typical dimensions:
0.1 micron x 0.1 micron area
10 nm thickness.
What is C?



http://i.cmpnet.com/eet/news/07/11/DC1502_UTH_samsung.gif

1 Bit Read/Write

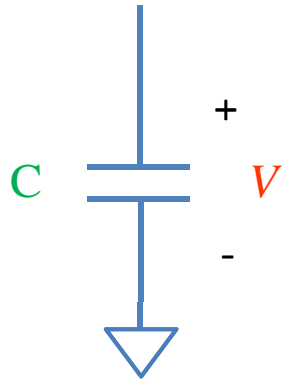


Example Problem #2

(Students): Find $i(t)$, $q(t)$

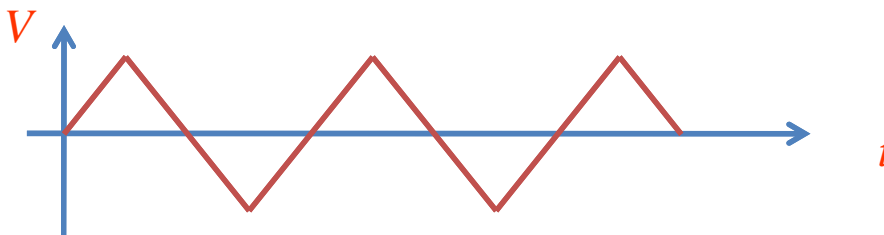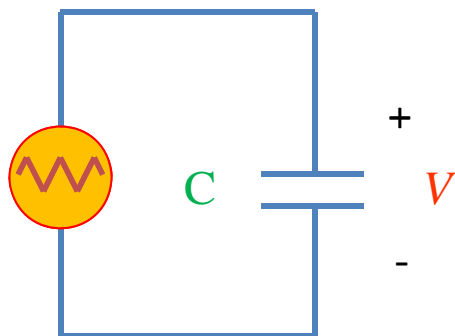

RC circuit


Find $V(t)$, $q(t)$, $i(t)$

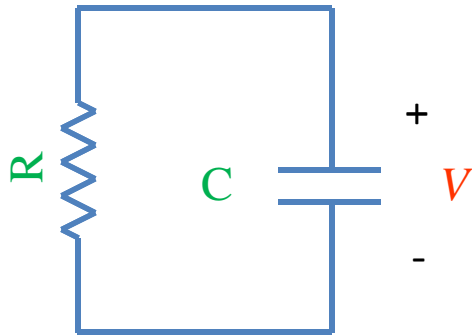


DRAM vs. SRAM

Example Capacitor Problem #2


Find $V(t)$, $q(t)$

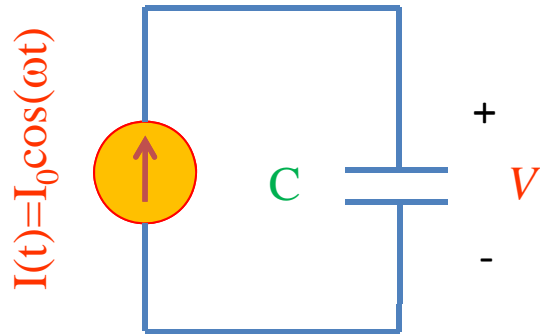

Parallel Capacitors

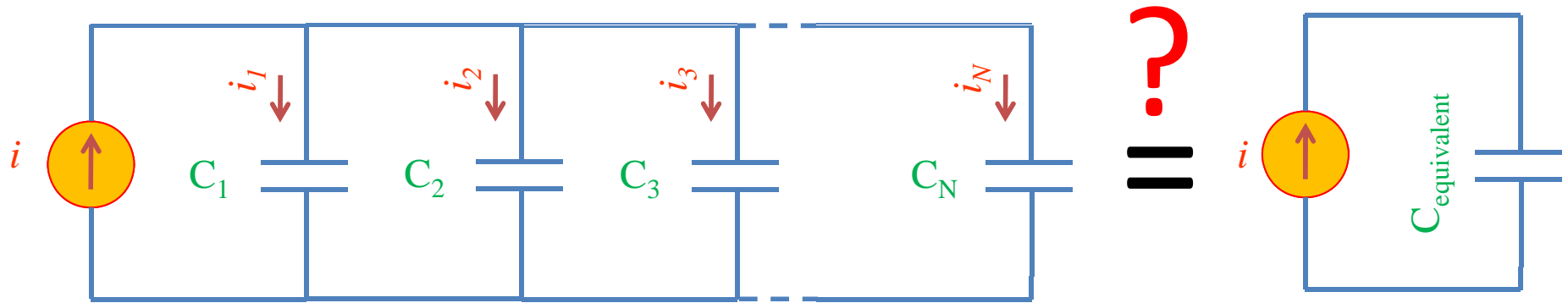


Series Capacitors

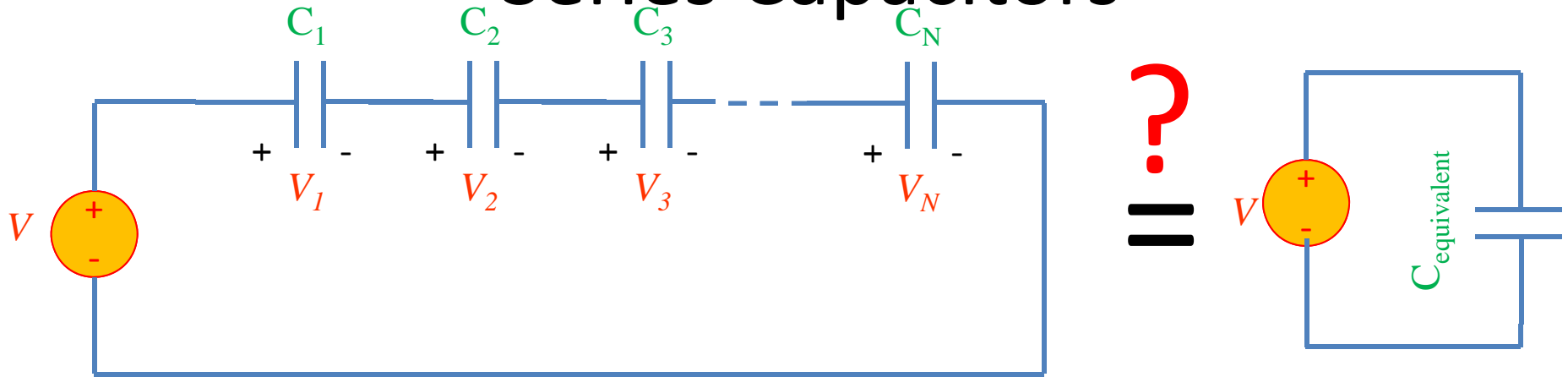


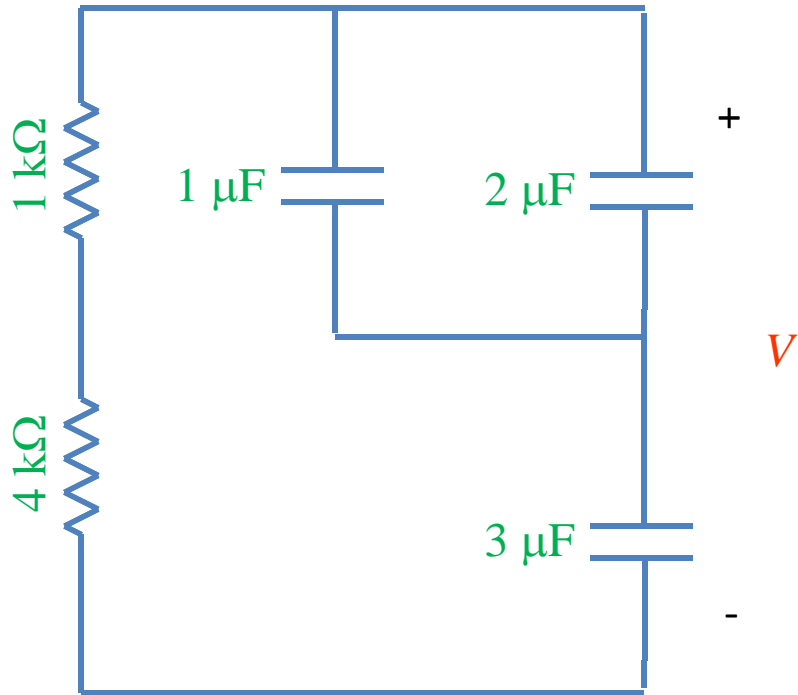Example problem #4

(Students) Find $V(t)$, given that $V(t=0) = 5$ Volts



Inductors

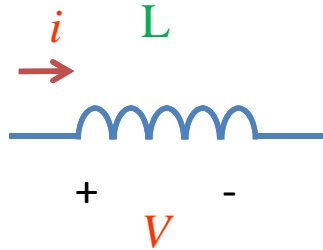

$$L = \frac{N^2 \mu A}{l}$$

A=area

l=wire length

N = # of turns



$\mu = 4 \pi 10^{-6}$ H/m

$$V = L \frac{di}{dt}$$


Henry[H]

$$V = L \frac{di}{dt} \Rightarrow i(t) = \frac{1}{L} \int V(t) dt$$

Series Inductors

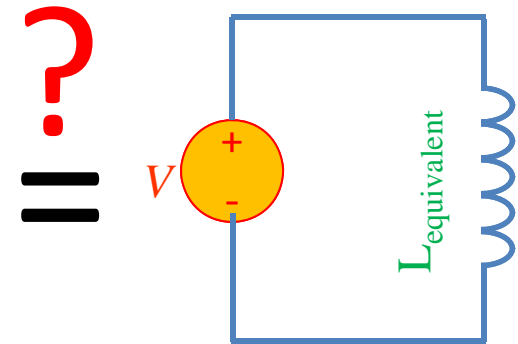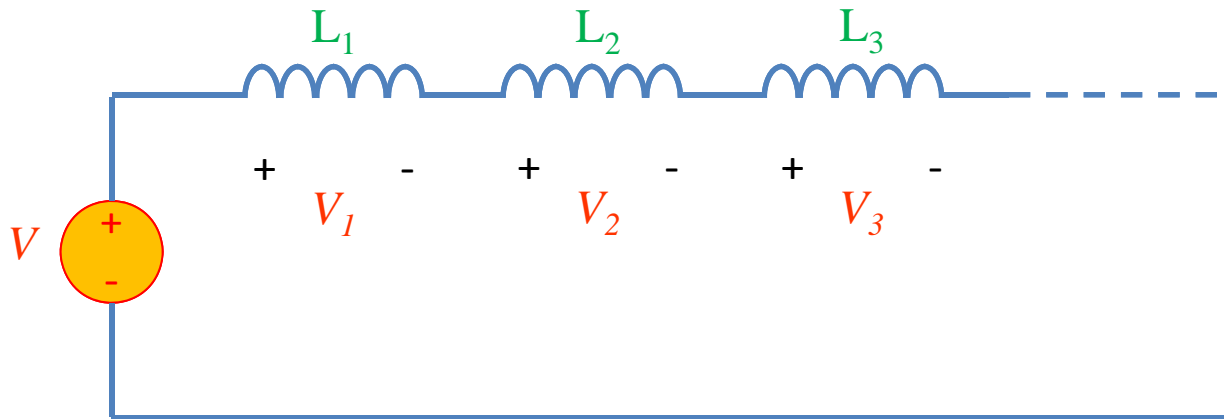


Parallel Inductors

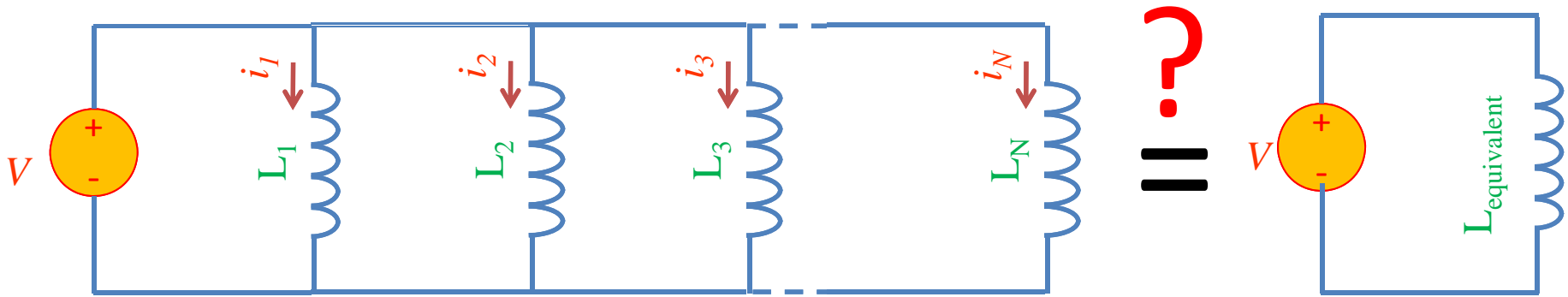



Example Inductor Problem

(Students): Find $V(t)$.

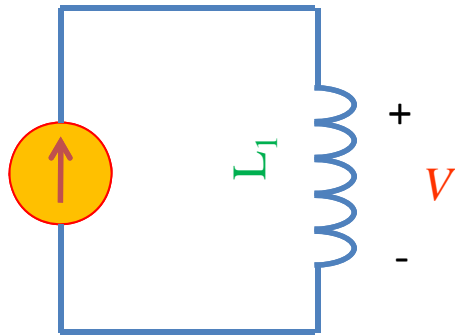


Example Inductor Problem #2

(Students): Find $i(t)$

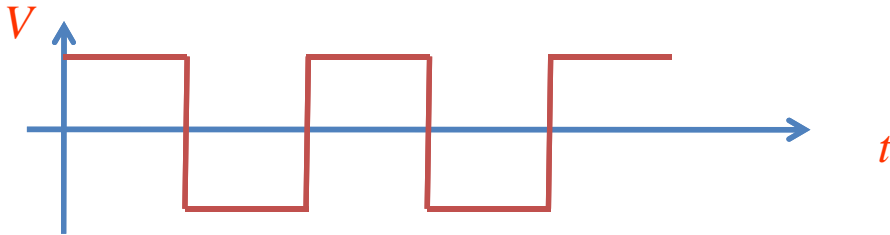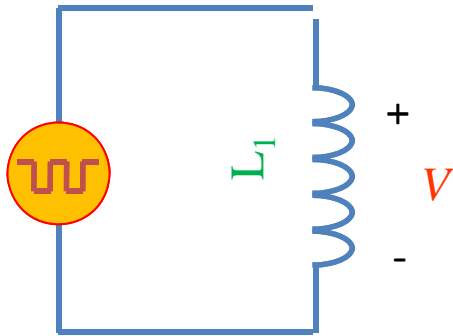


Example Inductor Problem #3

Find $V(t)$

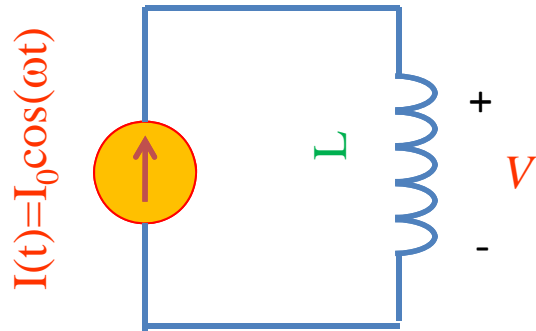


LR circuit

Find $V(t)$, $i(t)$

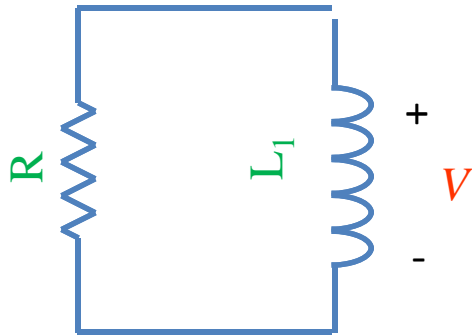


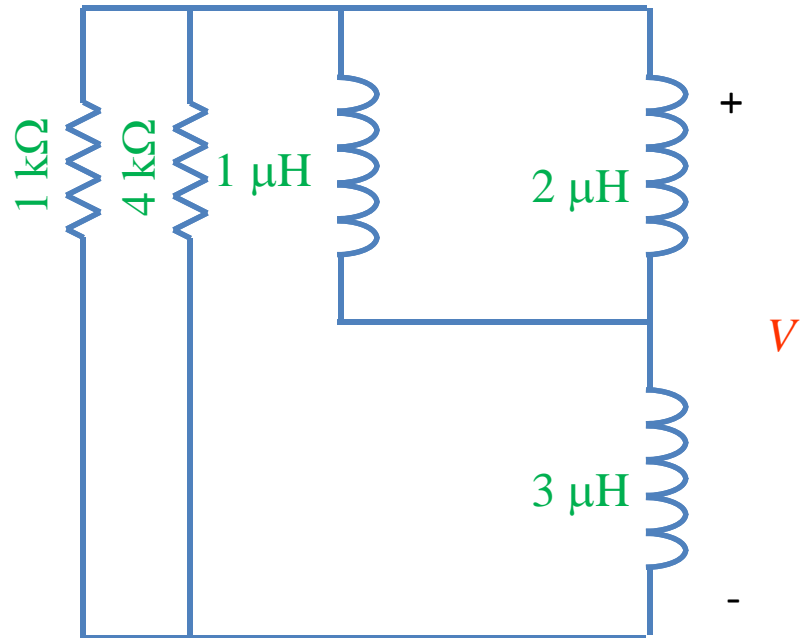Example LR problem

(Students) Find $V(t)$, given that $V(t=0) = 5$ Volts



Power

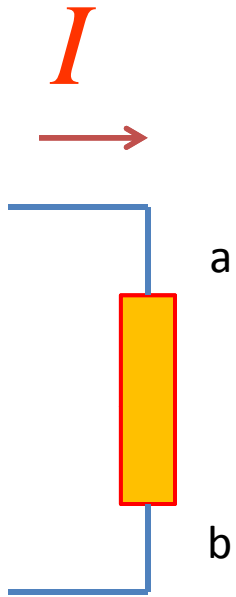

$$I \times V_{ab} = \text{power}$$


Watts [W] = Volt Amp [V-A]

Note: MKSA unit system:
Meters Kilogram Second Amp

Resistor:
Energy lost to heat...

Inductor or capacitor:
Energy **STORED** and can be recovered...

Energy stored

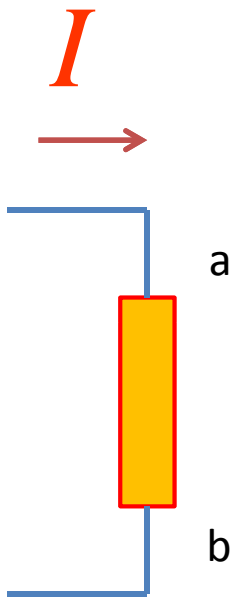

$$I \times V_{ab} = \text{power}$$

Energy:

$$W = \int P dt = \int I \cdot V dt$$




Capacitor stored energy:

$$\int I \cdot V dt = \int C \frac{dV}{dt} \cdot V dt = \frac{1}{2} CV^2 = \frac{Q^2}{2C}$$

Inductor stored energy:

$$\int I \cdot V dt = \int I \cdot L \frac{dI}{dt} dt = \frac{1}{2} LI^2$$

Symbol library

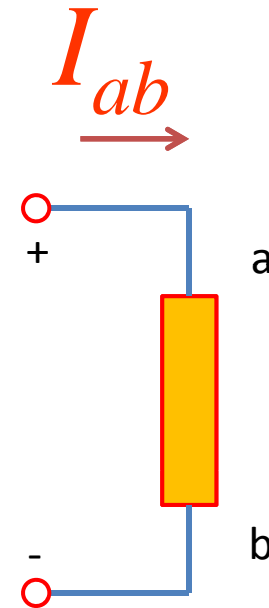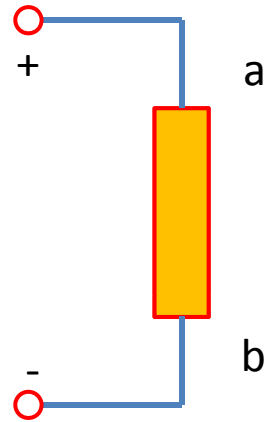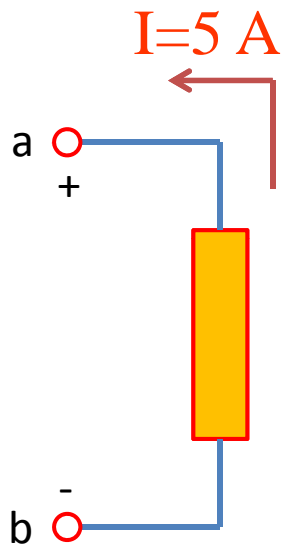

Symbol library

