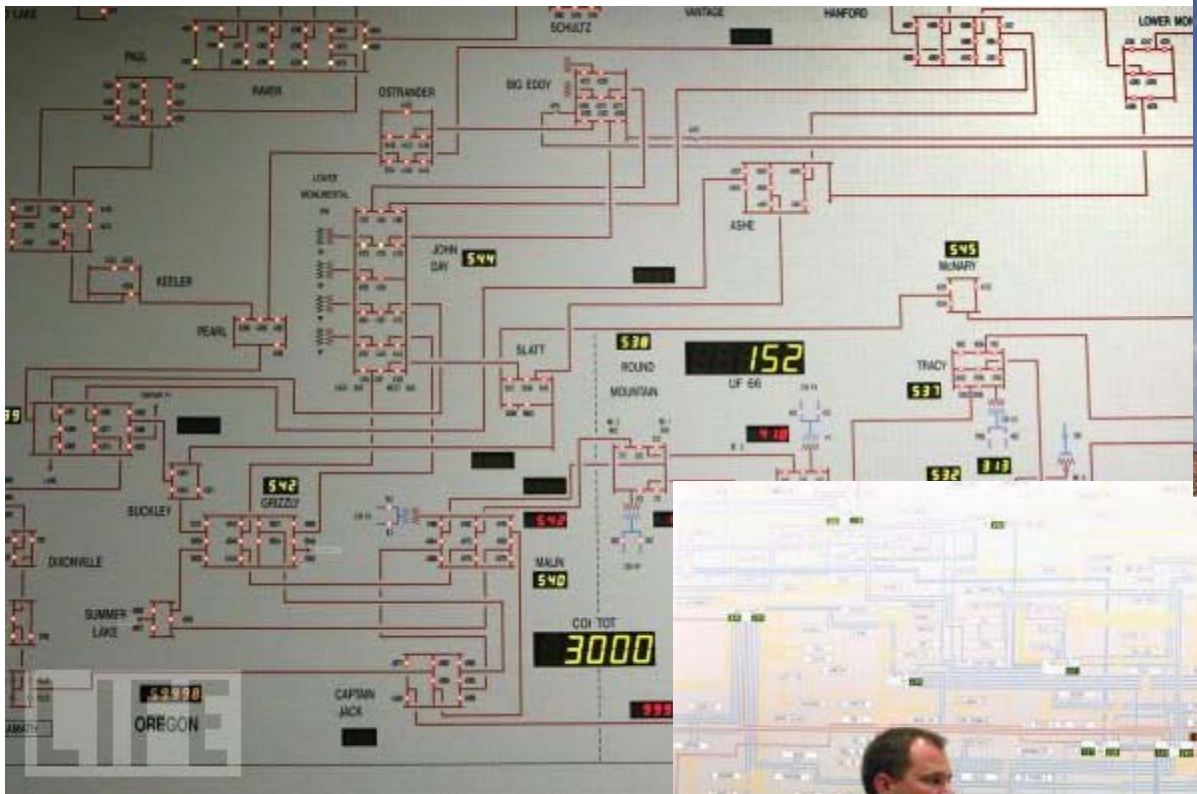


Announcements:

1. HW4 due Friday this week


EECS 70A: Network Analysis

Lecture 10



Example Capacitor Problem #2

Find $V(t)$, $q(t)$

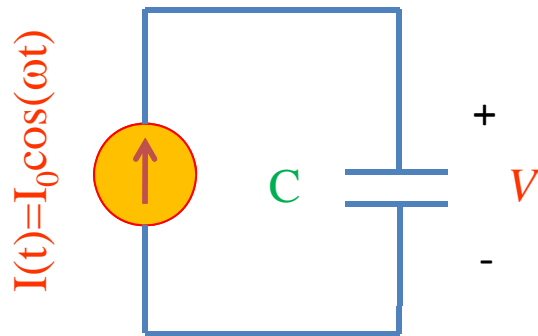

$$j \equiv \sqrt{-1} \quad q = CV \quad i = C \frac{dv}{dt}$$

$$V(t) = \frac{1}{C} \int i(t) dt \quad V = \frac{1}{C} \int i(t) dt$$

$$= \frac{1}{C} \int I_0 \cos(\omega t) dt = \frac{I_0}{C} \sin(\omega t)$$

$$I(t) = \text{Re} [I_0 e^{j\omega t}]$$

why? b.c.
because

Euler

$$e^{j\theta} = \cos\theta + j\sin\theta$$

$$z = x + jy$$

$$\text{Re}[z] = x$$

$$\rightarrow = \text{Re} [I_0 (\cos(\omega t) + j \sin(\omega t))] = I_0 \cos(\omega t)$$

$$V(t) = \frac{1}{C} \int \text{Re} [I_0 e^{j\omega t}] dt = \frac{I_0}{C} \text{Re} \left[\int e^{j\omega t} dt \right]$$

$$= \text{Re} \left[\frac{I_0}{C} \frac{1}{j\omega} e^{j\omega t} \right] = \text{Re} \left[\frac{1}{j\omega C} I_0 e^{j\omega t} \right]$$

phasor

$$\int e^{j\omega t} dt =$$

$$u = j\omega t$$

$$du = j\omega dt \Rightarrow dt = \frac{1}{j\omega} du$$

$$= \int e^u \frac{1}{j\omega} du = \frac{1}{j\omega} \int e^u du = \frac{1}{j\omega} e^u = \frac{1}{j\omega} e^{j\omega t}$$

$$\int e^u du = e^u$$

Phasors

$$I(t) = \text{Re} \left[\underbrace{I_0 e^{j\omega t}}_{\text{CURRENT PHASOR}} \right]$$

$$V(t) = \text{Re} \left[\underbrace{\frac{1}{j\omega C} I_0 e^{j\omega t}}_{\text{VOLTAGE PHASOR}} \right]$$


Voltage Phasor V

Current Phasor I

For a capacitor we have $V = I \frac{1}{j\omega C}$


Can apply KCL, KVL, nodal/mesh anal, "impedance"
Norton, Thev. to cap. circuits if we use
phasors.

Parallel Capacitors

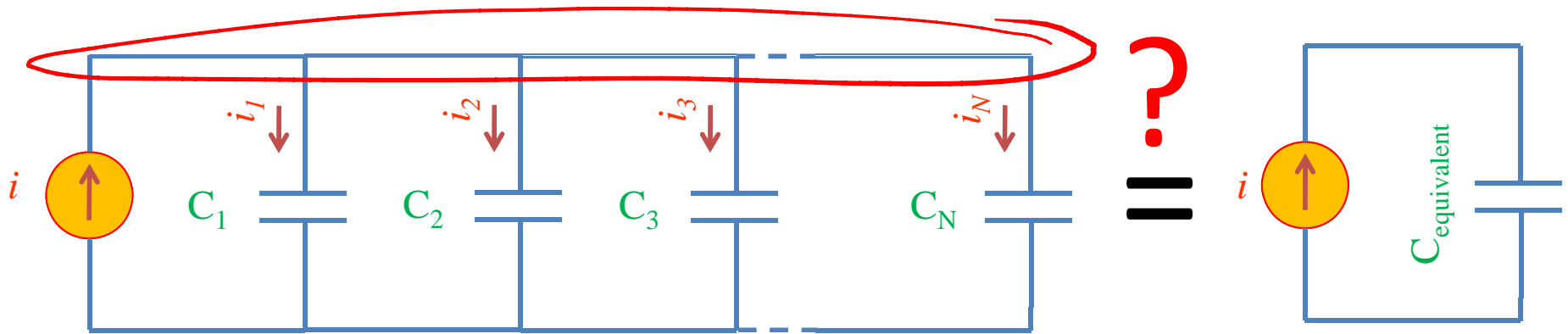

$$\begin{aligned}
 i &= i_1 + i_2 + \dots + i_N \\
 i_1 &= C_1 \frac{dV}{dt} \quad i_2 = C_2 \frac{dV}{dt} \quad \dots \quad \text{SAME } V \\
 i &= C_1 \frac{dV}{dt} + C_2 \frac{dV}{dt} + \dots + C_N \frac{dV}{dt} \\
 &= \frac{dV}{dt} \left[\sum_{k=1}^N C_k \right] \\
 & \quad \quad \quad \left. \vphantom{\sum_{k=1}^N C_k} \right] C_{eq} \\
 C_{eq} &= \sum_{k=1}^N C_k
 \end{aligned}$$

Series Capacitors

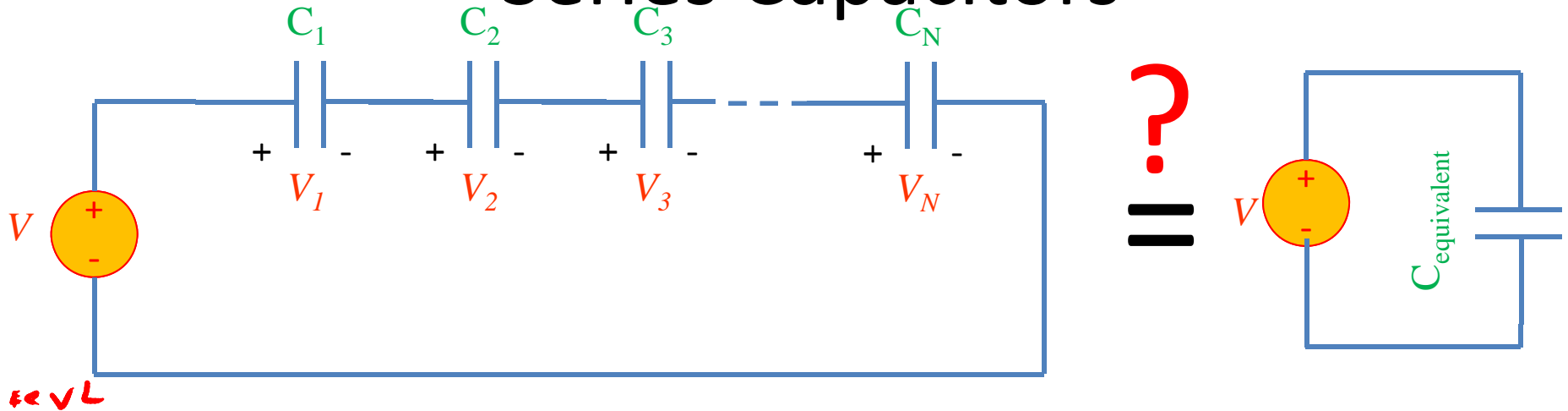

EEVL

$$V = V_1 + V_2 + \dots + V_N$$

$$V_1 = \frac{1}{C_1} \int i dt \quad V_2 = \frac{1}{C_2} \int i dt \quad \dots \quad \text{same } i$$


$$V = \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt + \dots + \frac{1}{C_N} \int i dt$$

$$= \int i dt \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right)$$


$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$

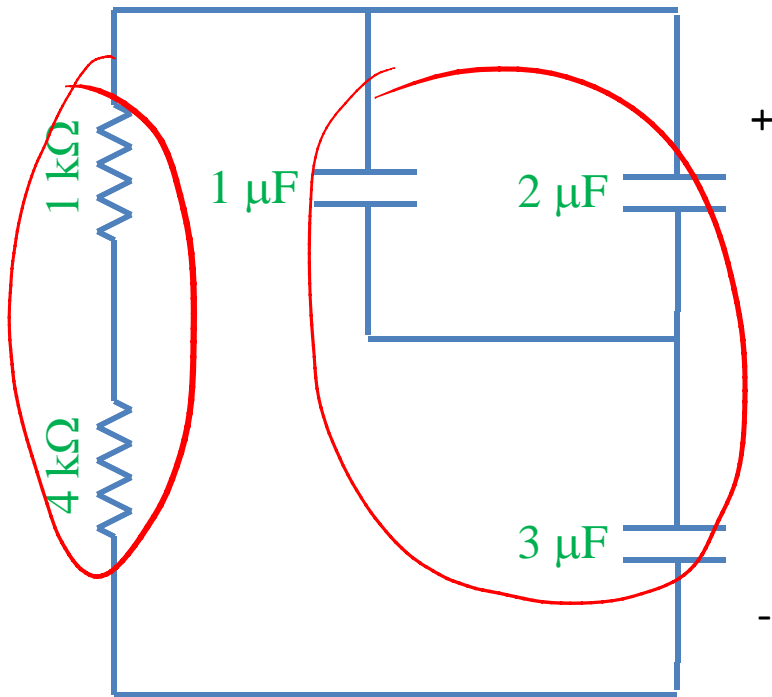Example problem #4 $V_c = V(t=0)e^{-t/RC}$

(Students) Find $V(t)$, given that $V(t=0) = 5$ Volts



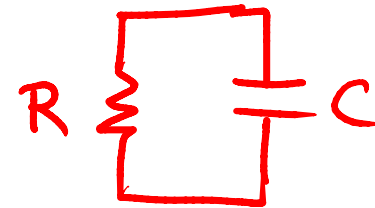
$$\begin{aligned} N &= 10^{-6} \\ K &= 10^3 \end{aligned}$$




$$V(t) = 5V e^{-t/5000 \times \frac{3}{2} 10^{-6} S}$$

$$R_{eq} = (4+1) k \Omega$$

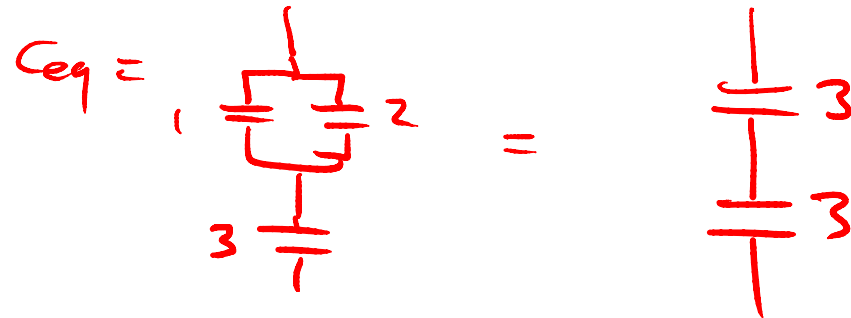

$$= \frac{1}{\frac{1}{3} + \frac{1}{3}} = \frac{3}{2} \mu F$$

Inductors

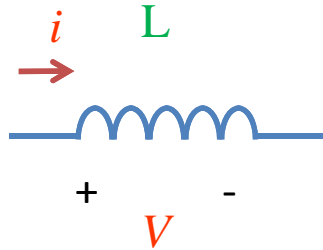

$$L = \frac{N^2 \mu A}{l}$$

A=area

l=wire length

N = # of turns

$\mu = 4 \pi 10^{-6}$ H/m

$$V = L \frac{di}{dt}$$


Henry[H]

compare $q = CV$

$$i = C \frac{dV}{dt}$$

$$V = L \frac{di}{dt} \Rightarrow i(t) = \frac{1}{L} \int V(t) dt$$

Series Inductors

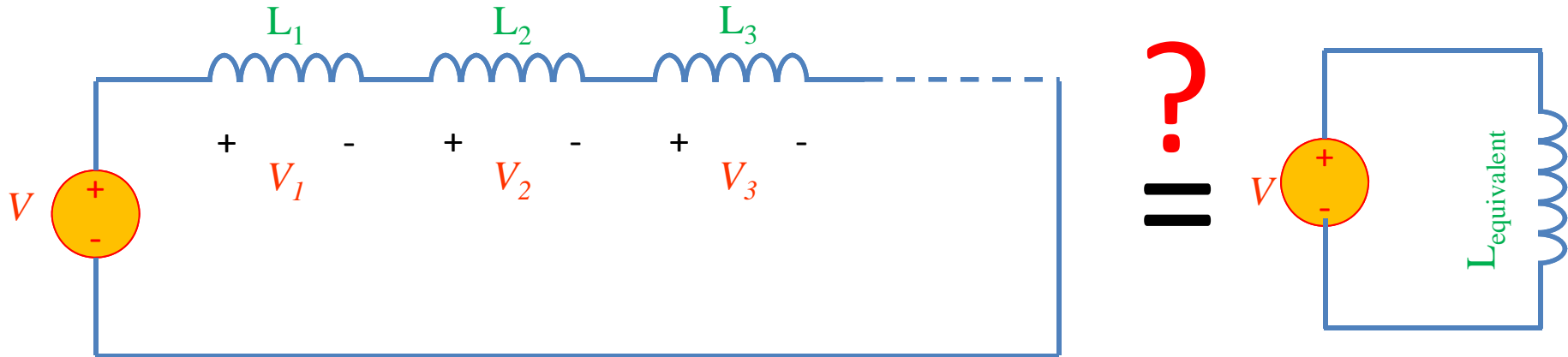

KVL $V = V_1 + V_2 + \dots + V_N$


$V_1 = L_1 \frac{di}{dt}$ $V_2 = L_2 \frac{di}{dt}$... i same

$$V = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots = \frac{di}{dt} (L_1 + L_2 + \dots + L_N)$$

L_{eq}

$$L_{eq} = L_1 + L_2 + \dots + L_N$$

Parallel Inductors

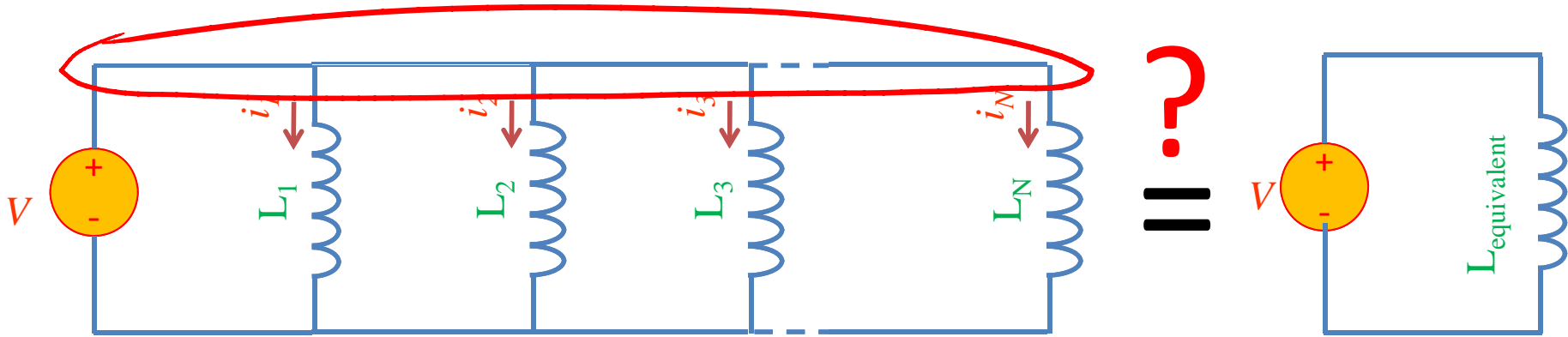

KCL $i = i_1 + i_2 + \dots + i_N$

$$i_1 = \frac{1}{L_1} \int v dt \quad i_2 = \frac{1}{L_2} \int v dt \quad \dots \quad \underline{\text{same } v}$$

$$i = \frac{1}{L_1} \int v dt + \frac{1}{L_2} \int v dt + \dots$$


$$= \int v dt \left[\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right]$$

$\underbrace{\hspace{10em}}_{\frac{1}{L_{eq}}}$


$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$

Example Inductor Problem

(Students): Find $V(t)$.


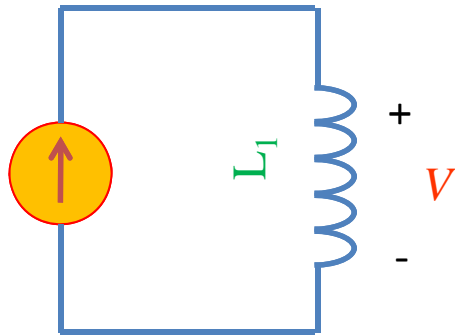


$$v = L \frac{di}{dt}$$

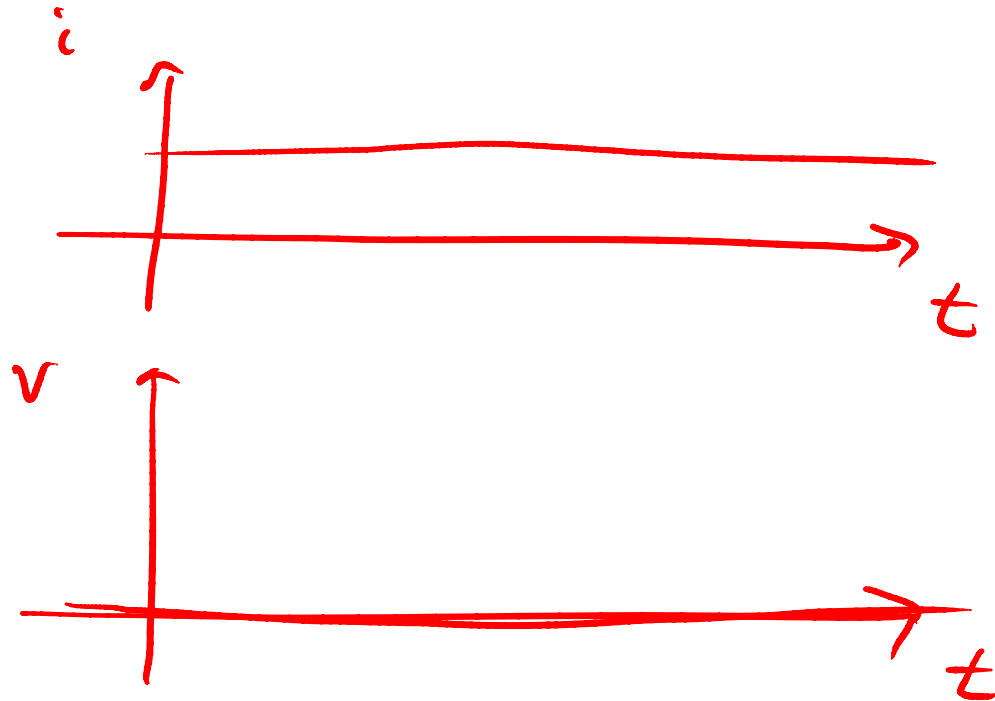

Example Inductor Problem #2

(Students): Find $i(t)$

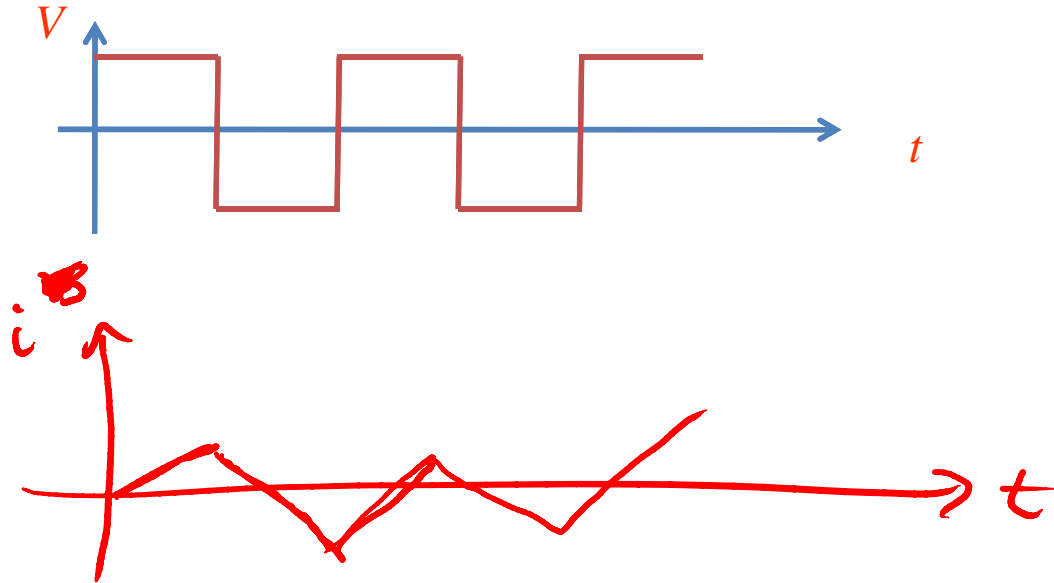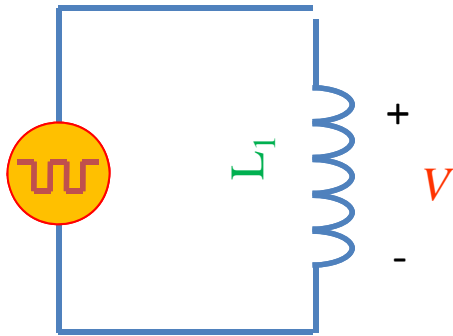


$$v = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int v dt$$

Example Inductor Problem #3

Find $V(t)$

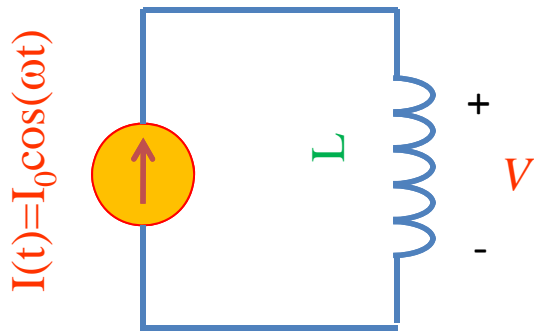

$$V = L \frac{di}{dt}$$

$$= L \frac{d}{dt} [I_0 \cos(\omega t)]$$

$$= -I_0 L \omega \sin(\omega t) \quad \checkmark$$

$$I(t) = \text{Re} \left[\underbrace{I_0 e^{j\omega t}}_{\text{current phasor } \mathbf{I}} \right] = \text{Re} \left[\mathbf{I} e^{j\omega t} \right]$$

$$V(t) = L \frac{d}{dt} \text{Re} \left[I_0 e^{j\omega t} \right] = \text{Re} \left[L I_0 \frac{d}{dt} e^{j\omega t} \right]$$

$$= \text{Re} \left[L I_0 j \omega e^{j\omega t} \right] = \text{Re} \left[\underbrace{I_0 j \omega L}_{\text{voltage phasor } \mathbf{V}} e^{j\omega t} \right]$$

$$\text{Inductor : } \mathbf{V} = \underbrace{j\omega L}_{\text{impedance}} \mathbf{I} \quad \text{---m}$$

“Impedance” = Z




$$V = Z I$$

KVL, KCL, Node/Mesh, Thev, Norton

$$V_R = i_R R$$

LR circuit

Find $V(t)$, $i(t)$

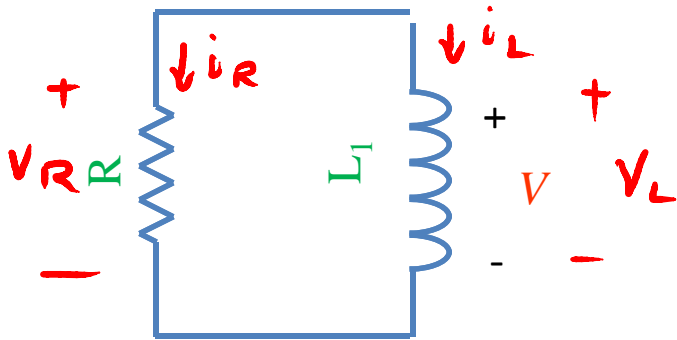

$$KVL \Rightarrow V_L = V_R$$

$$KCL \Rightarrow i_R = -i_L$$

$$L \frac{di_L}{dt} = i_R R$$


$$-i_L R = L \frac{di_L}{dt}$$

$$\Rightarrow \frac{di_L}{dt} = -\frac{1}{\tau} i_L$$

$$V_L = L \frac{di_L}{dt}$$


$$\tau \equiv \frac{L}{R} \quad \text{time constant}$$

$$i_L(t) = i_L(t=0) e^{-t/\tau}$$

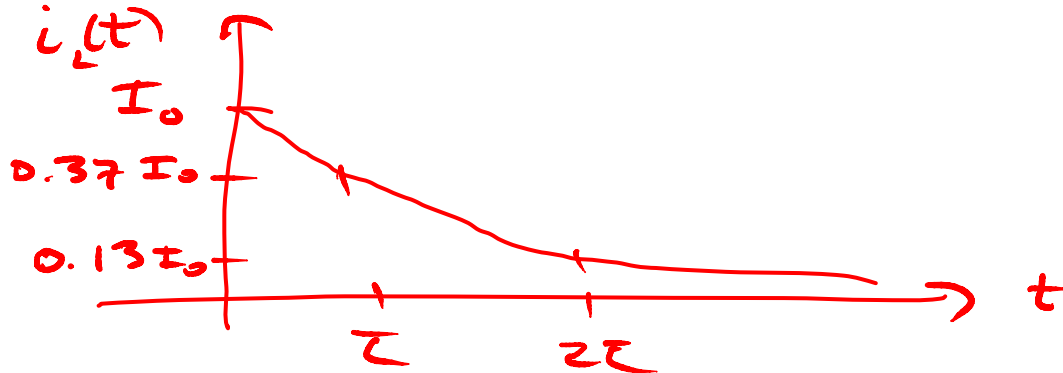

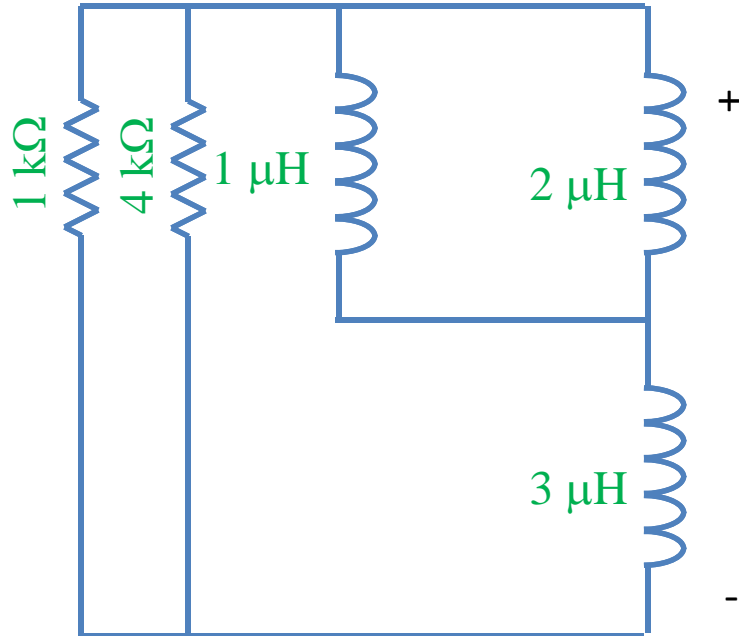Example LR problem

(Students) Find $V(t)$, given that $V(t=0) = 5$ Volts



Handwritten notes and equivalent circuit diagram:

$$\tau = \frac{L_{eq}}{R_{eq}}$$


$$R_{eq} = 4\text{ k}\Omega \parallel 1\text{ k}\Omega = \frac{4\text{ k}\Omega \cdot 1\text{ k}\Omega}{4\text{ k}\Omega + 1\text{ k}\Omega} = \frac{4}{5}\text{ k}\Omega$$

$$L_{eq} = (2\text{ }\mu\text{H} \parallel 1\text{ }\mu\text{H}) + 3\text{ }\mu\text{H} = \frac{2\text{ }\mu\text{H} \cdot 1\text{ }\mu\text{H}}{2\text{ }\mu\text{H} + 1\text{ }\mu\text{H}} + 3\text{ }\mu\text{H} = \frac{2}{3}\text{ }\mu\text{H} + 3\text{ }\mu\text{H} = \frac{11}{3}\text{ }\mu\text{H}$$

$$i_L = i(t=0) e^{-t/\tau}$$

$$i_L(t=0) = \frac{5\text{ V}}{R_{eq}}$$

Power

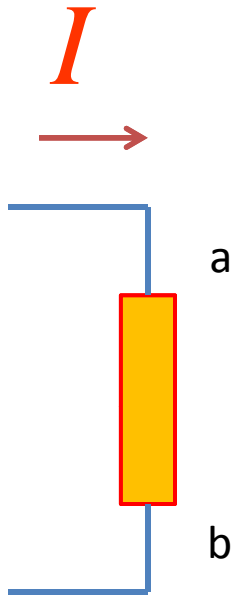

$$I \times V_{ab} = \text{power}$$


Watts [W] = Volt Amp [V-A]

Note: MKSA unit system:
Meters Kilogram Second Amp

Resistor:
Energy lost to heat...

Inductor or capacitor:
Energy **STORED** and can be recovered...

Energy stored

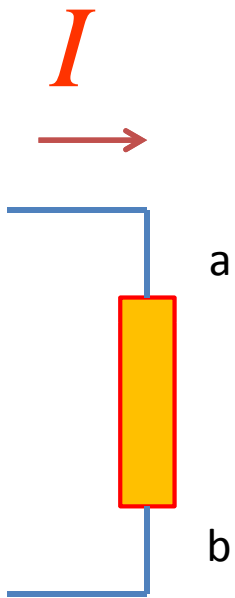

$$I \times V_{ab} = \text{power}$$

Energy:

$$W = \int P dt = \int I \cdot V dt$$




Capacitor stored energy:

$$\int I \cdot V dt = \int C \frac{dV}{dt} \cdot V dt = \frac{1}{2} CV^2 = \frac{Q^2}{2C}$$

Inductor stored energy:

$$\int I \cdot V dt = \int I \cdot L \frac{dI}{dt} dt = \frac{1}{2} LI^2$$

Symbol library

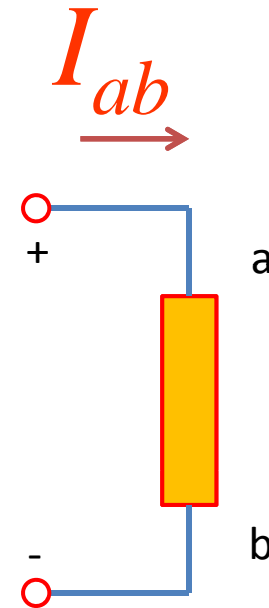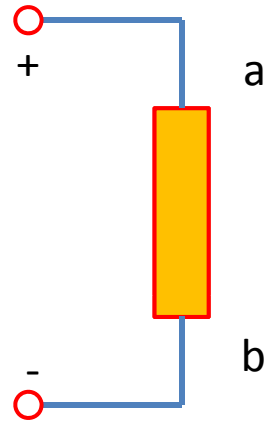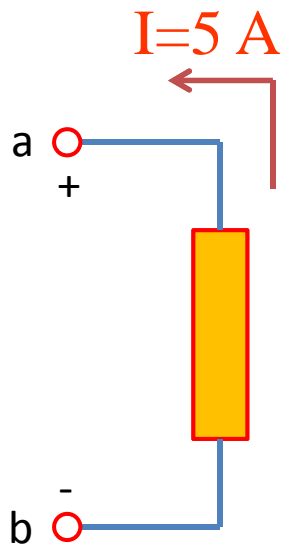

Symbol library

