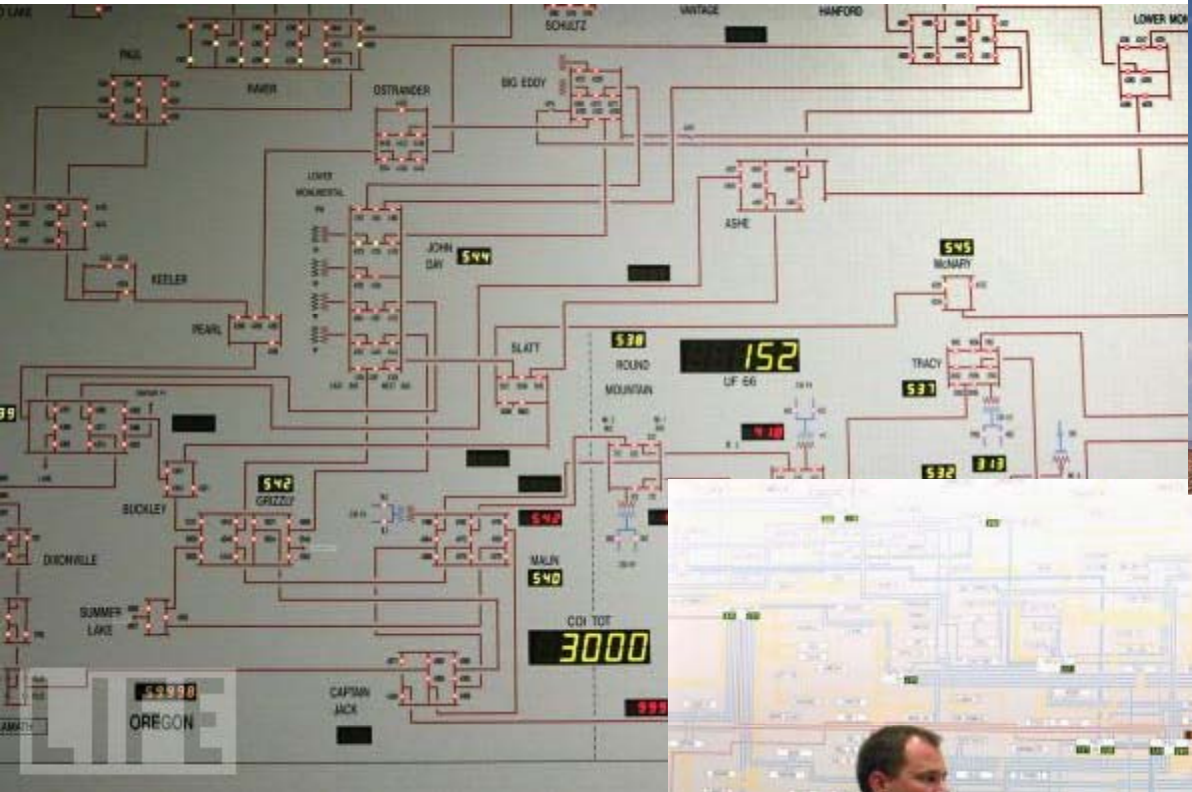


Announcements:


1. PSpice is installed in ECT 123 and EH 1131.
(Not required but you may use for HWs if you like.)
2. Next quiz (#4) will be due Monday night
3. HW4 due Wed next week (to be posted soon)
4. MT2 2 weeks from today (ch 1-6, part of 9)

EECS 70A: Network Analysis

Lecture 10



Capacitors

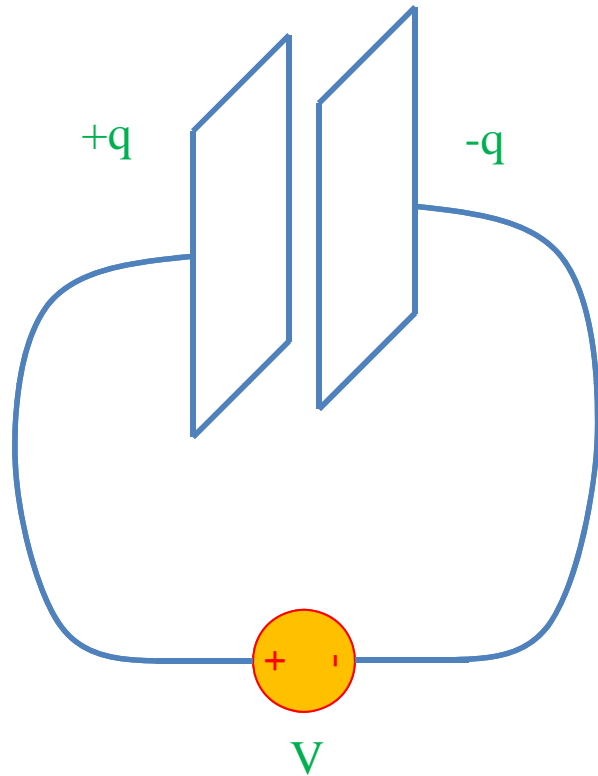

K usually > 1

$$q = CV$$

$$C = \frac{\epsilon A}{d}$$

A=area
d=plate separation

Farads[F] = Coulombs/Volt [C]/[V]


$$\epsilon_0 = 8.85 \times 10^{-12} \text{ F / m}$$

$$\epsilon = K\epsilon_0$$

Dielectric constant:


$$K = 3.9 \text{ SiO}_2$$

$$K = 25 \text{ HfO}_2$$

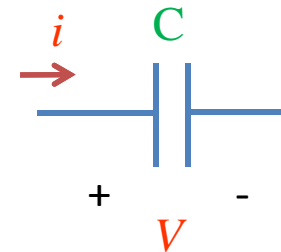

“High-K Dielectric”

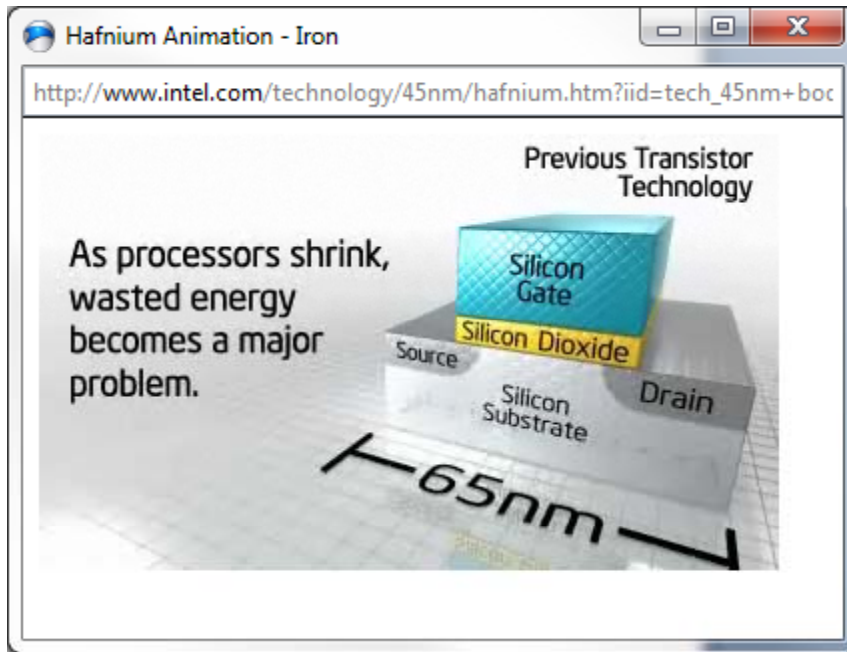http://www.intel.com/technology/45nm/hafnium.htm?iid=tech_45nm+body_animation_hafnium



Time dependence

$$q = CV \quad i = \frac{dq}{dt} = C \frac{dV}{dt}$$

q, V, i can depend on time !

Implicit:


$$q(t) = CV(t) \quad i(t) = \frac{dq(t)}{dt} = C \frac{dV(t)}{dt}$$

Will not always write (t), but it is assumed from now on.

$$i(t) = C \frac{dV(t)}{dt} \Rightarrow V(t) = \frac{1}{C} \int i(t) dt$$
$$\Rightarrow q(t) = \int i(t) dt$$

Example Capacitor Problem

Find $V(t)$, $q(t)$



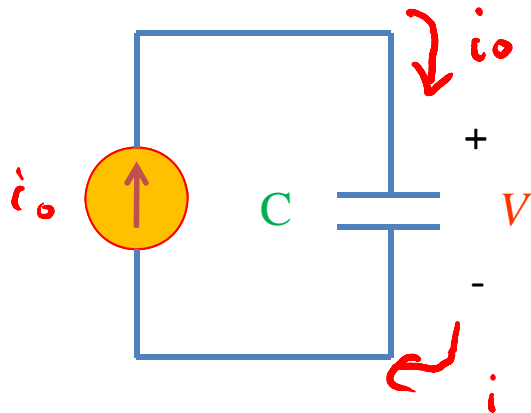


There is
Another physical
kind of current!
Displacement
current.

$$q = CV$$

$$i = C \frac{dV}{dt}$$
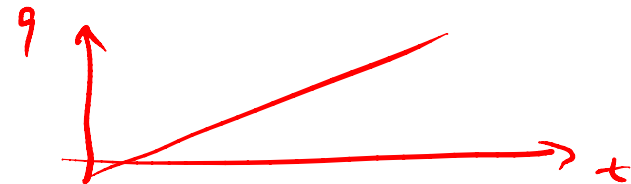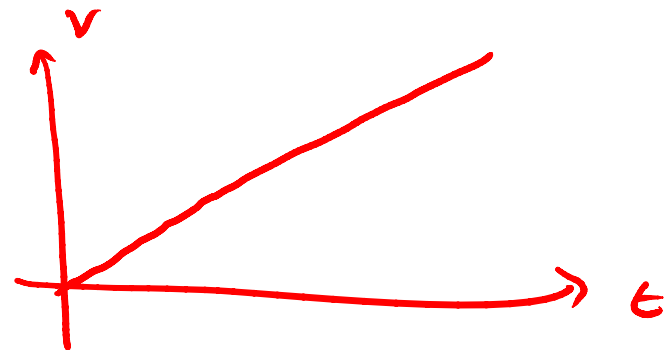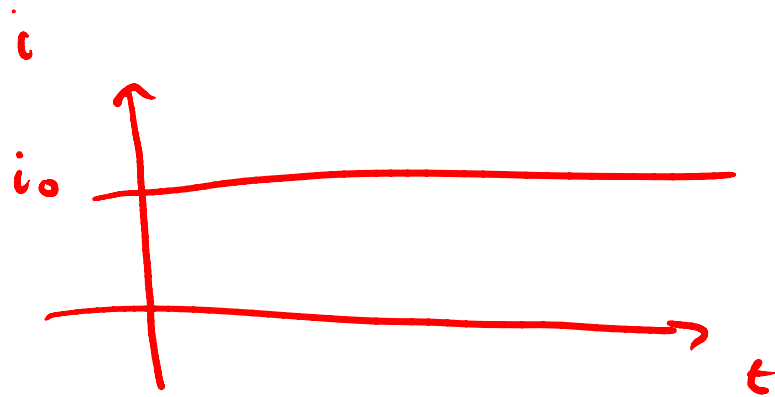
$$V = \frac{1}{C} \int i(t) dt$$
$$= \frac{1}{C} i_0 \int dt = \frac{i_0}{C} t$$



One-bit memory

ITRS

Roadmap

"Technology Node"

e.g. 65nm node
45nm node

Typical dimensions:



0.1 micron x 0.1 micron area

10 nm thickness.

What is C?



$$C = \frac{\epsilon_0 k A}{d}$$

0.1 μm

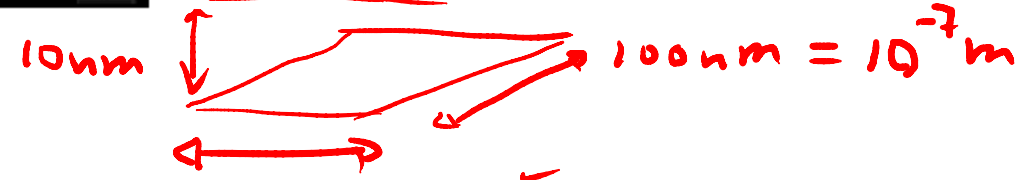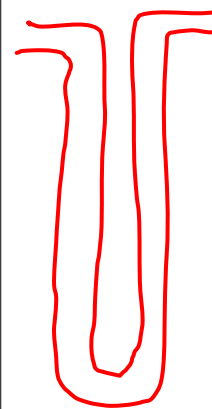

$$C = \frac{\epsilon A}{d} = \frac{10^{-12} \times 8.85 \times 10^{-12} \text{ F/m} \times [10^{-7} \text{ m}]^2}{10^{-9} \text{ m}}$$

F = 0.1 fF
Too small

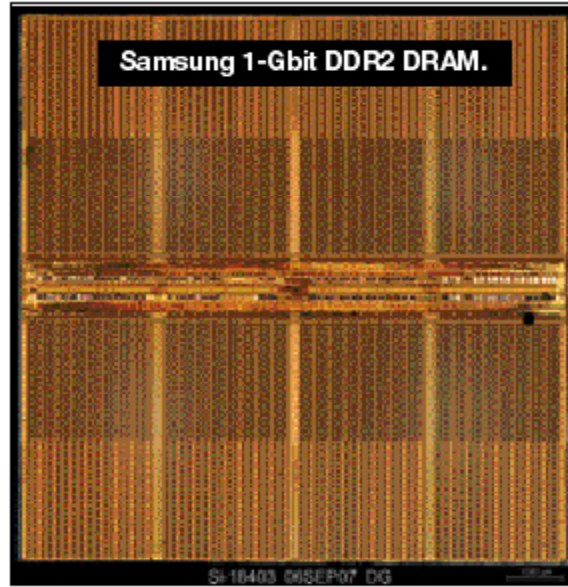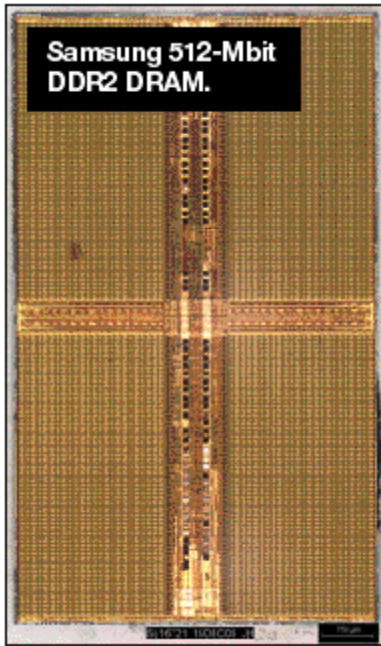

http://i.cmpnet.com/eet/news/07/11/DC1502_UTH_samsung.gif

Q = 0 bit 0


Q ≠ 0 bit 1

$$= 10^{1+1-12-14-1+9} = 10^{-16} \text{ F}$$

F Femto 10⁻¹⁵

REALITY

1 Bit Read/Write

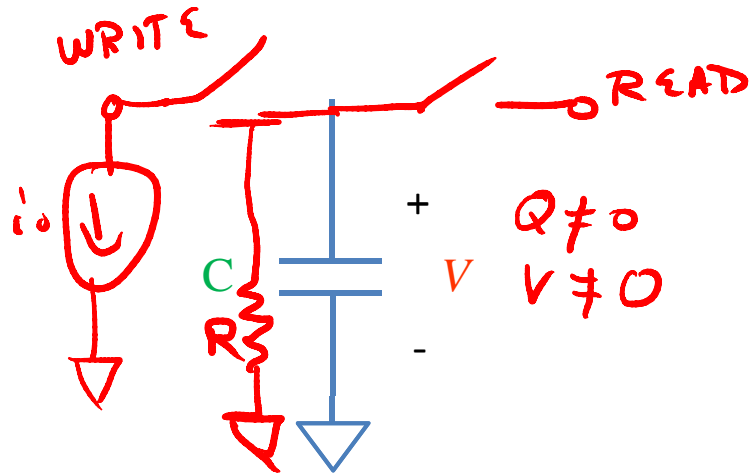


$$Q = CV$$

$$i = C \frac{dV}{dt}$$

$$q = \int i dt$$


TO READ,
CONNECT TO VOLTMETER

REFRESH RATE
every 10ms
DRAM
LD dynamic

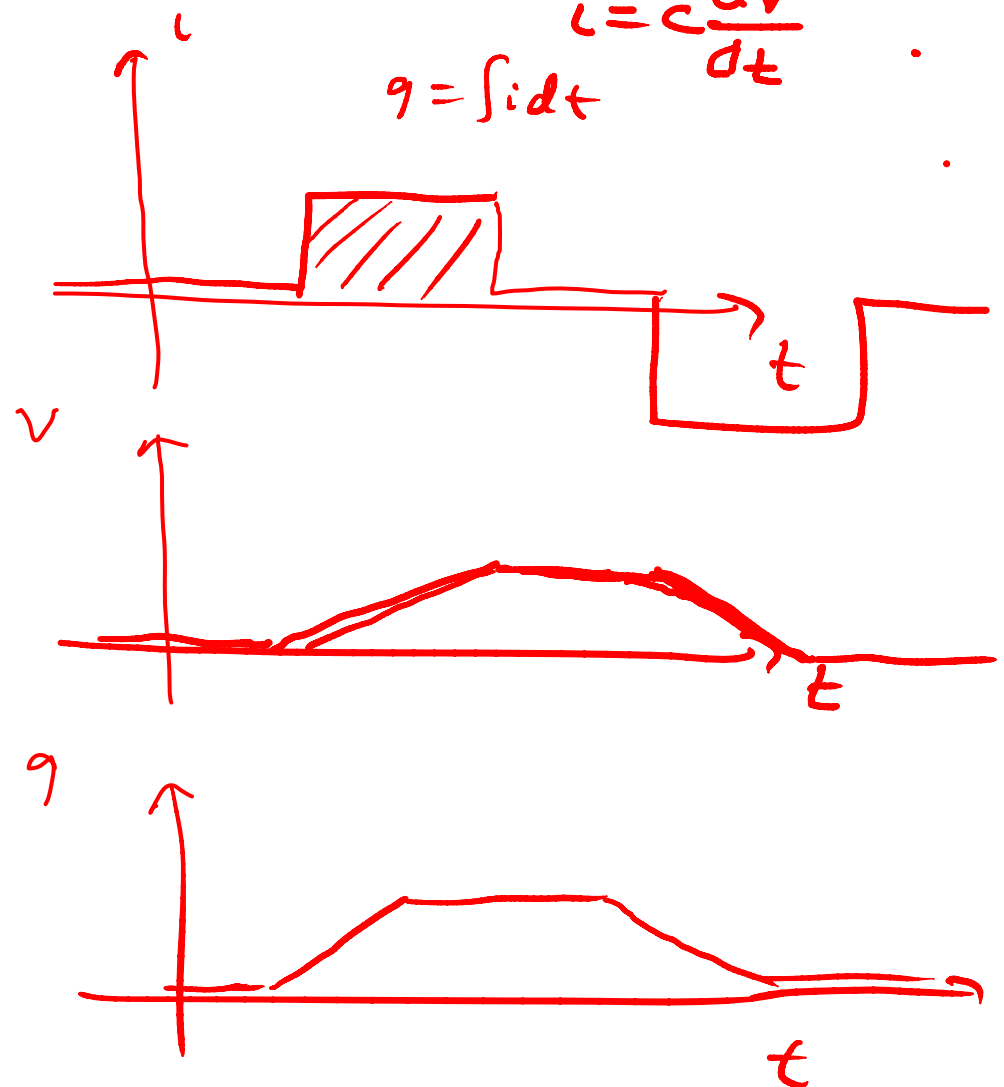

Example Problem #2




(Students): Find $i(t)$, $q(t)$

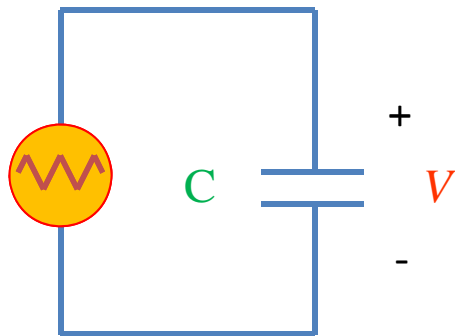


$$q = CV$$

$$i = C \frac{dV}{dt}$$

$$V = \frac{1}{C} \int i dt$$

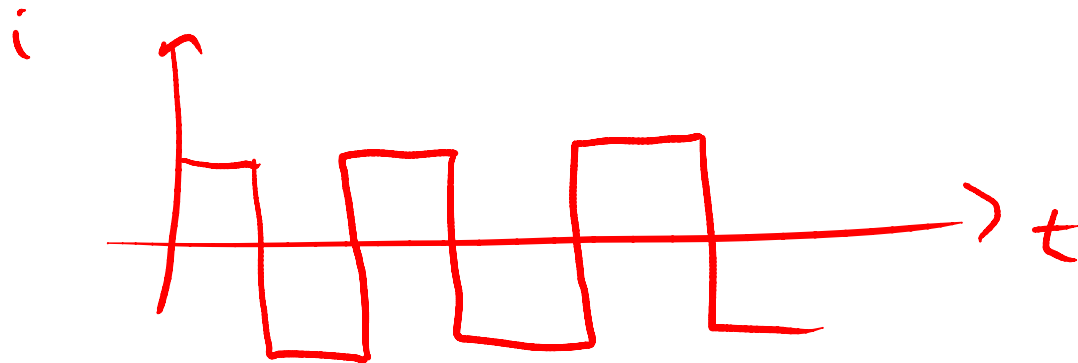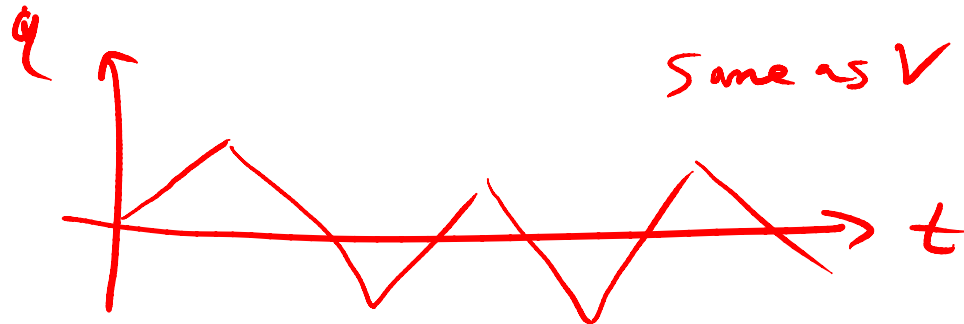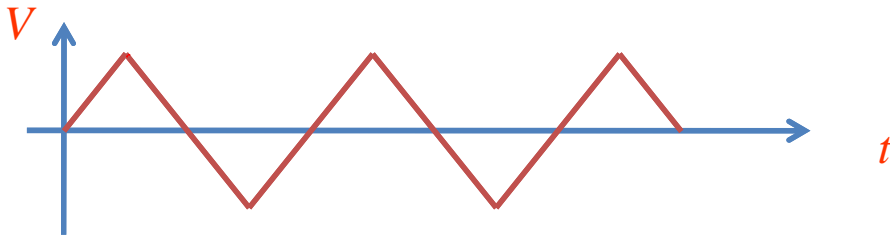

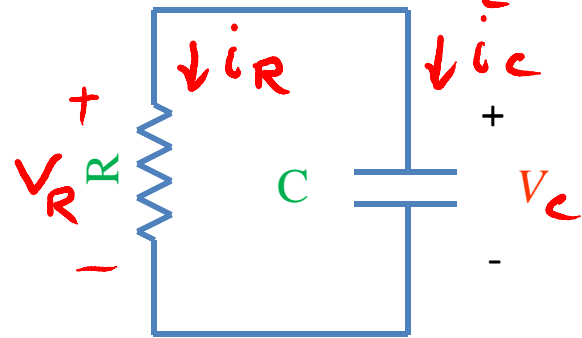
RESISTOR
 $i_R R = V_R = V_C = (-i_C)R$
 KVL $\Rightarrow V_R = V_C$
 Find $V(t), q(t), i(t)$
 KCL $\Rightarrow i_R = -i_C$



RC circuit

CAPACITOR
 $q = CV_C$

$$i_C = C \frac{dV_C}{dt}$$

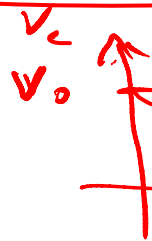

$$\frac{V_C}{R} = C \frac{dV_C}{dt}$$

$$\tau \equiv RC$$

$$\frac{dV(t)}{dt} = -\frac{1}{RC} V(t)$$


why?

Soln:

$$V(t) = V(t=0) e^{-t/RC}$$

Proof:
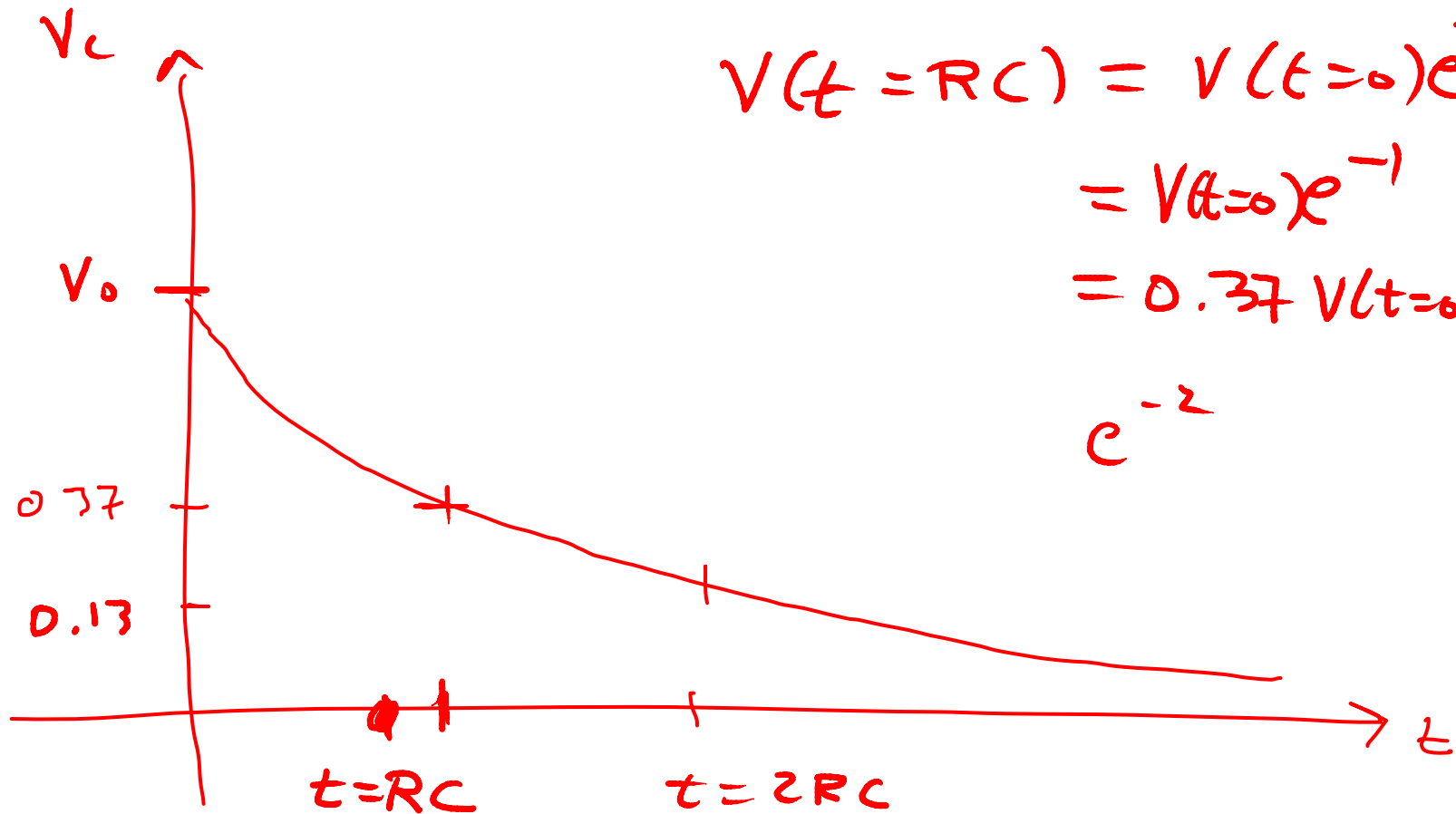
$$\begin{aligned} \frac{dV(t)}{dt} &= \frac{d}{dt} \left[V(t=0) e^{-t/RC} \right] \\ &= V(t=0) \frac{d}{dt} \left[e^{-t/RC} \right] = -\frac{1}{RC} \underbrace{V(t=0)}_{t/RC} \\ &= -\frac{1}{RC} V(t) \end{aligned}$$



$$V(t) = V(t=0) e^{-t/RC}$$

$$V(t=RC) = V(t=0) e^{-t/RC}$$

$$= V(t=0) e^{-1}$$


$$= 0.37 V(t=0)$$

$$e^{-2}$$


DRAM vs. SRAM

Example Capacitor Problem #2


Find $V(t)$, $q(t)$

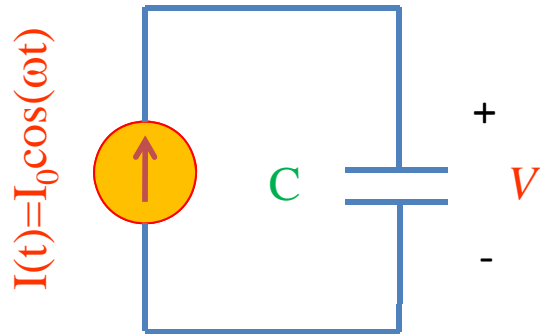

Parallel Capacitors

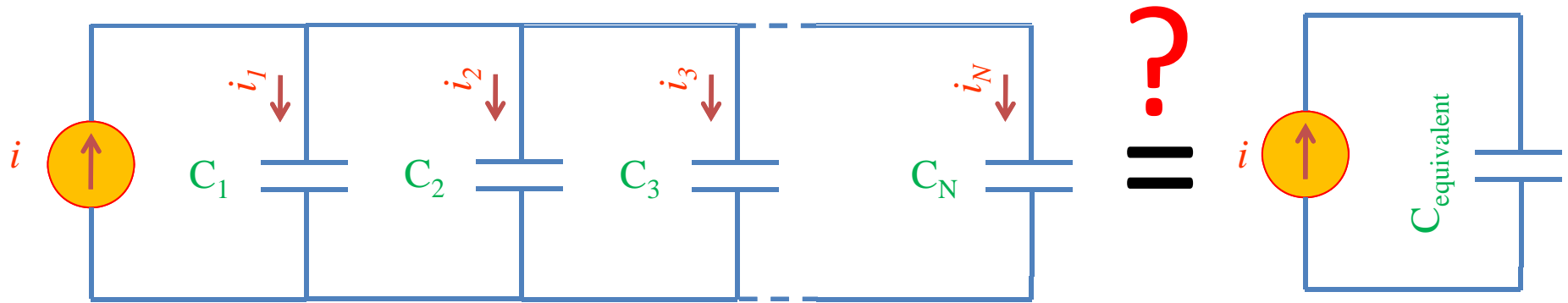


Series Capacitors

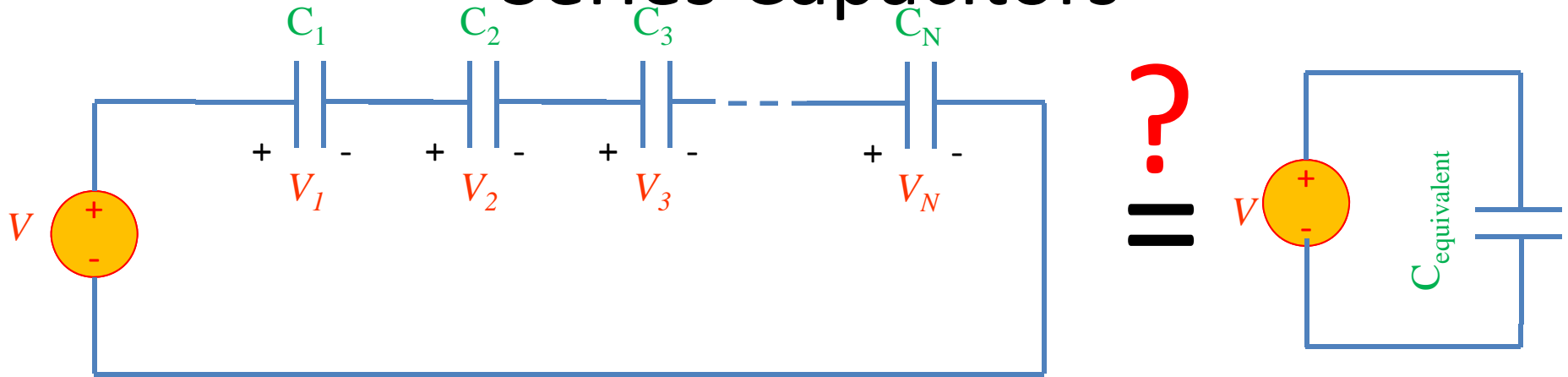


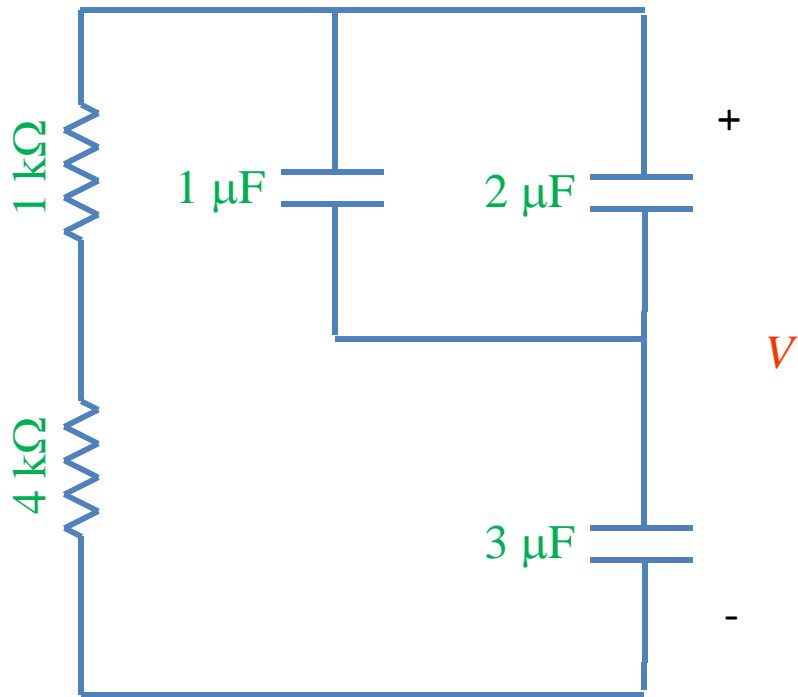Example problem #4

(Students) Find $V(t)$, given that $V(t=0) = 5$ Volts



Inductors

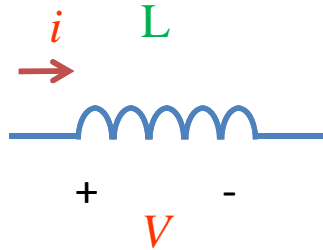

$$L = \frac{N^2 \mu A}{l}$$

A=area

l=wire length

N = # of turns


$\mu = 4 \pi 10^{-6}$ H/m

$$V = L \frac{di}{dt}$$


Henry[H]

$$V = L \frac{di}{dt} \Rightarrow i(t) = \frac{1}{L} \int V(t) dt$$

Series Inductors

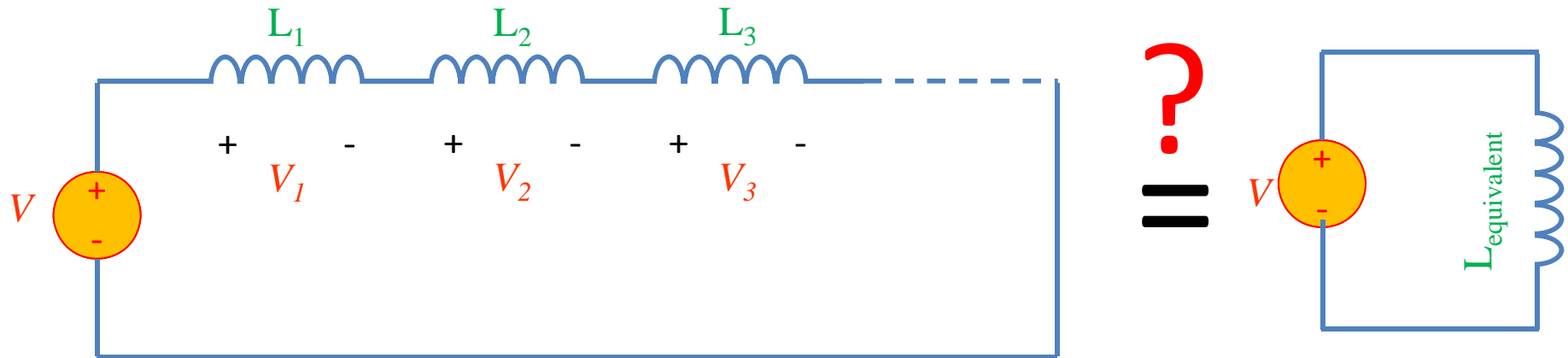


Parallel Inductors

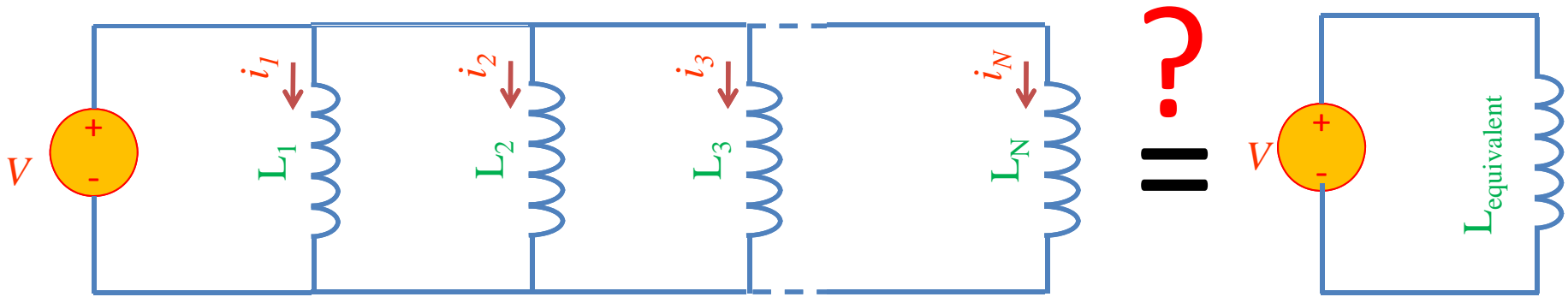



Example Inductor Problem

(Students): Find $V(t)$.

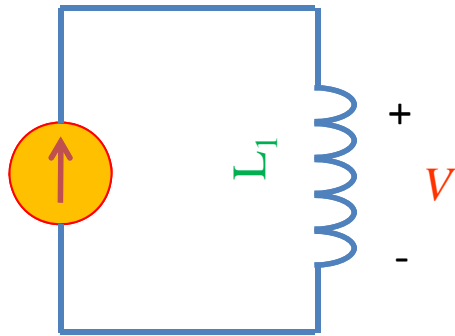


Example Inductor Problem #2

(Students): Find $i(t)$

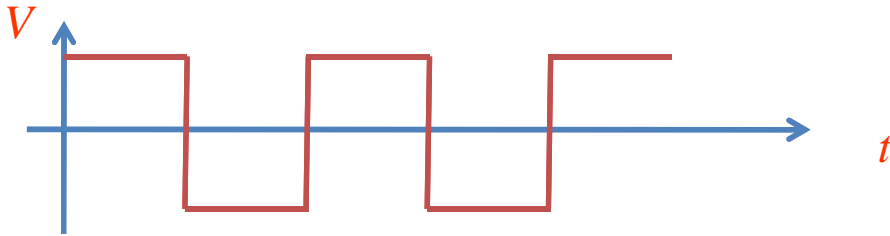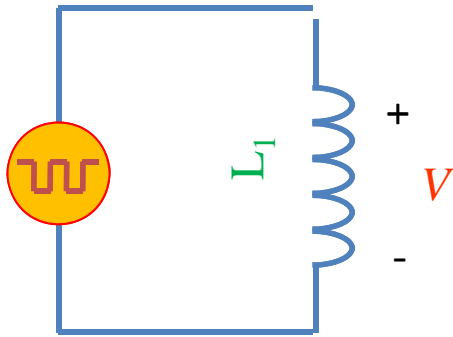


Example Inductor Problem #3

Find $V(t)$

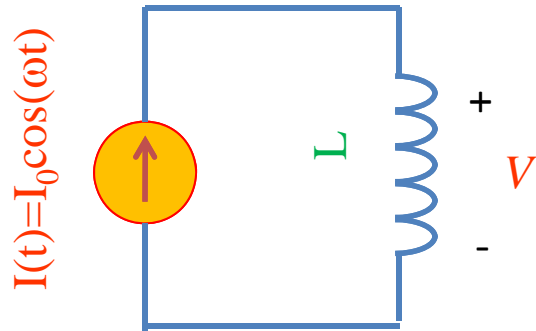


LR circuit

Find $V(t)$, $i(t)$

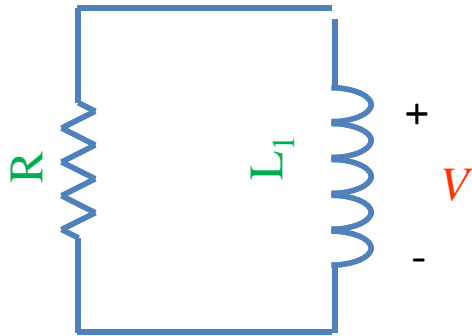


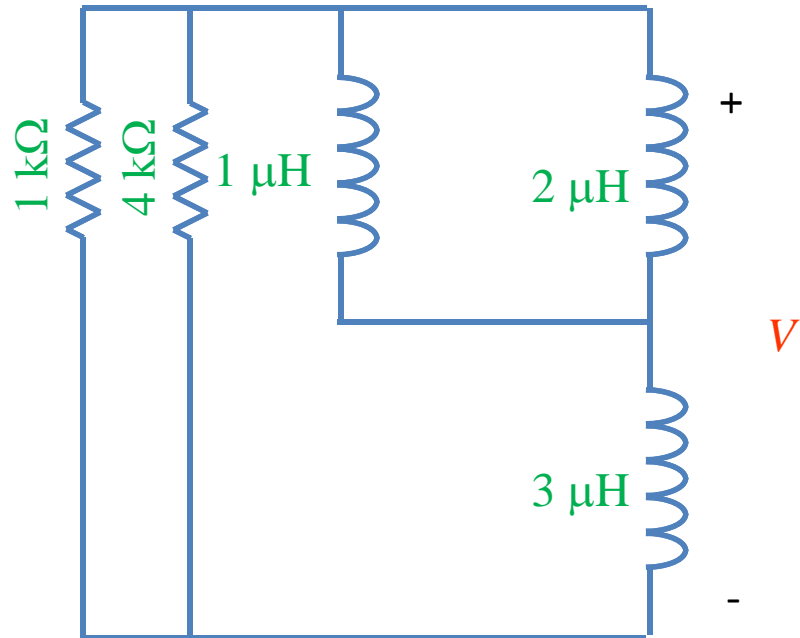Example LR problem

(Students) Find $V(t)$, given that $V(t=0) = 5$ Volts



Power

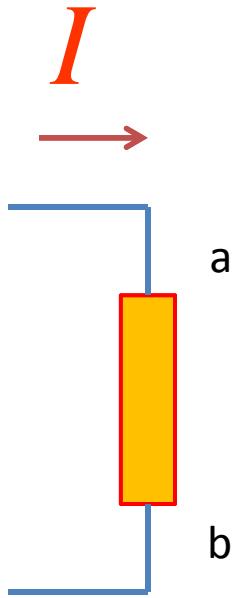

$$I \times V_{ab} = \text{power}$$


Watts [W] = Volt Amp [V-A]

Note: MKSA unit system:
Meters Kilogram Second Amp

Resistor:
Energy lost to heat...

Inductor or capacitor:
Energy **STORED** and can be recovered...

Energy stored

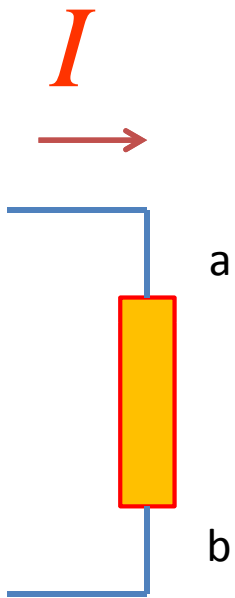

$$I \times V_{ab} = \text{power}$$

Energy:

$$W = \int P dt = \int I \cdot V dt$$




Capacitor stored energy:

$$\int I \cdot V dt = \int C \frac{dV}{dt} \cdot V dt = \frac{1}{2} CV^2 = \frac{Q^2}{2C}$$

Inductor stored energy:

$$\int I \cdot V dt = \int I \cdot L \frac{dI}{dt} dt = \frac{1}{2} LI^2$$

Symbol library

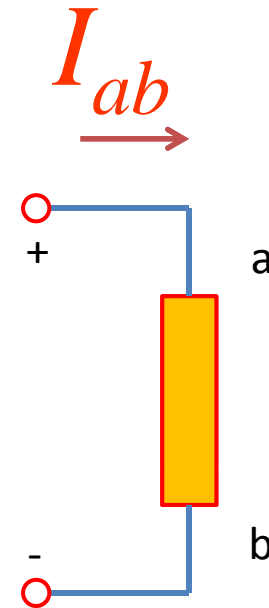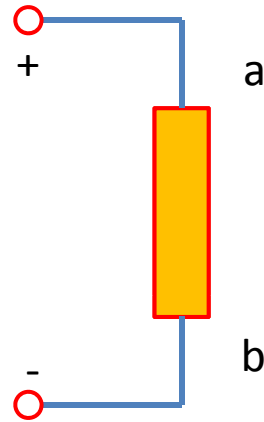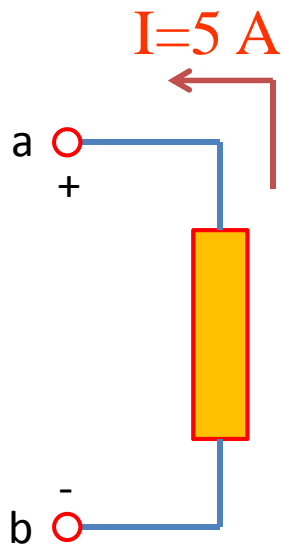

Symbol library

