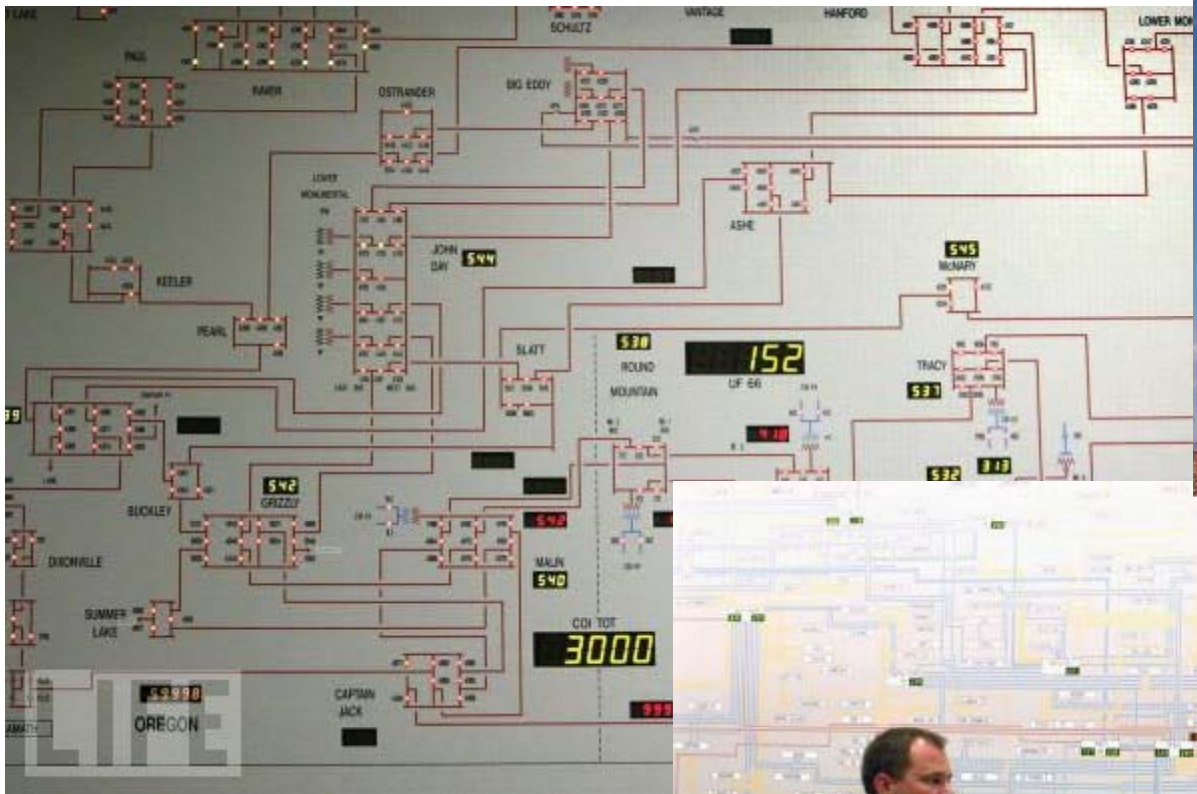


Announcements:


1. HW due tomorrow at 5.  
Hand in at MAE boxes (EG 2<sup>nd</sup> floor) OR  
To TA from 4-5 in discussion room ICF103

# EECS 70A: Network Analysis

## Lecture 11



# Power

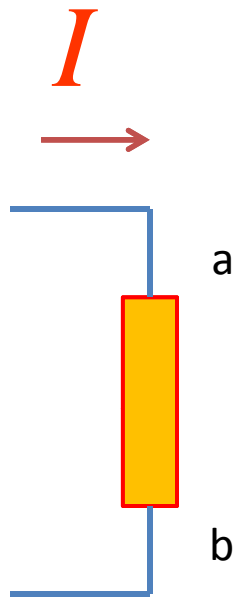

$$I \times V_{ab} = \text{power}$$


Watts [W] = Volt Amp [V-A]

Note: MKSA unit system:  
*Meters Kilogram Second Amp*

Resistor:  
Energy lost to heat...

Inductor or capacitor:  
Energy **STORED** and can be recovered...


# Energy stored

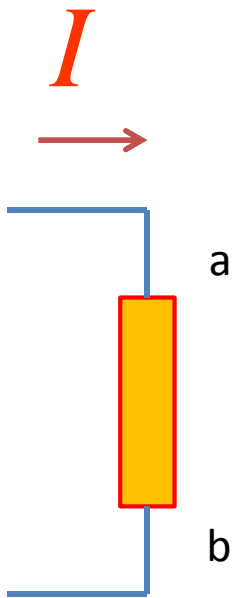

$$I \times V_{ab} = \text{power}$$

Energy:

$$W = \int P dt = \int I \cdot V dt$$

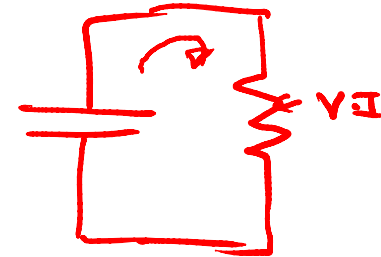

Capacitor stored energy:

$$\int I \cdot V dt = \int C \frac{dV}{dt} \cdot V dt = \frac{1}{2} CV^2 = \frac{Q^2}{2C}$$

$$Q = CV \quad \text{CAP}$$

$$I = C \frac{dV}{dt}$$

$$I \cdot V = C \frac{dV}{dt} V$$


Inductor stored energy:

$$\int I \cdot V dt = \int I \cdot L \frac{dI}{dt} dt = \frac{1}{2} LI^2$$

$$V = L \frac{dI}{dt} \quad \text{INDUCTOR}$$
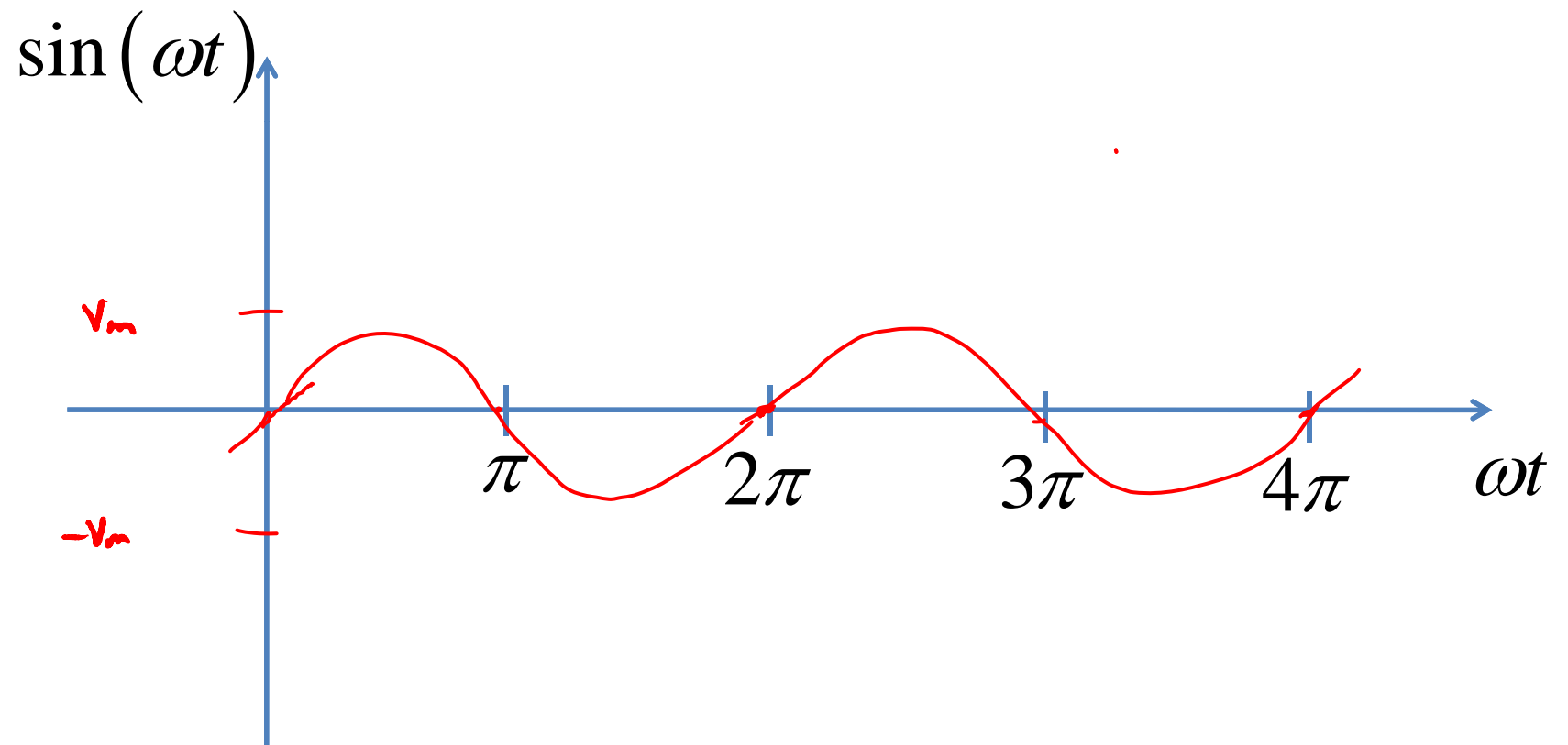
# Sine waves


$$V(t) = \underline{V_m} \sin(\omega t)$$


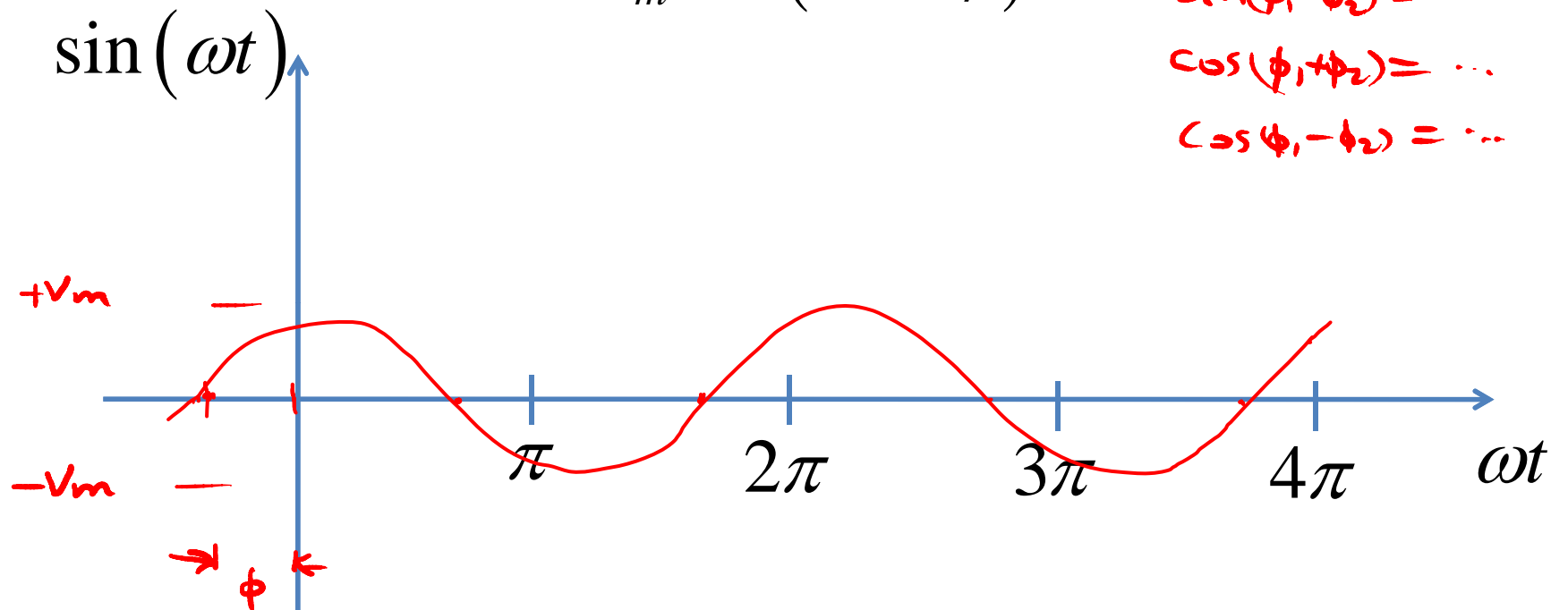
# Phase

$$V(t) = V_m \sin(\omega t + \phi)$$

$$\begin{aligned} \sin(\phi_1 + \phi_2) &= \dots \\ \sin(\phi_1 - \phi_2) &= \dots \\ \cos(\phi_1 + \phi_2) &= \dots \\ \cos(\phi_1 - \phi_2) &= \dots \end{aligned}$$



$$A \cos(\omega t) + B \sin(\omega t) = C \cos(\omega t - \theta)$$

$$\theta = \tan^{-1}\left(\frac{B}{A}\right)$$

$$C = \sqrt{A^2 + B^2}$$

✖ memorize

# Complex numbers


Euler  $e^{j\phi} = \cos\phi + j\sin\phi$

$$j \equiv \sqrt{-1} \quad \frac{1}{j} = -j$$

$$z = x + jy$$

$$z = re^{j\phi} = r(\cos\phi + j\sin\phi) = \underbrace{r\cos\phi}_{\text{Re}} + j\underbrace{r\sin\phi}_{\text{Im}}$$

$$z = r \angle \phi$$

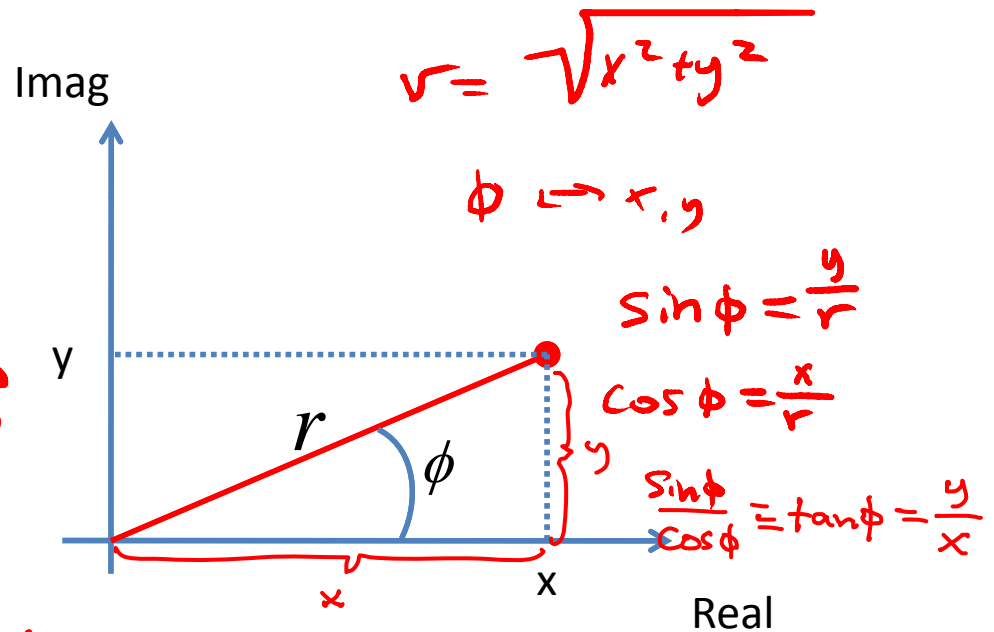

$$\text{Re}(z) = \text{Real}(z) = x$$

$$\text{Im}(z) = \text{Imag}(z) = y$$

$$\text{Re}(z) = r \cos\phi \quad \text{Im}(z) = r \sin\phi$$

$$\phi = \tan^{-1}\left[\frac{y}{x}\right]$$

# Complex algebra

$$\underline{z_1 = x_1 + jy_1 = r_1 e^{j\phi_1}} \quad z_2 = x_2 + jy_2 = r_2 e^{j\phi_2}$$

Addition:

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

Subtraction:

$$z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

Multiplication:

$$z_1 z_2 = (r_1 e^{j\phi_1})(r_2 e^{j\phi_2}) = r_1 r_2 e^{j\phi_1} e^{j\phi_2} = r_1 r_2 e^{j(\phi_1 + \phi_2)} = r_1 r_2 \angle(\phi_1 + \phi_2)$$

Division:

$$z_1 / z_2 = \frac{r_1 e^{j\phi_1}}{r_2 e^{j\phi_2}} = \frac{r_1}{r_2} \frac{e^{j\phi_1}}{e^{j\phi_2}} = \frac{r_1}{r_2} e^{j\phi_1} e^{-j\phi_2} = \frac{r_1}{r_2} e^{j(\phi_1 - \phi_2)}$$

Inversion:

$$1/z_1 = \frac{1}{r_1 e^{j\phi_1}} = \frac{1}{r_1} e^{-j\phi_1}$$

Square root:

$$\sqrt{z_1} = (r_1 e^{j\phi_1})^{1/2} = r_1^{1/2} (e^{j\phi_1})^{1/2} = r_1^{1/2} e^{j\phi_1/2}$$

Complex conjugate:

$$Z^* = x - jy = r e^{-j\phi}$$



# Euler relationship

$$e^{j\phi} = \cos \phi + j \sin \phi$$

$$\Rightarrow \cos \phi = \operatorname{Re}(e^{j\phi})$$

Phasors:

$$V(t) = V_m \cos(\omega t + \phi) = \operatorname{Re}\left(V_m e^{j(\omega t + \phi)}\right)$$

$$= \operatorname{Re}\left(\underbrace{V_m e^{j\phi}}_{\text{“Phasor”}} e^{j\omega t}\right)$$

“Phasor” **V**

(Complex #)


# Circuits



$$\mathbf{V} = \mathbf{I} R$$



$$\mathbf{V} = \mathbf{I} / j\omega C$$

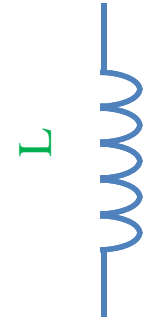

$$\mathbf{V} = j\omega L \mathbf{I}$$

“Impedance”

$$Z = R$$

$$Z = 1 / j\omega C$$

$$Z = j\omega L$$

KCL, KVL hold for relationship between  $\mathbf{V}$ ,  $\mathbf{I}$ .

# Series/Parallel Impedances




$$Z_{eq} = Z_1 + Z_2 + Z_3$$



$$Z_{eq}^{-1} = Z_1^{-1} + Z_2^{-1} + Z_3^{-1}$$
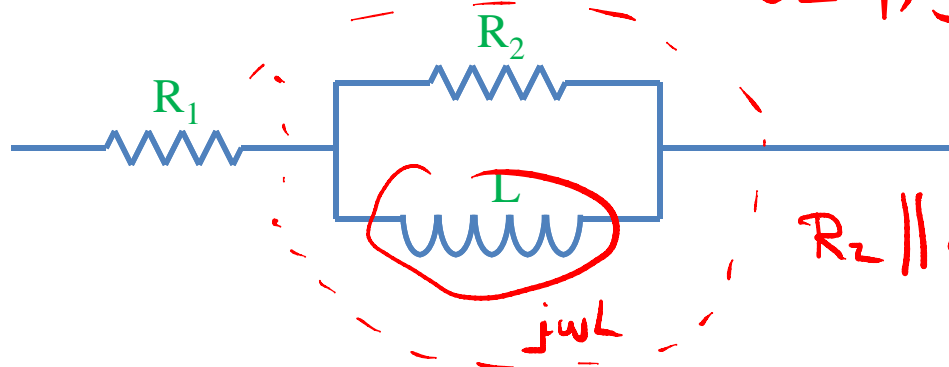
# Example problem #1

Find  $Z_{eq}$  for this circuit: (instructor)




$Re(z_{eq})$   
 $Im(z_{eq})$  ] ex. @ home

$$Z \equiv \frac{L}{R_2}$$

$$\begin{aligned}
 Z_{eq} &= R_1 + (R_2 \parallel j\omega L) = R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{j\omega L}} && R_2 \parallel j\omega L \\
 &= R_1 + \frac{j\omega L}{j\omega \frac{L}{R_2} + 1} = R_1 + \frac{j\omega L}{1 + j\omega L} && R_2 \parallel j\omega L \\
 &= R_1 + \frac{R_2 j\omega L}{j\omega L + R_2} && \lim_{\omega \rightarrow \infty} Z_{eq}
 \end{aligned}$$
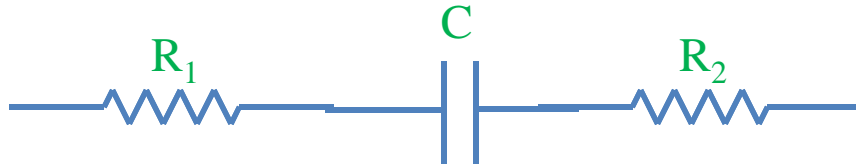
# Example problem #2

Find  $Z_{eq}$  for this circuit: (students)



$$\frac{1}{j} = -j$$
$$\frac{1}{j\omega C} = -j \frac{1}{\omega C}$$

$$Z_{eq} = R_1 + \frac{1}{j\omega C} + R_2 = \underbrace{(R_1 + R_2)}_{\text{Re}} + j \underbrace{\left(-\frac{1}{\omega C}\right)}_{\text{Im}}$$

$$\text{Re}(Z_{eq}) = R_1 + R_2$$


$$\text{Im}(Z_{eq}) = -\frac{1}{\omega C}$$

$$\lim_{\omega \rightarrow \infty} Z_{eq} = R_1 + R_2$$

$$Q = CV \quad I = C \frac{dV}{dt} \quad V = \frac{1}{C} \int I dt$$

# Phasor to voltage conversion $\downarrow \times j = -1$

$$I(t) = I_0 \cos(\omega t + \theta)$$

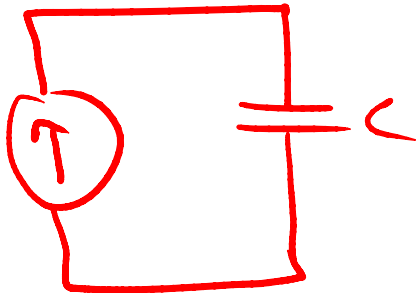

$$I = I_0 e^{j\theta} = I_0$$

$$\text{Re}\{z\} = X$$

$$V = \frac{1}{j\omega C} I$$

$$z = X + jy$$

$$\text{Find } V(t) = ? = \text{Re}\{V e^{j\omega t}\}$$

$$= \text{Re}\left[\frac{1}{j\omega C} I e^{j\omega t}\right] = \text{Re}\left[\frac{1}{j\omega C} I_0 e^{j\omega t}\right]$$

$$= \text{Re}\left[\left(-\frac{1}{\omega C}\right) j I_0 e^{j\omega t}\right] = -\frac{I_0}{\omega C} \text{Re}\{j e^{j\omega t}\}$$

$$= -\frac{I_0}{\omega C} \text{Re}\{j(\cos \omega t + j \sin \omega t)\} = -\frac{I_0}{\omega C} \underbrace{[-\sin(\omega t) + j \cos(\omega t)]}_{\text{Re}}$$

$$= \frac{I_0}{\omega C} \sin(\omega t)$$

# Example problem #3

Find  $i(t)$ ,  $V_1(t)$ ,  $V_2(t)$  for this circuit: (instructor)


$V(t) = V_0 \cos(\omega t)$   
 $V = V_0$   
 $Z_{eq} = R + \frac{1}{j\omega C}$   
 $I = \frac{V}{Z_{eq}}$   
 $i(t) = \text{Re} \left[ I e^{j\omega t} \right] = \text{Re} \left[ \frac{V}{Z_{eq}} e^{j\omega t} \right]$   
 $= \text{Re} \left[ \frac{V_0}{R + \frac{1}{j\omega C}} e^{j\omega t} \right] = \text{Re} \left[ \frac{V_0 j\omega RC}{1 + j\omega RC} e^{j\omega t} \right]$   
 $\cos \omega t + j \sin \omega t$





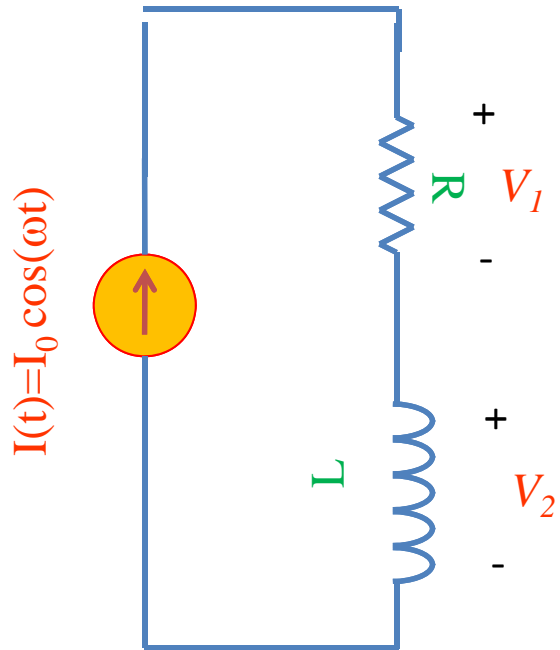
# Example problem #4


Find  $i(t)$ ,  $V_1(t)$ ,  $V_2(t)$  for this circuit: (students)




# Low pass filter

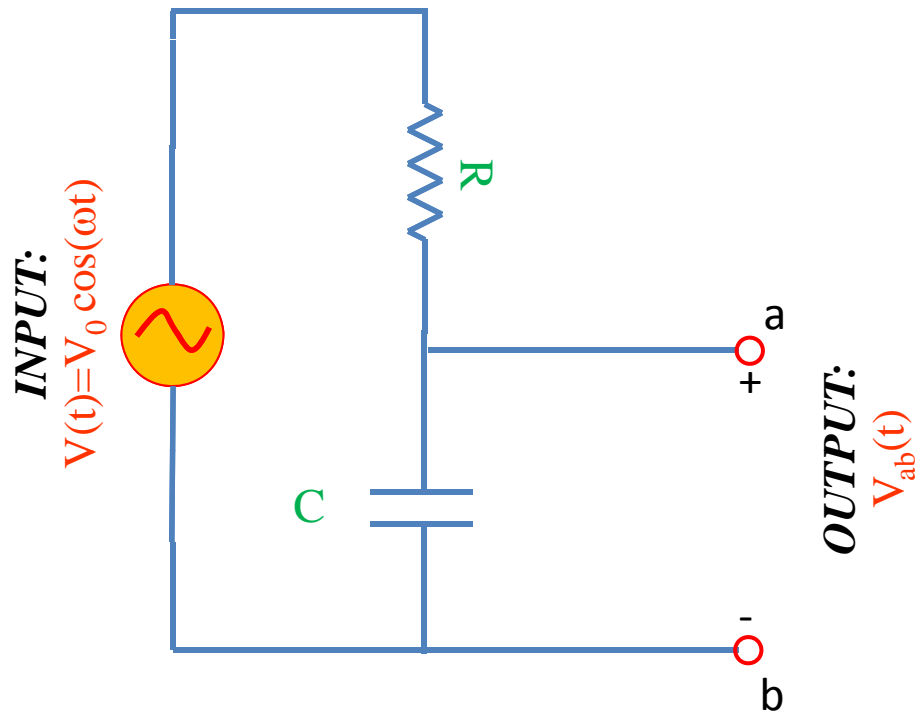




# High pass filter

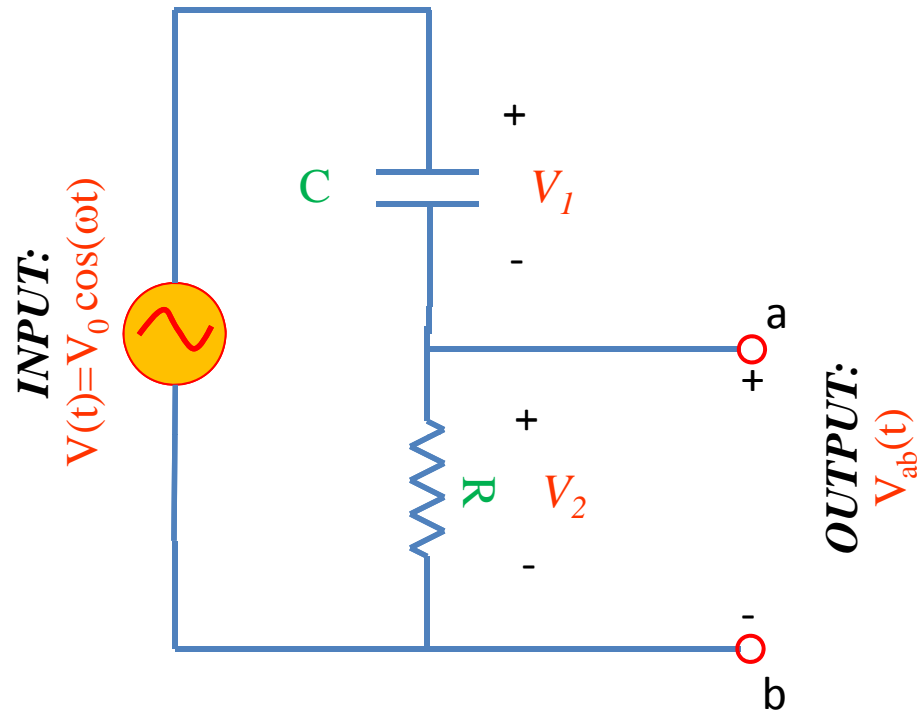

# Band pass filter (RLC)

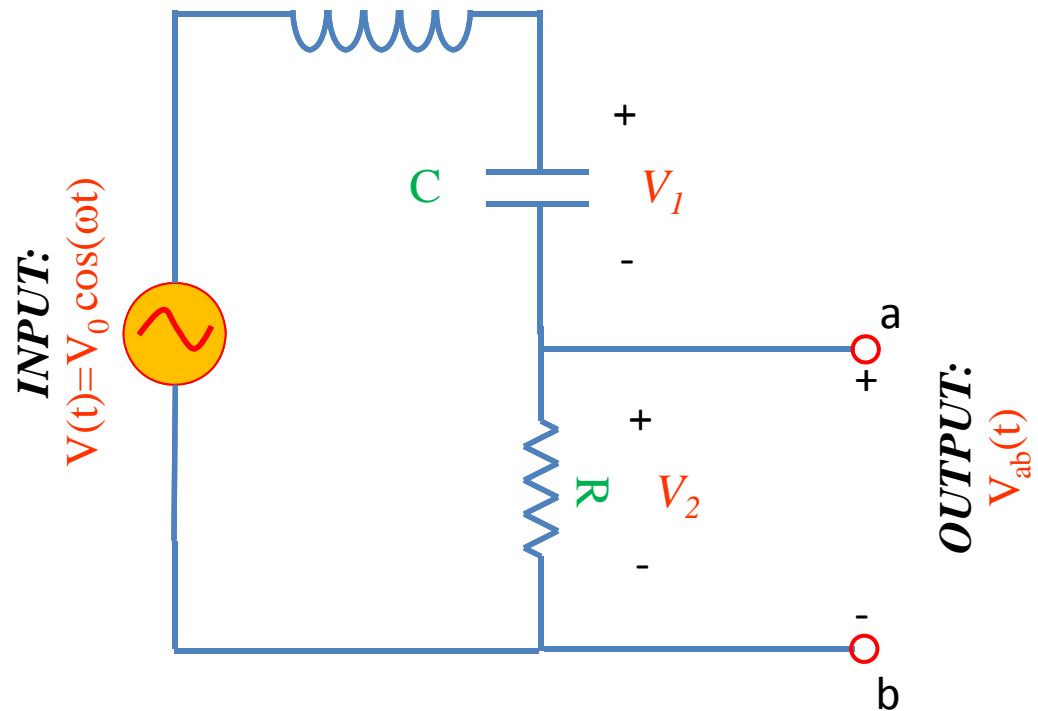

# Symbol library

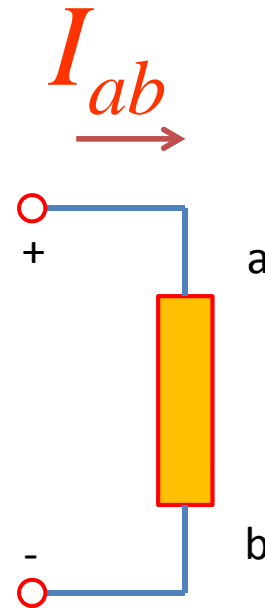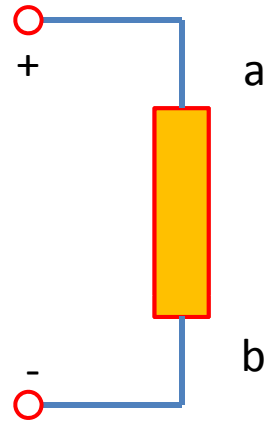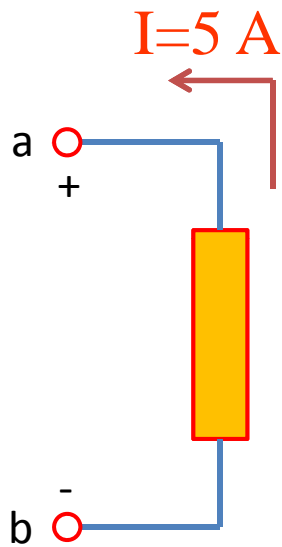

# Symbol library

