

Announcements:

1. HW5 due Wednesday
2. Midterm #2 is Thursday


EECS 70A: Network Analysis

Lecture 12

Today's Agenda

- KCL, KVL
- Nodal analysis
- Mesh analysis
- Thevenin/Norton theorem
- R,L,C series, parallel
- Impedances


Resistors

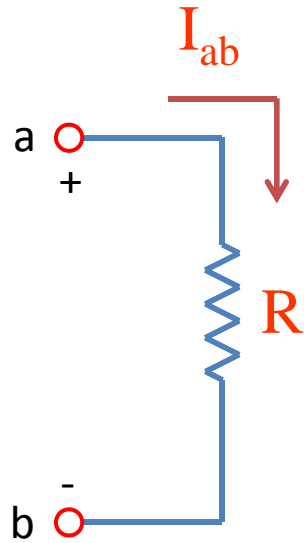

$$V_{ab} = I_{ab} \times R$$

Resistance units: Ohms [Ω]


Generalize: N resistors in parallel

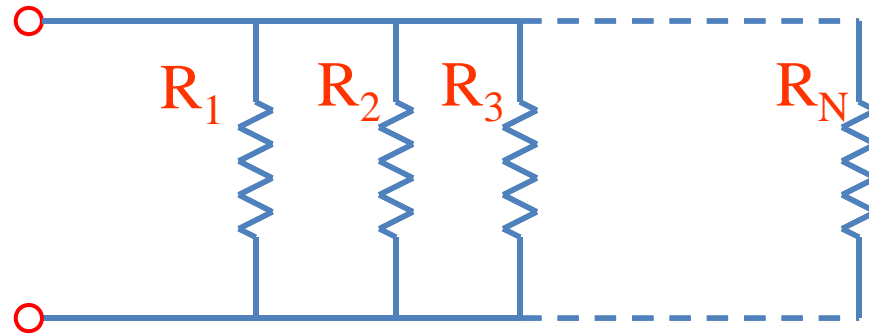

$$= \begin{array}{c} \text{---} \circ \\ | \\ \text{---} \text{---} \text{---} \text{---} \\ | \\ \text{---} \circ \end{array} R_{eq} \quad \frac{1}{R_{eq}} = \sum_{i=1}^N \frac{1}{R_i}$$


$R_1 \parallel R_2$ is notation for “ R_1 in parallel with R_2 ”

Generalize: N resistors in series

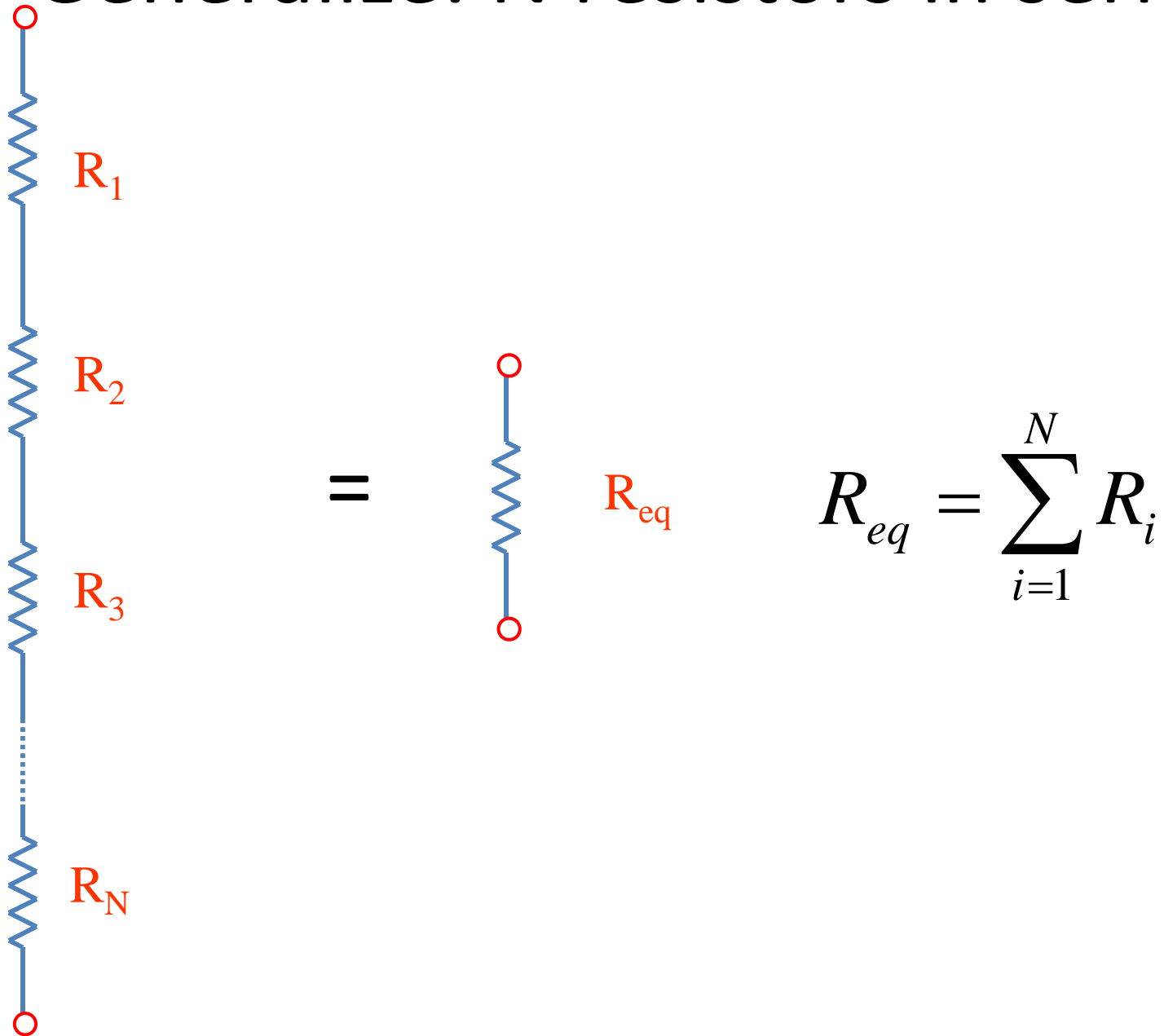

Kirchoff's current law

You have already seen:

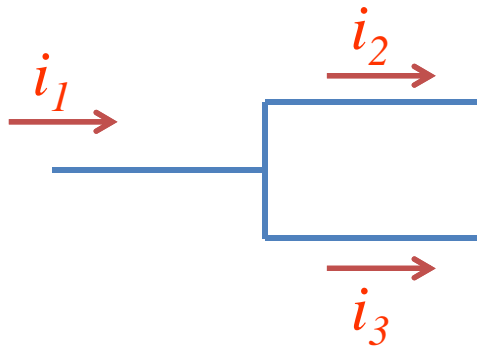

$$i_1 = i_2 + i_3$$

Like water in a river...

More generally:

Sum of currents *entering* node = sum of currents *leaving* node.

Stated as Kirchoff's current law (KCL):


$$\sum_{n=1}^N i_n = 0$$

Current *entering* a node: i_n positive
Current *leaving* a node: i_n negative

Kirchoff's voltage law


$$\sum_{n=1}^N v_n = 0$$

around *any* closed loop.

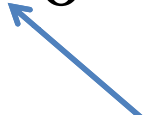


voltage *drops*


Sign of voltage drop

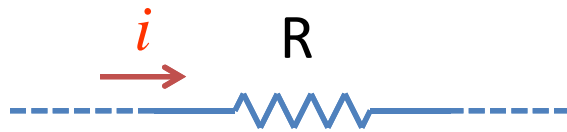


Voltage drop
 $= + i R$

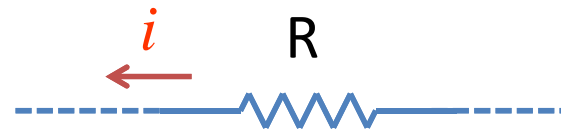

Voltage drop
 $= - i R$

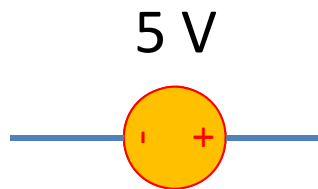

Voltage drop
 $= - 5 \text{ V}$

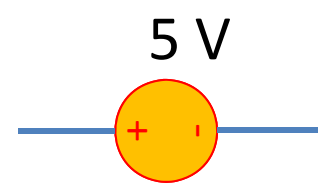



Voltage drop
 $= + 5 \text{ V}$

KVL example

If the voltage is *dropping* as you go around the loop, the voltage drop v_n is *positive*.

Apply KVL to the circuit below

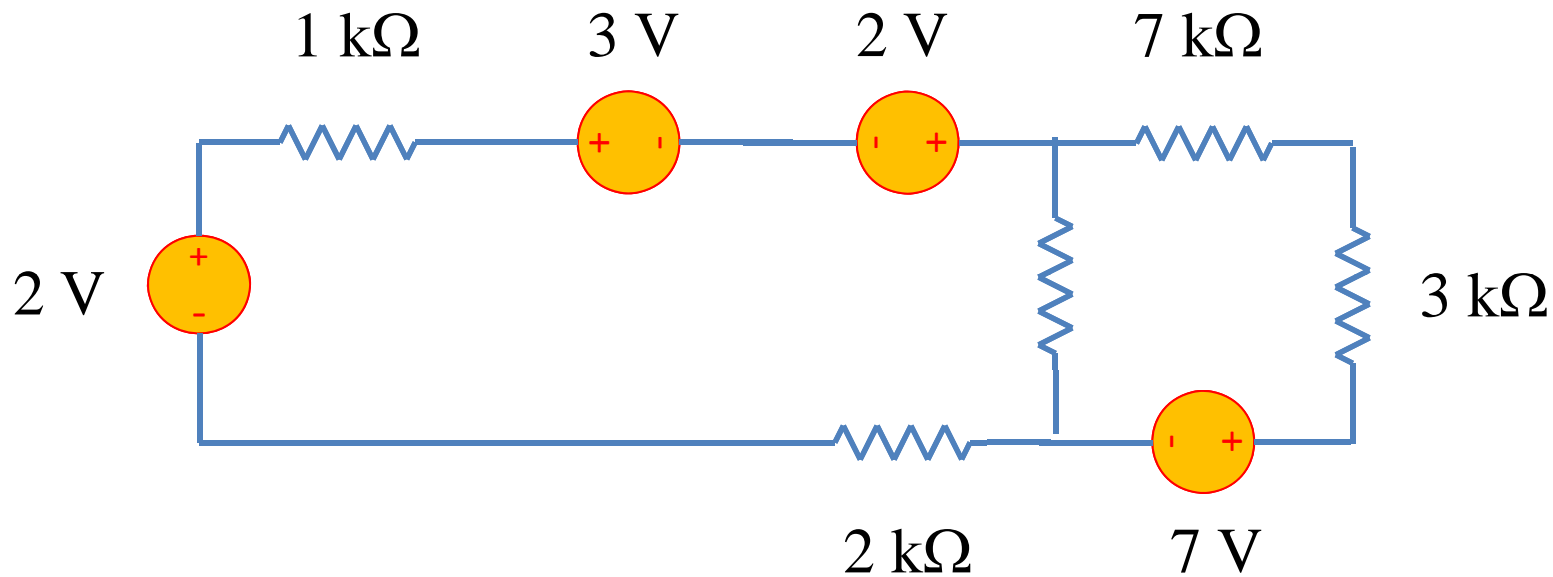

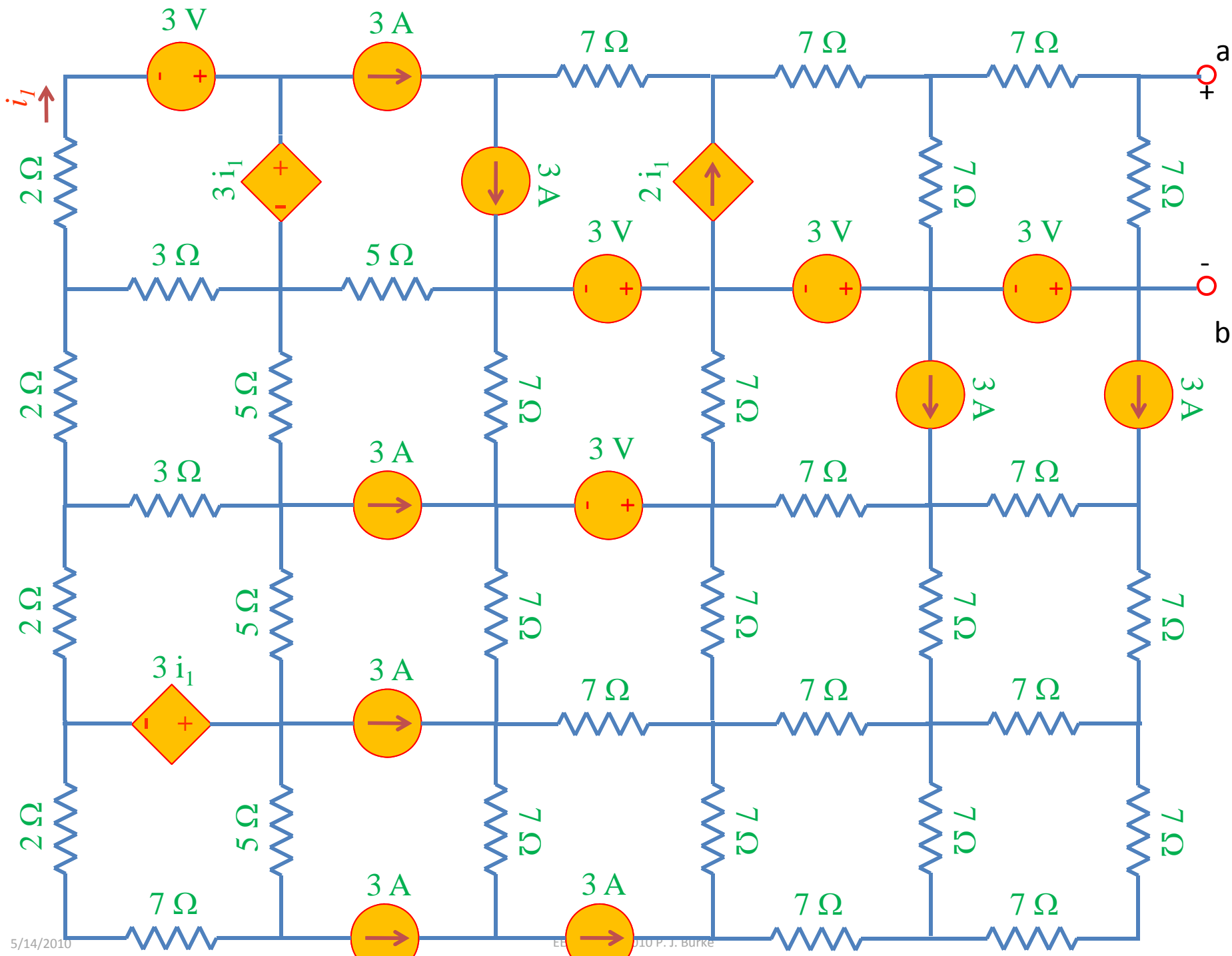


Nodal Analysis(Review)

Based on KCL, use node voltages as circuits variables.

1. Define a reference node.
2. Label remaining nodes (n-1 nodes) e.g. V_1, V_2, V_3, \dots
3. “Supernode”:
 1. Case 1: Voltage source connected to reference node: solves one node.
 2. Case 2: Voltage source not connected to reference: Define supernode
4. Apply KCL all nodes (& supernodes)
 1. Express all i's in terms of v's using Ohm's law
5. Apply KVL to loops with voltage source
6. Solve the n-1 simultaneous equations, to find V's
(e.g. using Kramer's rule)
7. Use Ohm's law to find the currents.

“Supernode”


A node with a voltage source in it...

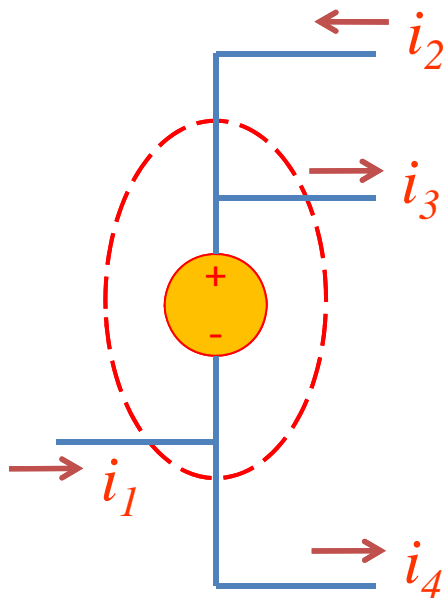


KCL:

Must define a supernode if a voltage source appears when doing nodal analysis...
(unless one end of voltage source connected to reference node)


Nodal analysis example 1

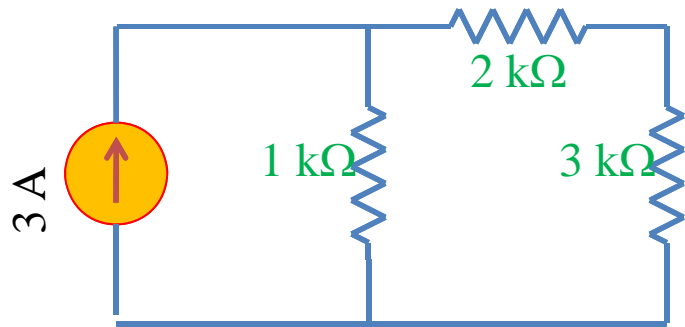

Nodal analysis example 2

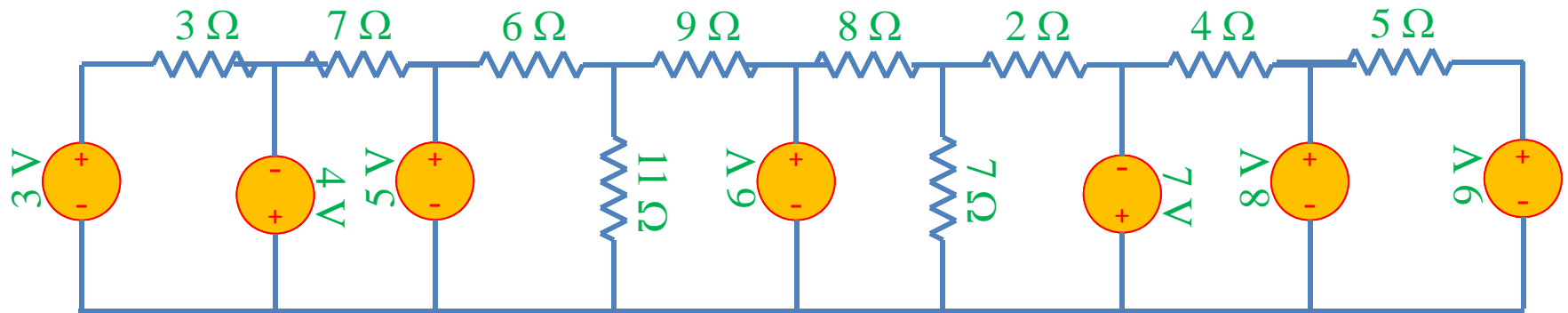


Nodal analysis example 3

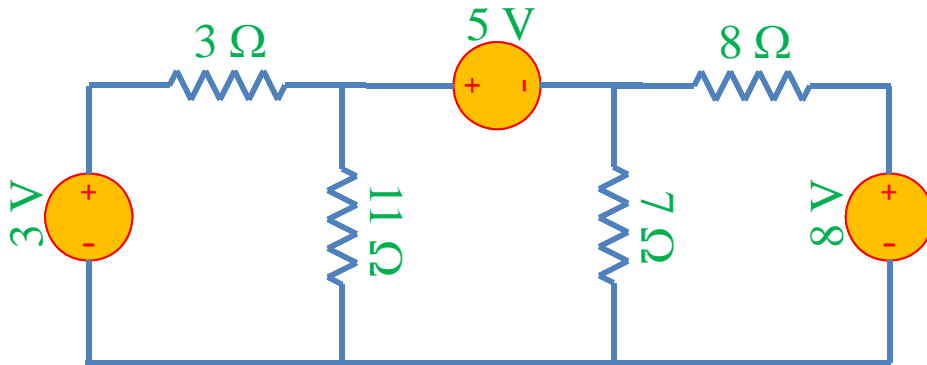


Mesh analysis summary

1. Assign mesh currents i_1, i_2, \dots, i_n
2. “Supermesh” (if current source present):
 1. Case 1: Source only on one side of mesh: Sets current
 2. Case 2: Create supermesh
3. Apply KVL to each mesh
4. Apply KCL to supermeshes
5. Solve for mesh currents (e.g. using Kramer’s rule)
6. Then solve for voltages


Mesh Analysis Example 1

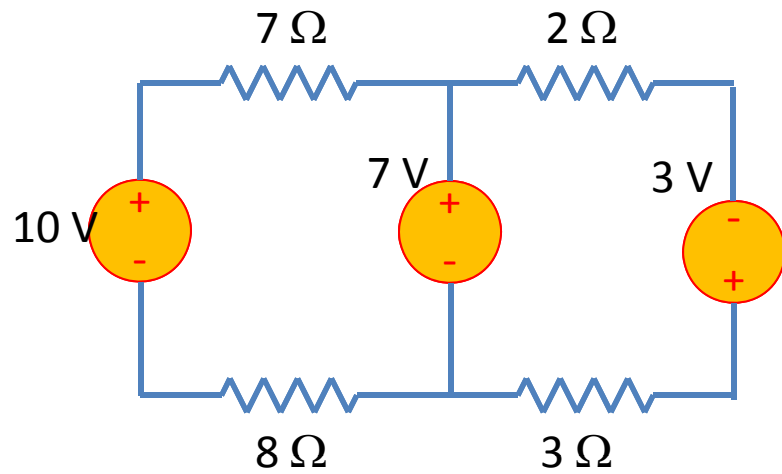


Mesh Analysis Example 2

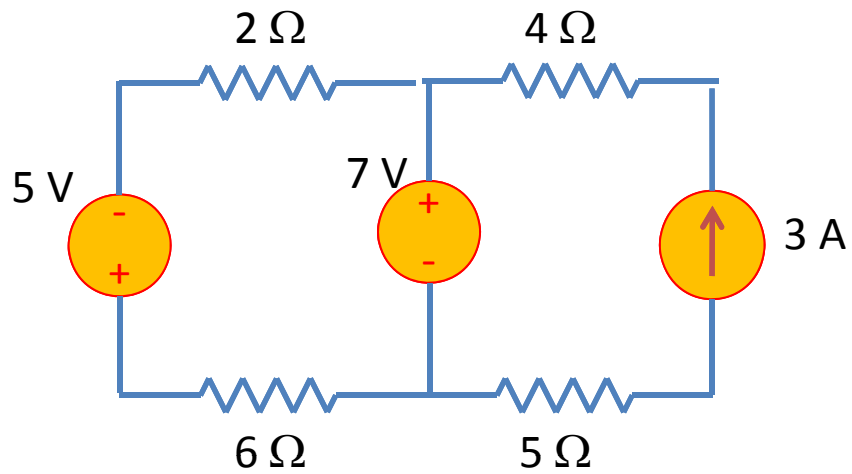

Mesh Analysis Example 3

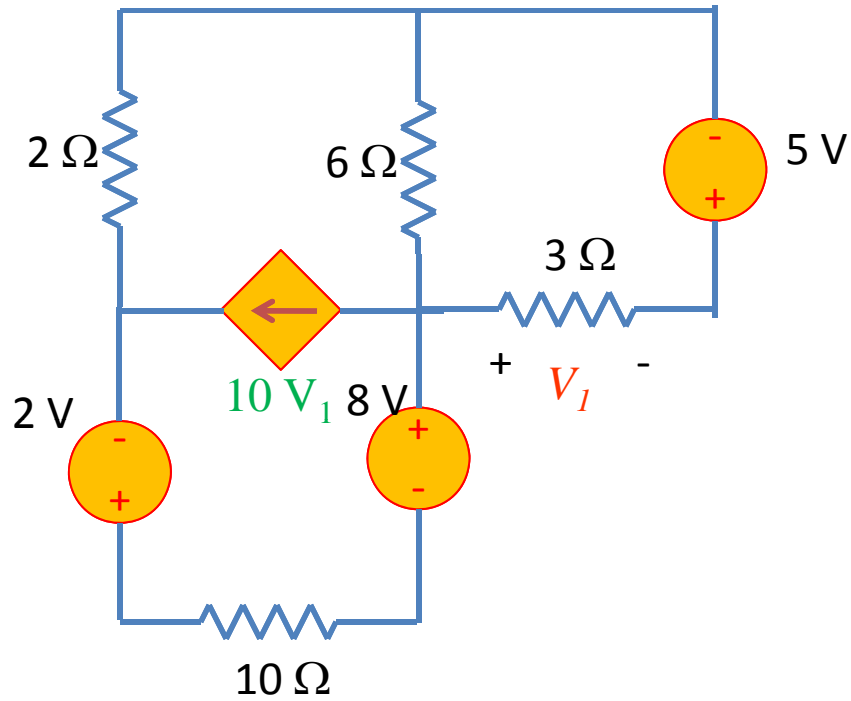

KCL application to supermesh

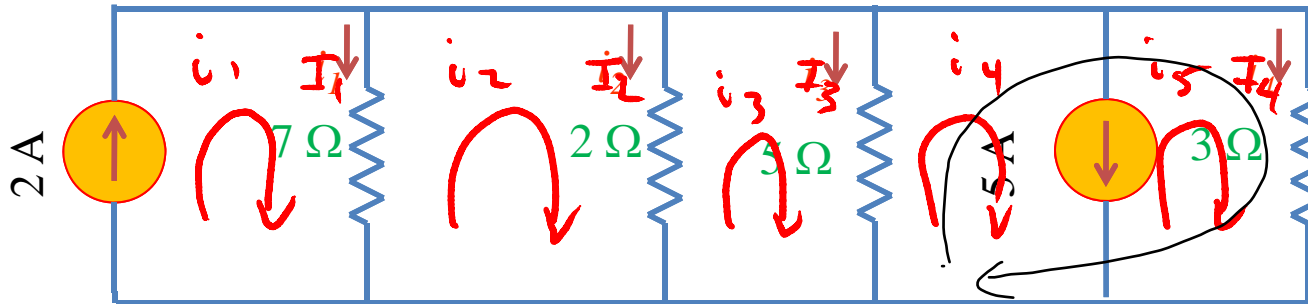


Supermesh

$$i_5 + 5A = i_4$$



Thevenin, Norton Theorems:

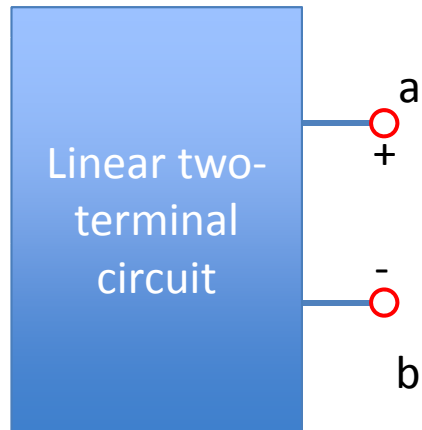

Thevenin:

1. Calculating V_{th} :

Connect nothing to a-b. Calculate voltage. This is V_{th} .

2. Calculating R_{th} :

Method 1:

Connect terminal a to b (short).

Calculate the current from a to b. This is call $I_{short\ circuit}$.

$$R_{th} = V_{th} / I_{short\ circuit}$$

Method 2:

Find the input resistance looking into terminals a-b after all the independent sources have been turned off.


(Voltage sources become shorts, current sources become opens.)

Trick (if dependent sources present):


Apply a 1 A current source to terminals a-b, find V_{ab}

$$R_{th} = V_{ab} / 1A.$$

Equivalent to:

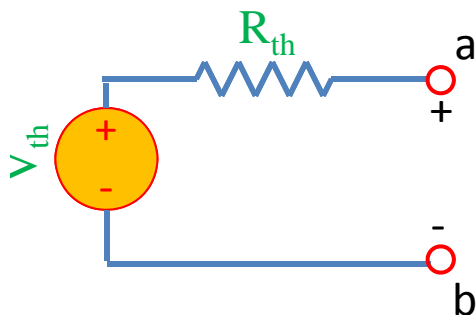

Equivalent to:

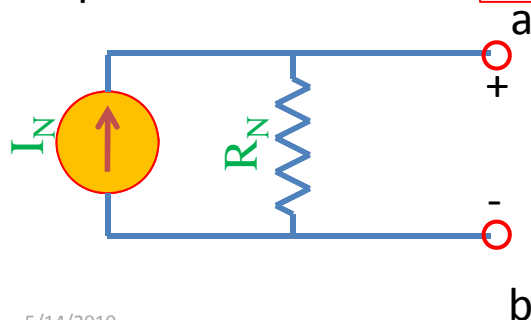

Norton:

1. Calculating R_N :


$$R_N = R_{th}$$

2. Calculating I_N :

$$I_N = V_{th} / R_{th}$$


Thevenin/Norton example 1

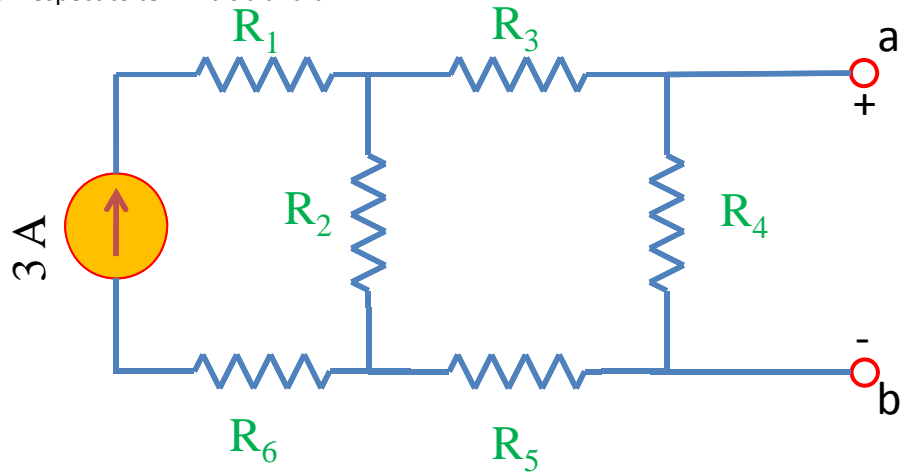Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:




Thevenin/Norton example 2

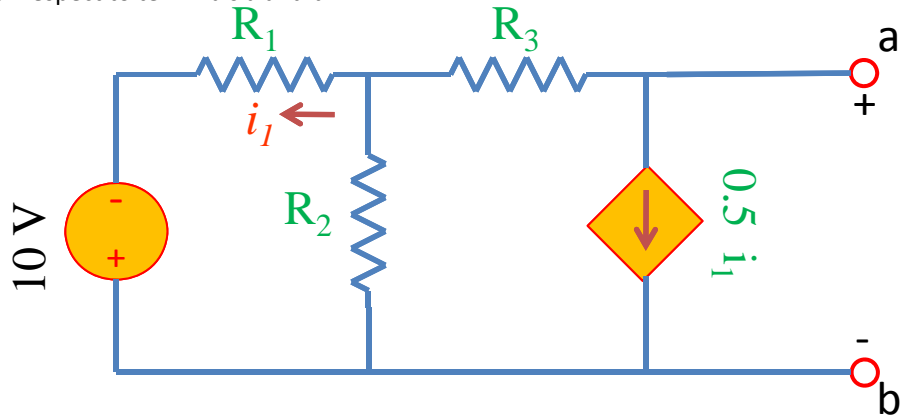Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:



Capacitors

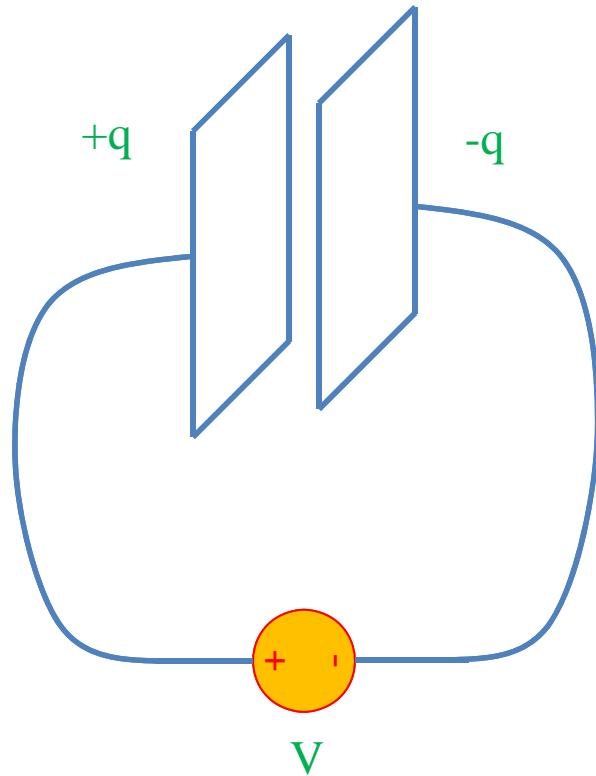

$$q = CV$$

$$C = \frac{\epsilon A}{d}$$

A=area
d=plate separation

Farads[F] = Coulombs/Volt [C]/[V]


$$\epsilon_0 = 8.85 \times 10^{-12} \text{ F / m}$$

$$\epsilon = K\epsilon_0$$


Dielectric constant:

$$K = 3.9 \text{ SiO}_2$$

$$K = 25 \text{ HfO}_2$$

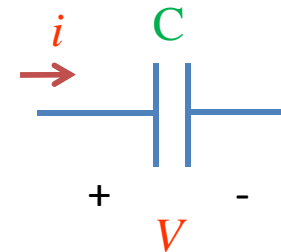


Parallel Capacitors

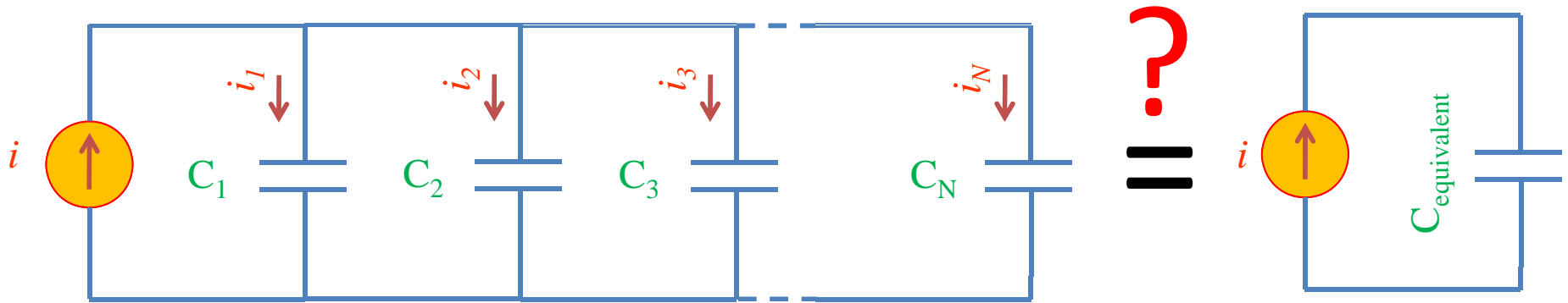

$$C_{eq} = \sum_{i=1}^N C_i$$


Series Capacitors

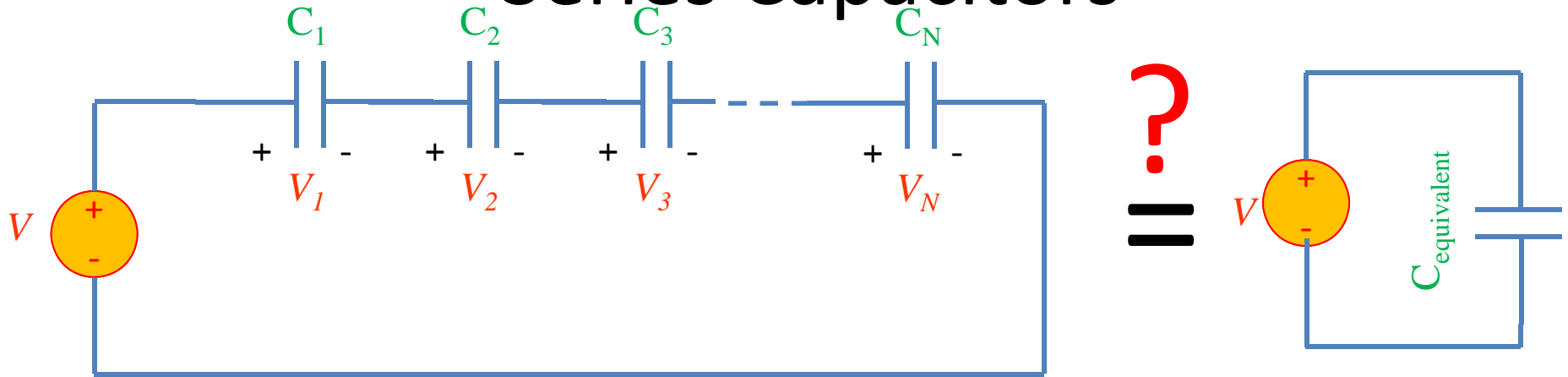


$$\frac{1}{C_{eq}} = \sum_{i=1}^N \frac{1}{C_i}$$

RC circuit

Find $V(t)$, $q(t)$, $i(t)$

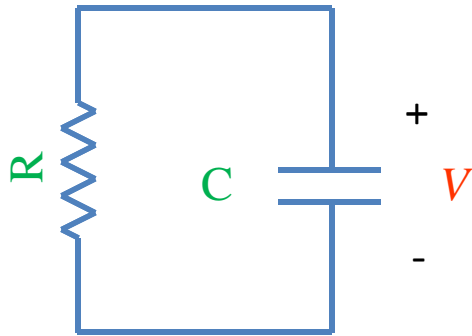

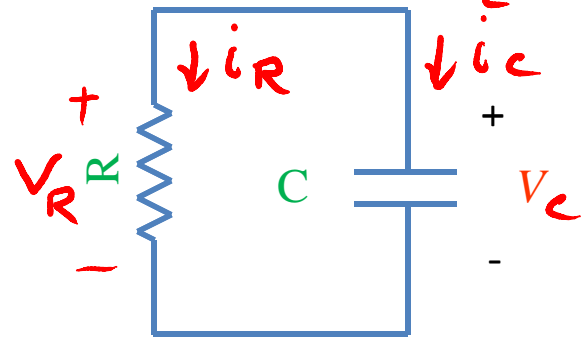
RESISTOR
 $i_R R = V_R = V_C = (-i_C)R$
 KVL $\Rightarrow V_R = V_C$
 Find $V(t), q(t), i(t)$
 KCL $\Rightarrow i_R = -i_C$



RC circuit

CAPACITOR
 $q = CV_C$

$$i_C = C \frac{dV_C}{dt}$$

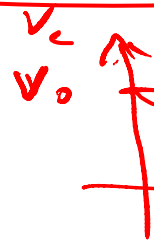

$$\frac{V_C}{R} = C \frac{dV_C}{dt} \quad \tau \equiv RC$$

$$\frac{dV(t)}{dt} = \text{why?} \frac{-1}{RC} V(t)$$

Soln:


$$V(t) = V(t=0) e^{-t/RC}$$

Proof:


$$\begin{aligned} \frac{dV(t)}{dt} &= \frac{d}{dt} \left[V(t=0) e^{-t/RC} \right] \\ &= V(t=0) \frac{d}{dt} \left[e^{-t/RC} \right] = -\frac{1}{RC} \underbrace{V(t=0)}_{\tau/RC} \\ &= -\frac{1}{RC} V(t) \end{aligned}$$

RC circuit

Find $V(t)$, $q(t)$, $i(t)$

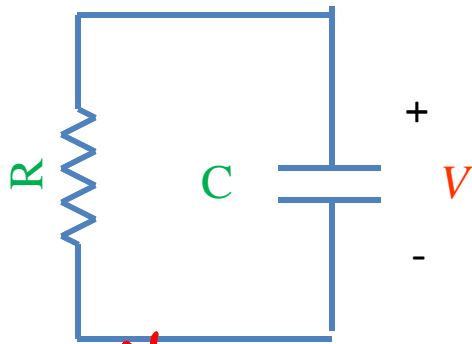


$$V(t) = V(t=0) e^{-t/RC}$$

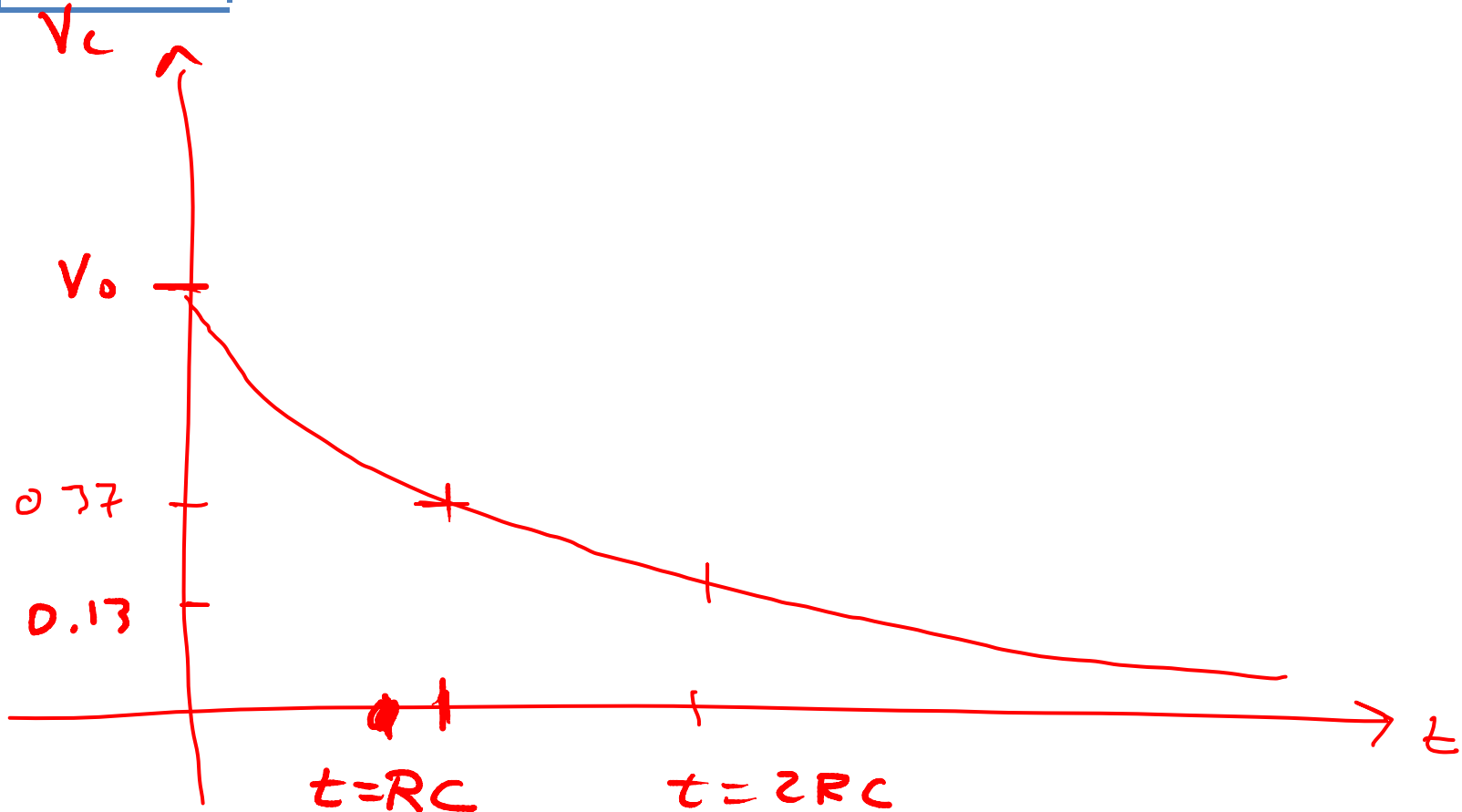


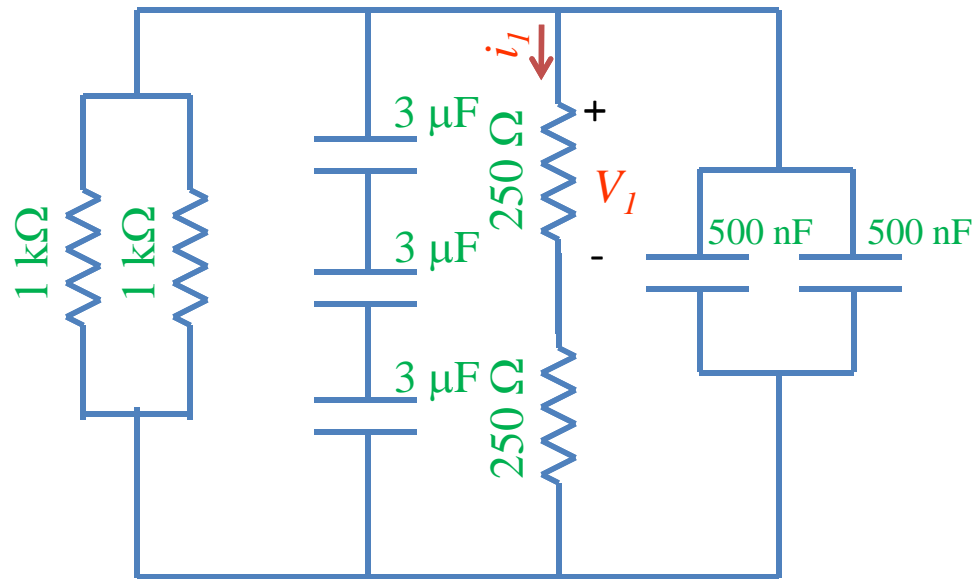Example RC problem 1

Find $i_1(t)$, given that $V_1(t=0) = 3$ Volts



Inductors

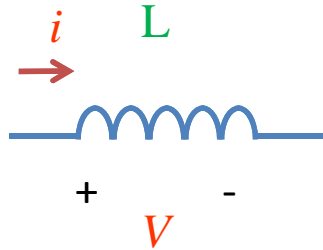

$$L = \frac{N^2 \mu A}{l}$$

A=area

l=wire length

N = # of turns


$\mu = 4 \pi 10^{-6}$ H/m

$$V = L \frac{di}{dt}$$

Henry[H]


$$V = L \frac{di}{dt} \Rightarrow i(t) = \frac{1}{L} \int V(t) dt$$

Series Inductors

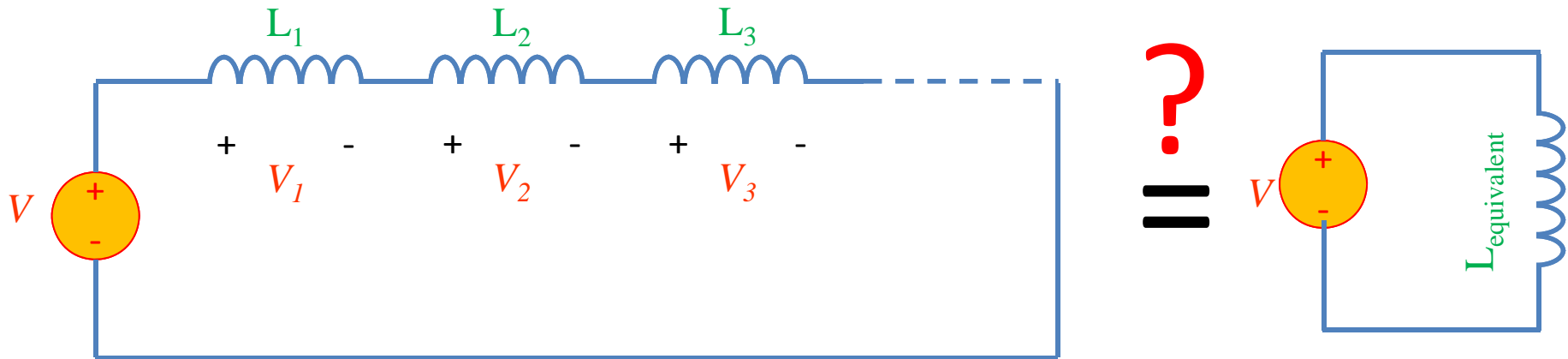

$$L_{eq} = \sum_{i=1}^N L_i$$

Parallel Inductors

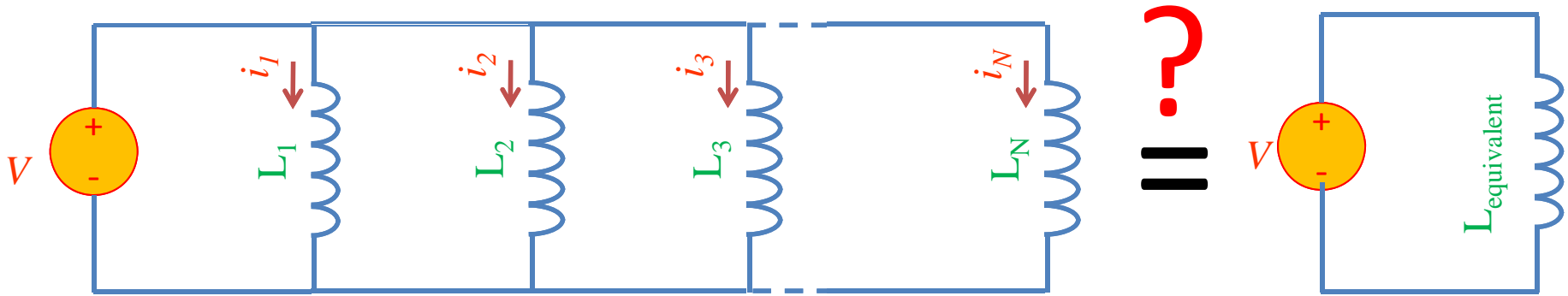


$$\frac{1}{L_{eq}} = \sum_{i=1}^N \frac{1}{L_i}$$

$$V_R = i_R R$$

LR circuit

Find $V(t)$, $i(t)$

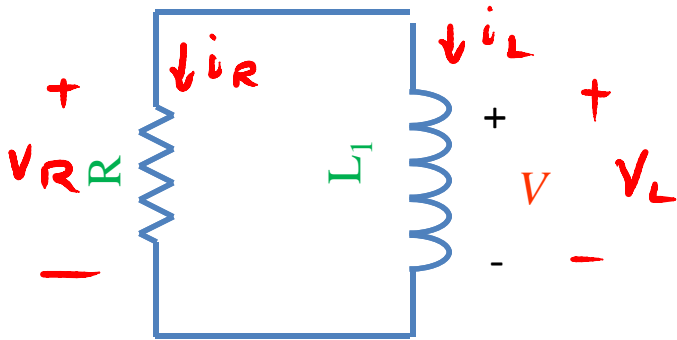

$$KVL \Rightarrow V_L = V_R$$

$$KCL \Rightarrow i_R = -i_L$$

$$L \frac{di_L}{dt} = i_R R$$


$$-i_L R = L \frac{di_L}{dt}$$

$$\Rightarrow \frac{di_L}{dt} = -\frac{1}{\tau} i_L$$

$$V_L = L \frac{di_L}{dt}$$

$$\tau \equiv \frac{L}{R} \quad \text{time constant}$$


$$i_L(t) = i_L(t=0) e^{-t/\tau}$$

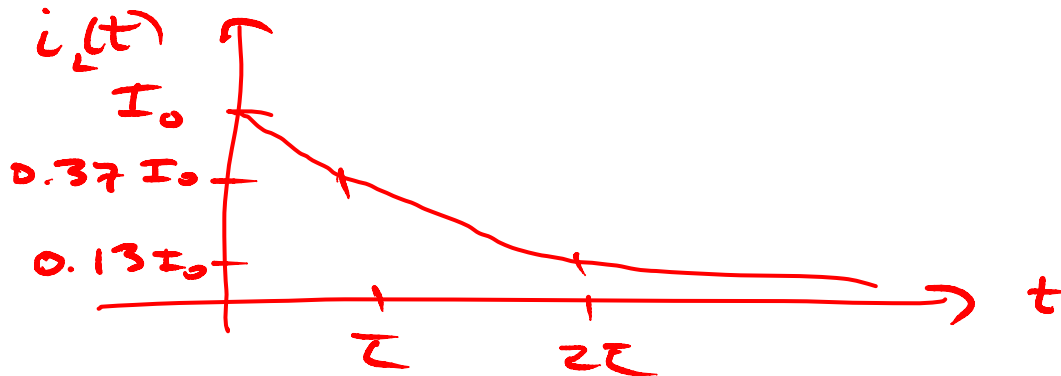

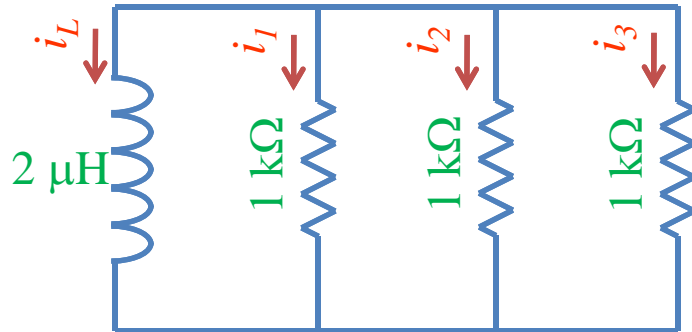
Example LR problem #1

(Students) Find $i_1(t)$ given $i_L(t=0) = 5$ A.

Hint: $i_1+i_2+i_3 = -i_L$. How are i_1, i_2, i_3 related?



Power

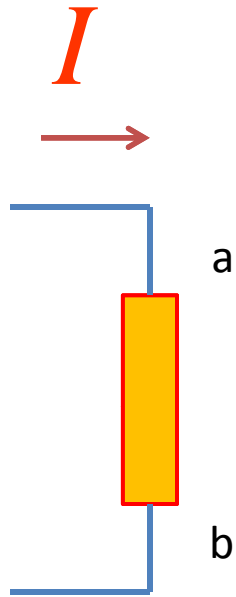

$$I \times V_{ab} = \text{power}$$


Watts [W] = Volt Amp [V-A]

Note: MKSA unit system:
Meters Kilogram Second Amp

Resistor:
Energy lost to heat...

Inductor or capacitor:
Energy **STORED** and can be recovered...

Energy stored

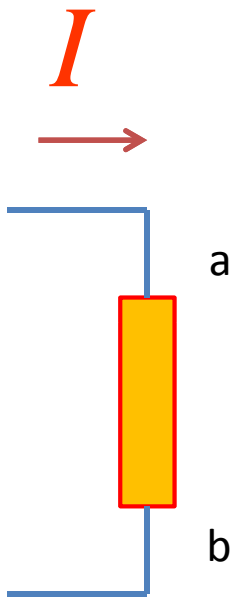

$$I \times V_{ab} = \text{power}$$

Energy:

$$W = \int P dt = \int I \cdot V dt$$

Capacitor stored energy:

$$\int I \cdot V dt = \int C \frac{dV}{dt} \cdot V dt = \frac{1}{2} CV^2 = \frac{Q^2}{2C}$$


Inductor stored energy:

$$\int I \cdot V dt = \int I \cdot L \frac{dI}{dt} dt = \frac{1}{2} LI^2$$


Circuits



$$\mathbf{V} = \mathbf{I} R$$

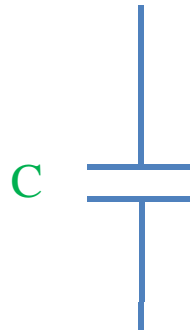

$$\mathbf{V} = \mathbf{I} / j\omega C$$

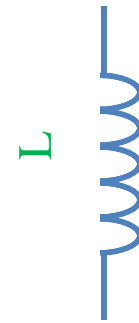

$$\mathbf{V} = j\omega L \mathbf{I}$$

“Impedance”

$$Z = R$$

$$Z = 1 / j\omega C$$

$$Z = j\omega L$$

KCL, KVL hold for relationship
between \mathbf{V} , \mathbf{I} .

Series/Parallel Impedances



$$Z_{eq} = Z_1 + Z_2 + Z_3$$



$$Z_{eq}^{-1} = Z_1^{-1} + Z_2^{-1} + Z_3^{-1}$$

Example Impedance Problem

Find Z_{eq} for this circuit: (students)

