

Announcements:

1. HW5 due Wednesday
2. Midterm #2 is Thursday, covers:
  1. Ch 1-6 (not 5)
  2. RC, LR circuits (small part of ch.7)
  3. Impedance calculation (like HW5) (small part of Ch 9)
  4. No diodes, transistors

# EECS 70A: Network Analysis

## Lecture 12

# Today's Agenda

X

- KCL, KVL ①
- Nodal analysis ③
- Mesh analysis ③
- Thevenin/Norton theorem ②
- R,L,C series, parallel ②
- Impedances ①  $\sin \cos$


$$\begin{array}{c} R \\ \text{---} \\ V = IR \end{array}$$

$$\begin{array}{c} C \\ \text{---} \\ + \text{---} \text{---} \\ Q = CV \\ i = C \frac{dV}{dt} \end{array}$$

$$\begin{array}{c} L \\ \text{---} \\ \text{---} \text{---} \\ V = L \frac{di}{dt} \end{array}$$

qex


# Resistors

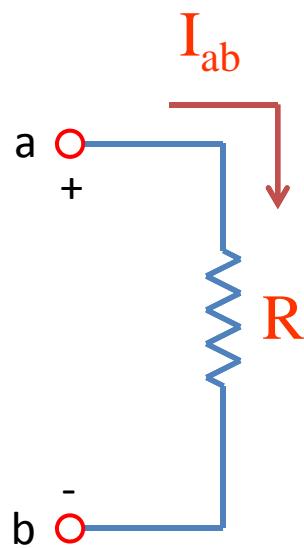

$$V_{ab} = I_{ab} \times R$$

Resistance units: Ohms [ $\Omega$ ]

# Generalize: N resistors in parallel

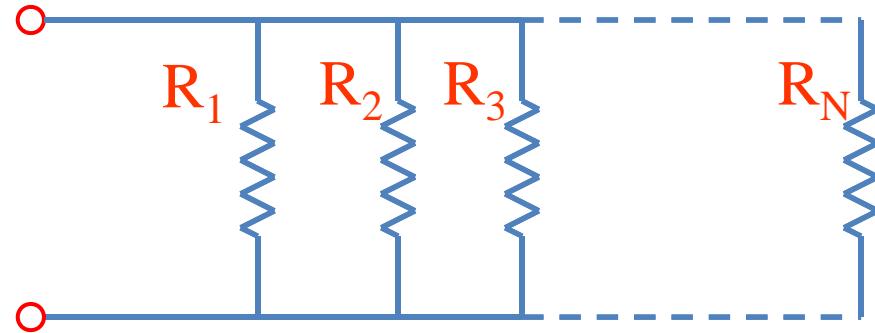


$$= \frac{1}{R_{eq}} = \sum_{i=1}^N \frac{1}{R_i}$$


The equivalent resistor  $R_{eq}$  is shown as a single vertical blue zigzag line connecting two red terminal circles.

$R_1 \parallel R_2$  is notation for “ $R_1$  in parallel with  $R_2$ ”


# Generalize: N resistors in series

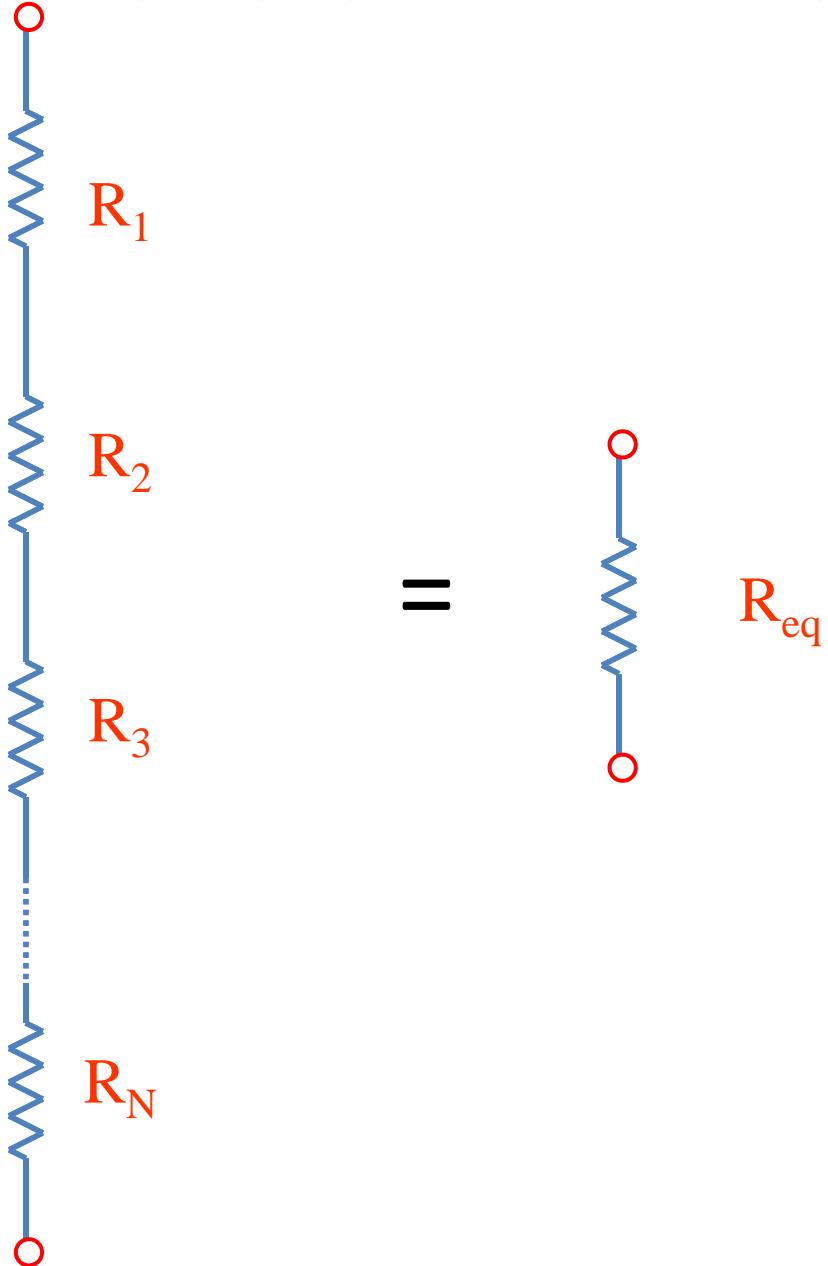

$$R_{eq} = \sum_{i=1}^N R_i$$

# Kirchoff's current law

You have already seen:

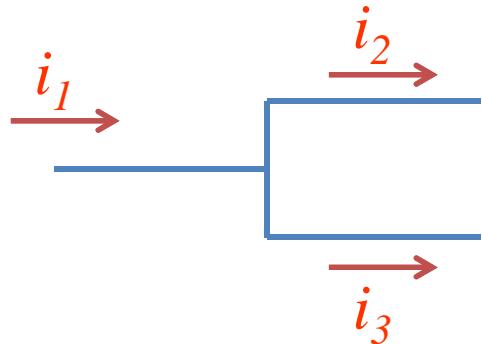

$$i_1 = i_2 + i_3$$

*Like water in a river...*

More generally:

Sum of currents *entering* node = sum of currents *leaving* node.

Stated as Kirchoff's current law (KCL):

$$\sum_{n=1}^N i_n = 0$$


Current *entering* a node:  $i_n$  positive  
Current *leaving* a node:  $i_n$  negative

# Kirchoff's voltage law


$$\sum_{n=1}^N v_n = 0 \quad \text{around } \textit{any} \text{ closed loop.}$$

*voltage drops*


# Sign of voltage drop

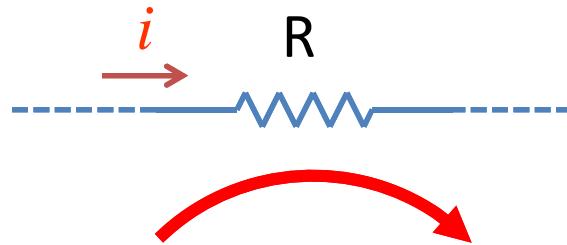


$$\text{Voltage drop} = + i R$$

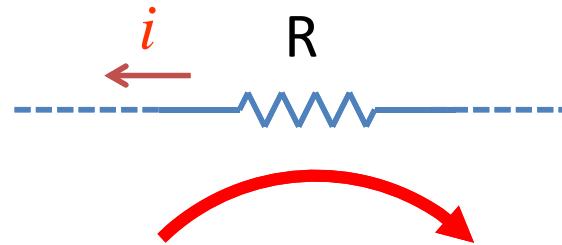

$$\text{Voltage drop} = - i R$$

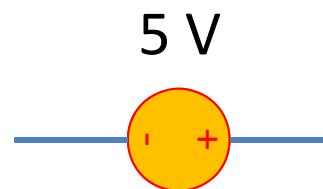

$$\text{Voltage drop} = - 5 \text{ V}$$

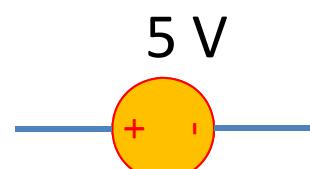


$$\text{Voltage drop} = + 5 \text{ V}$$

# KVL example

If the voltage is *dropping* as you go around the loop, the voltage drop  $v_n$  is *positive*.

Apply KVL to the circuit below

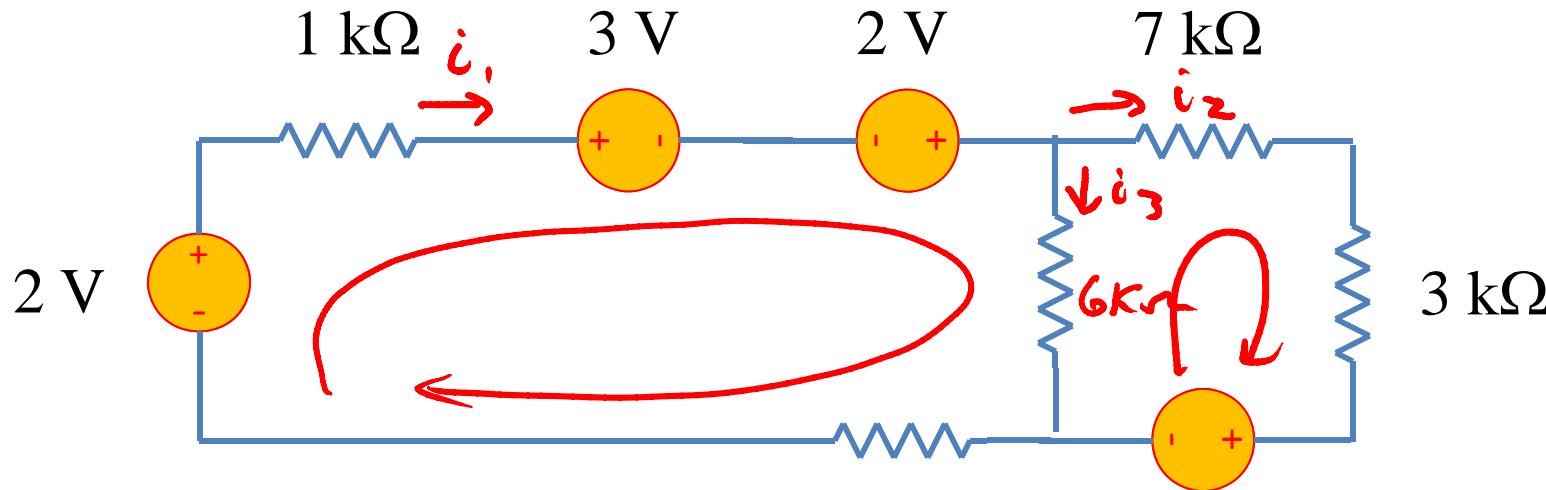


$$-2V + i_1 \cdot 1k\Omega + 3V - 2V + 6k\Omega i_3 + 2k\Omega i_1 = 0$$

$$-6k\Omega i_3 + 7k\Omega i_2 + 3k\Omega i_2 + 7V = 0$$

---


$$\text{Ex #2} \quad V = \frac{10A \cdot 1k\Omega}{1000\Omega} = 10,000V \quad V = 10,000V$$

$$= 10A \cdot 1000\Omega = 10,000V$$

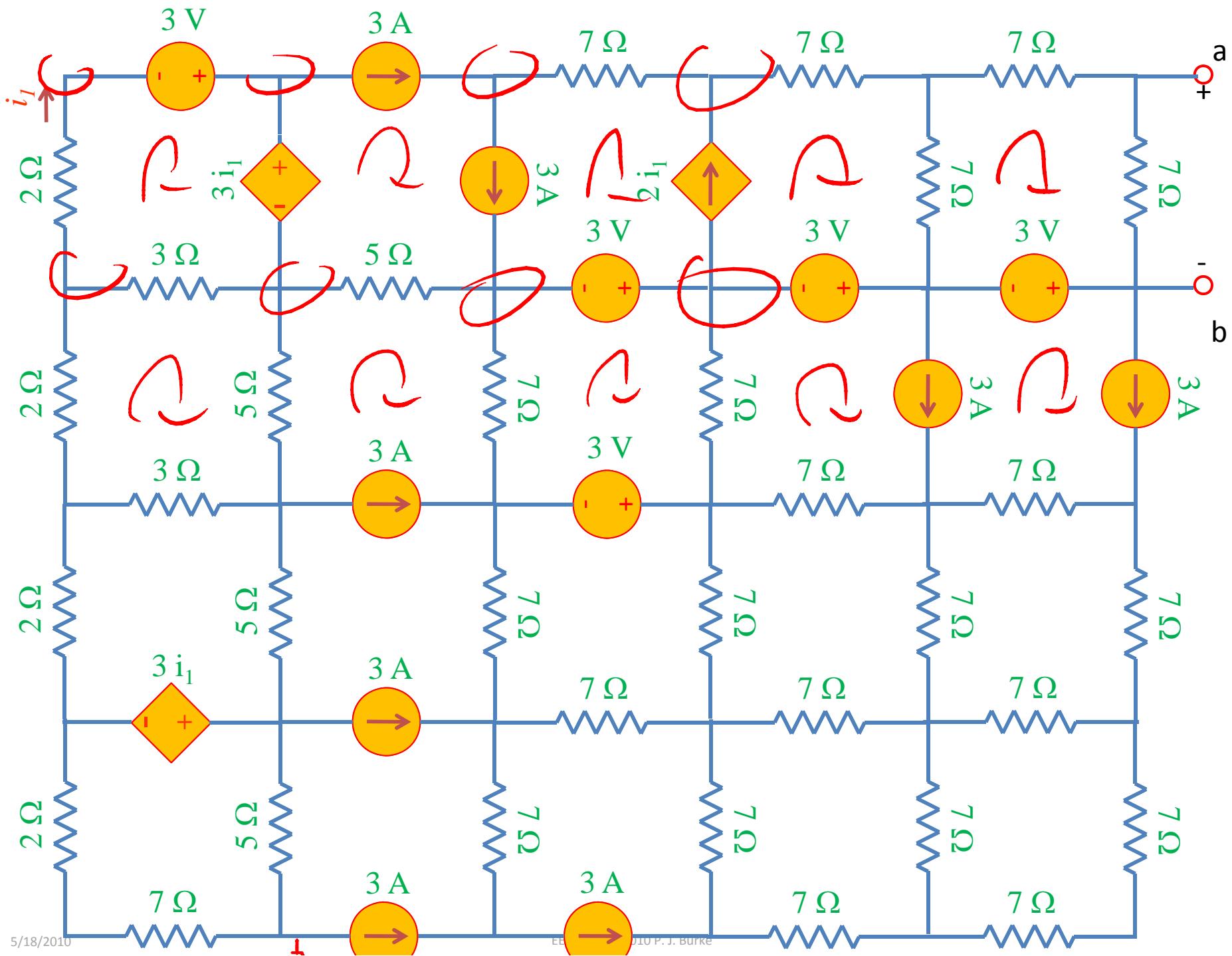


# Nodal Analysis(Review)

~~Based on KCL~~, use node voltages as circuits variables.

1. Define a reference node.
2. Label remaining nodes ( $n-1$  nodes) e.g.  $V_1, V_2, V_3, \dots$
3. “Supernode”:
  1. Case 1: Voltage source connected to reference node: solves one node.
  2. Case 2: Voltage source not connected to reference: Define supernode
- 4. Apply KCL all nodes (& supernodes)
  1. Express all  $i$ 's in terms of  $v$ 's using Ohm's law
- 5. Apply KVL to loops with voltage source
6. Solve the  $n-1$  simultaneous equations, to find  $V$ 's  
(e.g. using Kramer's rule)
7. Use Ohm's law to find the currents.

# “Supernode”

A node with a voltage source in it...

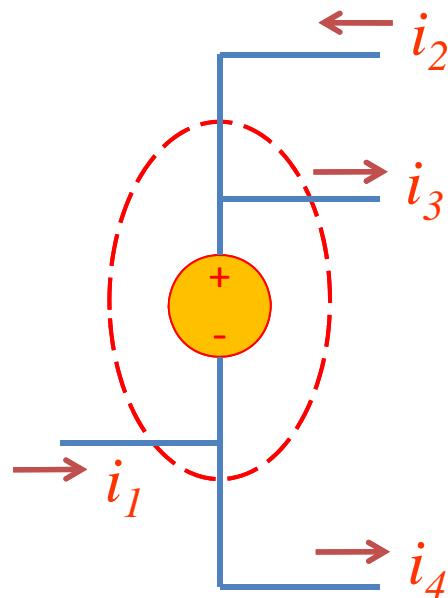


KCL:

$$\dot{e} \\ IN = OUT$$

$$i_1 + i_2 = i_3 + i_4$$

Must define a supernode if a voltage source appears when doing nodal analysis...  
(unless one end of voltage source connected to reference node)

# Nodal analysis example 1

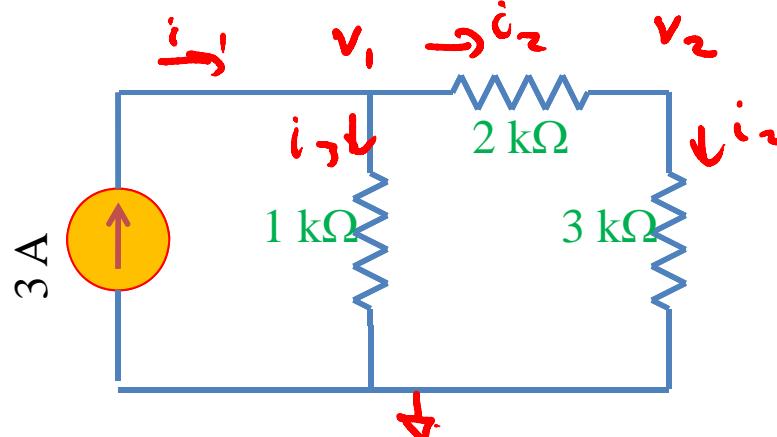

KCL @ N1

$$i_1 = i_2 + i_3$$

$$3A = \frac{V_1 - V_2}{2k\Omega} + \frac{V_1}{1k\Omega}$$

KCL @ N2

$$i_2 = i_3$$

$$\frac{V_1 - V_2}{2k\Omega} = \frac{V_2}{3k\Omega}$$

2 eq  $\Leftrightarrow$  2 unknowns.


Solve for  $V_1, V_2$ .

Back : Find  $i_1 = 3A$

$$i_2 = \frac{V_1 - V_2}{2k\Omega}$$

$$i_3 = \frac{V_1}{1k\Omega}$$

# Nodal analysis example 2

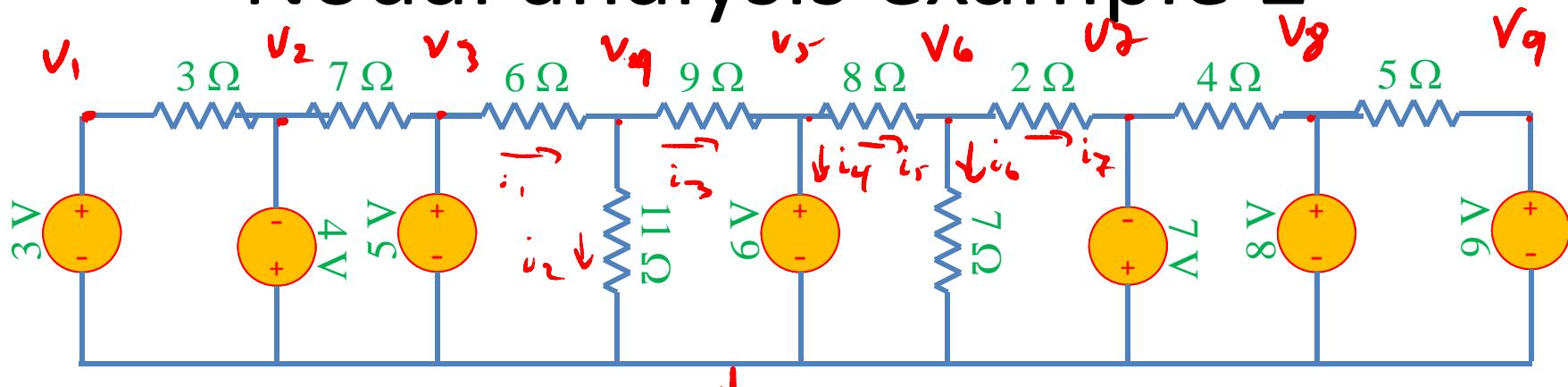

$$v_1 = 3V \quad v_2 = -4V \quad v_3 = 5V \quad v_4 = ???$$

$$v_5 = 6V \quad \cancel{v_6 = ??} \quad \cancel{v_7 = ??} \quad v_6 = ?? \quad v_7 = -7V$$

$$v_8 = 8V \quad v_9 = 9V$$

KCL @ NODE 4       $i_1 = i_2 + i_3 \Rightarrow \frac{v_3 - v_4}{6} = \frac{v_4 - 0}{11}$       FIND  $v_4$

$$\frac{v_3 - v_4}{6} = \frac{v_4}{11}$$

$$v_3 - v_4 = \frac{6}{11}v_4$$

$$v_3 = \frac{17}{11}v_4$$

KCL @ N6

$$i_5 = i_6 + i_7 \Rightarrow \frac{v_5 - v_6}{8} = \frac{v_6}{7} + \frac{v_6 - v_7}{2}$$

$$\frac{v_5 - v_6}{8} = \frac{v_6}{7} + \frac{v_6 - v_7}{2}$$

$$v_5 - v_6 = \frac{8}{7}v_6 + \frac{8}{2}(v_6 - v_7)$$

$$v_5 - v_6 = \frac{22}{7}v_6 - 4(v_6 - v_7)$$

$$v_5 - v_6 = \frac{10}{7}v_6 - 4v_7$$

$$v_5 = \frac{17}{7}v_6 - 4v_7$$


SIGN?

$$\frac{v_4 - v_5}{9} \rightarrow i_3$$

$$i_3 = \frac{v_4 - v_5}{9}$$

for  $v_1, v_2, \dots, v_9$   
next: FIND  $i_1, i_2, \dots, i_9$

# Nodal analysis example 3

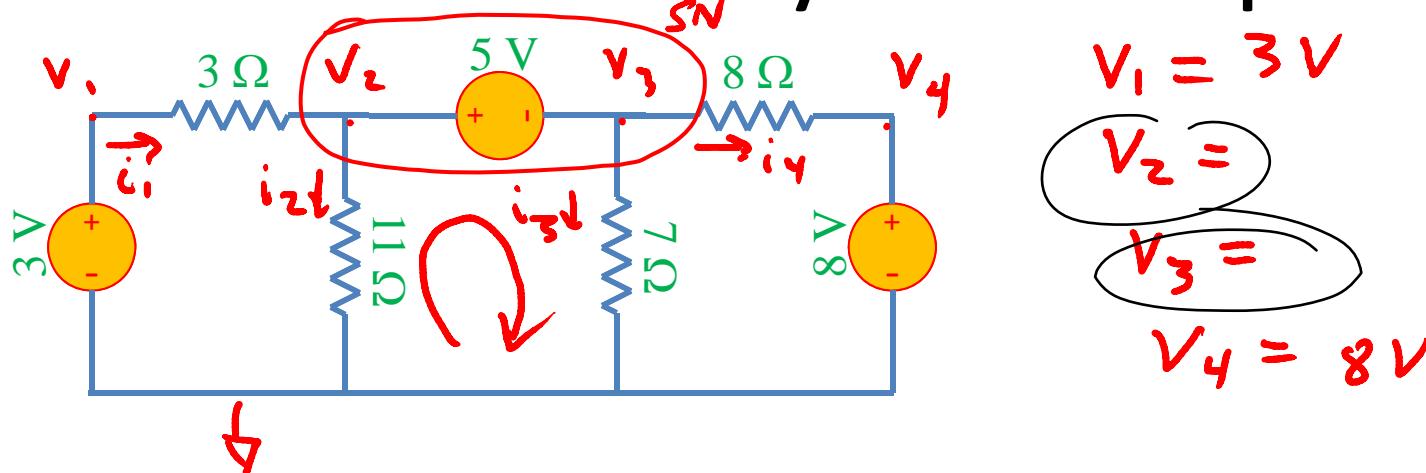

KCL @ ~~node 1~~ SN

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{v_1 - v_2}{3} = \frac{v_2}{11} + \frac{v_3}{7} + \frac{v_3 - v_4}{8}$$

5V      3Ω  
5      3

Node 1 node ignore

KVL loop containing voltage

$$-i_2 11 + 5v + i_3 7 = 0$$

$$- \left( \frac{v_2}{11} \right) 11 + 5v + \left( \frac{v_3}{7} \right) 7 = 0$$

Solve  $v_2, v_3$ .


Then: get ~~i1~~

currents from  
voltages


# Mesh analysis summary

1. Assign mesh currents  $i_1, i_2, \dots, i_n$  
2. “Supermesh” (if current source present):
  1. Case 1: Source only on one side of mesh: Sets current
  2. Case 2: Create supermesh
3. Apply KVL to each mesh
4. Apply KCL to supermeshes
5. Solve for mesh currents (e.g. using Kramer's rule)
6. Then solve for voltages

# Mesh Analysis Example 1

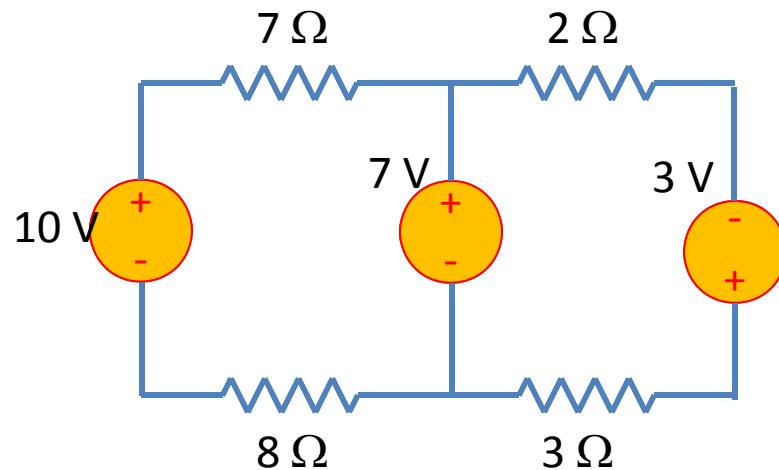


## Mesh Analysis Example 2

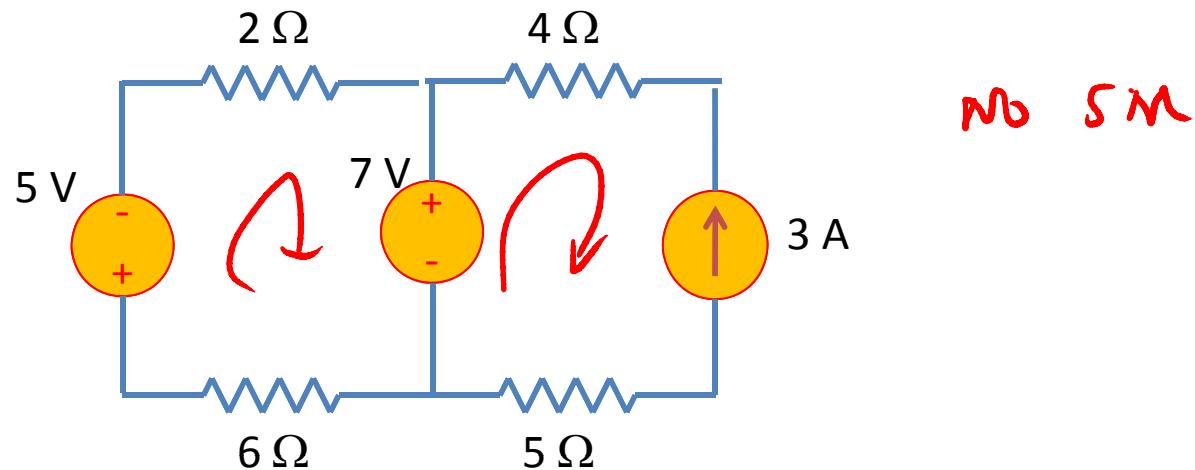

# Mesh Analysis Example 3

*3 unknowns*

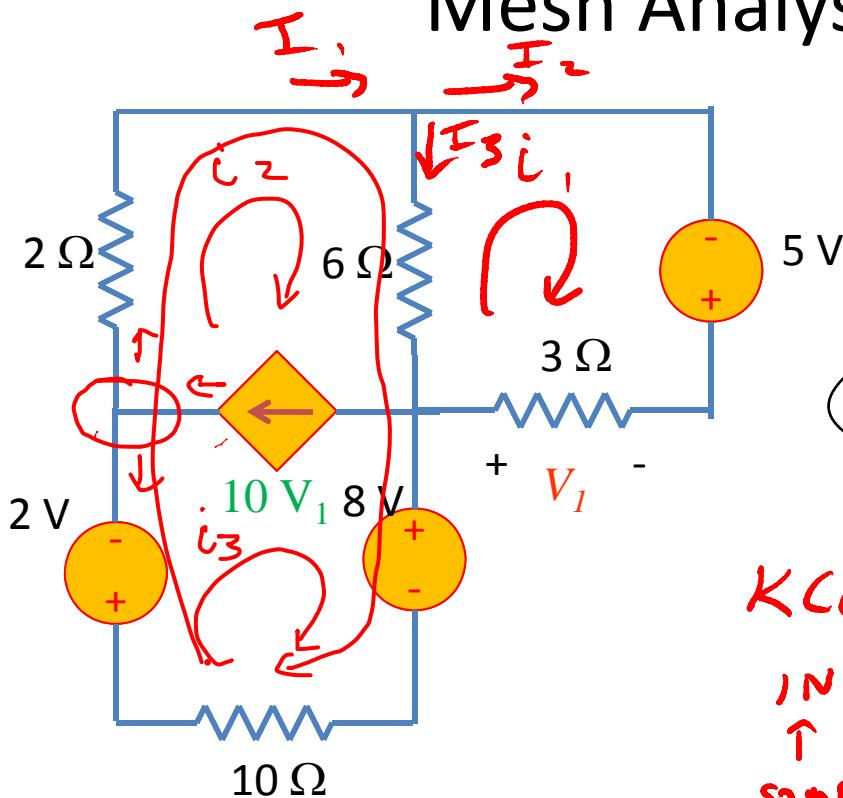

$$I_3 = i_2 - i_1$$

$$I_1 = i_2$$

$$I_2 = i_1$$

KVL MESH 1

$$(i_1 - i_2)6 - 5V + i_3 3 = 0$$

KVL SUPERMESH

$$2V + 2i_2 + 6(i_2 - i_1) \cancel{+ 8} + i_3 10 = 0$$

KCL to "+ junction"

$$\begin{matrix} \text{IN} = \text{OUT} \\ \uparrow \quad \nwarrow \\ \text{SOURCE} \quad \text{MESH} \end{matrix}$$


$$10V_1 = i_2 - i_3$$

Find  $i_1, i_2, i_3$


Find  $I_1, I_2, I_3$

Ohm Find voltages

# KCL application to supermesh

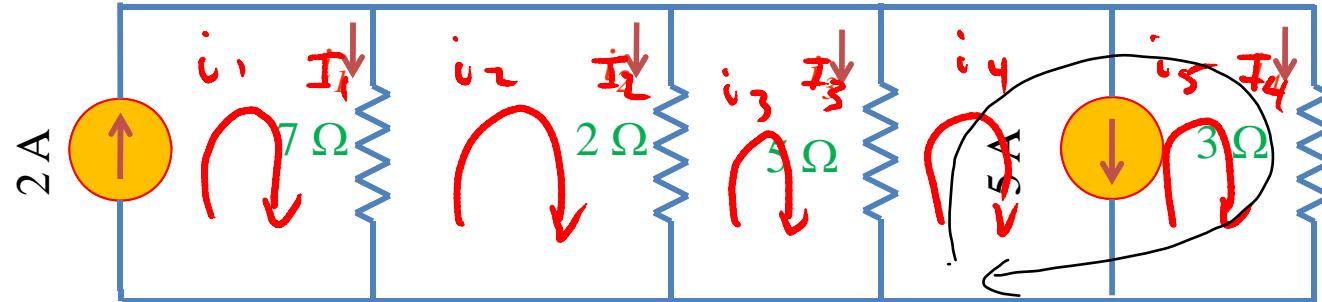


$$i_5 + 5A = i_4$$

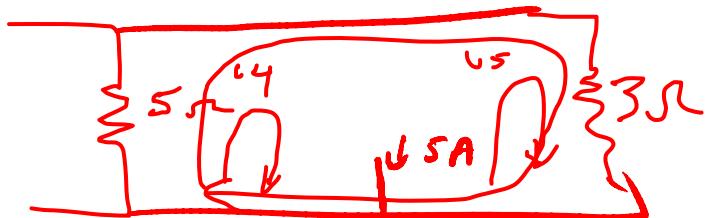


# Thevenin, Norton Theorems:



Equivalent to:

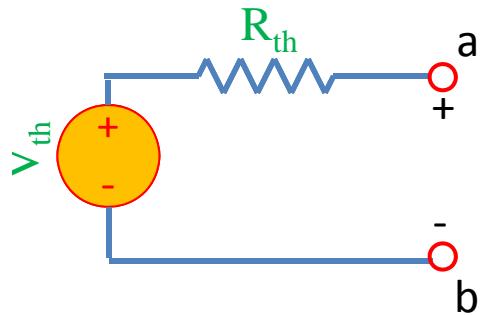

Equivalent to:

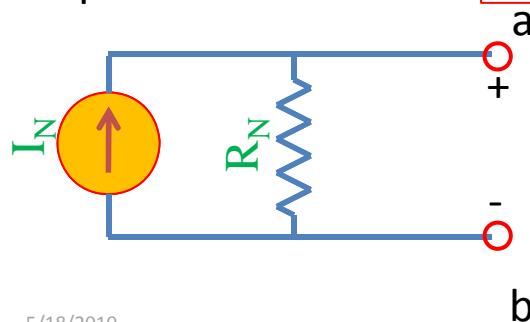

Thevenin:

## 1. Calculating $V_{th}$ :

Connect nothing to a-b. Calculate voltage. This is  $V_{th}$ .

## 2. Calculating $R_{th}$ :

### Method 1:

Connect terminal a to b (short).

Calculate the current from a to b. This is call  $I_{\text{short circuit}}$ .

$$R_{th} = V_{th} / I_{\text{short circuit}}$$

### Method 2:

Find the input resistance looking into terminals a-b after all the independent sources have been turned off.

(Voltage sources become shorts, current sources become opens.)

### *Trick (if dependent sources present):*

Apply a 1 A current source to terminals a-b, find  $V_{ab}$

$$R_{th} = V_{ab} / 1A. \quad \text{TRICK 2: APPLY 1V SOURCE TO AB}$$

FIND

$I_{ab}$

THEN

$$R_{th} = \frac{V_{ab}}{I_{ab}} = R_{12}$$

Norton:

## 1. Calculating $R_N$ :


$$R_N = R_{th}$$

## 2. Calculating $I_N$ :

$$I_N = V_{th} / R_{th}$$

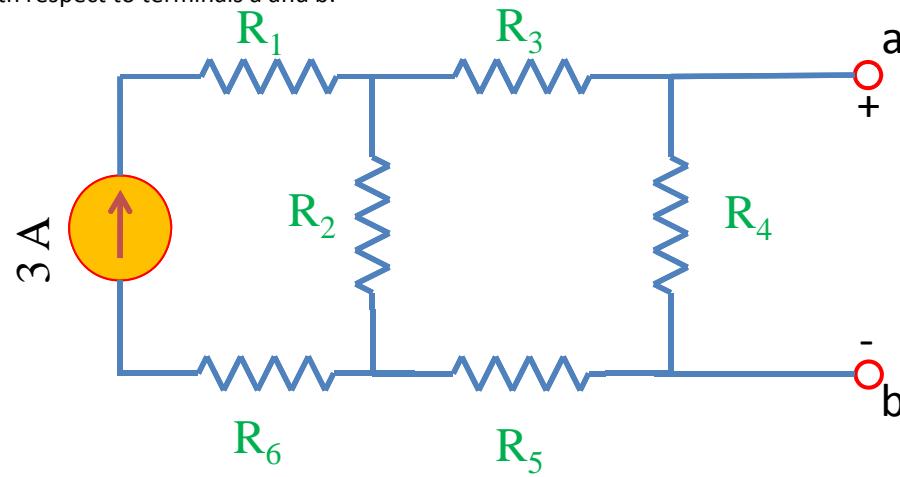
# Thevenin/Norton example 1

Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:


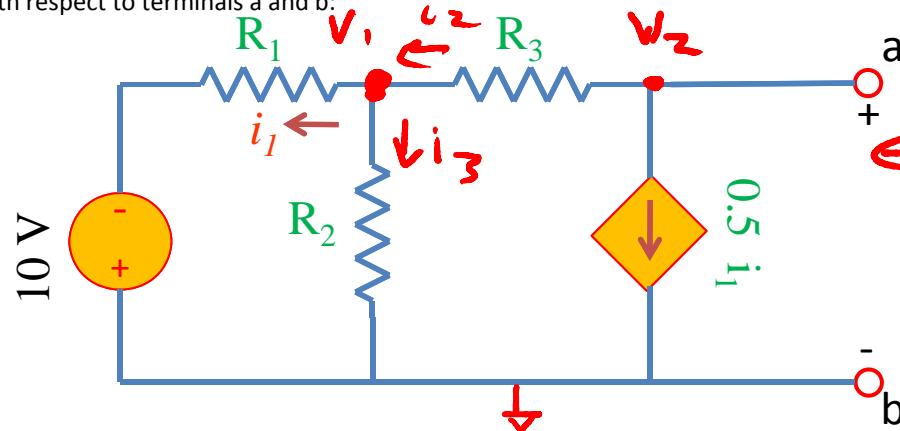
# Thevenin/Norton example 2

Find the Thevenin & Norton equivalent circuit of the circuit below with respect to terminals a and b:



1)  $V_{th}$ : Find  $V_{ab}$

KCL @ N1:

$$i_2 = i_1 + i_3$$

$$\frac{V_2 - V_1}{R_3} = \frac{V_1 + 10V}{R_1} + \frac{V_1}{R_2}$$


KCL @ N2:

$$i_2 = -0.5i_1$$

$$\frac{V_2 - V_1}{R_3} = -0.5 \left( \frac{V_1 + 10V}{R_1} \right)$$

FINDS  $V_1, V_2$

$$V_{ab} = V_2 \Rightarrow = V_{th}$$

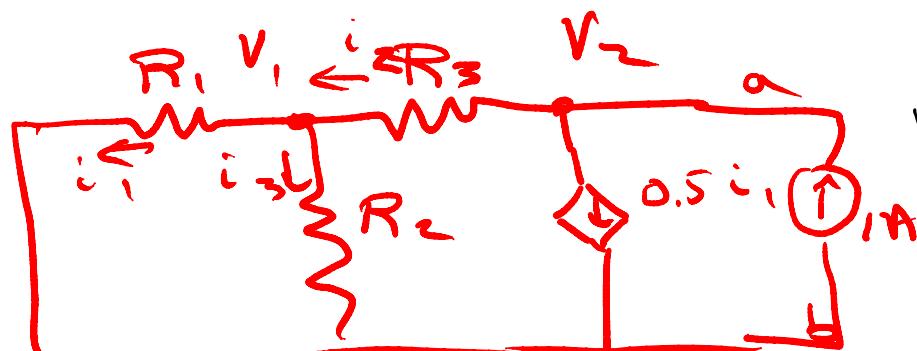

→ TRICK: APPLY 1A  
2 NODES KCL N1  
N2


SOLVE  $V_1, V_2$   
 $V_2 = V_{ab}$

$i_1 + i_3 = i_2 \Rightarrow \frac{V_1}{R_1} + \frac{V_1}{R_2} = \frac{V_2 - V_1}{R_3}$

$1A = \frac{1}{2}i_1 + i_2 = \frac{V_2 - V_1}{R_3} + \frac{1}{2}\frac{V_1}{R_2}$

$R_{th} = \frac{V_{ab}}{1A} = \frac{V_2 - V_1}{\frac{V_2 - V_1}{R_3} + \frac{1}{2}\frac{V_1}{R_2}}$

# Capacitors

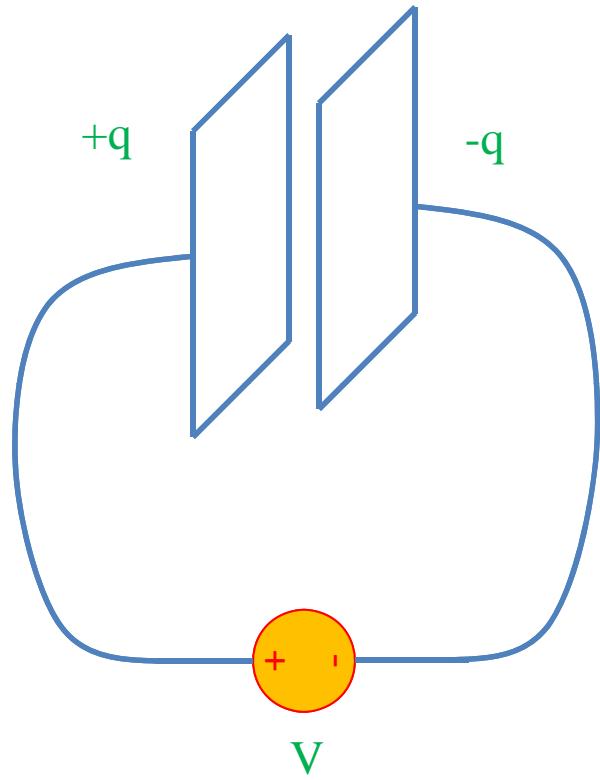

$$q = CV$$

$$C = \frac{\epsilon A}{d}$$

A=area  
d=plate separation

Farads[F] = Coulombs/Volt [C]/[V]


$$\epsilon_0 = 8.85 \times 10^{-12} F / m$$

$$\epsilon = K\epsilon_0$$


Dielectric constant:

$$K = 3.9 \text{ SiO}_2$$

$$K = 25 \text{ HfO}_2$$

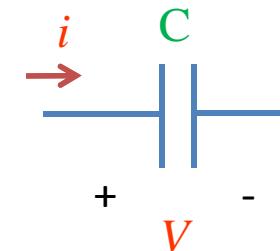


# Parallel Capacitors

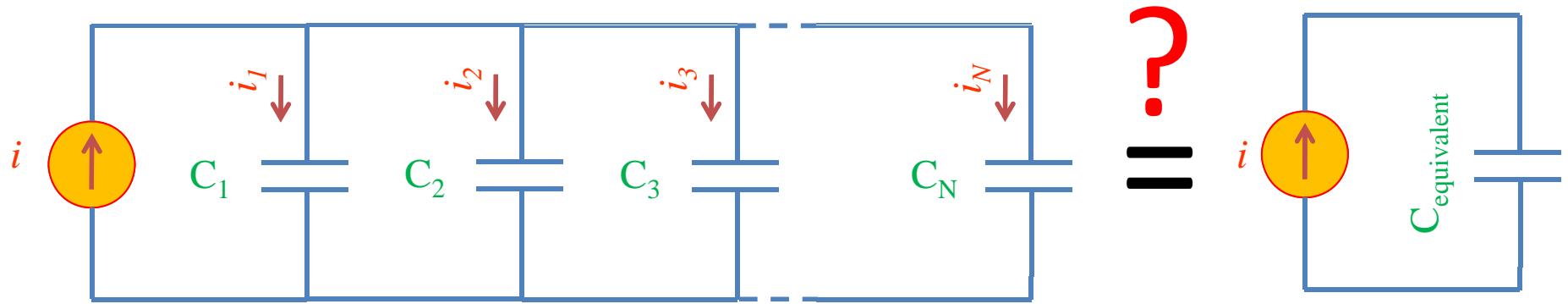

$$C_{eq} = \sum_{i=1}^N C_i$$


# Series Capacitors

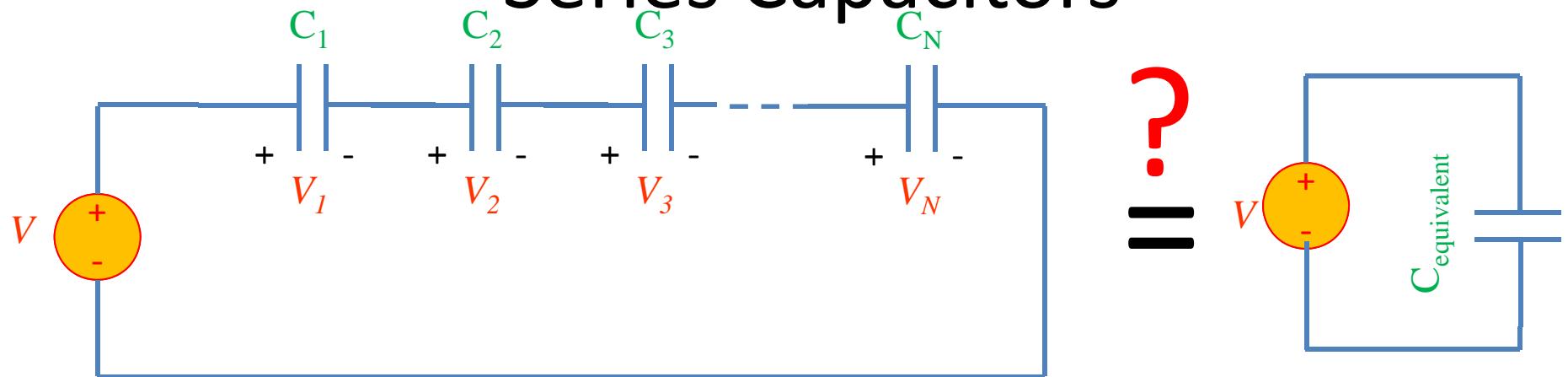

$$\frac{1}{C_{eq}} = \sum_{i=1}^N \frac{1}{C_i}$$

# RC circuit

Find  $V(t)$ ,  $q(t)$ ,  $i(t)$

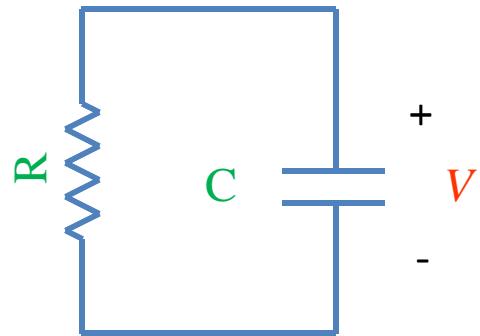


RESISTOR

$$i_R R = V_R = V_C = (-i_C)R$$

$$KVL \Rightarrow V_R = V_C$$

Find  $V(t)$ ,  $q(t)$ ,  $i(t)$

$$KCL \Rightarrow i_R = -i_C$$

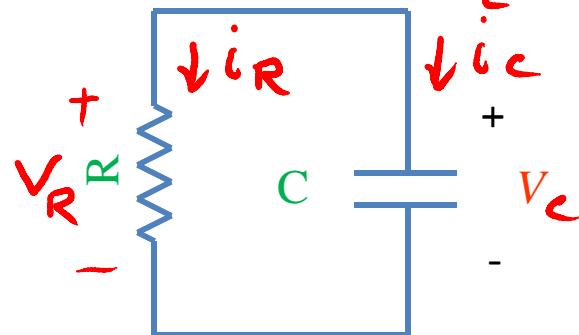


## RC circuit

CAPACITOR

$$q = CV_C$$

$$i_C = C \frac{dV_C}{dt}$$

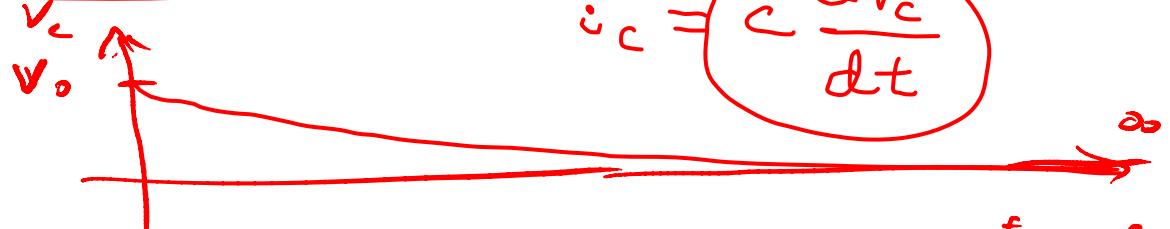

$$\frac{V_C}{R} = -C \frac{dV_C}{dt} \quad T = RC$$

$$\frac{dV(t)}{dt} = \frac{\text{why?}}{RC} V(t)$$

Soln:



$$V(t) = V(t=0) e^{-t/RC}$$

Proof:

$$\begin{aligned} \frac{dV(t)}{dt} &= \cancel{\frac{d}{dt} \left[ V(t=0) e^{-t/RC} \right]} \\ &= V(t=0) \cancel{\frac{d}{dt} \left[ e^{-t/RC} \right]} = -\frac{1}{RC} \cancel{V(t=0) e^{-t/RC}} \\ &= -\frac{1}{RC} V(t) \end{aligned}$$


# RC circuit

Find  $V(t)$ ,  $q(t)$ ,  $i(t)$

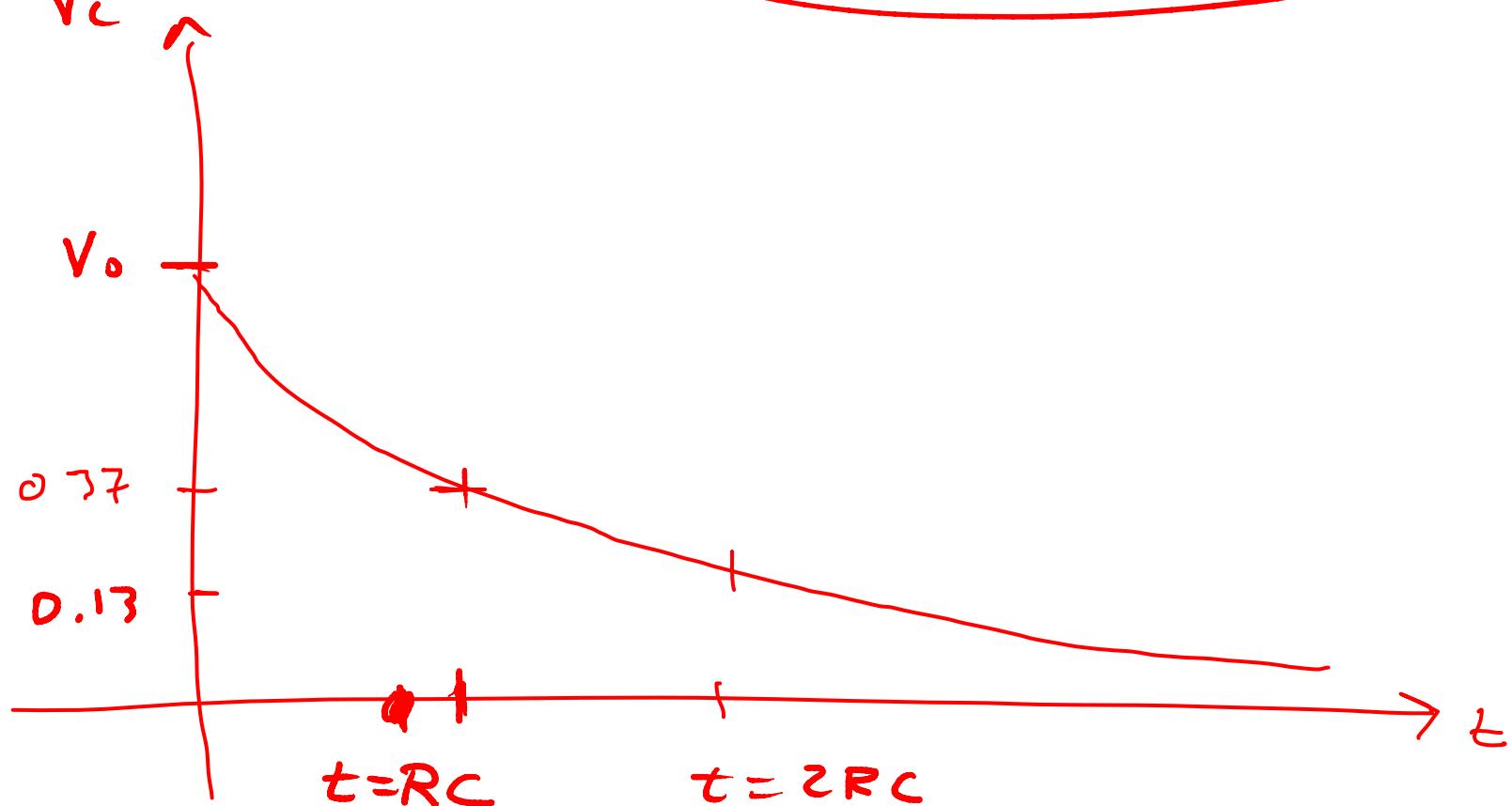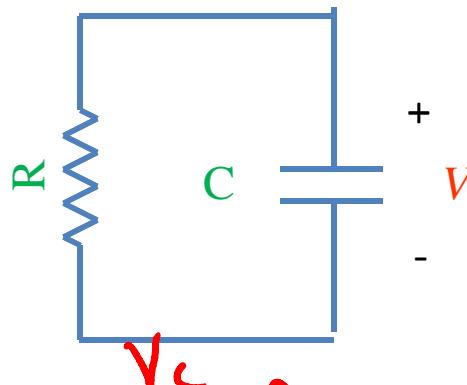

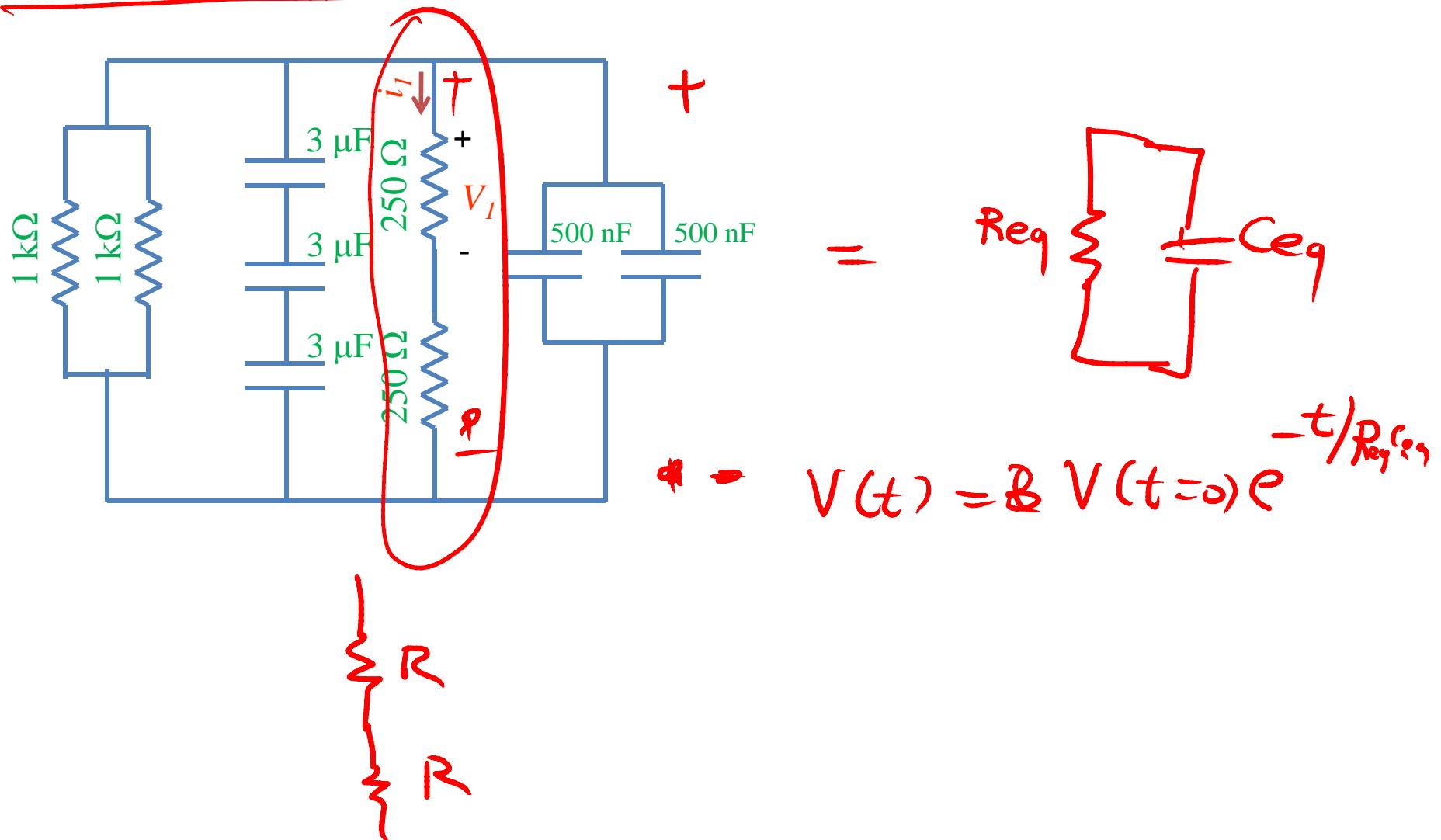
# Example RC problem 1

~~Find  $i_1(t)$ , given that  $V_1(t=0) = 3$  Volts~~



# Inductors

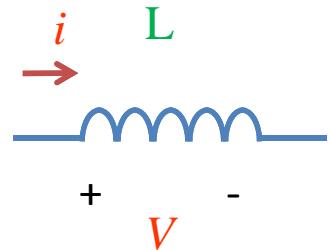

$$L = \frac{N^2 \mu A}{l}$$


A=area  
l=wire length  
N = # of turns  
 $\mu = 4 \pi 10^{-6} \text{ H/m}$

$$V = L \frac{di}{dt}$$

Henry[H]


$$V = L \frac{di}{dt} \Rightarrow i(t) = \frac{1}{L} \int V(t) dt$$

# Series Inductors

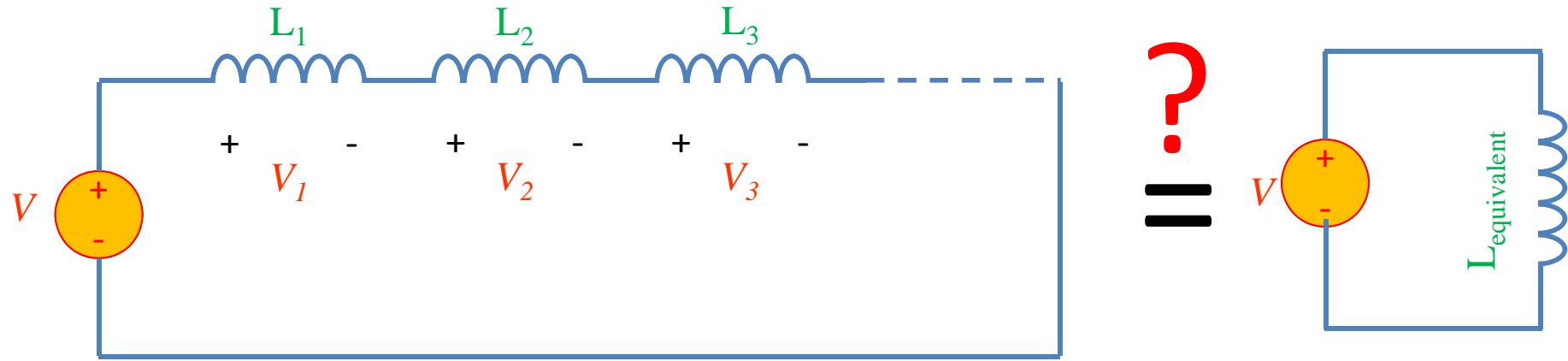

$$L_{eq} = \sum_{i=1}^N L_i$$

# Parallel Inductors

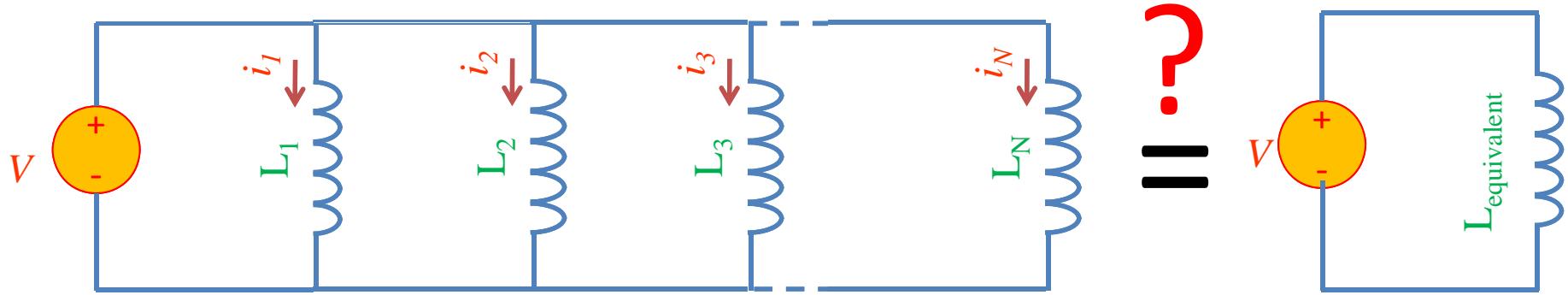


$$\frac{1}{L_{eq}} = \sum_{i=1}^N \frac{1}{L_i}$$

$$V_R = i_R R$$

## LR circuit

Find  $V(t)$ ,  $i(t)$

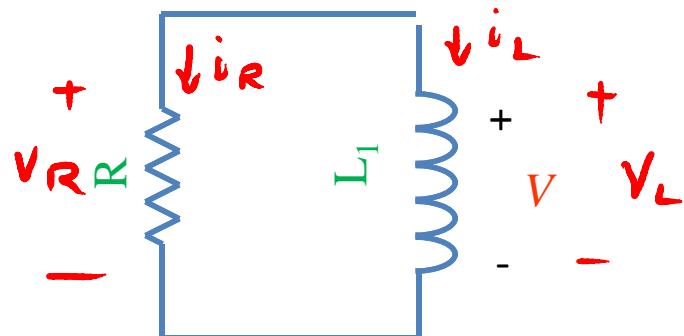

$$KVL \Rightarrow V_L = V_R$$

$$KCL \Rightarrow i_R = -i_L$$

$$L \frac{di_L}{dt} = i_L R$$


$$-i_L R = L \frac{di_L}{dt}$$

$$\Rightarrow \frac{di_L}{dt} = -\frac{1}{LR} i_L$$

$$V_L = L \frac{di_L}{dt}$$

$$I \equiv \frac{L}{R} \text{ time constant}$$


$$i_L(t) = i_L(t=0) e^{-t/\tau}$$

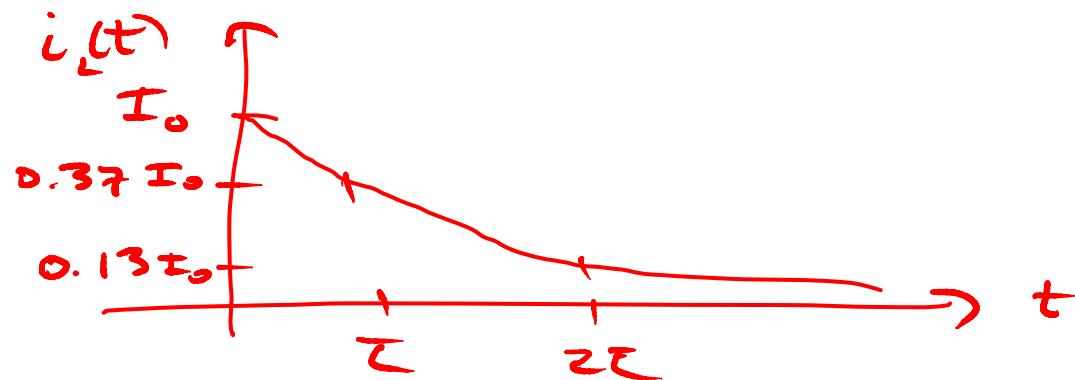
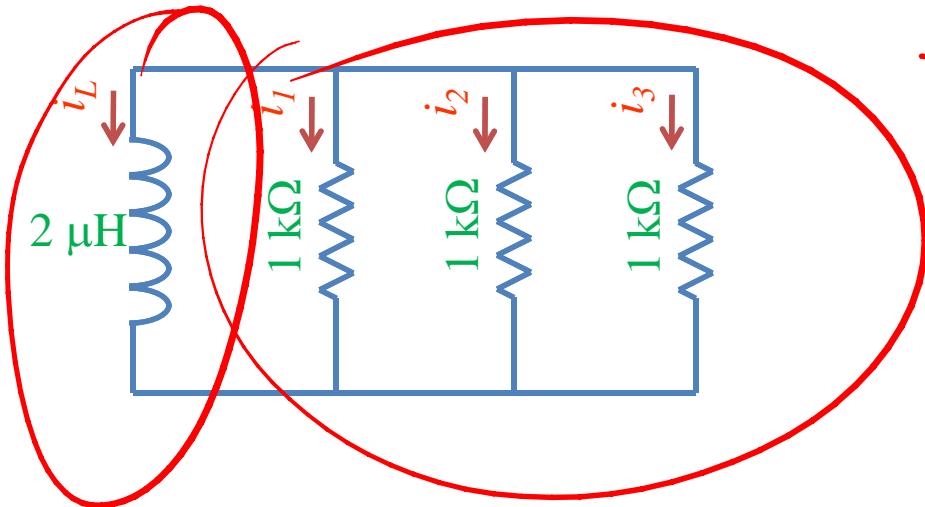
# Example LR problem #1


(Students) Find  $i_1(t)$  given  $i_L(t=0) = 5 \text{ A}$ .

Hint:  $i_1 + i_2 + i_3 = -i_L$ . How are  $i_1$ ,  $i_2$ ,  $i_3$  related?



$$-i_L = i_2 + i_1 + i_3$$

# Power

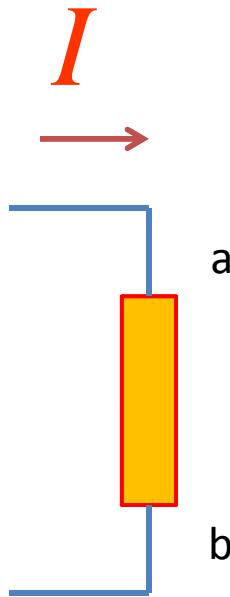

$$I \times V_{ab} = \text{power}$$


Watts [W] = Volt Amp [V-A]

Note: MKSA unit system:  
*Meters Kilogram Second Amp*

Resistor:  
Energy lost to heat...

Inductor or capacitor:  
Energy **STORED** and can be recovered...

# Energy stored

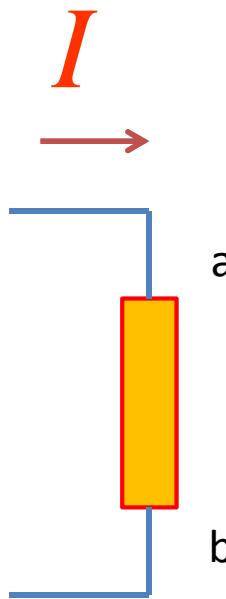

$$IxV_{ab} = power$$

Energy:

$$W = \int Pdt = \int I \cdot Vdt$$

Capacitor stored energy:

$$\int I \cdot Vdt = \int C \frac{dV}{dt} \cdot Vdt = \frac{1}{2} CV^2 = \frac{Q^2}{2C}$$

Inductor stored energy:

$$\int I \cdot Vdt = \int I \cdot L \frac{dI}{dt} dt = \frac{1}{2} LI^2$$

# Circuits

The diagram shows three circuit components: a resistor ( $R$ ), a capacitor ( $C$ ), and an inductor ( $L$ ). The resistor is represented by a blue zigzag line with a green label  $R$ . The capacitor is a blue parallel plate with a green label  $C$  and a red voltage  $V$  across it, with '+' at the top and '-' at the bottom. The inductor is a blue coil with a green label  $L$  and a red voltage  $V$  across it, with '+' at the top and '-' at the bottom.

$$V = I R$$
$$C$$
$$V = I/j\omega C$$
$$L$$
$$V = j\omega L I$$

“Impedance”

$$Z = R$$

$$Z = 1/j\omega C$$

$$Z = j\omega L$$

KCL, KVL hold for relationship  
between  $V$ ,  $I$ .

# Series/Parallel Impedances



$$Z_{eq} = Z_1 + Z_2 + Z_3$$



$$Z_{eq}^{-1} = Z_1^{-1} + Z_2^{-1} + Z_3^{-1}$$

# Example Impedance Problem

Find  $Z_{eq}$  for this circuit: (students)

