

Announcements:

1. Final HW due Friday of 10th week
2. Professor Burke's office hours this week:
Tu 9:30-11:30 (EH 2230)
Th 9:30-11 (EG 2232)
Th 2-3:30 (EH 2230)
3. Exam will cover all of Ch. 9 (not delta-Y),
and part of Ch. 14 (14.1 14.2 14.3 14.5 14.6 14.7)

EECS 70A: Network Analysis

Lecture 15

Conversion procedures

$$\mathbf{i}(t) \rightarrow \mathbf{I}$$

$$i(t) = I_m \cos(\omega t + \phi) \Rightarrow \mathbf{I} = I_m e^{j\phi}$$

$$\mathbf{v}(t) \rightarrow \mathbf{V}$$

$$v(t) = V_m \cos(\omega t + \phi) \Rightarrow \mathbf{V} = V_m e^{j\phi}$$

$$\mathbf{I} \rightarrow \mathbf{i}(t)$$


$$i(t) = \operatorname{Re}(\mathbf{I} e^{j\omega t})$$

$$\mathbf{V} \rightarrow \mathbf{v}(t)$$

$$v(t) = \operatorname{Re}(\mathbf{V} e^{j\omega t})$$

For the exam, you should know how to carry out these procedures.

Conversion procedures

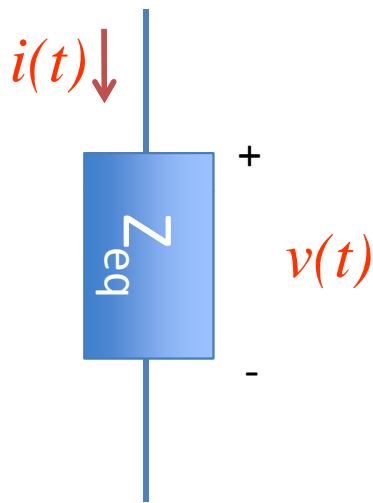

Given $i(t)$ find $v(t)$:

$$i(t) \rightarrow \mathbf{I} \rightarrow \mathbf{V} = \mathbf{I} Z_{eq} \rightarrow v(t)$$

Given $v(t)$ find $i(t)$:


$$v(t) \rightarrow \mathbf{V} \rightarrow \mathbf{I} = \mathbf{V} / Z_{eq} \rightarrow i(t)$$

For the exam, you should know how to carry out these procedures.

Complex numbers

Euler's relationship:

$$e^{j\phi} = \cos \phi + j \sin \phi$$

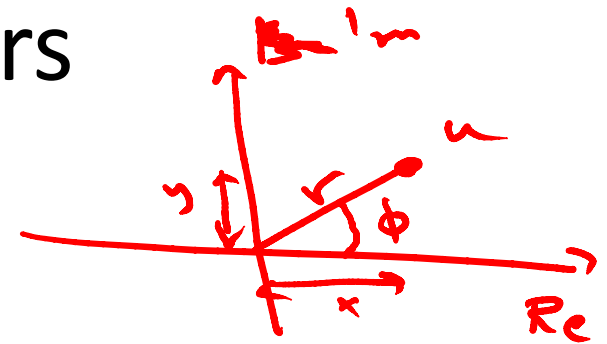

Memorize

Need to be able to manipulate complex numbers, e.g. given:

$$u = \frac{A + jB}{C + jD} \quad (A, B, C, D \text{ all real})$$

Class: Find $|u|$ in terms of r, ϕ :
 $u = r e^{j\phi}$
 $|u| = r$

- Find $\text{Re}(u)$, $\text{Im}(u)$
- Express u as $x + jy$, $r e^{j\phi}$
- Find $\text{Re}(u e^{j\omega t})$

• Find $|u| = \sqrt{\text{Re}(u)^2 + \text{Im}(u)^2}$

Did some of this in office hours..

“Transfer Function” $H(\omega)$



Could define $\frac{V_{out}(t)}{V_{in}(t)}$

Too complicated for arbitrary circuits and arbitrary waveforms.

Instead define $\frac{V_{out}}{V_{in}}$

assume periodic functions
i.e.

Transfer Function

$$H(\omega) \equiv \frac{V_{out}}{V_{in}}$$

$$V_{in}(t) = V_{in,m} \cos(\omega t + \phi_{in})$$
$$V_{out}(t) = V_{out,m} \cos(\omega t + \phi_{out})$$

Note: $\frac{V_{out}(t)}{V_{in}(t)}$ and $\frac{V_{out}}{V_{in}}$ will depend on ω .

REAL Significance of $H(\omega)$

$$V_{in}(t) = V_{in,m} \cos(\omega t + \phi_{in})$$

$$\bar{V}_{in} = V_{in,m} e^{j\phi_{in}}$$

$$V_{out}(t) = V_{out,m} \cos(\omega t + \phi_{out})$$

$$\bar{V}_{out} = V_{out,m} e^{j\phi_{out}}$$

$$H(\omega) \equiv \frac{\bar{V}_{out}}{\bar{V}_{in}} = \frac{V_{out,m} e^{j\phi_{out}}}{V_{in,m} e^{j\phi_{in}}}$$

$$= \frac{V_{out,m}}{V_{in,m}} \frac{e^{j\phi_{out}}}{e^{j\phi_{in}}} = \frac{V_{out,m}}{V_{in,m}} e^{j(\phi_{out} - \phi_{in})}$$

$$|H(\omega)| = \frac{V_{out,m}}{V_{in,m}}$$

tells us important info.

about amplitude of output signal.





Aside $E_{real} \neq real$

"Bode plot." $|E e^{j\phi}| = E$
 log-log typical
 $|H(\omega)|_{dB} \equiv 20 \log |H(\omega)|$
 Decibel

RC transfer function

FIND $H(\omega)$

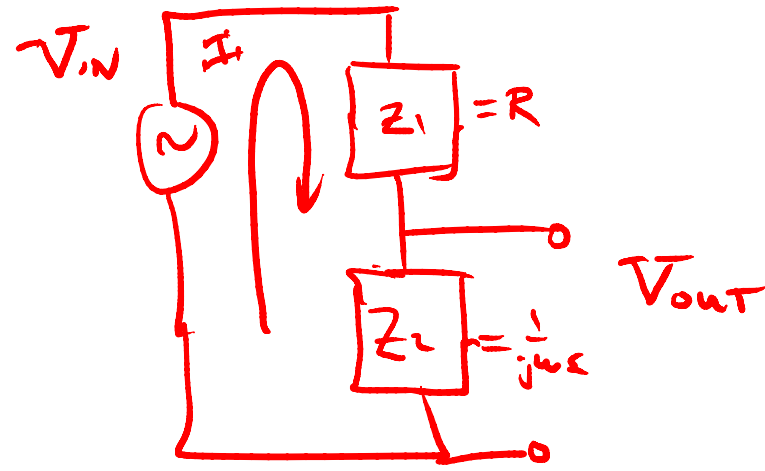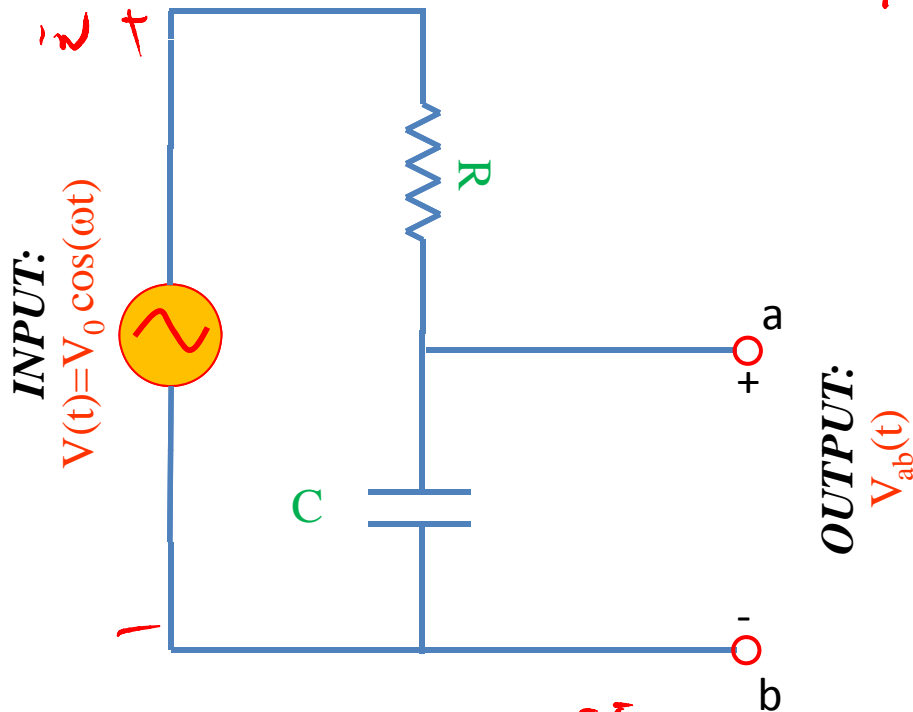

$$I = \frac{V_{IN}}{Z_1 + Z_2}$$

$$V_{OUT} = I Z_2 = \frac{V_{IN}}{Z_1 + Z_2} Z_2$$

$$\Rightarrow \frac{V_{OUT}}{V_{IN}} = \frac{Z_2}{Z_1 + Z_2} = \frac{1}{1 + j\omega RC} = \underline{\underline{H(\omega)}}$$


Magnitude of H

$$\tau \equiv RC$$

$$|H(\omega)| = \left| \frac{1}{1 + jRC\omega} \right| = \left| \frac{1}{1 + j\omega\tau} \right|$$


$$= \frac{1}{\sqrt{1 + (\omega\tau)^2}}$$

LPF

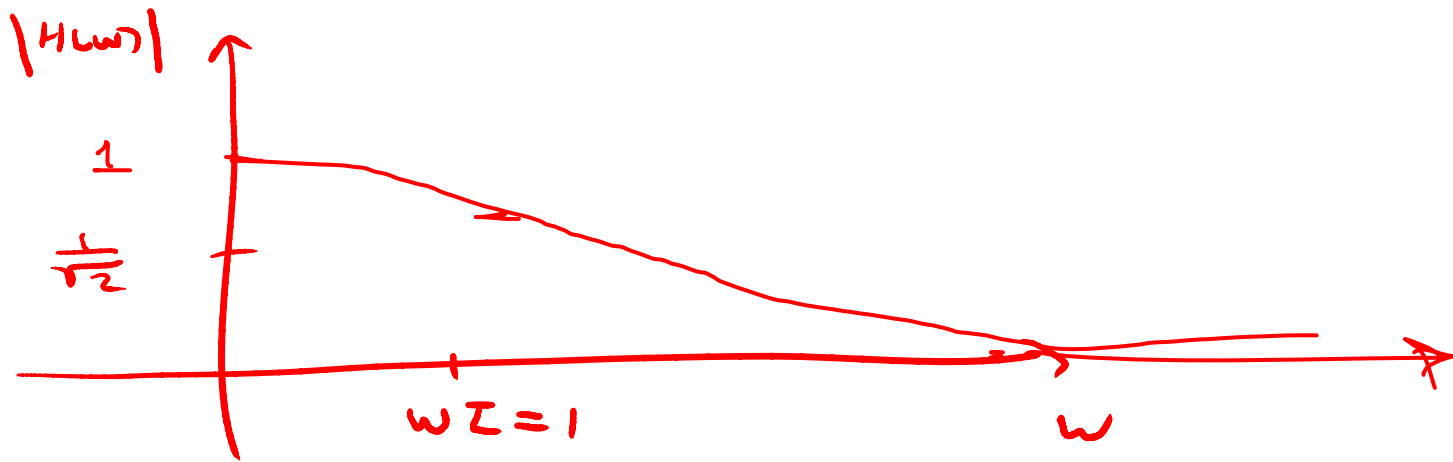

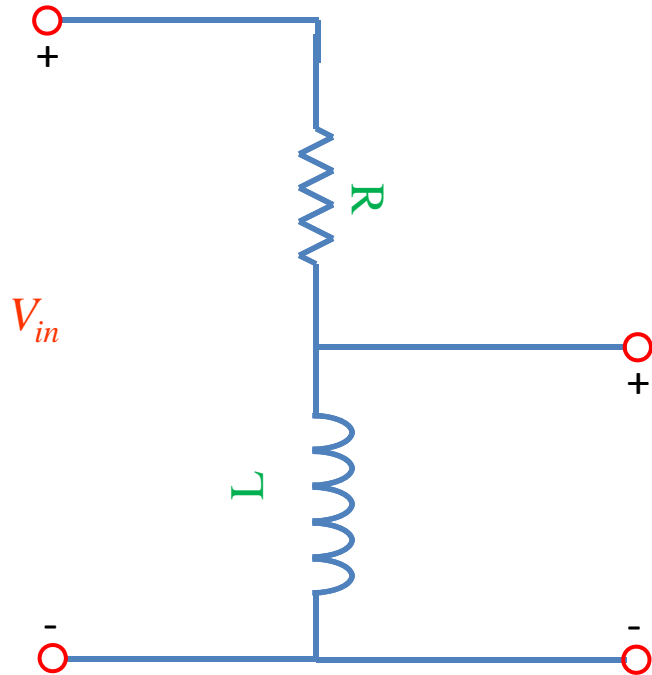Example problem


Find $H(\omega)$ for this circuit, then sketch the magnitude of $H(\omega)$ vs ω : (students)



STEP 1: DRAW AS IMPEDANCES

STEP 2: $\frac{V_{out}}{V_{in}} = H(\omega)$ RECALL VOLTAGE DIVIDER

STEP 3: $|H(\omega)|$

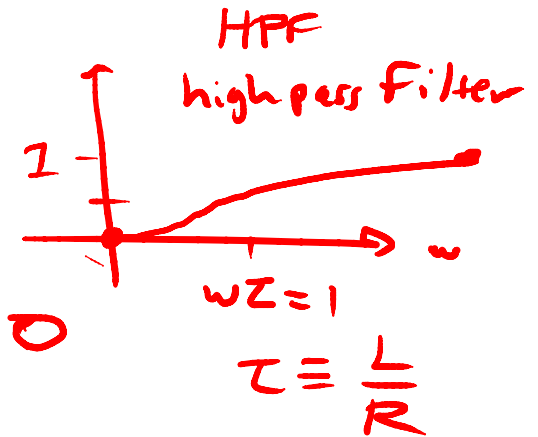


V_{out}

$$\lim_{\omega \rightarrow 0} H(\omega) = 0$$

$$\lim_{\omega \rightarrow \infty} H(\omega) = 1$$

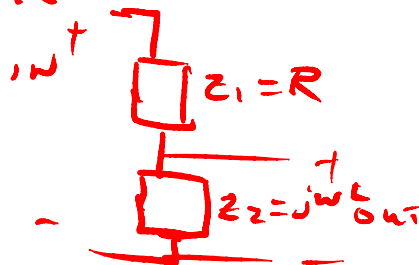
$$\begin{aligned}
 H(\omega) &= \frac{j\omega L \frac{1}{R}}{R + j\omega L \frac{1}{R}} \\
 &= \frac{j\omega \frac{L}{R}}{1 + j\omega \frac{L}{R}} \\
 &= \frac{j\omega \tau}{1 + j\omega \tau}
 \end{aligned}$$




$$\begin{aligned}
 \frac{V_{out}}{V_{in}} &= \frac{Z_2}{Z_1 + Z_2} \\
 &= \frac{j\omega L}{R + j\omega L}
 \end{aligned}$$

Band pass filter (RLC)


FIND $H(\omega)$, SKETCH $|H(\omega)|$ VS ω

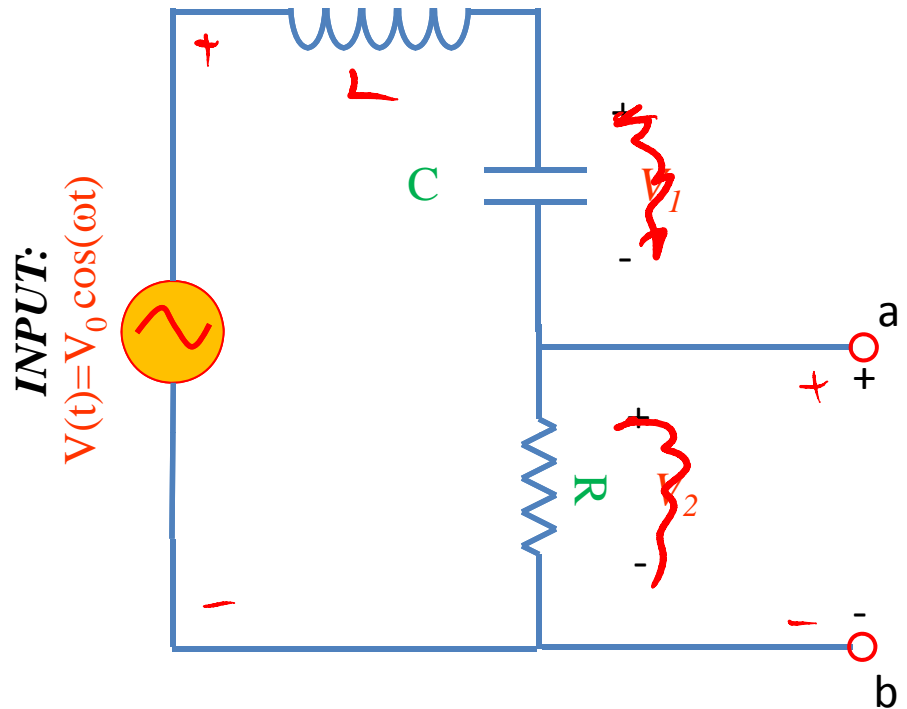

OUTPUT:
 $V_{ab}(t)$

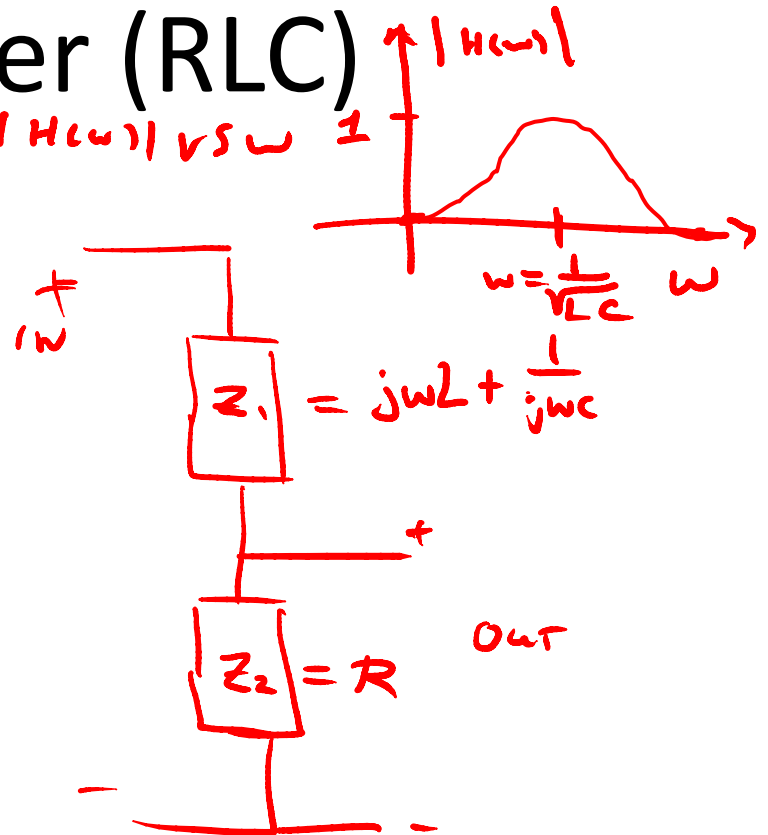
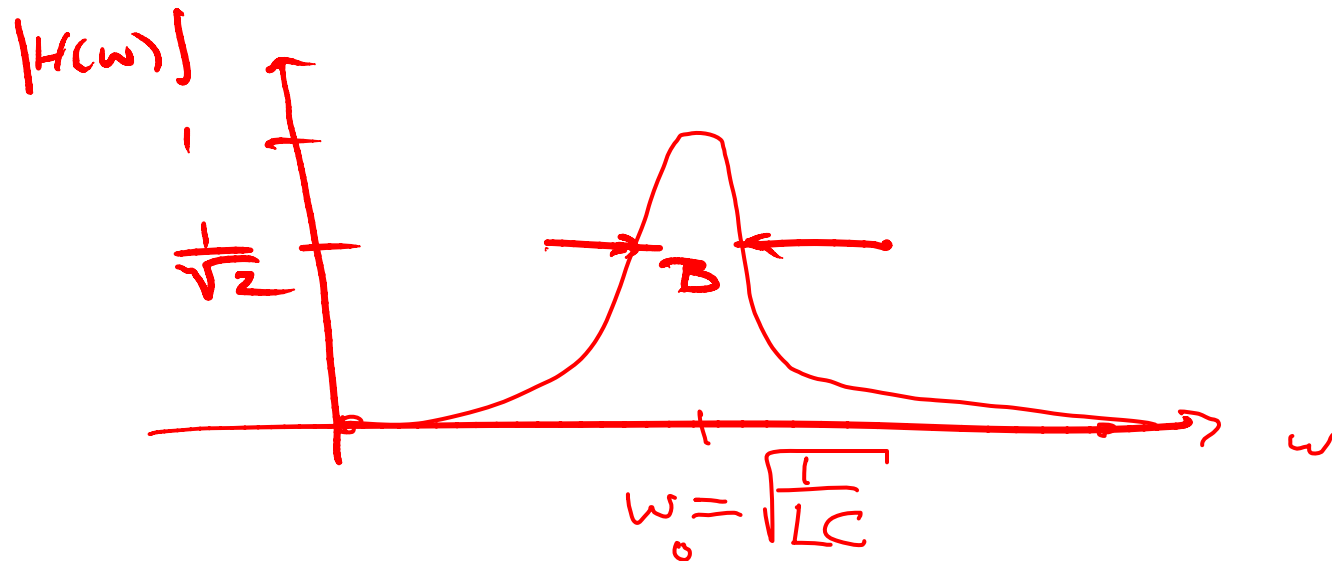
$$\begin{aligned}
 H(\omega) &= \frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} \\
 &= \frac{R}{R + j(\omega L - \frac{1}{\omega C})} = \frac{R}{R + j \frac{L}{\omega} (\omega^2 - \frac{1}{LC})}
 \end{aligned}$$



$$B = \frac{R}{L}$$

$$\frac{\omega_0}{B} \equiv Q \text{ quality factor}$$

$$= \frac{\omega_0 L}{R} \text{ or } \frac{1}{\omega_0 RC}$$

VERY IMPORTANT IN COMMUNICATIONS




<http://www.peachparts.com/shopforum/showthread.php?t=256624>

Resonance



Tacoma Narrows Bridge (1940)

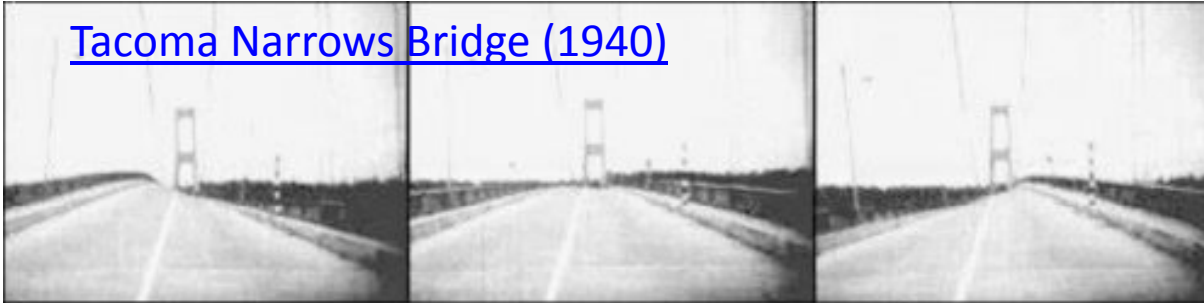

Nov 7, 1940



<http://www.youtube.com/watch?v=3mclp9QmCGs>

Tesla

